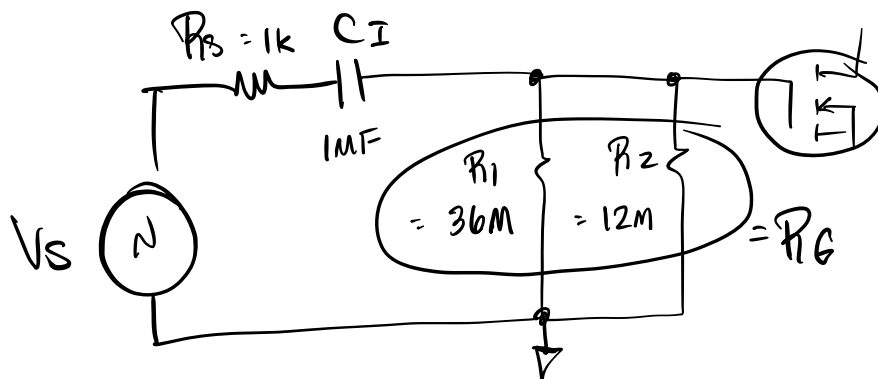


Common-Source LF AC Circuit

- .. like CE, the impedances of the capacitors become important at low frequencies

LF Input Circuit



- .. the equivalent resistance seen by C_I is $R_S + R_G$

$$\therefore f_{L(in)} = \frac{1}{2\pi \cdot C_I (R_S + R_G)}$$


$$f_{L(in)} = \frac{1}{2\pi \cdot 1 \times 10^{-6} (1k + 9G)}$$

$$f_{L(in)} = 0.01768 \text{ Hz}$$

- .. high input resistance makes very low cutoff frequency!

LF Output Circuit

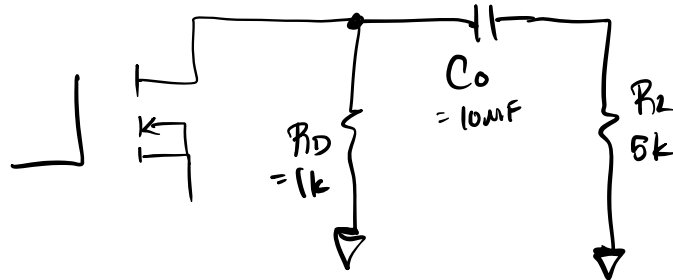.. assume r_o is sufficiently large to be neglected




.. thus, the resistance "seen" by C_o is $R_L + R_D$

$$\therefore f_{L(OUT)} = \frac{1}{2\pi C_o (R_L + R_D)}$$

$$f_{L(OUT)} = \frac{1}{2\pi \cdot 10 \times 10^{-6} (5k + 1k)} = \underline{2.653 \text{ Hz}}$$

LF Source Circuit

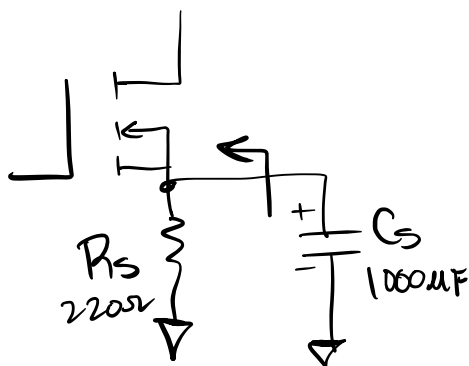

.. we found with the BJT CE amplifier that the resistance seen by CE

is $R_E \parallel \frac{1}{g_m}$
.. exactly the case with C_S !

$$f_L(s) = \frac{1}{2\pi C_S (R_S \parallel \frac{1}{g_m})}$$

$$\frac{1}{g_m} = \frac{1}{14.11} = 0.07087 \text{ k}\Omega$$

↑
mA/V

or 70.87 Ω

$$\therefore 220\Omega \parallel 70.87\Omega = \underline{53.60\Omega}$$


$$f_L(s) = \frac{1}{2\pi \cdot 1000 \times 10^{-6} \cdot 53.60} = \underline{2.969 \text{ Hz}}$$

-- $f_L(s)$ and $f_L(\text{out})$ are very close together; not a dominant pole situation!

-- thus, expected -3dB $f_L > f_L(s)$

Common-Source HF SSM

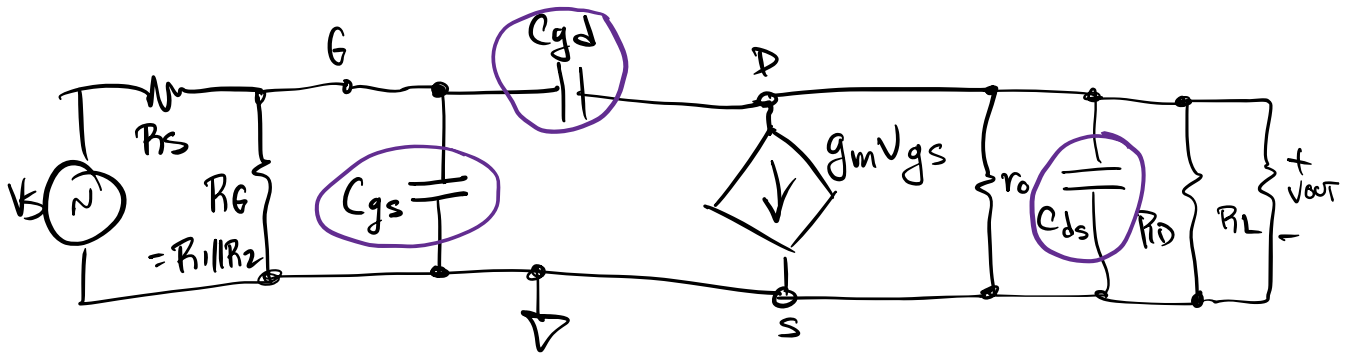-- Similar situation as common-emitter; we add gate-to-source and gate-to-drain capacitances; but unlike the BJT, we now have drain-to-source capacitance as well!



∴ FET data sheets don't give us values for these interelectrode capacitances directly; rather, they list C_{iss} (input capacitance), C_{oss} (output capacitance), and C_{rss} (reverse transfer capacitance), from which we must deduce C_{gs} , C_{gd} , and C_{ds} , knowing:

$$C_{iss} = C_{gs} + C_{gd} \quad \leftarrow \text{gate stuff}$$

$$C_{oss} = C_{gd} + C_{ds} \quad \leftarrow \text{drain stuff}$$

$$C_{rss} = C_{gd}$$

$$\therefore C_{gs} = C_{iss} - C_{rss}$$

$$C_{gd} = C_{rss}$$

$$C_{ds} = C_{oss} - C_{rss}$$

∴ in this example:

$C_{iss} = 40 \text{ pF}$	} typical for small, n-channel enhancement-type MOSFET
$C_{oss} = 15 \text{ pF}$	
$C_{rss} = 5 \text{ pF}$	

$$C_{gs} = C_{iss} - C_{rss} = 40 - 5 = \underline{35 \text{ pF}}$$

$$C_{gd} = C_{rss} = \underline{5 \text{ pF}}$$

$$C_{ds} = C_{oss} - C_{rss} = 15 - 5 = \underline{10 \text{ pF}}$$

$f_H(\text{in})$:


.. as with the CE amplifier, with C_{gd} between the input and output of an inverting amplifier, it's Miller Time!

$$C_{gd}(\text{in}) = C_{gd} (1 - A_{v2})$$

\swarrow -11.52

$$= 5 (1 - -11.52) = \underline{62.6 \text{ pF}}$$

equivalent HF SSM at input :

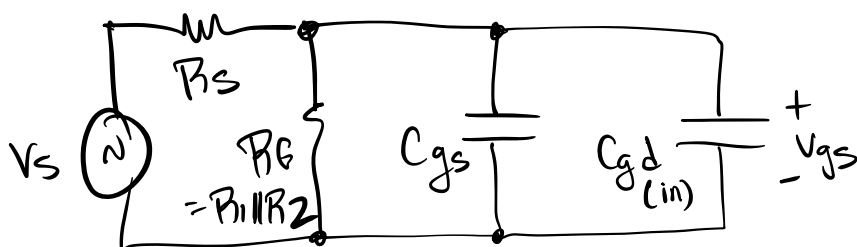

.. With one source transformation we can show that the equivalent resistance seen by the parallel capacitance is $R_s || R_G$.

thus,
$$f_{H(in)} = \frac{1}{2\pi (R_s \parallel R_E) (C_{gs} + C_{gd(in)})}$$

$$f_{H(in)} = \frac{1}{2\pi (1k \parallel 9M) (35p + 62.6p)}$$

$\hookrightarrow = 1k\Omega$

$$f_{H(in)} = 1.63 \text{ MHz}$$


$f_{H(out)} :$

∴ Miller Time at the output due to C_{gd} is

$$C_{gd(out)} = C_{gd} \left(1 - \frac{1}{A_{v2}} \right)$$

$$= 5 \left(1 - \frac{1}{-11.52} \right) \approx \underline{\underline{5 \text{ pF}}}$$

∴ equivalent HF SSM at output :

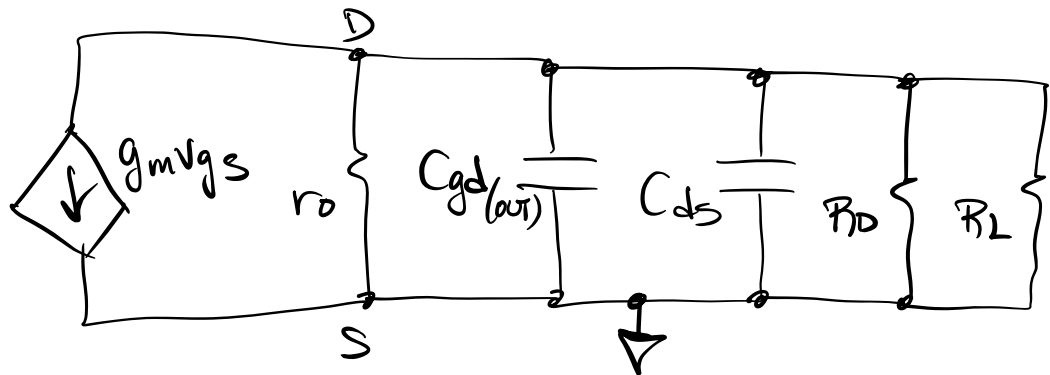

∴ equivalent resistance seen by parallel capacitance is

$$r_o \parallel R_D \parallel R_L = R_D' \parallel R_L ;$$

thus,

$$f_{H(our)} = \frac{1}{2\pi (R_D' \parallel R_L) (C_{ds} + C_{gd(our)})}$$

$$= \frac{1}{2\pi (.8164k) (10p + 5p)}$$

↑
from last
lecture

$$f_{H(our)} = 13 \text{ MHz}$$

∴ thus, like CE BJT amplifier, the input pole dominates

$$\text{and } f_H \approx 1.63 \text{ MHz}$$