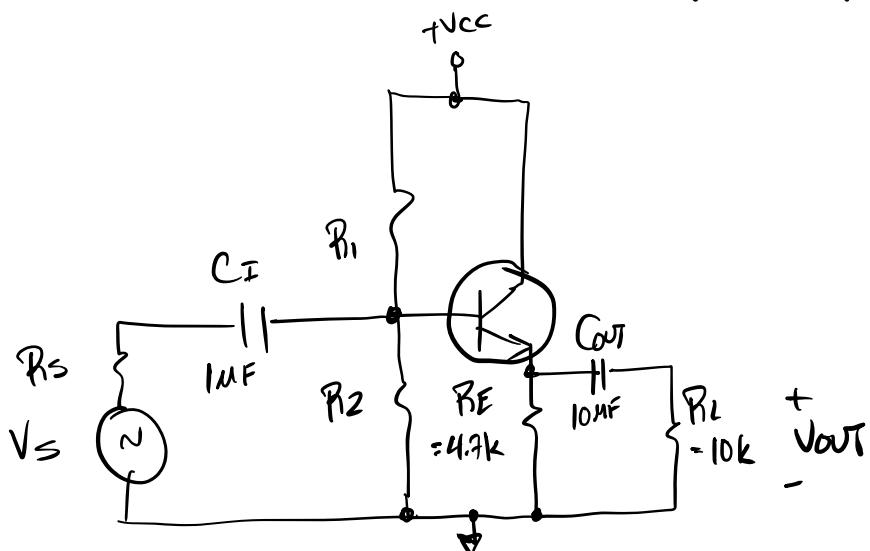


Voltage Followers

.. let's consider an alternate way of configuring our common-emitter voltage amplifier:



.. Note the 4.7k collector resistor has been moved to the emitter and, more importantly, the output is now taken here.


because the output voltage may be considered the small-signal emitter voltage v_e , and we know amplifier output is a function of $g_m v_{be}$, then:

$$V_{out} \propto v_{be} = V_b - v_e$$

$$V_{out} \propto V_{in} - V_{out}$$

- thus, this configuration works with 100% negative feedback,
 i.e., $\beta = 1$
- with the collector no longer used as an output terminal,
 we can connect it directly to V_{CC} ,
 which is at AC ground; thus, it is a
Common-collector amplifier
- entire output subtracted from input

Mid-Frequency Small-Signal Model of CC

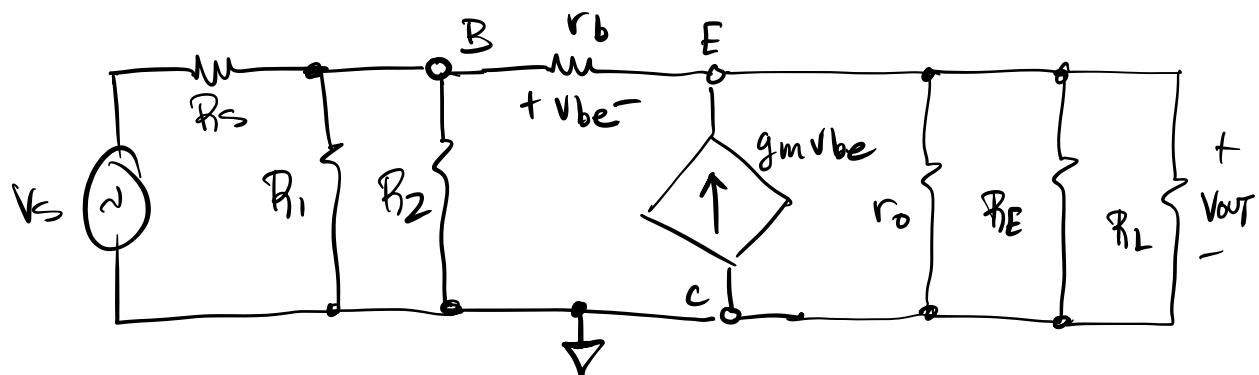

- because AC emitter current $[g_m V_{BE}]$ causes a positive V_{OUT} across $r_o \parallel R_E \parallel R_L$, the common-collector amplifier is Non-inverting.

- the open-loop gain of the amplifier, temporarily ignoring the 100% local feedback mechanism and the effects of r_b (more later), is:

$$A_{VO} = g_m (r_o \parallel R_E \parallel R_L)$$

- this is reduced by feedback to:

$$A_V = \frac{A_{VO}}{1 + \beta A_{VO}} = \frac{g_m (r_o \parallel R_E \parallel R_L)}{1 + 1 \cdot g_m (r_o \parallel R_E \parallel R_L)}$$

- if A_{VO} is sufficiently high in value, then

$$A_V \approx \frac{\cancel{g_m (r_o \parallel R_E \parallel R_L)}}{g_m (r_o \parallel R_E \parallel R_L)} \approx 1$$

or 0dB, non-inverting

- checking this, our common-emitter amplifier with identical circuit values had an open-loop gain of 263.3 (ignore the inverting part) yes,
 ≈ 1
↓

- With 100% negative feedback, this is $A_V = \frac{263.3}{1 + 1 \cdot 263.3} = \underline{0.9962}$

- another way to look at the operation of a common-collector amplifier: consider that a silicon BJT's base-to-emitter voltage is nearly constant @ 0.7V.
- thus, an applied AC signal at the base will cause the emitter to "follow" this waveform, just 0.7V more negative
- another term for this amplifier:
emitter follower
- the common-drain/source follower using FETs works exactly the same way
- both are known as voltage followers, as is the op-amp version [next section!]
- because the feedback is taken in parallel with the output and in series with the input, it is parallel-derived / series-applied
 - ↓ lowers R_{out}
 - ↓ raises R_{in}

Input Resistance of CC/Emitter Follower

- We showed that R_{in} for a CE amplifier was:

$$R_{in} = R_1 \parallel R_2 \parallel r_b$$

\downarrow
small-signal base-to-emitter
resistance

- Series-applied negative feedback only increases r_b , because R_1 and R_2 are external to the feedback mechanism,

thus, $r_b' = r_b (1 + \beta A_{vo})$

$$= 2.173 k \left(1 + 1.263.3\right)$$


$$r_b' = \underbrace{574.3 k}_{\Omega}$$

- now $r_b' \gg R_1 \parallel R_2$; so R_{in} has been usefully increased to

$$\boxed{R_{in}' \approx R_1 \parallel R_2}$$

- remember, r_b is dependent on BJT beta;
good riddance!!!
- this is a moot point with FET source followers; no r_b !
- self-biased JFET can achieve GSR range R_{in} !!!

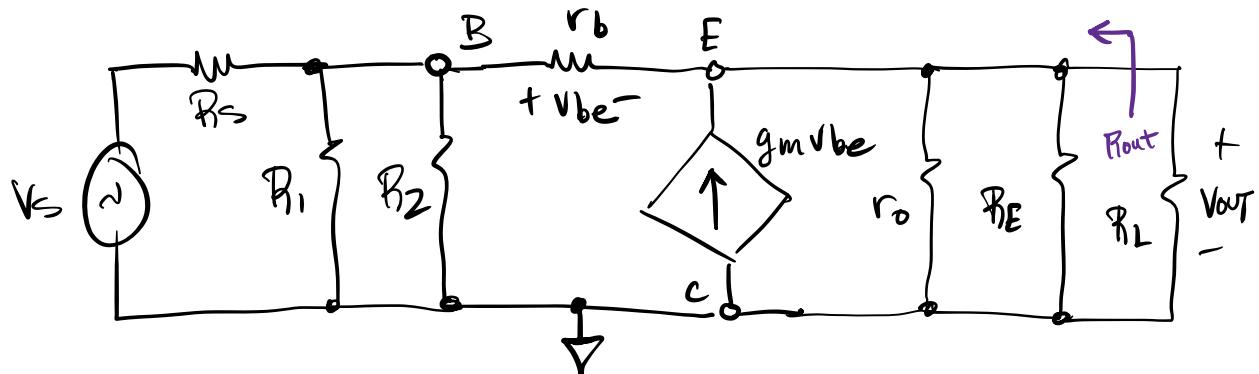Output Resistance of CC / Emitter Follower



-- from the perspective of R_L , the open-loop output resistance (again, abstract concept!) is $R_E \parallel r_o$; this is reduced due to shunt-derived negative feedback to:

$$R_{out} = \frac{R_E \parallel r_o}{1 + \beta A_{vo}}$$

-- the open-loop gain A_{vo} from the perspective of R_L is $g_m (R_E \parallel r_o)$;

$$\therefore R_{out} = \frac{R_E \parallel r_o}{1 + 1 \times g_m (R_E \parallel r_o)}$$

-- as usual, if A_{vo} is a high value, then

$$R_{out} \approx \frac{\cancel{R_E \parallel r_o}}{g_m (\cancel{R_E \parallel r_o})} \rightarrow R_{out} \approx \frac{1}{g_m}$$

- remember looking into the emitter from the perspective of C_E ? Yep, $\frac{1}{g_m}$.
 - for this follower, $R_{out} = \frac{1}{92.05 \text{ mA/V}} = 0.0186 \text{ k}\Omega$
 - or $R_{out} = 10.86 \text{ }\Omega$ (Wow!)
 - same deal w/ FETs; $\frac{1}{g_m}$.
 - note that due to \approx unity gain, Miller Effect input capacitance is not a thing
 - we can perform HF small-signal analysis to show that HF input capacitance is
- $$C_{IN(HF)} \approx C_{be}$$
- \uparrow
 collector is at AC ground
 not amplified/inverted
- negative feedback nullifies C_{be} the same way it greatly increased r_b
 - thus, for 50Ω source resistance, the HF cutoff would be
- $$f_H \approx \frac{1}{2\pi \cdot R_s \cdot C_{IN(HF)}} = \frac{1}{2\pi \cdot 50 \cdot 4_P} = \underline{\underline{795.8 \text{ MHz}}}$$

- What do we do with an amplifier that provides no voltage amplification, but has high R_{in} and low R_{out} , and low input C?
- buffer sensitive sources from problematic loads

ex: What if, instead of $R_L = 10k\Omega$, our common-emitter amp needs to drive $R_L = 600\Omega$ in parallel with $C_L = 2nF$ cable capacitance

Very realistic scenario!

- recall that the gain of the CE amplifier is $\approx A_{v2} = -g_m (R_C || r_o || R_L)$
- Now we have reduced R_L significantly!

$$A_{v2} = -92.05 (4.7k \parallel 38.02k \parallel 0.600k)$$

new R_L !

$$= -48.3 \text{ or } 33.7 \text{ dB}$$

- We just lost 15 dB of gain; itself bad enough, probably means less gain available for negative feedback, increasing distortion and worsening freq. response
- plus, that 2nF cable capacitance "sees" an equivalent resistance of CE Rout ($\approx R_c$) in parallel w/ R_L ; together, this forms a LPF:

$$f_H(C_L) = \frac{1}{2\pi \cdot C_L \cdot (R_c \parallel R_L)}$$


$$= \frac{1}{2\pi \cdot 2n \cdot (4.7k \parallel 0.600k)}$$

$$\hookrightarrow = 532.1 \text{ Hz}$$

$$= 149.6 \text{ kHz} \quad \leftarrow \text{dominates system;} \\ \text{--- not good!}$$

- instead, use an emitter follower to buffer the CE amplifier from nasty Z_L ; CE now sees negligible loading (no R_L in gain equation, no bias network if direct-coupled, negligible load capacitance)

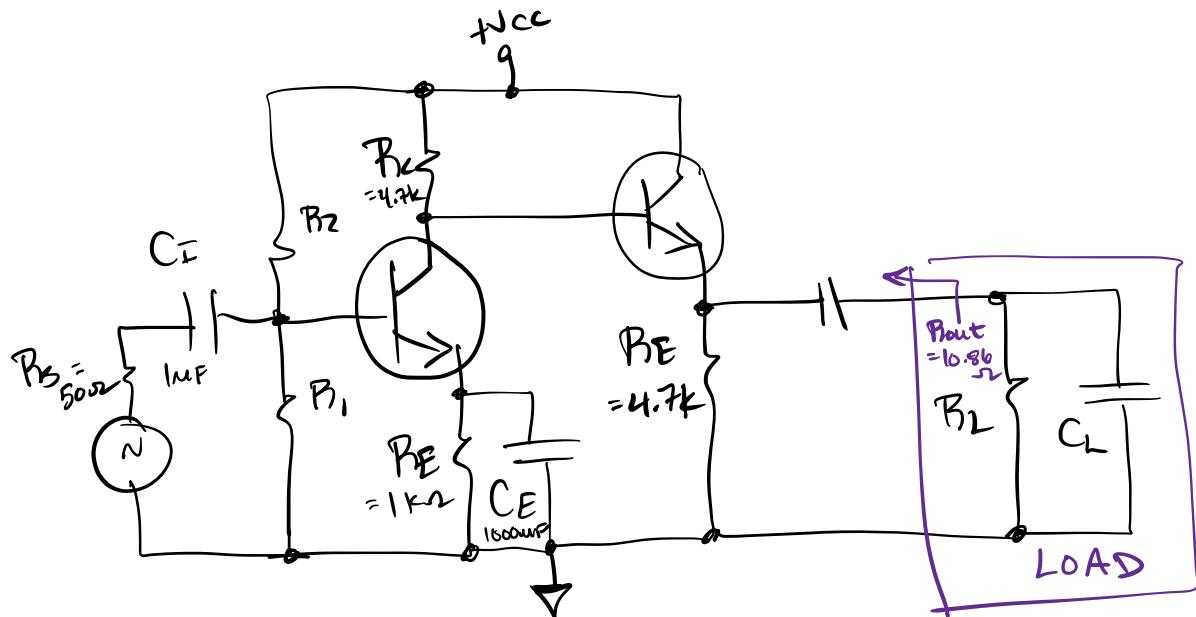- .. harsh Z_L of $600\Omega \parallel 2nF$ is now driven from R_{out} of follower



- .. practically no loss of gain between $R_{out} = 10.86\Omega$ and $R_2 = 600\Omega$, and C_L "sees" an equivalent resistance of $R_2 \parallel R_{out} = 600\Omega \parallel 10.86\Omega \simeq 10.86\Omega$

$$f_H(\text{out}) = \frac{1}{2\pi \cdot C_L \cdot R_{out}}$$

$$= \frac{1}{2\pi \cdot 2n \cdot 10.86}$$

$$f_H(\text{out}) = 7.32 \text{ MHz}$$

Much better!

- .. so we have analyzed an amplifier configuration that uses shunt-derived / series applied negative feedback with $B = 1$ or 100% to create a voltage follower that can be a powerful solution for driving difficult loads
- .. Negative feedback FTW !!!