

Session # 16: **Precision through differences: Wheatstone Bridge** **Notes**

These notes are drawn from *Alexander and Sadiku*, 2013, *O'Malley*, 2011, WIKIPEDIA, and other sources. They are intended to offer a summary of topics to guide you in focused studies. You should augment this handout with notes taken in class, reading textbook(s), and working additional example problems.

Learning Objective: In this module, we consider a technique used to measure small differences when an absolute reference may be unavailable. The resulting circuit configuration is known as the *Wheatstone Bridge*.

The Wheatstone bridge (or resistance bridge) circuit is used in applications where a precision measurement is desired. The guiding principle being the relative precision of observing a zero (or null) is higher than that of measuring some non-zero value. Any technique, including the Wheatstone configuration, relies on at least one (usually three) precision elements.

Consider the circuit below:

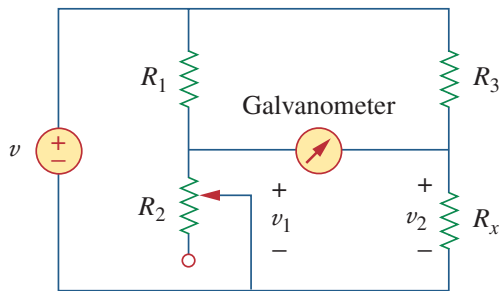


Figure 4.63

The Wheatstone bridge; R_x is the resistance to be measured.

The variable resistance is adjusted until no current flows through the galvanometer, which is essentially a d'Arsonval movement operating as a sensitive current-indicating device, like an ammeter, in the μA range. When a null occurs (no current flow), it follows that $v_1 = v_2$. Hence, we have the equivalent ratios:

$$v_1 = v_2 \implies \frac{R_1}{R_2} = \frac{R_3}{R_x}$$

and any algebraic equivalent.

The estimated value of R_x is only as precise as the precision of the other circuit elements: resistors R_1 and R_3 , and precision variable resistor R_2 .



Homework: None (You may look at Chapter 4 # 90, 91)

- (a) Find i when $R = 4\ \Omega$.
 (b) Determine the maximum power from the box.

$R(\Omega)$	$V(V)$	$i(A)$
2	3	1.5
8	8	1.0
14	10.5	0.75

4.87 A transducer is modeled with a current source I_s and a parallel resistance R_s . The current at the terminals of the source is measured to be 9.975 mA when an ammeter with an internal resistance of $20\ \Omega$ is used.

- (a) If adding a $2\text{-k}\Omega$ resistor across the source terminals causes the ammeter reading to fall to 9.876 mA, calculate I_s and R_s .
 (b) What will the ammeter reading be if the resistance between the source terminals is changed to $4\text{ k}\Omega$?

4.88 Consider the circuit in Fig. 4.144. An ammeter with internal resistance R_i is inserted between A and B to measure I_o . Determine the reading of the ammeter if: (a) $R_i = 500\ \Omega$, (b) $R_i = 0\ \Omega$. (Hint: Find the Thevenin equivalent circuit at terminals a - b .)

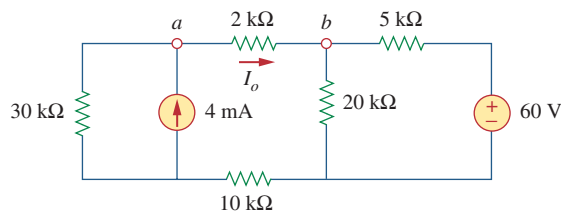


Figure 4.144
For Prob. 4.88.

4.89 Consider the circuit in Fig. 4.145. (a) Replace the resistor R_L by a zero resistance ammeter and determine the ammeter reading. (b) To verify the reciprocity theorem, interchange the ammeter and the 12-V source and determine the ammeter reading again.

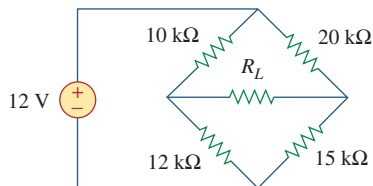


Figure 4.145
For Prob. 4.89.

4.90 The Wheatstone bridge circuit shown in Fig. 4.146 is used to measure the resistance of a strain gauge. The adjustable resistor has a linear taper with a maximum value of $100\ \Omega$. If the resistance of the strain gauge is found to be $42.6\ \Omega$, what fraction of the full slider travel is the slider when the bridge is balanced?

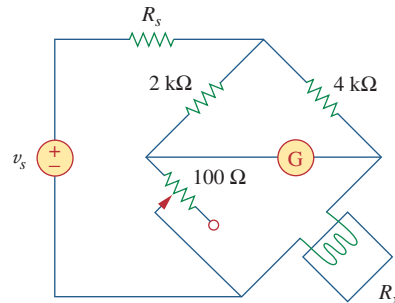


Figure 4.146
For Prob. 4.90.

4.91 (a) In the Wheatstone bridge circuit of Fig. 4.147, select the values of R_1 and R_3 such that the bridge can measure R_x in the range of 0 – $10\ \Omega$.

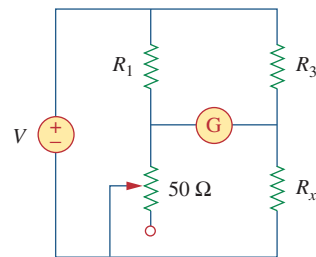


Figure 4.147
For Prob. 4.91.

(b) Repeat for the range of 0 – $100\ \Omega$.

***4.92** Consider the bridge circuit of Fig. 4.148. Is the bridge balanced? If the $10\text{-k}\Omega$ resistor is replaced by an $18\text{-k}\Omega$ resistor, what resistor connected between terminals a - b absorbs the maximum power? What is this power?

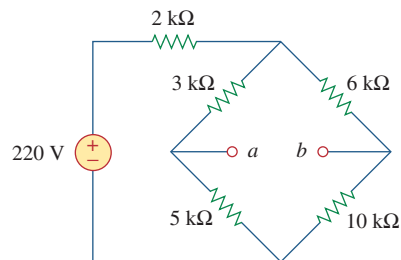


Figure 4.148
For Prob. 4.92.