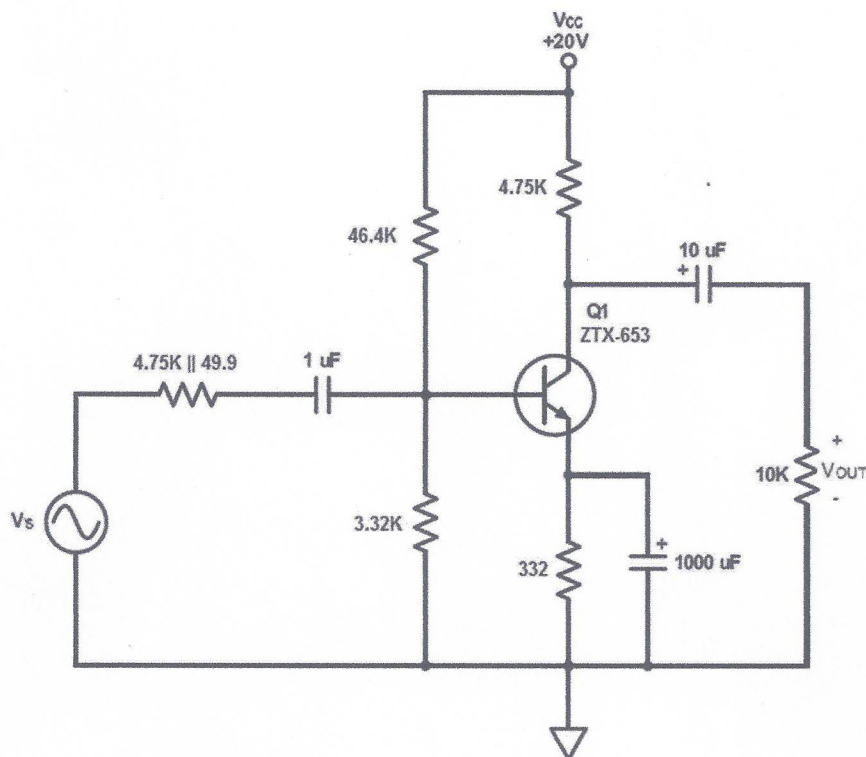


Determine the D.C. operating point of the following circuit ( $I_C$  and  $V_{CE}$ ) if base current may be assumed negligible. Check  $P_{diss}$  and verify that the transistor is operating in the active region.



$$V_B = 20 \left( \frac{3.32}{3.32 + 46.4} \right) = 1.335 \text{ V} \quad (+1)$$

$$V_E = V_B - 0.7 = 0.6355 \text{ V} \quad (+1)$$

$$I_E = \frac{0.6355}{332} = 0.001914 \text{ A} \quad \text{or } 1.914 \text{ mA} \quad (+1)$$

$$\therefore I_C \approx 1.914 \text{ mA} \quad (+1)$$

$$V_C = 20 - 1.914 \text{ mA} \cdot 4.75 \text{ k} = 10.91 \text{ V} \quad (+1)$$

$$\therefore V_{CE} = 10.91 - 0.6355 = 10.27 \text{ V} \quad (+1)$$

$$P_{diss} = 1.914 \text{ mA} \cdot 10.27 \text{ V} = 19.66 \text{ mW} \quad (+1)$$

$V_{BE} = 0.7 \text{ V}$  yes  
 $V_{CE} > 0.2 \text{ V}$  active  
 (+1)

Calculate the parameters  $g_m$ ,  $r_b$ , and  $r_o$  if  $\beta = 200$  and the Early voltage  $|V_A|$  is 250 V. Include a unit with each answer.

$$g_m = 35 I_C = 35 \cdot 1.914 = \underline{67 \text{ mA/V}} \quad (+2)$$

$$r_b = \frac{\beta}{g_m} = \frac{200}{67} = \underline{2.985 \text{ k}\Omega} \quad (+2)$$

$$r_o = \frac{|V_A|}{I_C} = \frac{250}{1.914} = \underline{130.6 \text{ k}\Omega} \quad (+2)$$

Determine the mid-frequency gain  $A_v$  and  $A_v(\text{dB})$ .

$$r_b' = 46.4k \parallel 3.32k \parallel 2.985k \\ = 1.520k \quad (+)$$

$$R_s = 4.75k \parallel 49.9 = 0.04938k \quad (+)$$

$$V_{be} = V_s \left( \frac{1.520}{1.520 + 0.04938} \right) = 0.9685 V_s \quad (+)$$

$$R_c' = 130.6k \parallel 4.75k \parallel 10k = 3.143k \quad (+)$$

$$V_{out} = -g_m V_{be} R_c' = -67 \cdot 0.9685 V_s \cdot 3.143k$$

$$A_v = \frac{V_{out}}{V_s} = -203.9 \quad (+)$$

$$\text{or } 46.2 \text{ dB inverting } (+)$$

Determine the high-frequency input and output capacitances using Miller's Theorem if  $C_{BC} = 5.6 \text{ pF}$  and  $C_{BE} = 24 \text{ pF}$ . Compute the input and output HF cutoff frequencies and the approximate overall high-frequency cutoff,  $f_H$ .

gain between  $V_{be}$  and  $V_{out}$ :

$$-g_m \cdot R_c' = -67 \cdot 3.143 = -210.6 \quad (+1)$$

$$\therefore C_{BC(IN)} = 5.6 (1 - -210.6) = 1185 \text{ pF} \quad (+1)$$

$$C_{IN} = 1185 + 24 = 1209 \text{ pF} \quad (+1)$$

$$f_{H(IN)} = \frac{1}{2\pi \cdot 1209 \text{ p} \cdot 0.04783 \text{ k}} = 2.752 \text{ MHz} \quad (+1)$$

$R_s \parallel R_b'$   
 $= 1.520 \text{ k} \parallel 0.04938 \text{ k} = 0.04783 \text{ k} \quad (+1)$

$$C_{BC(OUT)} = 5.6 \left(1 - \frac{1}{-210.6}\right) \approx 5.6 \text{ pF} \quad (+1)$$

$$f_{H(OUT)} = \frac{1}{2\pi \cdot 5.6 \text{ p} \cdot 3.143 \text{ k}} = 9.042 \text{ MHz} \quad (+1)$$

$\downarrow$   
 $R_c'$

$$f_{H(IN)} \gg f_{H(OUT)}$$

$$\therefore f_H \sim 2.752 \text{ MHz} \quad (+1)$$

Compute the three LF cutoff frequencies and the approximate overall low-frequency cutoff,  $f_L$ .

$$R_{CE} = \frac{1}{g_m} \parallel R_E = \frac{1}{67m} \parallel 332 = \underline{14.28 \Omega} \quad (+1)$$

$$f_{CE} = \frac{1}{2\pi \cdot 14.28 \cdot 1000 \times 10^{-6}} = \underline{11.14 \text{ Hz}} \quad (+1)$$

$$R_{Cout} = R_L + (R_E \parallel r_o) = 10k + (4.75k \parallel 130.6k) \\ = 14.58k \quad (+1)$$

$$f_{Cout} = \frac{1}{2\pi \cdot 14.58k \cdot 10\mu} = \underline{1.091 \text{ Hz}} \quad (+1)$$

$$R_{Cin} = R_S + R_b' = .04938k + 1.520k = \underline{1.569k} \quad (+1)$$

$$f_{Cin} = \frac{1}{2\pi \cdot 1 \times 10^{-6} \cdot 1.569k} = \underline{101.4 \text{ Hz}} \quad (+1)$$

$$= \text{dominant pole; } f_L \approx \underline{101.4 \text{ Hz}} \quad (+1)$$