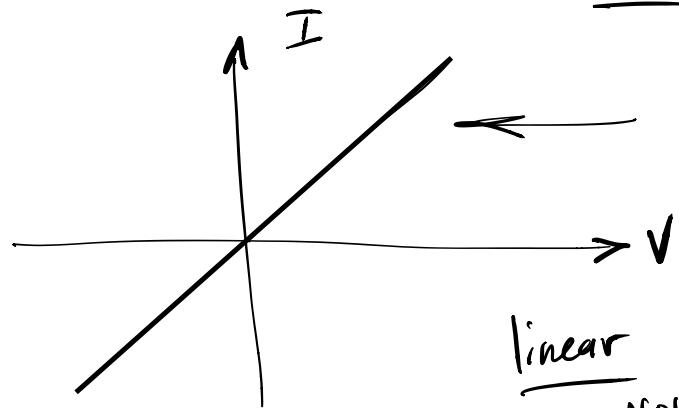


Non-Linear Devices


resistor :




$$\text{slope} = \frac{\Delta I}{\Delta V} = \frac{1}{R}$$

linear relationship between
voltage and current

diode :

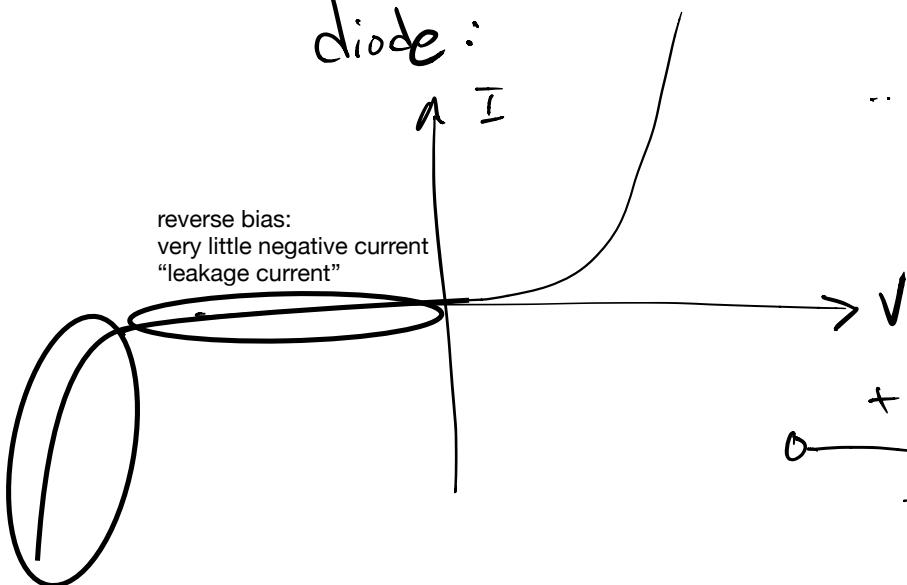

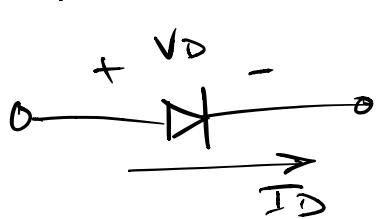- not just non-linear,
not much (ideally zero)
current at
negative voltages!



reverse break:
too much negative current

Conductors : easily pass current , low resistance

Ag Al Cu

insulators ($\alpha/k/a$ dielectrics) : high resistance

glass, plastic, rubber, etc..

Semiconductors : Unique place in between

elemental : Ge 
germanium

alloy : nichrome, brass

used in resistance wire
for wirewound resistors

- atomic structure of material determines
current flow properties !

• Silicon is very abundant on planet Earth
→ most important semiconducting material

• elemental Si has no free electrons and thus high
resistance

• "doping" is the addition of other chemicals
to change electronic characteristics


Si doped with boron \rightarrow p-type silicon

Si doped with phosphorus \rightarrow n-type silicon

pn junction : n-type and p-type sandwich

\rightarrow results in a silicon diode.

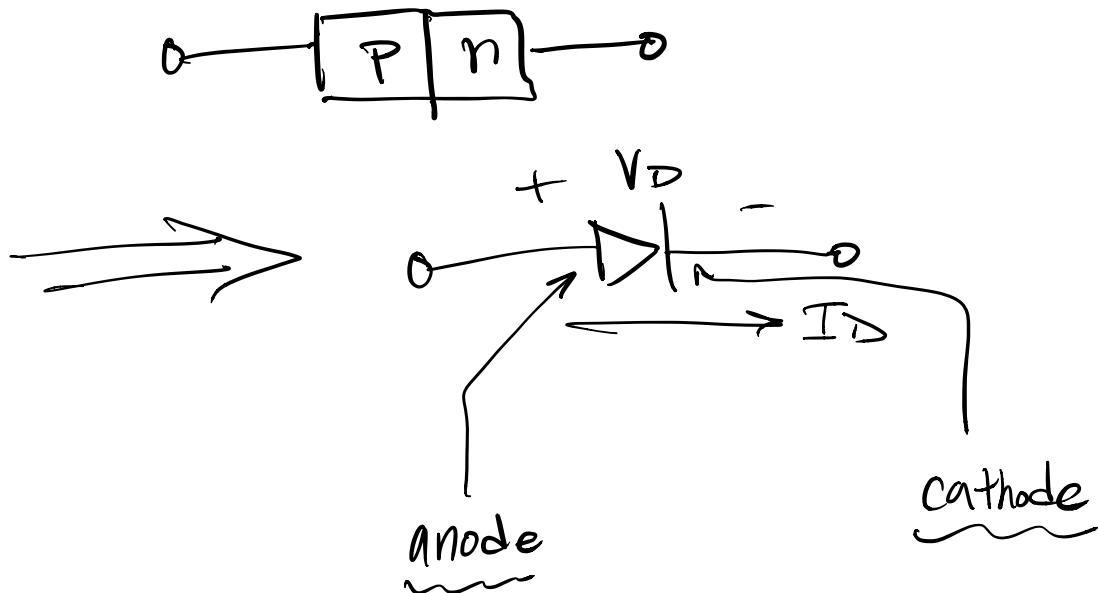pn junction: p stands for positive,
n stands for negative




.. if V_D is positive; i.e., the anode is more positive than the cathode, I_D will flow from anode to cathode and the diode is said to be

forward biased.

[electrons are flowing from cathode to anode]

.. if V_D is negative, i.e. anode negative with respect to cathode, very little current will flow [unless V_D becomes very negative] and the diode is reverse biased.

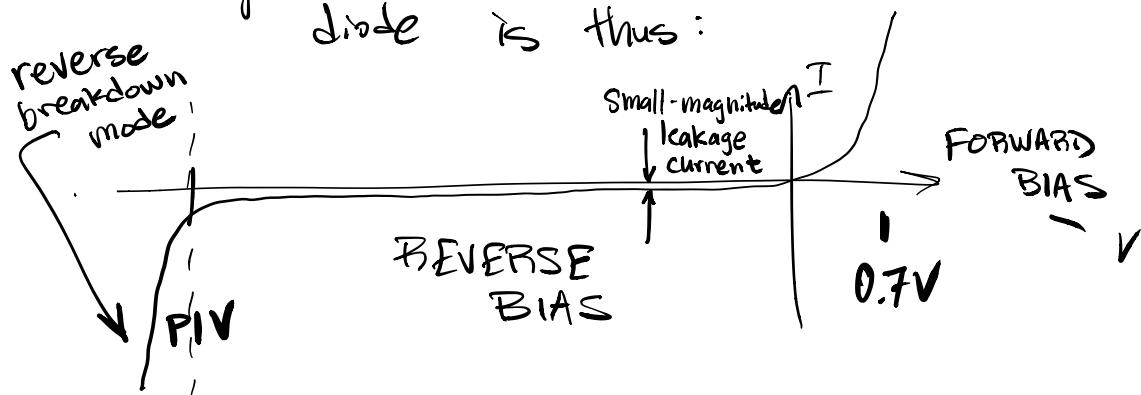.. voltage - to - current relationship for p-n silicon diode is thus:



-- note: for Si diode, current rapidly increases above $\sim 0.7\text{V}$ [① room temperature; smaller voltage as $T \uparrow$]


∴ We often use a Constant drop model

for forward-biased Si diode of

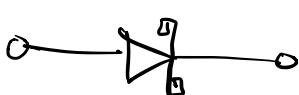0.7V_{min} .

- germanium diodes have lower V_D of $\sim 0.2\text{V}$
 - much more leakage current in reverse-bias
 - worse temperature coefficient

- Schottky diodes have $V_D \sim 0.15$ to 0.4V




but much more sensitive to reverse breakdown

→ low PIN rating
peak inverse voltage


↳ essentially maximum negative V_D before breakdown

- .. what are diodes good for?

ex: reverse-polarity protection

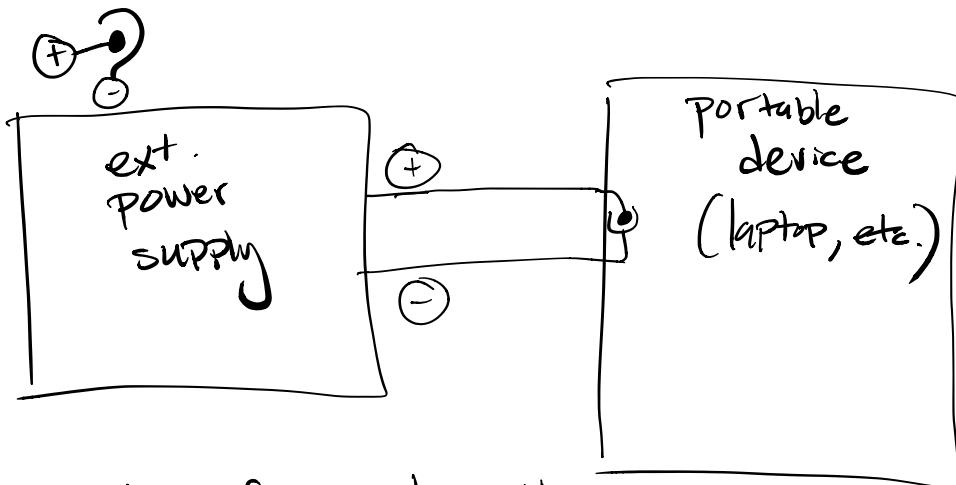


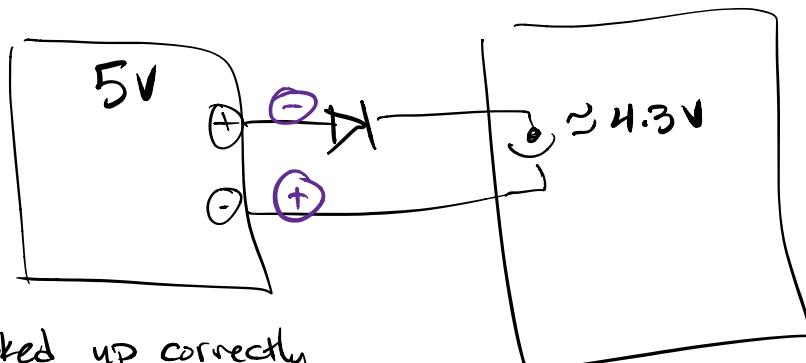- .. what if you have the wrong power supply and polarity is reversed? BAD things happen!
- .. use a diode to essentially prevent current flow if backward



- .. hooked up correctly, forward-biased; lose $\sim 0.7V$ if Si
- .. hooked up backwards, reverse biased; doesn't work

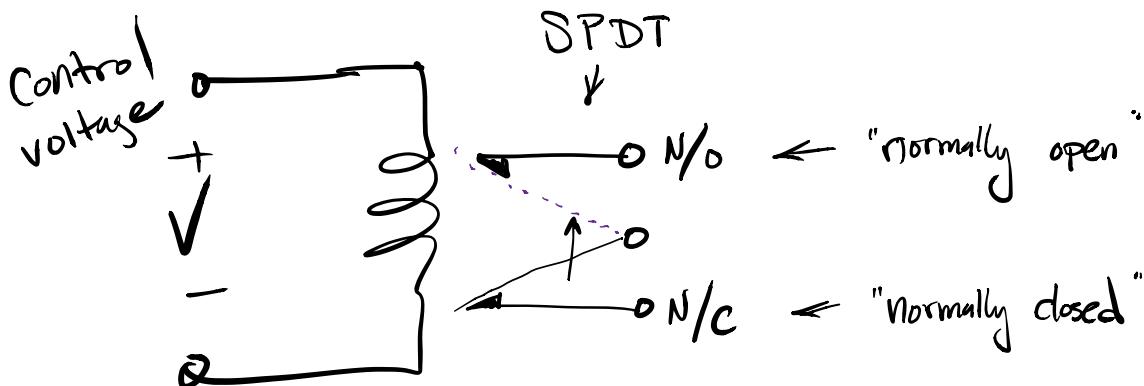
- transient suppressor (aka flyback diode)
- introduce electromechanical relay
- Uses solenoid to open or close switch contacts w/ external voltage





- solenoid is inductive
- switching voltage into coil \rightarrow no big deal
- switching OFF : interrupts current in inductor
 - \longrightarrow large back EMF spike

$$V_L(t) = L \frac{d_i(t)}{dt}$$

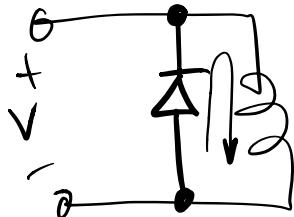• Solution: add a diode in parallel w/ relay coil \rightarrow clamps voltage to "0.7V" when switching off



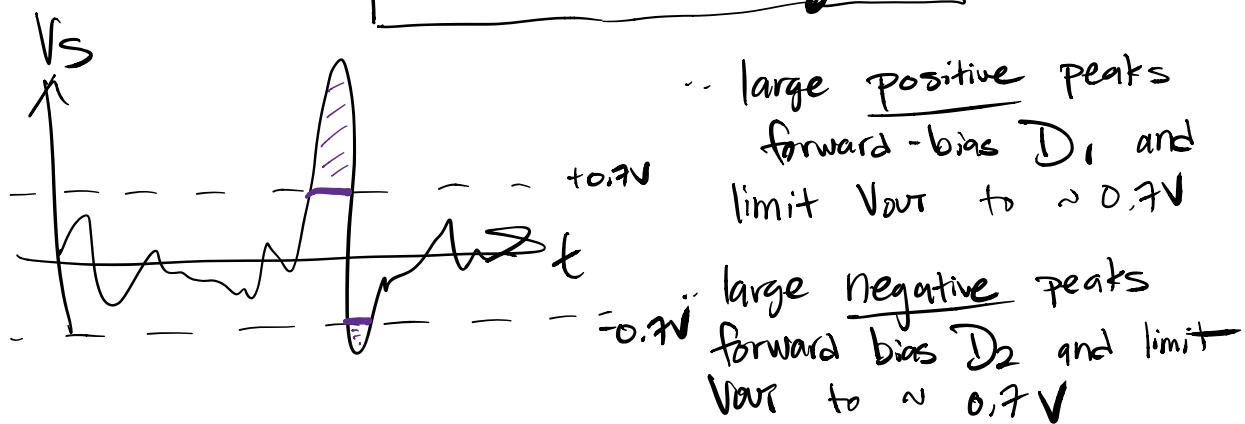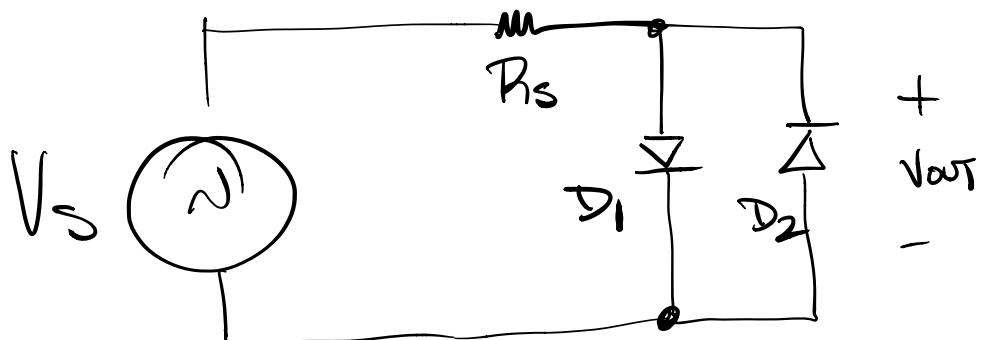
Ex: clipping circuit: What if we need some time-varying signal to be limited to a certain magnitude?



LED

"light emitting diode"

- forward-bias: 1.8 - 2.2 V,

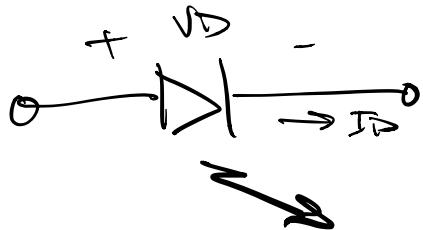

depending on color

\uparrow
determined
by
doping!

"cheap red LED" $\approx 1.8V$


- usually become visible @ $\approx 1mA$

"good brightness" @ 10 mA

max. current: 30 mA or so

- LEDs do have relatively low PIV rating and are sensitive to reverse breakdown

ex:

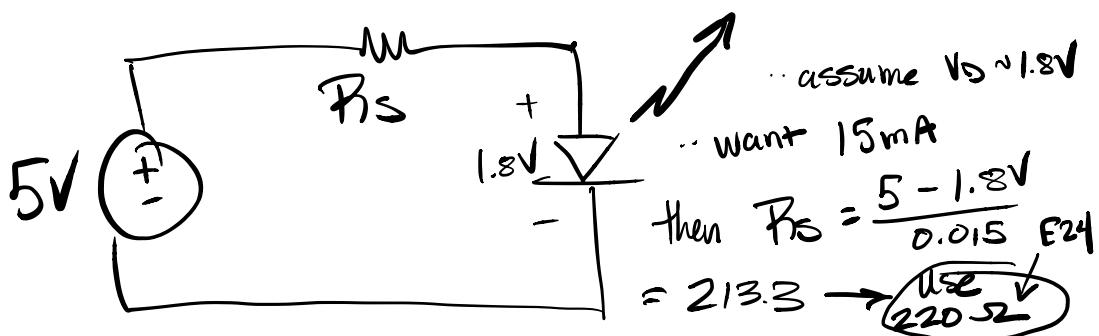

• check power in resistor :

$$P = I^2 R = 0.015^2 \cdot 220 = \underline{\underline{0.0495 \text{ W}}}$$

1-Watt resistors in lab just fine!