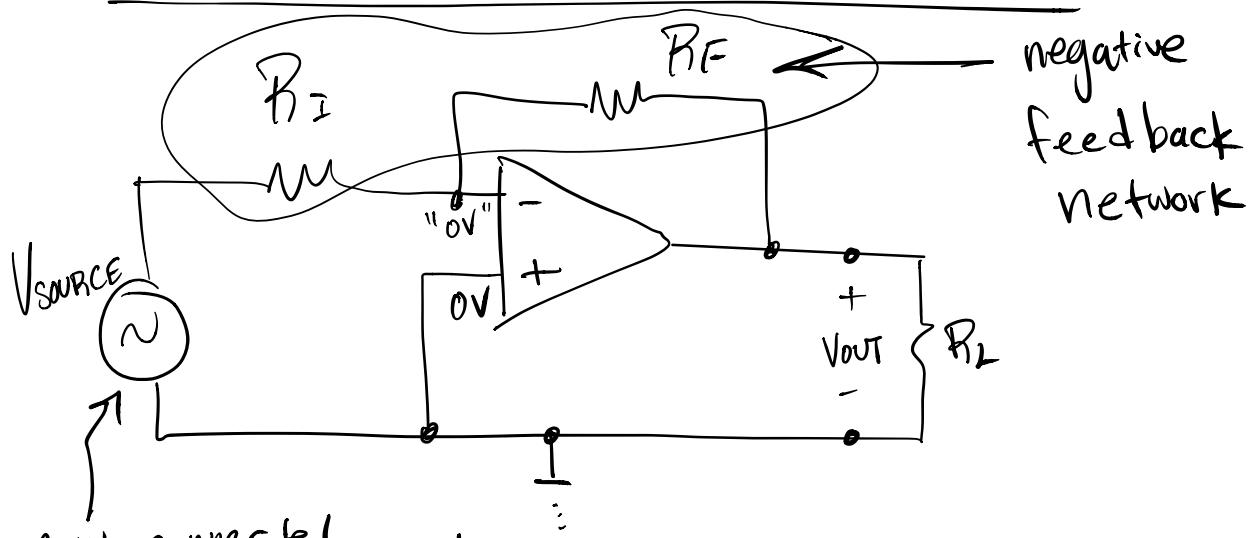


Inverting Voltage Amplifier



Now connected
to V_{in}^- , not V_{in}^+ !

- ideal op-amp : $V_{\text{in}}^+ = V_{\text{in}}^-$


- V_{in}^+ is connected to ground.

$$\therefore \underbrace{V_{\text{in}}^+}_{= 0} = 0$$

$$\rightarrow V_{\text{in}}^- = V_{\text{in}}^+ = \underbrace{0}_{= 0}$$

- V_{in}^- is at virtual ground.

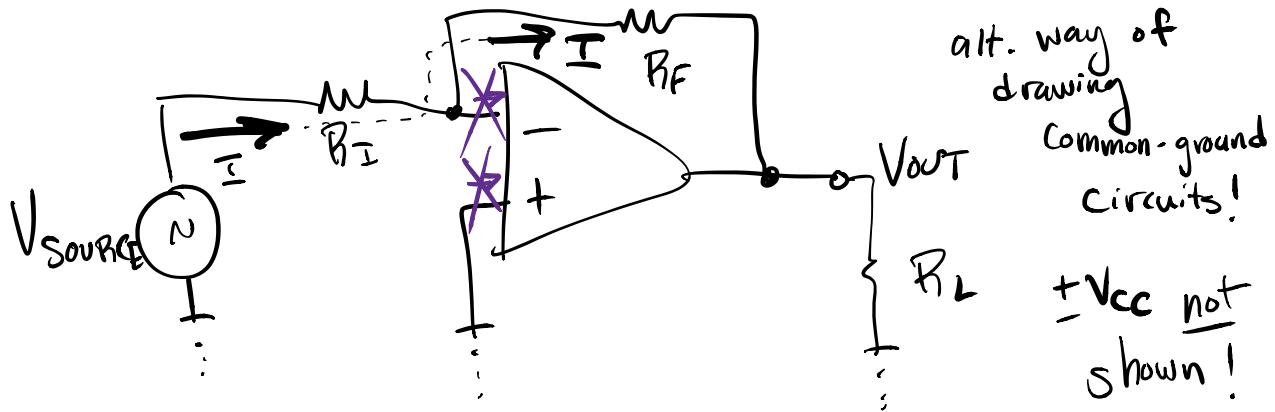- not directly connected to ground, but effectively at very close to OV!



- no input current to op-amp itself;
 $\therefore I$ must flow through R_F
 due to KCL!

$$I = \frac{V_{SOURCE} - 0}{R_I} \quad (\text{at input})$$

$$I = \frac{0 - V_{out}}{R_F} \quad (\text{through } R_F)$$

$$\frac{V_{SOURCE}}{R_I} = \frac{-V_{out}}{R_F}$$

$$\frac{V_{out}}{V_{SOURCE}} = -\frac{R_F}{R_I}$$

- So, once again, gain of circuit is determined by the ratio of two resistors; fantastic!
- Note: no "1 + " term, like non-inverting circuit; and there is a negative sign, so this circuit inverts like single-device amplifier we talked about first

ex: if $R_F = 100\text{k}\Omega$

$$R_I = 10\text{k}\Omega$$

$$\therefore \frac{V_{out}}{V_{source}} = -\frac{100\text{k}}{10\text{k}} = -10$$

or $20 \log_{10}(10)$

$$= 20 \text{ dB,}$$


inverting

· if $V_{\text{source}} = 1.2 \text{ V}$, then

$$V_{\text{out}} = -12 \text{ V}$$

· if $V_{\text{source}} = 30 \text{ mV RMS} @ 1 \text{ kHz}$, square wave

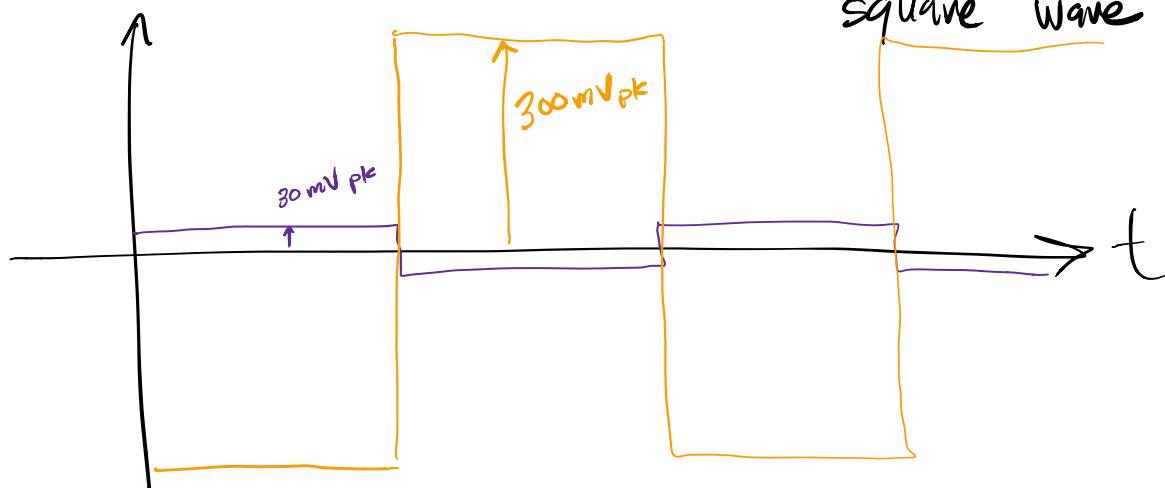then $V_{\text{out}} = 300 \text{ mV RMS} @ 1 \text{ kHz}$ inverted





remember : $\sqrt{\text{RMS}} = \sqrt{\text{pk}}$ for square wave !

also : unlike non-inverting amplifier, can achieve fractional gain if $R_F < R_I$

[non-inverting : $A_v \geq 1$]

practical circuit using $\mu\text{A}741$ op-amp
ca. 1968, still used

DIP8

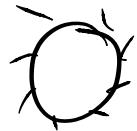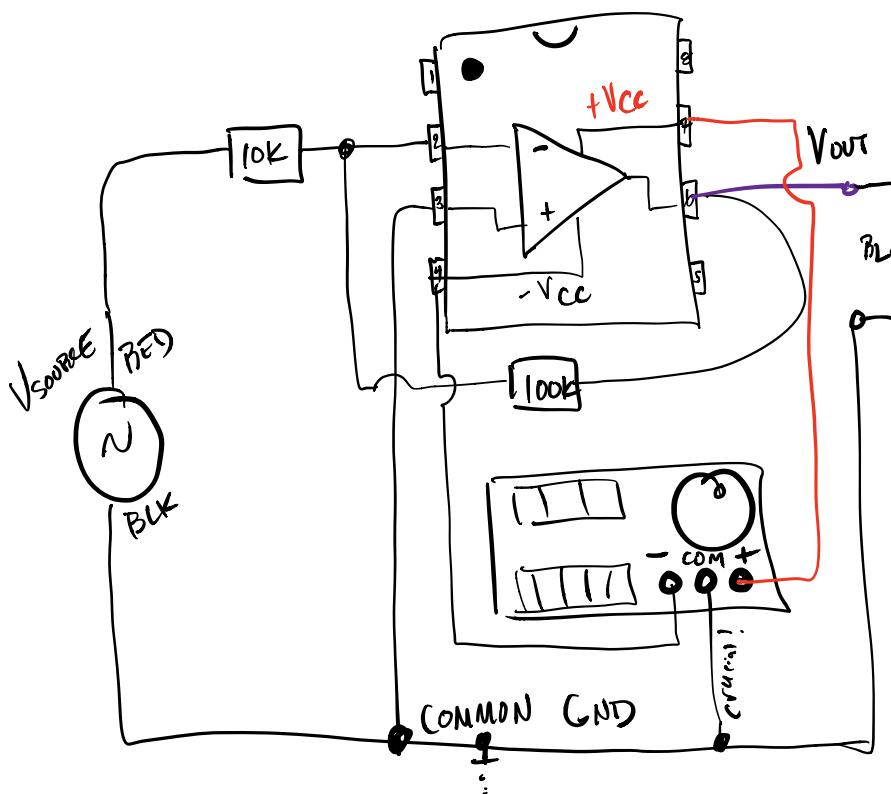

SMD package

good layout practice:
RF directly
between V_{out}
and V_{in^-} to
avoid instability

$\mu\text{A}741$: max. V_{cc} of $\pm 18\text{V}$

lab: $\pm 15\text{V}$

it turns out the magnitude of V_{cc} determines the maximum output voltage of circuit.

.. in general, for most practical op-amps:

$$V_{\text{out}}(\text{max.}) = \pm (V_{\text{cc}} - 2)$$

... so if $V_{\text{cc}} = \pm 15\text{V}$ [15V "rails"],

$$\underbrace{V_{\text{out}}(\text{max.})}_{=} = \pm 13\text{V}$$

ex: Non-inverting amplifier w/ $R_F = 33\text{k}\Omega$
 $R_I = 6.2\text{k}\Omega$

$$\frac{V_{\text{out}}}{V_{\text{source}}} = 1 + \frac{33k}{6.2k} = \underline{\underline{6.323}}$$

· let's input $V_{\text{source}} = 1\text{V}$ (D.C.)
then $V_{\text{out}} = 6.323\text{V}$

$\angle^+ V_{\text{out max}} (\text{fine})$

- What if $V_{\text{SOURCE}} = 5V$ (D.C.)

then $V_{\text{OUT}} = 5 \cdot 6.323 = 31.61V$

~~31.61V~~

$> +13V$

V_{OUT} will in fact saturate


at $V_{\text{OUT}} = 13V$. ~~(error)~~

ex: $V_{\text{SOURCE}} = 2V_{\text{RMS}}$ sine wave

$$V_{\text{SOURCE}}(\text{peak}) = 2 \cdot \sqrt{2} = 2.828 V_{\text{pk}}$$

then $V_{\text{OUT}} = 2.828 \cdot 6.323 = 17.88V$

~~17.88V~~

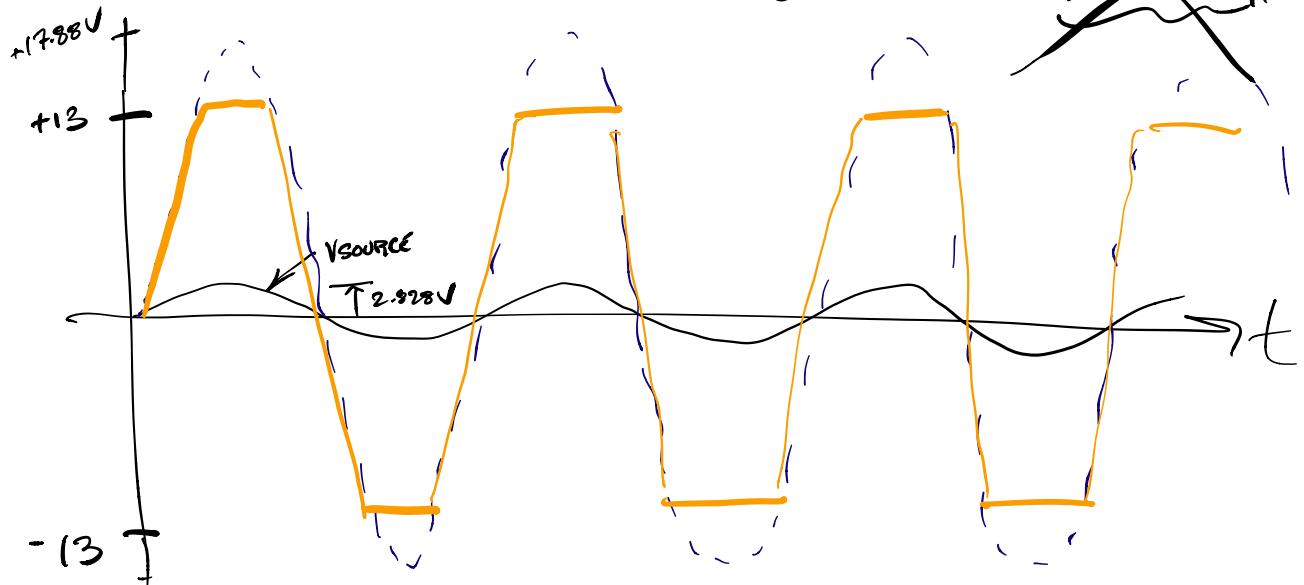


- Waveform would saturate every time it exceeds $\pm 13V$
 - called clipping of waveform
- in addition to output voltage limitations of practical op-amp circuits, real opamps also have finite current capability.

MA741 : $i_{out(max)} = \pm 25mA$

ex: inverting configuration, $R_F = 8.2k\Omega$
 $R_I = 1k\Omega$

$$\text{oo} \quad \frac{V_{out}}{V_{source}} = \frac{-R_F}{R_I} = \frac{-8.2k}{1k} = -8.2$$

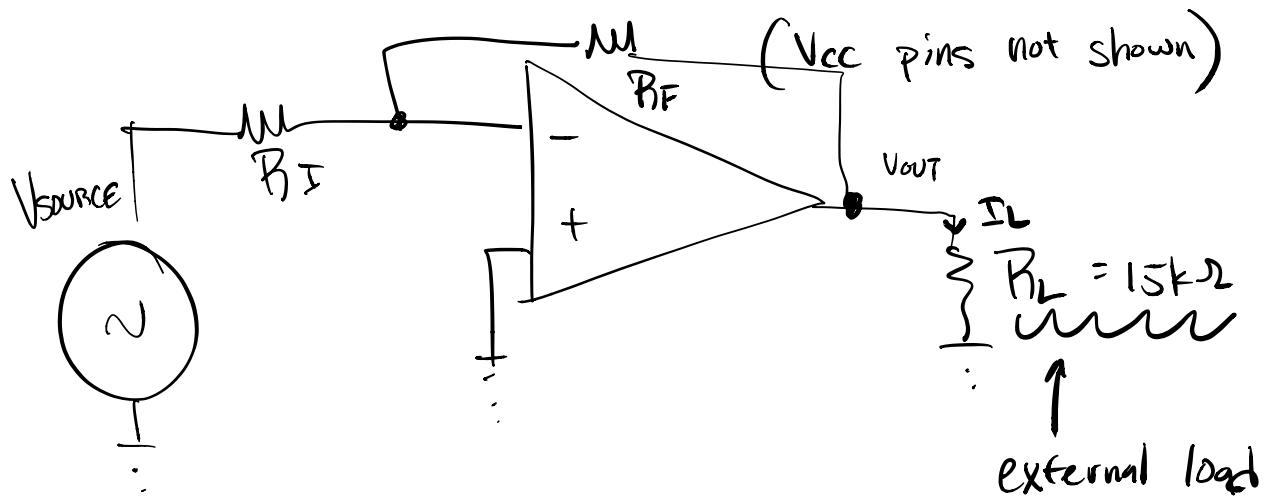- let's say $V_{source} = 1V$, $R_L = \underbrace{15k\Omega}$



$$V_{OUT} = 1V - 8.2 = -\underline{8.2V}$$

$$I_L = \frac{V_{OUT}}{R_L} = \frac{-8.2}{15k} = -0.5467 \text{ mA}$$

$$|-0.5467| < 25 \text{ mA} \quad \checkmark$$

∴ what if $R_L = 120\Omega$?

then $I_L = \frac{-8.2}{120} = -0.06833 \text{ A}$

or -68.33 mA

$$68.33 > 25 \text{ mA}$$

• op-amp will saturate at $I_L = 25 \text{ mA}$

actual V_{OUT} will be

$$-25 \text{ mA} \cdot 120 \Omega = -3 \text{ V} \\ (\text{error!})$$

• in general: small op-amps like
 $\underbrace{k\Omega}_{\text{range}}$ resistors

• also: op-amp must drive current in R_F !

• $k\Omega$ -range for R_F also good idea!

Homework: design op-amp circuit that will achieve

• gain of $\underbrace{36}_{\text{}}$

• determine max. V_{SOURCE} if $V_{\text{CC}} = \pm 12 \text{ V}$

• determine min. R_L if $I_{\text{out(max)}} = \pm 40 \text{ mA}$