


Homework: RLC High-pass

$$L = 2.2 \text{ mH}$$

$$R = 16\Omega$$

$$C = 3.3 \mu\text{F}$$

- sketch circuit, determine  $\omega_0$ ,  $f_0$ , and  $Q$ ,
- describe freq. response (i.e., Butterworth etc.),
- describe transient response (i.e., overdamped, etc..),
- determine  $H(\omega_0)$ ,  $H(2\omega_0)$ , and  $H(0.5\omega_0)$   
(Mag. in dB and phase),
- sketch  $|H(\omega)|$  and  $\angle H(\omega)$ .

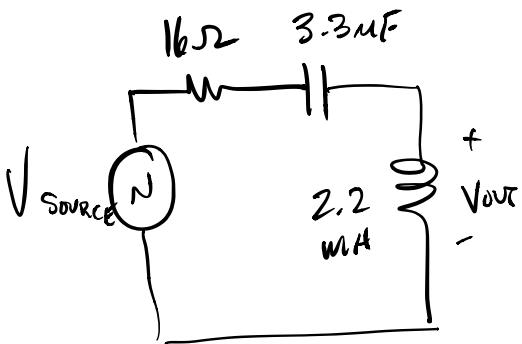

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2.2 \text{ m} \cdot 3.3 \mu\text{F}}} = 11.74 \text{ krad/s}$$

$$= 11.74 \text{ kHz}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{OR } \frac{\omega_0}{2\pi} \Rightarrow 1.868 \text{ kHz}$$

$$Q_{\text{series}} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{16} \sqrt{\frac{2.2 \text{ m}}{3.3 \mu\text{F}}} = 1.614$$

quite Underdamped in time domain!

Ringing and overshoot in transient response

$Q > 0.707 \Rightarrow \text{Chebyshev}$

$$|H(\omega_0)| \text{ (dB)} = 20 \log_{10} Q = 20 \log_{10} 1.614 \Rightarrow +4.2 \text{ dB } @ \omega_0$$

"+4 Chebychev" or whatever

$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + j\omega \frac{\omega_0}{Q} + \omega_0^2}$$

↑ 2nd-order HPF transfer function

$$H(2\omega_0) = \frac{(j \cdot 2\omega_0)^2}{(j \cdot 2\omega_0)^2 + j \cdot 2\omega_0 \frac{\omega_0}{Q} + \omega_0^2}$$

$$= \frac{j^2 \cdot 4\omega_0^2}{j^2 \cdot 4\omega_0^2 + j \cdot 2\frac{\omega_0^2}{Q} + \omega_0^2}$$

$$H(2\omega_0) = \frac{-4}{-4 + \frac{2j}{Q} + 1}$$

$$H(2\omega_0) = \frac{-j}{-3 + \frac{2j}{1.614}} \Rightarrow 1.232 \angle +22.44^\circ$$

A polar plot showing a point at magnitude 1.232 and phase angle +22.44°. The horizontal axis is labeled with a wavy line and an arrow pointing right. The vertical axis is labeled with a wavy line and an arrow pointing down.


$$H(0.5\omega_0) = \frac{(j \cdot 0.5\omega_0)^2}{(j \cdot 0.5\omega_0)^2 + j \cdot 0.5\omega_0 \cdot \frac{\omega_0}{Q} + \omega_0^2}$$

$$= \frac{-0.25 \cancel{\omega_0^2}}{-0.25 \cancel{\omega_0^2} + \frac{j 0.5 \cancel{\omega_0^2}}{Q} + \cancel{\omega_0^2}}$$

$$H(0.5\omega_0) = \frac{-0.25}{0.75 + \frac{j 0.5}{1.614}} \Rightarrow 0.309 \angle 157.56^\circ$$

A polar plot showing a point at magnitude 0.309 and phase angle 157.56°. The horizontal axis is labeled with a wavy line and an arrow pointing right. The vertical axis is labeled with a wavy line and an arrow pointing down.

We now have three data points with which to sketch  $|H(\omega)|$  and  $\angle H(\omega)$ !

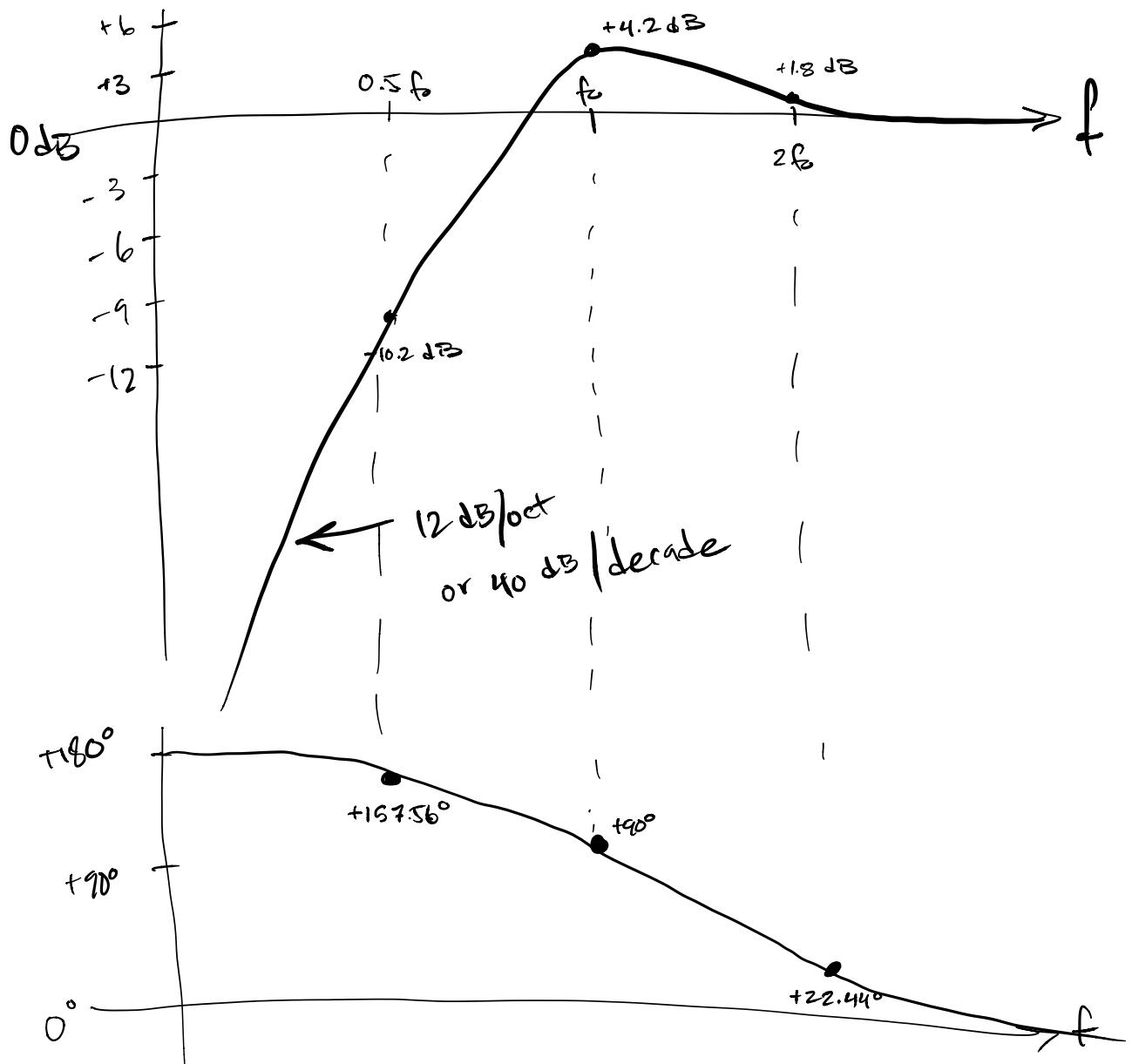

check this in LTSPICE !!!

homework: parallel RLC bandpass

$$L = 2.2 \text{ H} \quad C = 2.0 \text{ nF} \quad R = 47 \text{ k}\Omega$$

solution:

$$f_0 = 2.4 \text{ kHz}$$

$$Q_{\parallel} = R \sqrt{\frac{C}{L}} = \underline{1.486}$$

"underdamped" w/ ringing + overshoot

"+3.44 Chebychev"

- We know  $Q = \frac{f_0}{f_H - f_L}$

We also know  $f_0 = \sqrt{f_H f_L}$

$$\therefore f_H - f_L = \frac{f_0}{Q} = \frac{2400}{1.486} = \underline{1615 \text{ Hz}}$$

$$\rightarrow f_H = \underline{1615 + f_L}$$

$$f_H f_L = f_0^2 = 2400^2 = 5760000$$

$$\therefore f_L = \frac{5760000}{f_H} = \frac{5760000}{1615 + f_L}$$


$$\underline{f_L = 1725} \quad \therefore f_H = 1725 + 1615 = \underline{3340}$$

# Active Filters

- let's look at a classic series-RCL

Butterworth low-pass filter w/  $f_c = 10 \text{ Hz}$

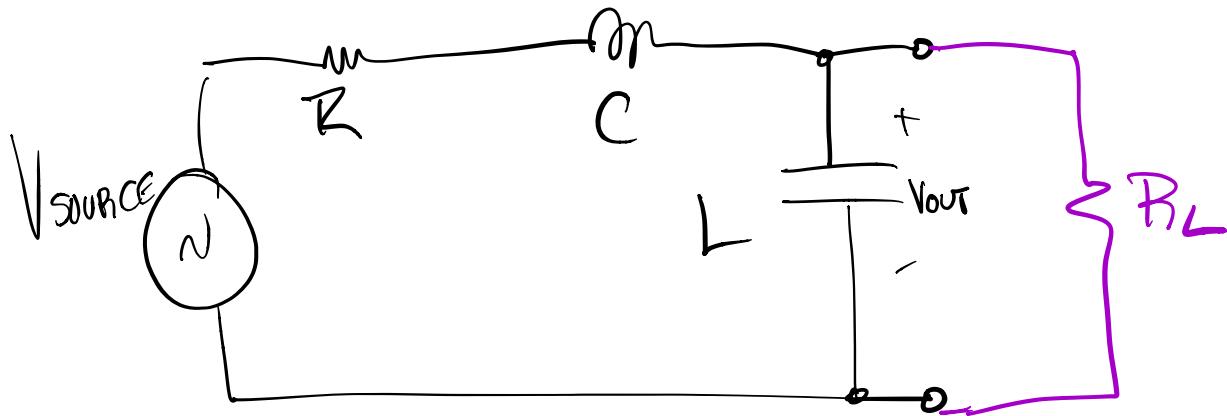$Q = 0.707$ ,  
flat magnitude  
response



PICK  $C = 1 \mu\text{F}$ ; then

$$Q_{\text{series}} = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow L = \frac{1}{\omega_0^2 C}$$


$$\text{then } L = \frac{1}{(2\pi \cdot 10)^2 \cdot 1 \times 10^{-6}} = \underbrace{253 \text{ H}}_{!!!}$$

- this is an alarmingly large value !!!

- big
- heavy
- expensive
- probably lots of winding resistance (mess up filter response) and stray capacitance (will introduce an entirely separate RLC circuit itself.)
- subsequent loading of the circuit makes it all worse!!! (scaling factor, Q needs recalculated, etc..)
- the solution: get rid of that inductor !!!
- in 1955, R.P. Sallen and E.L. Key developed a universal active filter algorithm in which many different filters may be developed by placing four impedances around a voltage amplifier in different configurations
  - original paper : pretty rough!

many implementations; we're going to discuss the
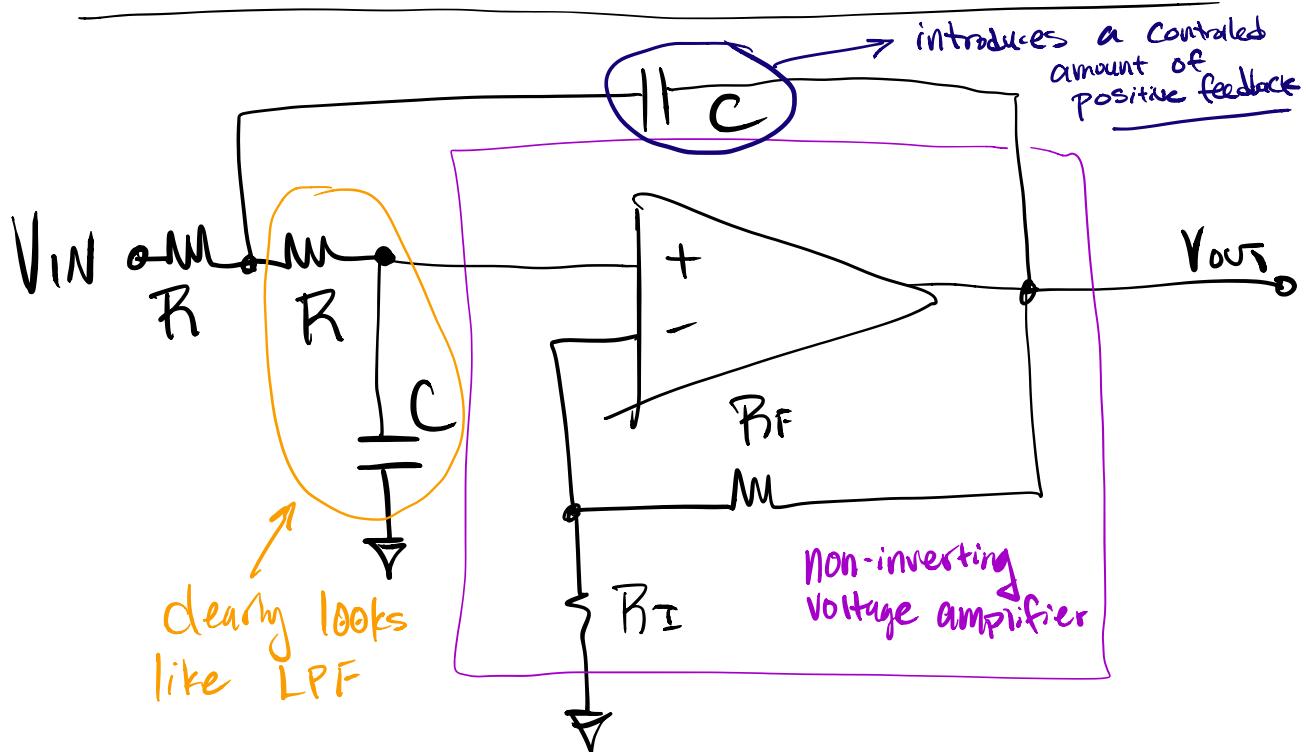
## Sallen-Key Equal-Component 2nd Order Low-Pass Filter



1.) Pick  $C$

2.) then  $R = \frac{1}{2\pi f_0 C}$  OR  $R = \frac{1}{\omega_0 C}$

3.) set  $R_F$  and  $R_I$  to the exact op-amp gain needed to achieve the desired  $Q$

.. for this circuit only:

$$A_v = 3 - \frac{1}{Q}$$

design active filter using the Sallen-Key Equal-Component configuration to realize a 2nd-order Butterworth LPF  
w/  $f_c = 10 \text{ Hz}$

1) pick  $C = 1 \mu\text{F}$

2) then  $R = \frac{1}{2\pi \cdot 1 \times 10^{-6} \cdot 10} = 15915.52$

nearest E96 value:

$$15.8 \text{ k}\Omega \quad 1\%$$


3.)  $A_v = 3 - \frac{1}{Q} = 3 - \frac{1}{0.707} = 1.586$

$\therefore 1.586 = 1 + \underbrace{\frac{R_F}{R_I}}_{\text{non-inverting!}} \Rightarrow$  sets midband gain  
to  $20 \log_{10} 1.586 \approx 4 \text{ dB}$

$$\frac{R_F}{R_I} = 0.586$$

Pick  $R_F = 10 \text{ k}\Omega 1\%$

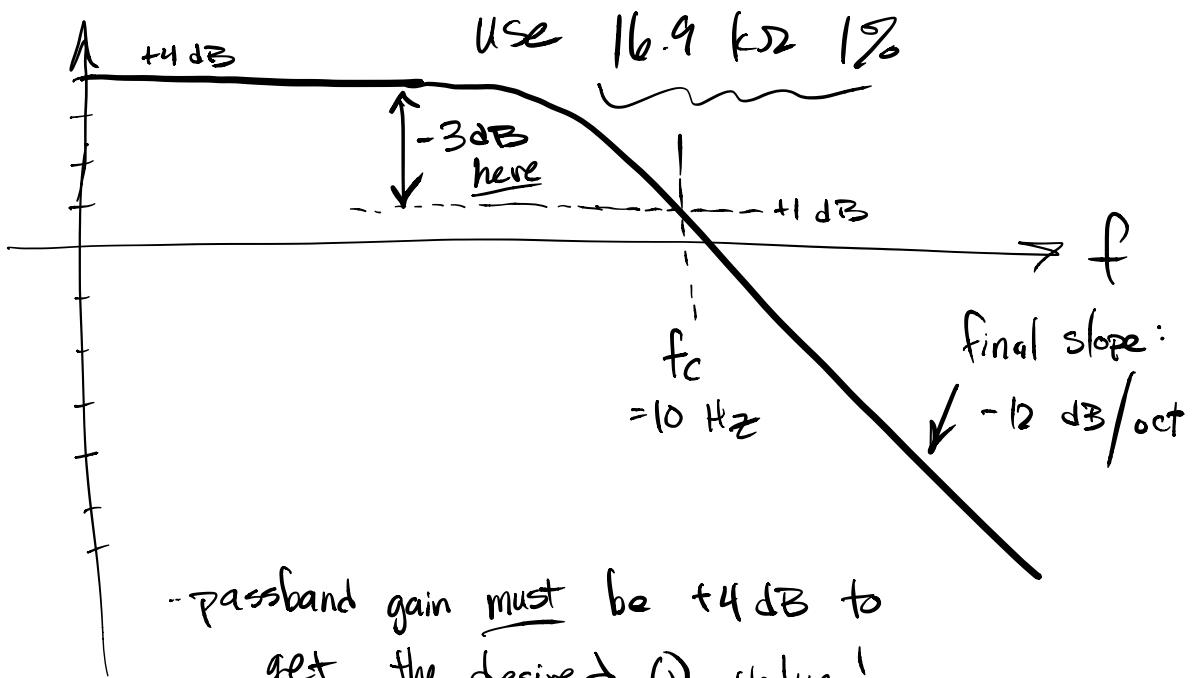then  $R_I = \frac{10k}{0.586} = 17.078 \text{ k}\Omega$



- Often, we specify filters with a  $-3 \text{ dB}$  corner frequency  $f_c$  that is different from  $f_0$ 
  - for Butterworth,  $|H(\omega)|$  is  $-3 \text{ dB}$  @  $f$ !

- for other Q-values, need frequency scaling factor (FSF) :

Bessel	1.2736
Butterworth	1.000
+3 dB Chebychev	0.7194

where  $FSF_{(\text{low-pass})} = \frac{f_o}{f_c}$

$$FSF_{(\text{high-pass})} = \frac{f_c}{f_o}$$

- ex: 2nd-order Bessel w/  $f_c = \underbrace{800 \text{ Hz}}$

$$FSF_{(\text{low-pass})} = \frac{f_o}{f_c} \Rightarrow f_o = 1.2736 \cdot 800 \\ = \underbrace{1019 \text{ Hz}}$$

- for Bessel, we know  $|H(j\omega)| = -4.77 \text{ dB}$

