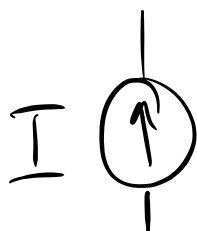


Constant-Current Sources and Sinks

- we have considered "perfect" voltage and current sources since our introduction to electricity!



- voltage sources are comparatively easy to visualize
 - battery: pretty good approximation!
 - regulated power supplies: maintain constant voltage over required range of load current
- but how do we do a current source?




-- ideal current source:


- constant current at any voltage, AC or DC
 - can dissipate any power
 - infinite Norton equivalent impedance
- no simple battery-like device approximates this!
 - but we can make them out of transistors.

Current Source vs. Current Sink

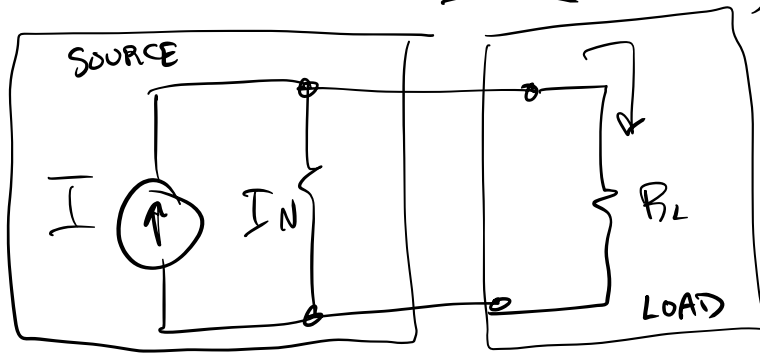-- current source supplies current; i.e., into a load, etc..




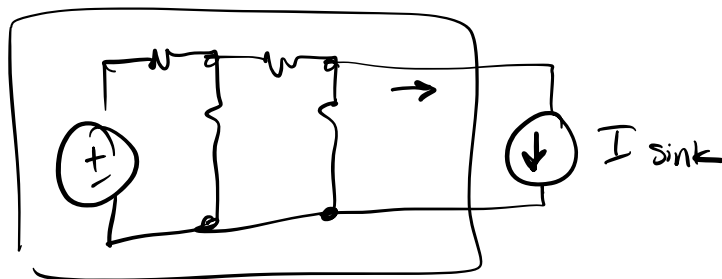-- current sink receives and maintains constant current, usually to ground (or $-V_{CC}$, etc.)



- we can design transistor circuits of either type
- main figure of merit for a current source/sink is its Norton or shunt impedance; we can also call this the output impedance or resistance

Basic BJT Current Sink

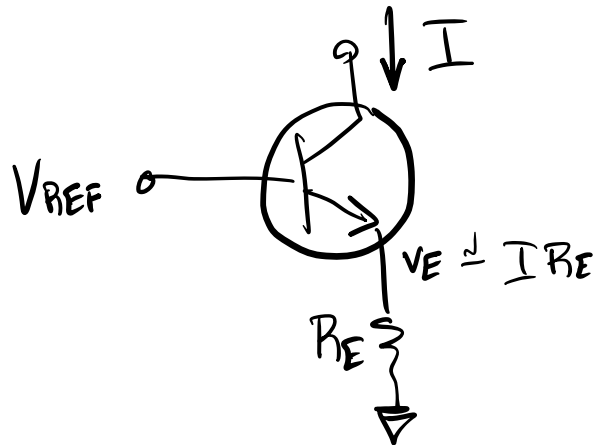

.. since we know $V_{BE} \approx 0.7V$ for Si transistors,
we can set V_{REF} to a known voltage;

$$\text{then } V_E = V_{REF} - 0.7 \approx I R_E$$

$$R_E = \frac{V_{REF} - 0.7}{I}$$

.. ex: $V_{REF} = 5V$, need $2mA$ current sink

$$\text{then } R_E = \frac{5 - 0.7}{2} = \underline{2.15 k\Omega}$$

.. coincidentally, this is an E96 1%
resistor value.

.. the output resistance of this current sink would ordinarily be $r_o = \frac{|V_A|}{I_C}$;

but in this case the unbypassed R_E , this increases to

$$\underline{r_{out} = \beta R_E + r_o}$$

ex: $V_A = 100V$, $\beta = 200$


$$r_o = \frac{100}{2} = \underline{50 \text{ k}\Omega}$$

$$\beta R_E = 200 \cdot 2.150 = \underline{430 \text{ k}\Omega}$$

thus, $r_{out} = 480 \text{ k}\Omega$ [pretty good!]

Basic BJT Current Source

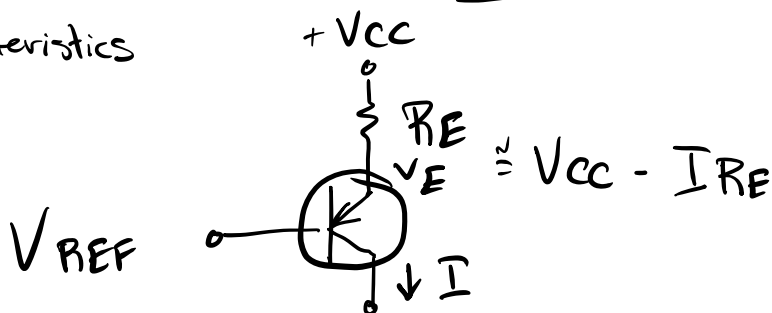.. we can just as easily use a PNP transistor and R_E to make current source with similar characteristics



.. since $V_{BE} \approx -0.7$ for PNP Si,

$$V_E = V_{REF} + 0.7 \approx V_{CC} - I R_E$$

$$\rightarrow \boxed{R_E = \frac{V_{CC} - (V_{REF} + 0.7)}{I}}$$

.. ex: $V_{REF} = 5V$, $I = 2mA$, $V_{CC} = 12V$:

$$R_E = \frac{12 - (5 + 0.7)}{2} = \underline{3.15 k\Omega}$$


use 3.16 k Ω 1%

$$r_{out} = \beta R_E + r_o$$

$$= 200 \cdot 3.16 + 50k$$

$$\underline{r_{out} = 682 k\Omega} \quad (\text{nice!})$$

Basic BJT Current Mirror

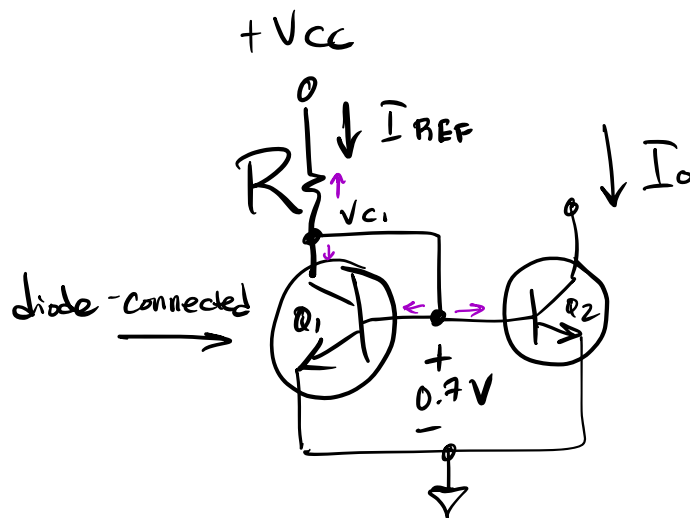

~ great importance in integrated circuit design!

.. we know $V_{BE} \sim 0.7V$; then with both emitters grounded,

$$\underline{V_{B1} = V_{B2} = V_{c1} = 0.7}$$

$$\underline{I_{REF} = \frac{V_{cc} - 0.7}{R}}$$

.. to determine I_O , use KCL @ V_{c1} .

$$-I_{REF} + I_{c1} + I_{B1} + I_{B2} = 0$$

.. assuming transistors are perfectly matched and operating at the same temperature, $I_{B1} = I_{B2} = I_B$
 $I_{c1} = I_{c2} = I_C$

$$\begin{aligned} \text{then } I_{REF} &= I_C + 2 I_B \\ &= I_C + \frac{2 I_C}{\beta} \end{aligned}$$

$$I_{REF} = I_C \left(1 + \frac{2}{\beta} \right)$$

.. the output current I_O is then

$$I_O = I_{C2} = I_C$$

$$\frac{I_O}{I_{REF}} = \frac{I_C}{I_C \left(1 + \frac{2}{\beta} \right)} = \frac{1}{1 + \frac{2}{\beta}}$$

.. if $\beta = 200$, then

$$\frac{I_O}{I_{REF}} = \frac{1}{1 + \frac{2}{200}} = \underline{0.9901}$$

✓ we don't like any dependence on β !

$$\text{or } I_O = 0.9901 I_{REF}$$

.. output resistance of basic BJT current mirror


$$\text{is } r_o = \frac{|V_A|}{I_O}$$

if $V_A = 100V$, $I_O = 2mA$,

$$r_o = \frac{100}{2} = 50k\Omega \text{ (not great!)}$$

Wilson Current Mirror

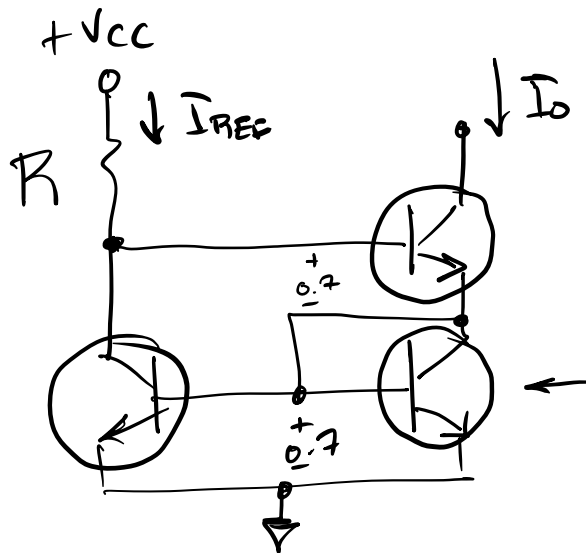- .. strives to solve both the $\frac{I_o}{I_{REF}}$ issue and poor r_{out} :



- .. we now have two V_{BE} drops between ground and

$$V_{C1} = V_{B2} ; \text{ thus,}$$

$$I_{REF} = \frac{V_{CC} - 2 \cdot 0.7}{R}$$

$$\rightarrow R = \frac{V_{CC} - 2 \cdot 0.7}{I_{REF}}$$

- .. we can perform similar analysis as the basic BJT current mirror to show that

$$I_o = I_{REF} \left(\frac{1}{1 + \frac{2}{\beta^2}} \right)$$

and $r_{out} = \frac{\beta}{2} r_o$

~ thus, if $\beta = 200$ and $r_o = 50k\Omega$,

$$I_o = I_{REF} \left(\frac{1}{1 + \frac{2}{200^2}} \right) = .99995 I_{REF}$$

$$r_{out} = \frac{\beta}{2} \cdot r_o$$


$$= \frac{200}{2} \cdot 50k = \underline{\underline{5M\Omega}} \text{ (really good!)}$$

for $I_o = 2mA$ and $V_{CC} = +12V$,

$$R = \frac{12 - 2 \cdot 0.7}{2} = 5.3k\Omega$$

use $5.36k, 1\%$

MOSFET Current Mirror

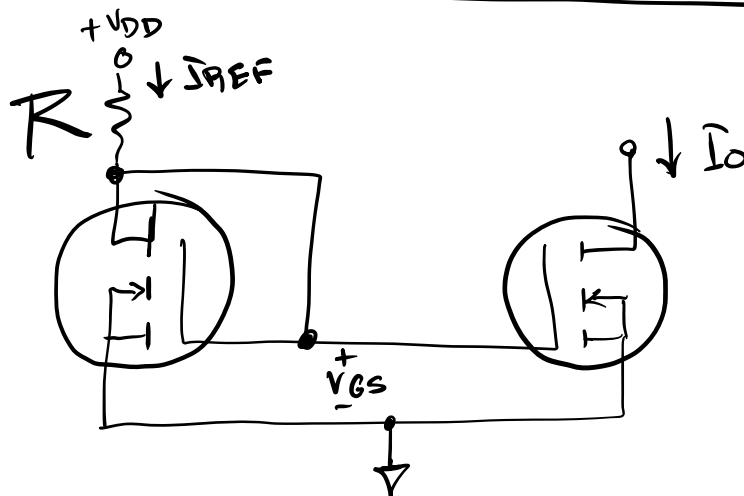

$$I_o = I_{REF} = \frac{V_{DD} - V_{GS}}{R} \rightarrow R = \frac{V_{DD} - V_{GS}}{I_o}$$

$r_{out} = r_o$ (not great)




-- we can use $I_D = K (V_{GS} - V_t)^2$ to determine V_{GS} for desired I_D

-- we need to improve that route!

MOSFET Cascode Current Mirror

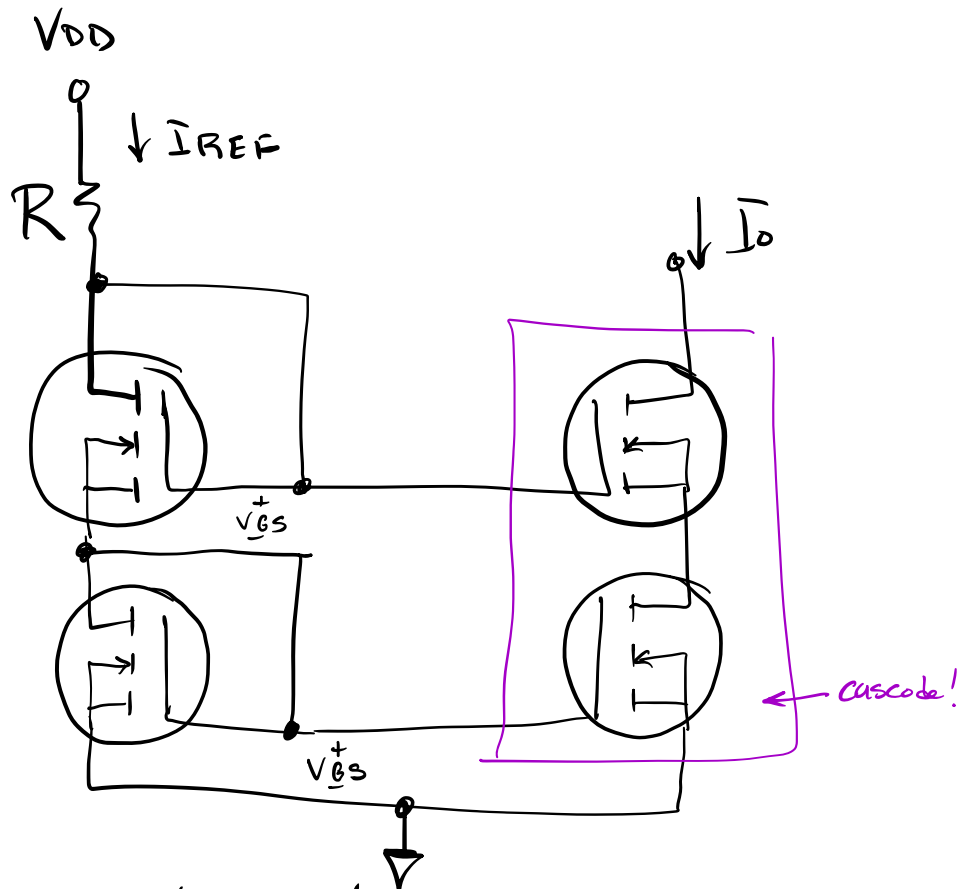- even better than Wilson MOSFET Current Mirror!



$$I_O = I_{REF} = \frac{V_{DD} - 2V_{GS}}{R} \rightarrow R = \frac{V_{DD} - 2V_{GS}}{I_O}$$

.. recall that the basic BJT current sink had an unbypassed R_E , which increased r_{out} by βR_E

.. now we have another MOSFET's r_o , which increases r_{out} much more:

$$\underline{r_{out} = g_m r_o^2}$$

ex: $V_{DD} = 24V$, $I_D = 2mA$, $r_o = 50k\Omega$

MOSFET: $K = 10 mA/V^2$, $V_t = 1.2V$

$$I_D = K (V_{GS} - V_t)^2$$

$$\rightarrow V_{GS} = \sqrt{\frac{I_D}{K}} + V_t$$

$$= \sqrt{\frac{2}{10}} + 1.2$$

$$\underline{V_{GS} = 1.647 V}$$

$$\text{then } R = \frac{V_{DD} - 2V_{GS}}{I_D} = \frac{24 - 2 \cdot 1.647}{2}$$

$$R = 10.353k\Omega, \text{ use } \underline{10.5k\ 1\%}$$

.. to get r_{out} , need g_m :

$$g_m = 2\sqrt{K I_D}$$
$$= 2\sqrt{10 \cdot 2}$$

$$g_m = 8.944 \text{ mA/V}$$

$$r_{out} = g_m r_o^2$$

just looking at multipliers!

$$= 8.944 \cancel{\text{m}} \cdot 50\cancel{\text{k}}^2$$
$$= 22360\text{k}$$

or $r_{out} = 22.36 \text{ M}\Omega$ ← get outta here!!!