
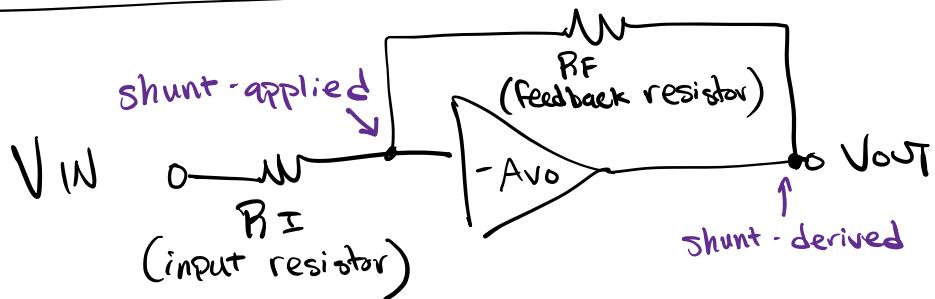


Shunt/Shunt Feedback Voltage Amplifier

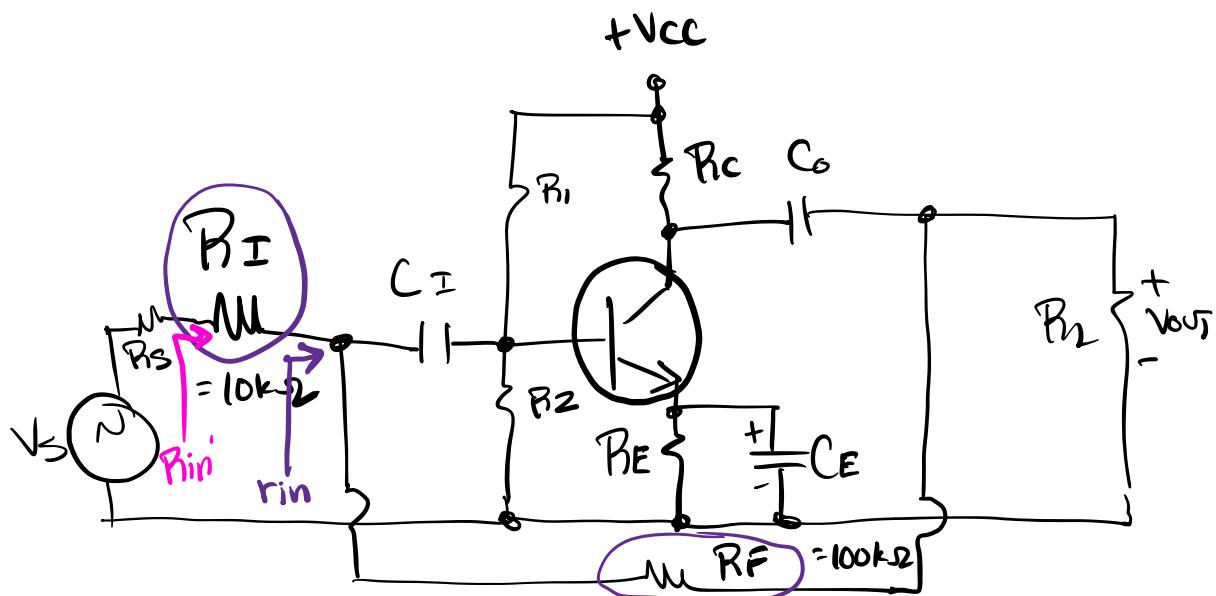

- We can apply a shunt-derived / shunt-applied external feedback loop around any inverting amplifier
- thus, it works with single-transistor amplifiers (common-emitter, common-source), cascodes, etc.

ex: common-emitter example



- the β network for this amplifier is the ratio of input and output resistors;
$$\boxed{\beta = \frac{R_I}{R_F}}$$
- recall from our analysis that the CE amplifier has an A_{v2} of -271.5 ; thus, $\underbrace{A_{v0} = 271.5}_{\text{(inverting)}}$
- the closed loop gain, using the feedback equation, is:

$$A_v = \frac{-A_{v0}}{1 + \beta A_{v0}} = \frac{-A_{v0}}{1 + \frac{R_I}{R_F} \cdot A_{v0}}$$

$$A_v = \frac{-271.5}{1 + \frac{10k}{100k} \cdot 271.5} = \underline{-9.645}$$

or 19.68 dB
(inverting)

- Note that if βA_{v0} is a sufficiently large value,
 $1 + \beta A_{v0} \approx \beta A_{v0}$

$$A_v \approx \frac{-A_{v0}}{\cancel{\beta A_{v0}}} = -\frac{1}{\beta} = \frac{-1}{R_I/R_F}$$

$$\boxed{A_v \approx -\frac{R_F}{R_I}}$$

Look familiar?
(inverting op-amp equation!)

- Using the approximation:

$$A_v \approx \frac{-100k}{10k} = -10 \text{ or } 20 \text{ dB}$$

(inverting)

- close enough? yes!!!

- Note that if $R_F = R_I$, the gain is approximately -1;

- thus, it can be a unity-gain inverter and
in the vacuum tube era it was commonly
referred to as an anode follower

[rather than cathode follower, analogous to
emitter/source follower]

→ Charles Boegli: greatly expanded
on this ca. early 60's

Output Resistance of Shunt/Shunt Amplifier

- CE output resistance ($R_{c\parallel r_o} \approx R_c$) will be reduced by shunt-derived feedback to:

$$R_{out}' = \frac{R_{out}}{1 + \beta A_{vo}}$$

\leftarrow denominator of feedback equation

$$R_{out} = \frac{4.185k}{1 + \frac{10k}{100k} \cdot 271.5} = 0.1487k\Omega$$


← check that lecture!

or 148.7Ω


- usefully low for driving $k\Omega$ -range loads and cable capacitance

Input Resistance of Shunt/Shunt Amplifier

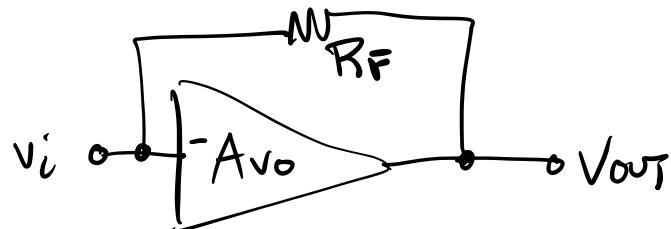- this is a bit trickier to analyze!
- first, consider the effect of R_F on the impedance of the input of the amplifier:



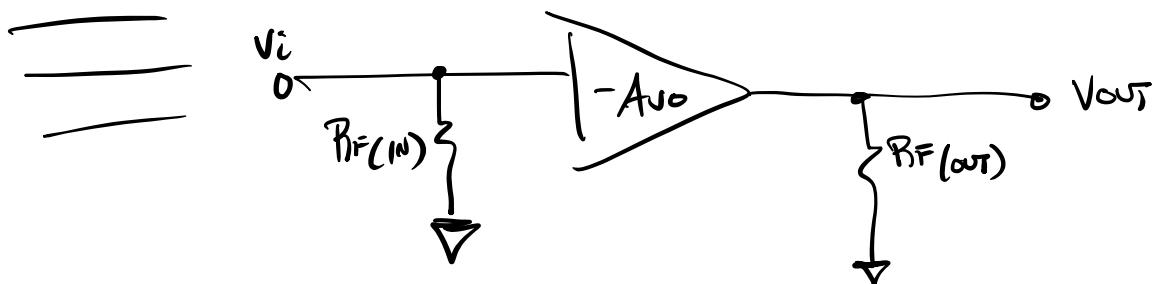- We would like to determine equivalent shunt impedances at the input and output terminals



- that's right, it's Miller Time!
- We already know $R_{IF(IN)} = \frac{R_F}{1 - A_v}$

$$R_{IF(OUT)} = \frac{R_F}{1 - \frac{1}{A_v}}$$


$$R_{IF(IN)} = \frac{100k}{1 - (-271.5)} = 0.3670 \text{ k}\Omega$$

or 367 Ω

- this is a quite low value that reinforces the notion that shunt-applied negative feedback lowers input resistance and creates current input [ideal ammeter: short]

$$R_{IF(OUT)} > \frac{100k}{1 - \frac{1}{-271.5}} \approx 100k \quad (\text{treat like output load})$$

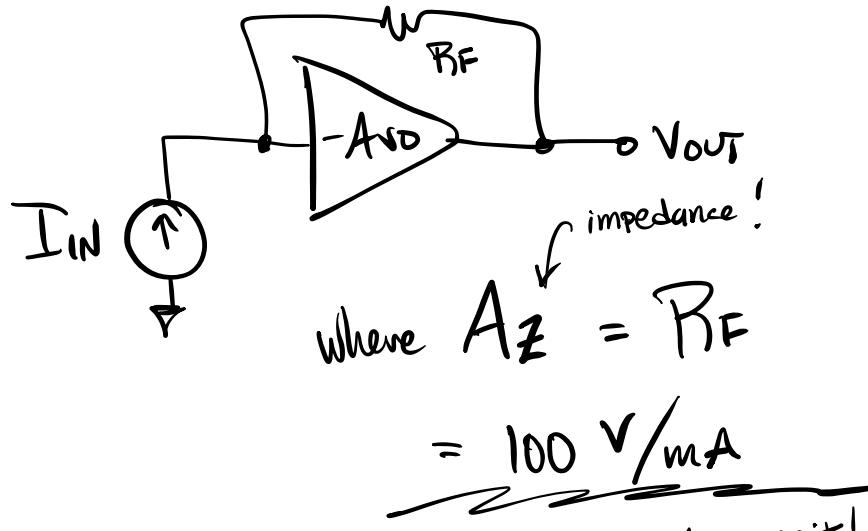- very high open-loop gain will make $R_{IF(IN)}$ even lower \rightarrow virtual ground
- in fact, the feedback transimpedance amplifier omits R_I and is used as a Current-to-voltage converter



- .. back to the shunt/shunt voltage amplifier, the net input (shunt) resistance is:-

$$r_{in} = R_F \parallel r_{in}$$

$\hookrightarrow R_1 \parallel R_2 \parallel r_b$ for CE

$$= 0.367k \parallel 1.735k = \underbrace{0.3029\text{ k}\Omega}_{}$$

- .. the input resistance of the whole amplifier, as seen by V_s , is thus:-

$$r_{in}' = r_{in} + R_I$$

.. if $R_I \ggg r_{in}$,

$$r_{in}' \approx R_I$$

- this example: $\underline{R_{in} \approx 10\text{k}\Omega}$

.. Not great, but not unusable for many applications

High-Frequency Response of Shunt/Shunt Amplifier

- the net HF input capacitance is computed the usual way; in this example,

$$C_{BE} + C_{BC(\text{IN})} = \underbrace{1102 \text{ pF}}_{\substack{\uparrow \\ \text{Miller Time!}}}$$


- this forms a low-pass filter with $R_I \parallel r_{in}$
- Since $R_I \ggg r_{in}$, we can neglect R_I (and R_S)

$$\begin{aligned} \text{thus, } f_{H(\text{IN})} &\approx \frac{1}{2\pi \cdot (C_{BE} + C_{BC(\text{IN})}) \cdot r_{in}} \\ &= \frac{1}{2\pi \cdot 1102 \times 10^{-12} \cdot 302.9} \\ f_{H(\text{IN})} &= 476.8 \text{ kHz} \end{aligned}$$

- .. note: compared to open-loop bandwidth of 2.97 MHz,
high-frequency response is actually worse,
despite the application of negative feedback!
- .. Why ??
- .. open-loop $f_{H(1N)}$ assumed $R_S = 50\Omega$ in parallel
with $R_b' = 1.735 k\Omega$
- .. now response is dominated by $r_{in} = \frac{R_F}{1 - A_V}$
- .. we can reduce R_F to get a lower r_{in} ,
extending bandwidth; but then to maintain
the same B and thus overall gain, we'd
have to also lower R_I , lowering r_{in}' !
- .. classic engineering tradeoff !!!

Low-Frequency Response of Shunt/Shunt

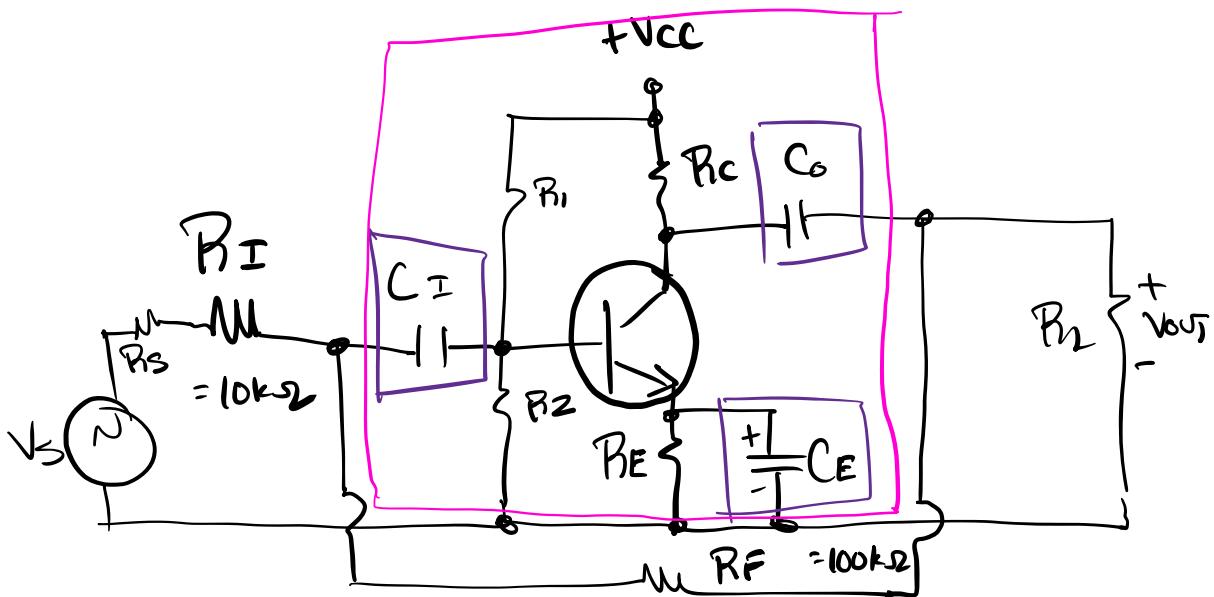- .. this is also a bit tricky to analyze!




- because C_I , C_o , and C_E are all inside the negative feedback loop, the final low-frequency cutoff f_L is subject to negative feedback and will be lowered by $1 + \beta A_v$ (good!)
- but since we have three low-frequency poles inside a negative feedback loop, we are likely to have problems
 - each pole has a max. phase shift of $+90^\circ$
[1st-order high-pass filter!]
 - two poles inside a negative feedback loop will approach $+180^\circ$, which is equivalent to a polarity inversion

- this is starting to turn negative feedback into positive feedback (oscillator!)
- three poles approaches $+270^\circ$, almost certain to cause LF instability

Mitigation strategies :

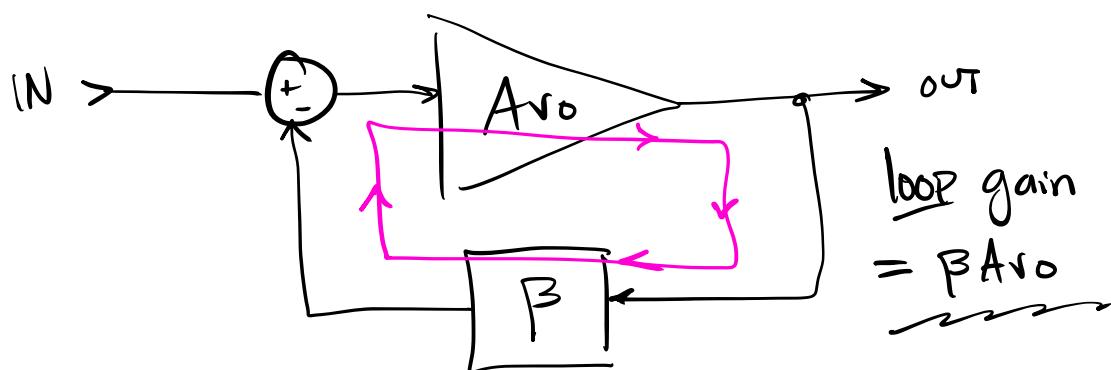1.) Spacing LF poles

- we can ensure LF stability if the two most dominant poles are spaced apart by the loop gain.
 \hookrightarrow highest f




- in this amp, loop gain $= \frac{R_F}{R_I} \cdot A_{vo}$
 $= \frac{1}{10} \cdot 271.5 = \underline{\underline{27.15}}$

- thus, if the pole caused by C_o was 1 Hz,
we could make the pole caused by C_E 27.15 Hz,
and the pole at the input $\lll 1 \text{ Hz}$
(so the C_o and C_E poles dominate)

- Could mean awkward component values, but feasible

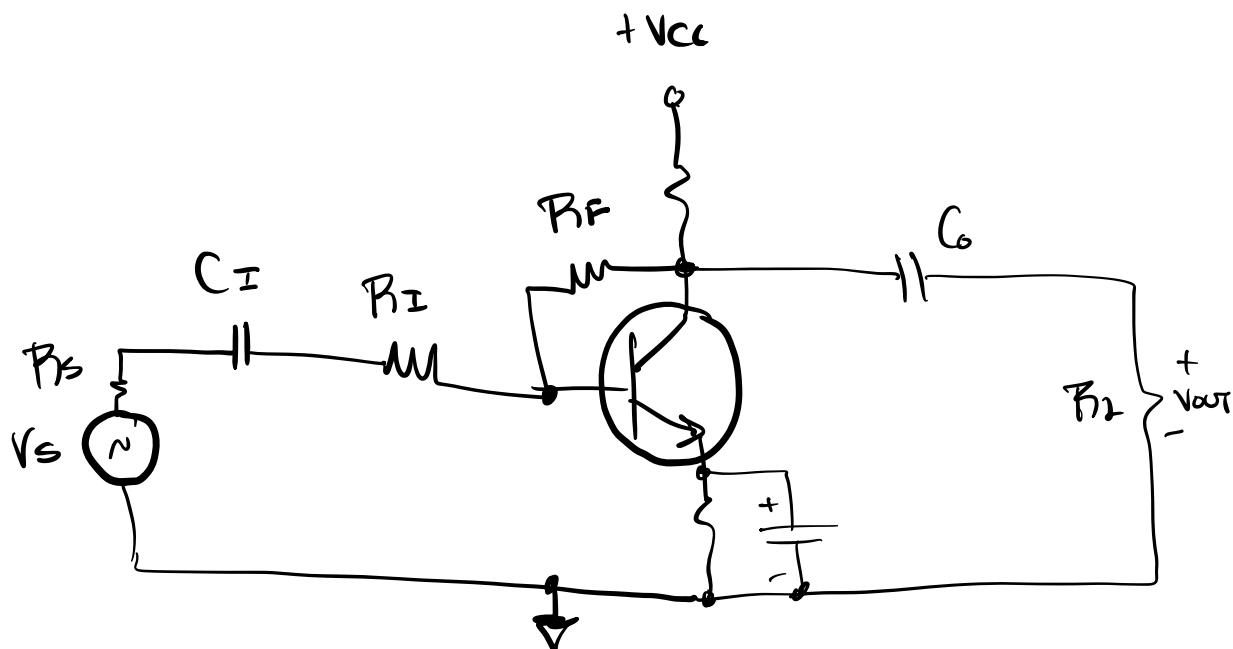2) reconfigure negative feedback loop to not include all three caps!



- Note that R_F has replaced R_I in the bias network.
So R_2 will probably need to be recomputed for
correct bias!

Now only CE is inside the feedback loop;
guaranteed to be stable, and its $f_L(CE)$
 is reduced (a lot!) by feedback

- tradeoff: C_I and C_o are not subject to
 negative feedback

~ another engineering tradeoff!

- this does simplify some computations:

$$f_{L(IN)} \approx \frac{1}{2\pi \cdot C_I \cdot R_I}$$

↳ assuming $R_{in} \ll R_I$;
 "virtual ground"

$$= \frac{1}{2\pi \cdot 1 \times 10^{-6} \cdot 10k} = \underbrace{15.92 \text{ Hz}}$$

(better than 89 Hz!)

$$f_{L(OUT)} \approx \frac{1}{2\pi \cdot C_o \cdot R_L}$$

↳ assumes $R_L \ll R_{out}$ due
 to neg. feedback

$$= \frac{1}{2\pi \cdot 10 \times 10^{-6} \cdot 10k} = \underbrace{1.592 \text{ Hz}}$$

$f_L(CE)$ was previously determined to be 14.6 Hz

this is reduced by feedback to:

$$f_L(CE) = \frac{f_L(CE)}{1 + \beta A_{v0}} = \frac{14.6}{1 + \frac{10k}{10k} \cdot 271.5}$$
$$= \underbrace{0.5187 \text{ Hz}}$$

so the dominant pole is $f_L(IN)$;

$$f_L \approx \underbrace{15.92 \text{ Hz}}$$