

Op-Amp Circuits Part One

- last time : single active (three-terminal) device could make a linear amplifier.
 - huge development!
 - several shortcomings; big one is that overall performance (actual linearity, amount of gain, etc.) depended heavily on device itself and a high level of variability unit-to-unit

My invention : Negative feedback

Harold Black, Western Electric (1928)


concept: output, or fraction of the output of an amplifier, is subtracted from the input

- reduces voltage gain; but corrects errors in gain, linearity, etc..

Operational Amplifier

- multistage voltage amplifier with extremely high Voltage gain, whose final performance is determined by negative feedback.
- results in "near-perfect" processing of signals, without variability due to individual devices such as transistors.
- developed in 1940s for use in analog computers
- by 1960's : monolithic integrated circuit (I.C.) chip

Ideal Op-Amp

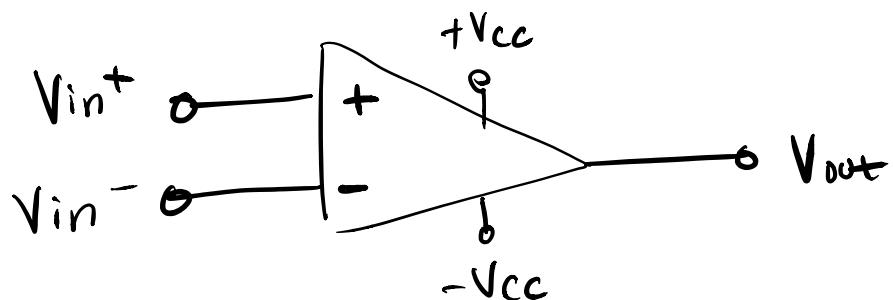

key features:

- differential input $(V_{in^+} - V_{in^-})$
w/ infinite R_{in} and therefore zero
input current, like an ideal voltmeter
- infinite voltage gain
$$\underbrace{A_V(\text{o.l.})}_{\text{open-loop}} = \infty$$
- perfect frequency response
(i.e., no high- or low-pass filter)
- zero R_{out} ; i.e. perfect voltage source
② output, drive any load
- no such thing as ideal op-amp, but they are
perfect enough for our applications!

TWO Rules:


- these will allow us to develop a transfer function ($\frac{V_{out}}{V_{source}}$) for many negative-feedback circuits using an ideal op-amp :

$$1.) V_{in^+} = V_{in^-}$$

What?

- an ideal op-amp has infinite open-loop gain
- by definition:
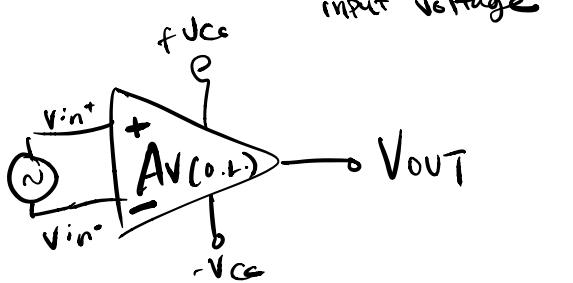
$$V_{out} = \underbrace{(V_{in^+} - V_{in^-})}_{\text{differential input voltage}} \cdot A_{V(\text{o.l.})}$$



.. as $A_{v(0.1)} \rightarrow \infty$, $V_{in^+} - V_{in^-} \rightarrow 0$

$$\therefore \underbrace{V_{in^+} = V_{in^-}}$$


2.) $i_{in^+} = 0$

$i_{in^-} = 0$

.. this is because $R_{in} = \infty$

.. how do we use these rules?

Non-inverting Voltage Amplifier

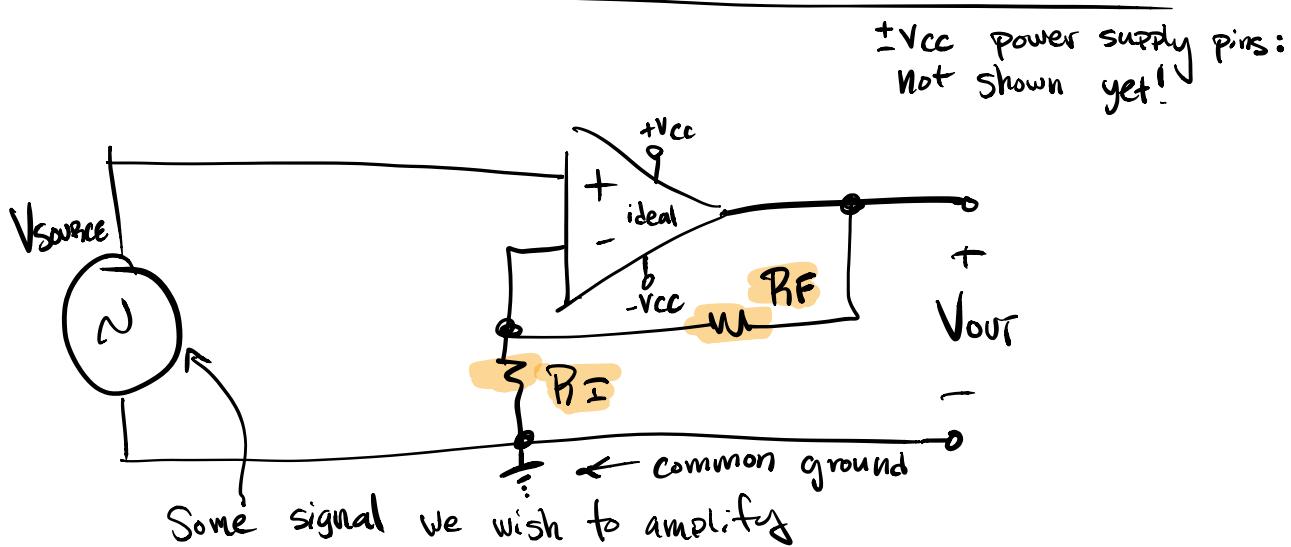

- R_F and R_I constitute a negative feedback loop!
- thus a voltage-divided fraction of V_{out} is subtracted from V_{source} !
- ideal: $V_{in^+} = V_{in^-}$ (rule #1)

$$V_{in^+} = V_{source}$$

$$\underbrace{V_{in^-}}_{= V_{out} \left[\frac{R_I}{R_F + R_I} \right]} = V_{out} \left[\frac{R_I}{R_F + R_I} \right]$$

$$\therefore V_{source} = V_{out} \left[\frac{R_I}{R_F + R_I} \right]$$

$$\frac{V_{out}}{V_{source}} = \frac{R_F + R_I}{R_I}$$

\downarrow Voltage gain of non-inverting amplifier

$$\therefore A_V = 1 + \frac{R_F}{R_I}$$

- Voltage gain of circuit - if we assume op-amp is ideal is based on the ratio of a couple resistors and not active device characteristics!

HUGE !!!

- We can use cheap, high-precision resistors and get very precise amplification

$$\text{ex: } R_F = 100 \text{ k}\Omega$$

$$R_I = 10 \text{ k}\Omega$$

$$A_v = 1 + \frac{R_F}{R_I}$$


$$= 1 + \frac{100k}{10k} = 11 \quad \left[\begin{array}{l} \text{or } 20 \log_{10}(11) \\ = 20.8 \text{ dB} \end{array} \right]$$

ex: if $V_{\text{source}} = 5 \text{ mV}_{\text{pp}}$ @ 1 kHz, $V_{\text{out}} = 55 \text{ mV}_{\text{pp}}$ @ 1k


if $V_{\text{source}} = -1 \text{ V}_{\text{DC}}$, $V_{\text{out}} = -11 \text{ V}_{\text{DC}}$

- Many small-signal op-amps use the 8-Pin DIP Package

- pins go CCW from top, starting

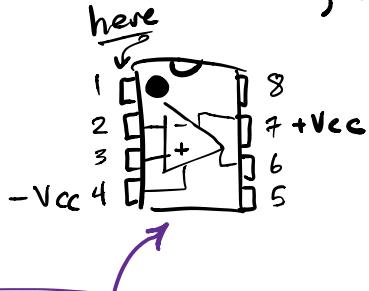

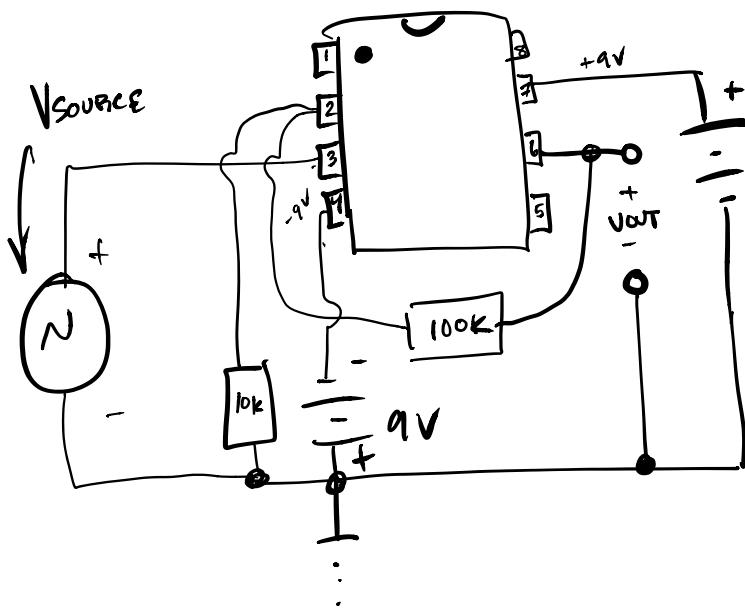Wrong Pinout in
Video lecture!!!
Corrected here!



Classic op-amp:

UA741

- introduced in 1968
- cheap! \$3 then,
More like 25¢ now

- CPI calculator online:
\$3 in 1968 money is
how much in 2020 dollars?

UA741 Works with
up to $\pm 18\text{V}$ Vcc

- need bipolar
power supply so
Vout can go pos.
or negative!