

homework: design voltage regulator $[R_s \text{ and } Z_{\text{ener}}, \text{ w/ power ratings}]$

to take voltage from center-tapped 350-0-350 power supply and produce $V_L = \underline{300V}$

① $\underline{I_L = 0 - 30 \text{ mA}}$

solution: first, go back to raw power supply specs;

$$V_{\text{peak}} = 494.3 \text{ V}$$


$$V_{\text{ripple}} = 16.67 \text{ V}_{\text{P-P}}$$

$$\rightarrow V_L = 486 \text{ V} \quad \left. \vphantom{\begin{matrix} V_{\text{peak}} \\ V_{\text{ripple}} \end{matrix}} \right\} \text{② } I_L = 200 \text{ mA}$$

∵ since max. load current is only 30 mA here, ripple will be much lower and we can simply

use $\underline{V_{\text{RAW}} \approx 494.3 \text{ V}}$

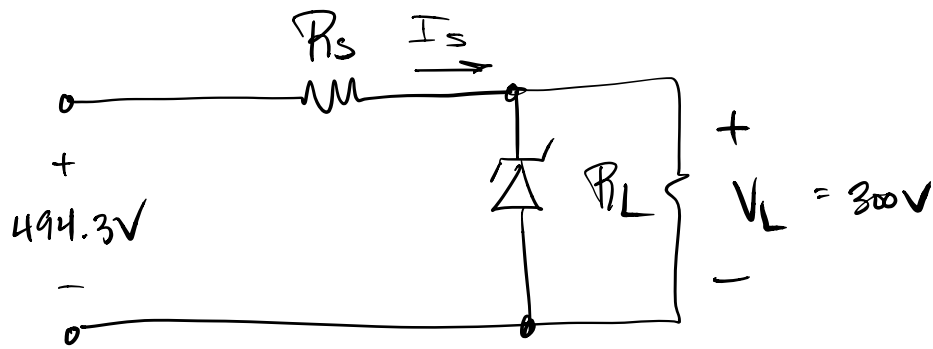* this ripple is at 200mA, at 30mA it becomes negligible



.. assume $I_{Z_{min.}} = 2\text{mA}$ will ensure regulation

.. then
$$I_s = I_{Z_{min}} + I_{L_{max}} = 2 + 30$$
$$= \underline{32\text{ mA}}$$

.. "constant" input voltage simplifies computation!

$$R_s = \frac{V_{IN} - V_L}{I_s} = \frac{494.3 - 300}{32}$$

$$\underline{R_s = 6.072\text{ k}\Omega}$$

use $5.6\text{ k}\Omega$ [round down to nearest E24]

$$P_{R_s} = \frac{V^2}{R} = \frac{(494.3 - 300)^2}{5.6\text{ k}} = \underline{6.741\text{ W}}$$

use 10 W resistor, preferably 15 or 20W!

∴ max power in zener occurs when V_{in} is high $\rightarrow 494.3$
 and I_L is low
 $\downarrow I_L = 0$

$$I_Z = I_S - I_L = 32 - 0 = \underline{32 \text{ mA}}$$

$$\begin{aligned} \text{then } P_Z &= V_Z \cdot I_Z \\ &= 300 \cdot 0.032 \end{aligned}$$


$$\underline{P_Z = 9.6 \text{ W}}$$

∴ hard to find a 300V zener over 5W;
 instead, use three 100V 5W
 Zener diodes in series

Total power
 dissipation: 15W

1N5378B

45¢ ea. on
 Mouser.com

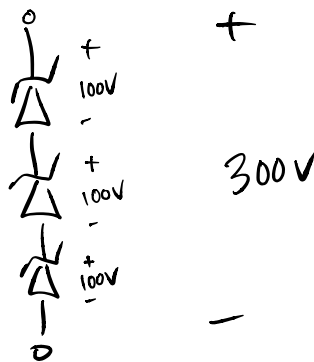

Midwest Surplus Electronics may have 'em!