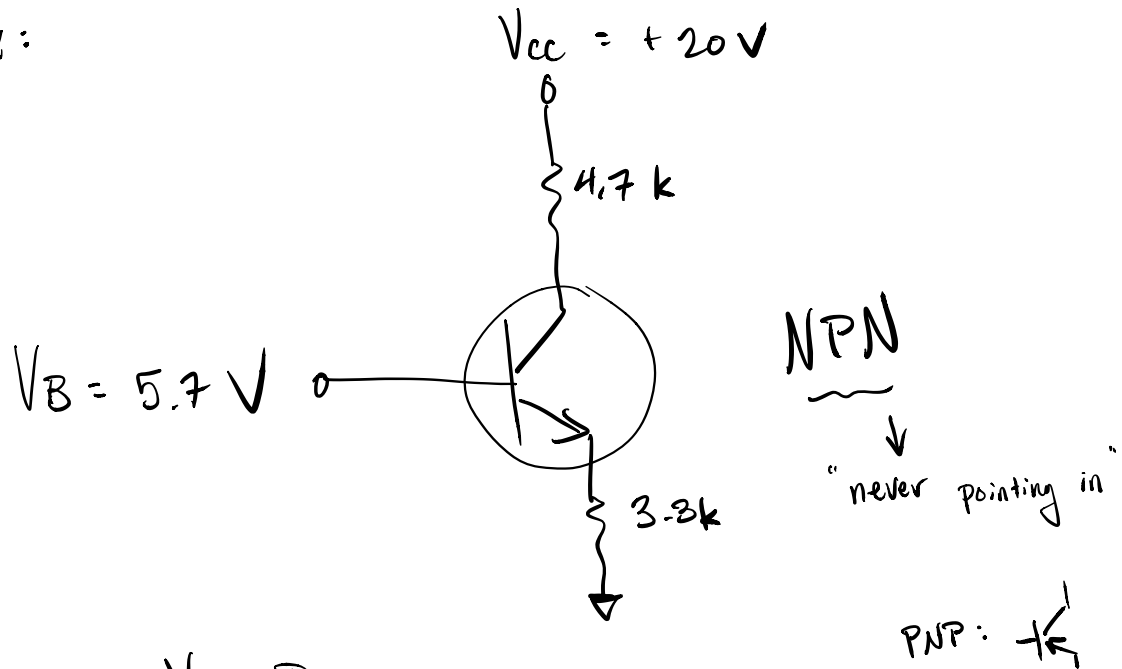


BJT Active Region Circuits

ex:



.. determine $V_E, I_E, I_B, I_C,$
 $V_C,$ and V_{CE} if $\beta = 100$

.. first, assume transistor is ON and operating
in active region.


NPN: $V_{BE} \approx 0.7V$ (Si)

$$\underline{V_{BE} = V_B - V_E}$$

$$\therefore V_E = V_B - V_{BE}$$

$$= 5.7V - 0.7 = \underline{5V}$$

↑
known!

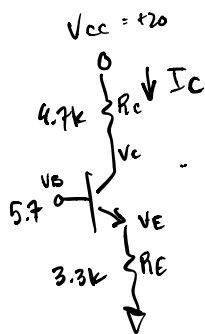

then $I_E = \frac{V_E}{R_E} = \frac{5V}{3.3k} = \underline{1.515mA}$

$$I_E = I_B (1 + \beta)$$

$$\rightarrow I_B = \frac{I_E}{1 + \beta} = \frac{1.515}{101} = 0.015mA$$

or $\underline{15\mu A}$

$$I_C = \beta I_B$$

$$= 100 \cdot 0.015 = \underline{1.5mA}$$

$$V_C = V_{CC} - R_C I_C = 20 - 4.7k \cdot 1.5mA = \underline{12.95V}$$

.. finally, $V_{CE} = V_C - V_E$

$$= 12.95 - 5 \approx \underline{8V}$$

.. practical transistors have ratings, just like diodes


2N3904

.. mid 1960s

.. still made today!

.. NPN Silicon small-signal transistor

.. usually in TO-92 package

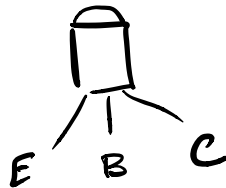

at 0 current

$$V_{CE0}(\max) = \underline{40V} \quad \leftarrow \quad \Rightarrow \quad 8V \text{ (OK!)}$$

$$V_{EB0}(\max) = \underline{6V} \quad \leftarrow \quad \text{implies reverse bias of base-to-emitter junction} < 6V \text{ (we're not reverse-biased!)}$$

$$\beta = 100 \text{ (typical)}$$

$$\text{Min.} : 30 \quad @ \quad I_c = 100 \text{ mA}$$

$$\text{Max.} : 300$$

$$I_c (\text{max}) = \underline{200 \text{ mA}} \quad \leftarrow 1.5 \lll 200 \text{ (ok!)}$$

$$P_{\text{diss}} (\text{max}) = 625 \text{ mW}$$

- better check!


$$P_{\text{diss}} = I_c \cdot V_{CE}$$

$$= 1.5 \cdot 8 = \underline{12 \text{ mW}}$$


(OK !!!)

(side note : V_{CC} power supply voltage)
 \downarrow
 collector !!!

.. let's do a PNP example (book!)

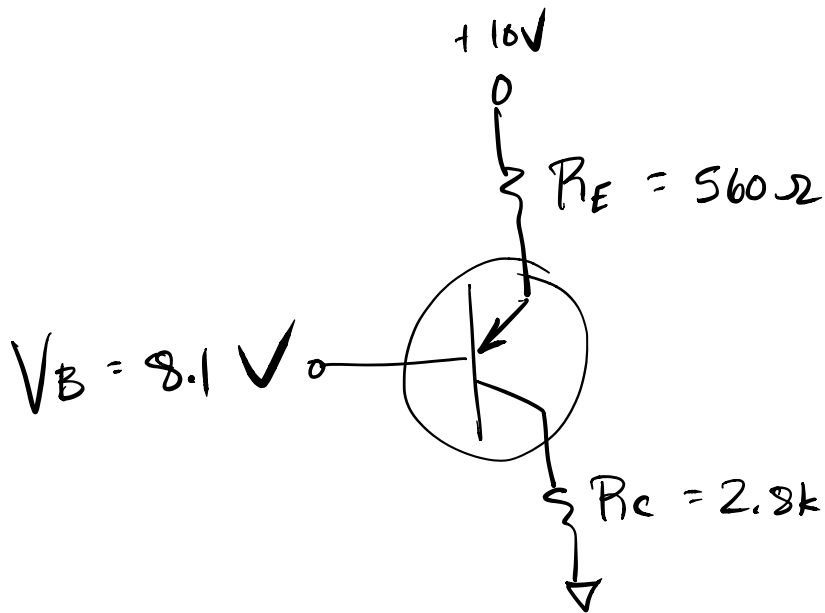

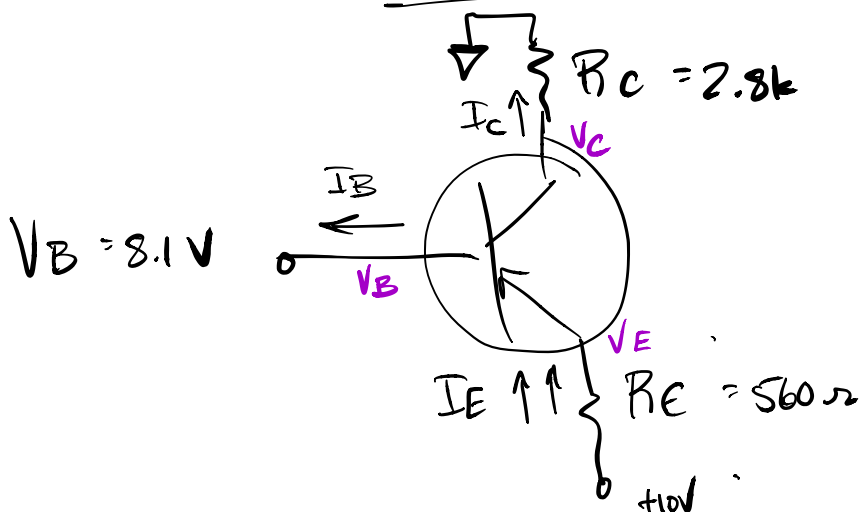.. Joe Tritschler recommends drawing PNP circuits with collector on top and emitter on bottom!



for PNP Si transistor, $V_{BE} = -0.7V$

$$V_E = V_B - V_{BE}$$

$$= 8.1 - (-0.7) = \underline{8.8V}$$

$$I_E = \frac{10 - V_E}{R_E} = \frac{10 - 8.8}{560}$$

$$\underline{I_E = 2.14 \text{ mA}}$$

$$I_E = I_B (1 + \beta)$$

$$\rightarrow I_B = \frac{I_E}{1 + \beta} = \frac{2.14}{101}$$

$$\underline{I_B = 0.0212 \text{ mA (or } 21.2 \mu\text{A)}}$$

$$I_C = \beta I_B = 100 \cdot 0.0212 = \underline{2.12 \text{ mA}}$$

- Watch current direction !!!!!

$$\underline{V_c - I_c R_c = 0}$$

$$\rightarrow V_c = I_c R_c$$

$$= 2.84 \cdot 2.12 \text{ V}$$

$$= \underline{5.94 \text{ V}}$$

$$\begin{aligned} \text{then } V_{CE} &= V_c - V_E \\ &= 5.94 - 8.8 \end{aligned}$$

$$\underline{V_{CE} = -2.86 \text{ V}}$$

yes! Negative voltage!

- practical PNP small-signal transistor:

2N3906

.. complement to 2N3904!
^ same ratings!

