

## 4.APPLICATIONS OF THE LAPLACE TRANSFORM

# Applications of the Laplace Transform


## Contents

- Overview, 132
- 4-1 s-Domain Circuit Element Models, 132
- 4-2 s-Domain Circuit Analysis, 134
- 4-3 Electromechanical Analogues, 140
- 4-4 Biomechanical Model of a Person
  - Sitting in a Moving Chair, 146
- 4-5 Op-Amp Circuits, 149
- 4-6 Configurations of Multiple Systems, 154
- 4-7 System Synthesis, 157
- 4-8 Basic Control Theory, 160
- 4-9 Temperature Control System, 167
- 4-10 Amplifier Gain-Bandwidth Product, 171
- 4-11 Step Response of a Motor System, 174
- 4-12 Control of a Simple Inverted
  - Pendulum on a Cart, 178
- Summary, 183
- Problems, 183
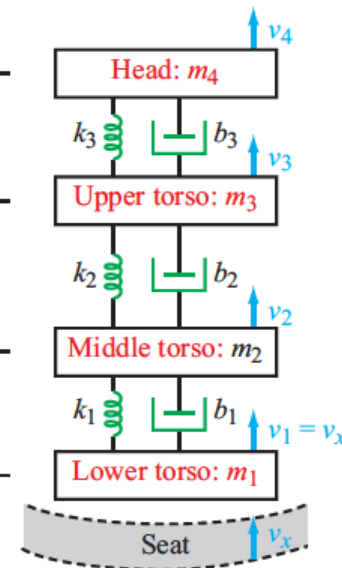
## Objectives

Learn to:

- Use s-domain circuit element models to analyze electric circuits.
- Use electromechanical analogues to simulate and analyze mechanical systems.
- Use op-amp circuits to implement systems.
- Develop system realizations that conform to specified transfer functions.
- Employ feedback control techniques to improve system performance and stability



The Laplace-transform tools learned in the previous chapter are now applied to model and solve a wide variety of *mechanical and thermal systems*, including how to compute the movement of a passenger's head as the car moves over curbs and other types of pavements, and how to design *feedback loops* to control *motors* and heating systems.

# s-Domain Circuit Element Models

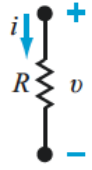

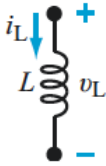
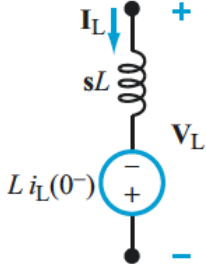
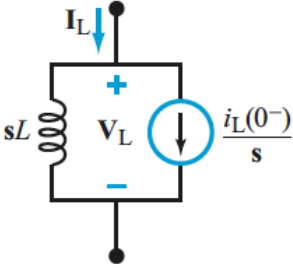
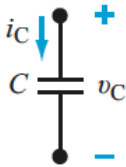
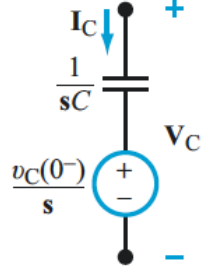
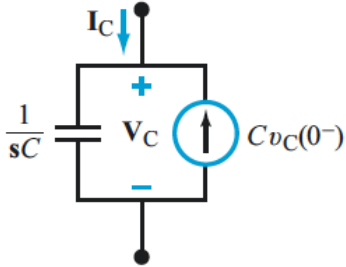
► The s-domain transformation of circuit elements incorporates initial conditions associated with any energy storage that may have existed in capacitors and inductors at  $t = 0^-$ . ◀

$$v = Ri \iff V = RI.$$


$$v = L \frac{di}{dt} \iff V = sLI - L i(0^-).$$

$$i = C \frac{dv}{dt} \iff I = sCV - C v(0^-),$$


**Table 4-1:** Circuit models for  $R$ ,  $L$ , and  $C$  in the  $s$ -domain.

Time-Domain	s-Domain
<p><b>Resistor</b></p>  <p><math>v = Ri</math></p>	 <p><math>V = RI</math></p>
<p><b>Inductor</b></p>  <p> <math display="block">v_L = L \frac{di_L}{dt}</math> <math display="block">i_L = \frac{1}{L} \int_{0^-}^t v_L dt' + i_L(0^-)</math> </p>	<div style="display: flex; align-items: center; justify-content: space-around;"> <div style="text-align: center;">  <p><math>V_L = sLI_L - L i_L(0^-)</math></p> </div> <div style="text-align: center; color: red; font-weight: bold;">OR</div> <div style="text-align: center;">  <p><math>I_L = \frac{V_L}{sL} + \frac{i_L(0^-)}{s}</math></p> </div> </div>
<p><b>Capacitor</b></p>  <p> <math display="block">i_C = C \frac{dv_C}{dt}</math> <math display="block">v_C = \frac{1}{C} \int_{0^-}^t i_C dt' + v_C(0^-)</math> </p>	<div style="display: flex; align-items: center; justify-content: space-around;"> <div style="text-align: center;">  <p><math>V_C = \frac{I_C}{sC} + \frac{v_C(0^-)}{s}</math></p> </div> <div style="text-align: center; color: red; font-weight: bold;">OR</div> <div style="text-align: center;">  <p><math>I_C = sC V_C - C v_C(0^-)</math></p> </div> </div>
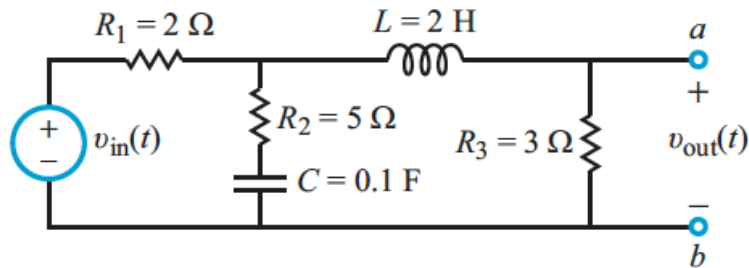
# Example 4-1: Interrupted Voltage Source




(a) Time domain

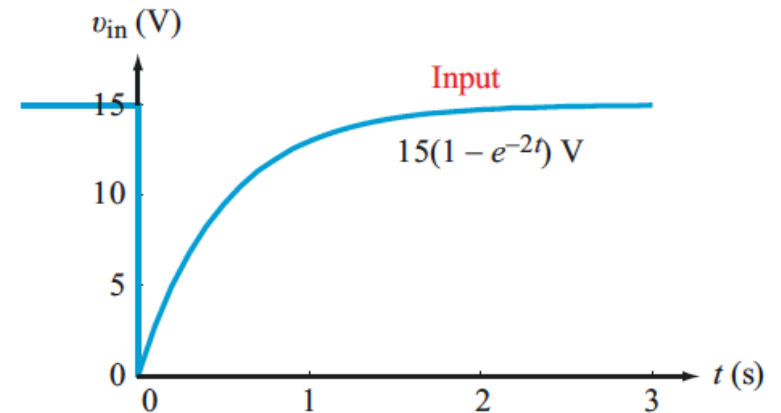

(b) Waveform of  $v_{in}(t)$


Initial Conditions:

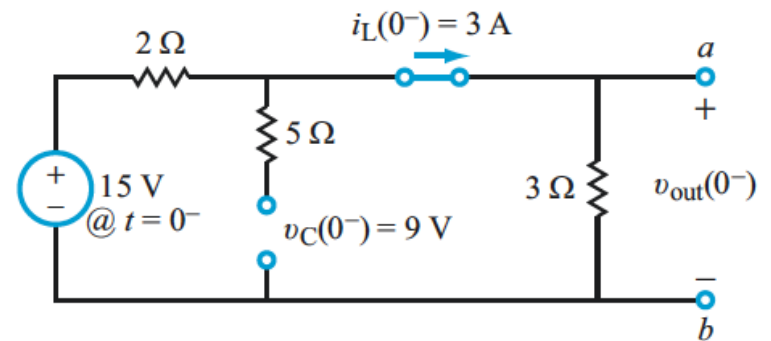


(d) At  $t = 0^-$

$$v_C(0^-) = 9\text{ V}, \quad i_L(0^-) = 3\text{ A}, \quad \text{and} \quad v_{out}(0^-) = 9\text{ V}$$
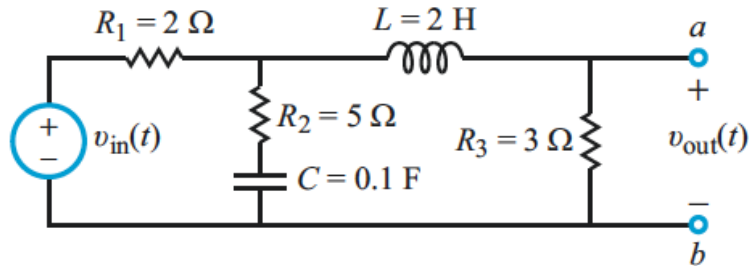
# Example 4-1: Interrupted Voltage Source



(a) Time domain

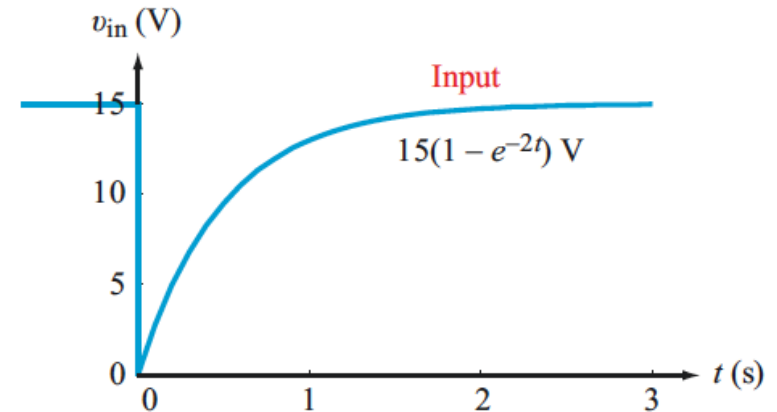


(b) Waveform of  $v_{in}(t)$



$$V_{in}(s) = \frac{15}{s} - \frac{15}{s+2}$$

**Time Domain**

**s-Domain**

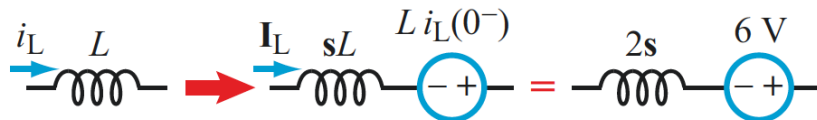


and

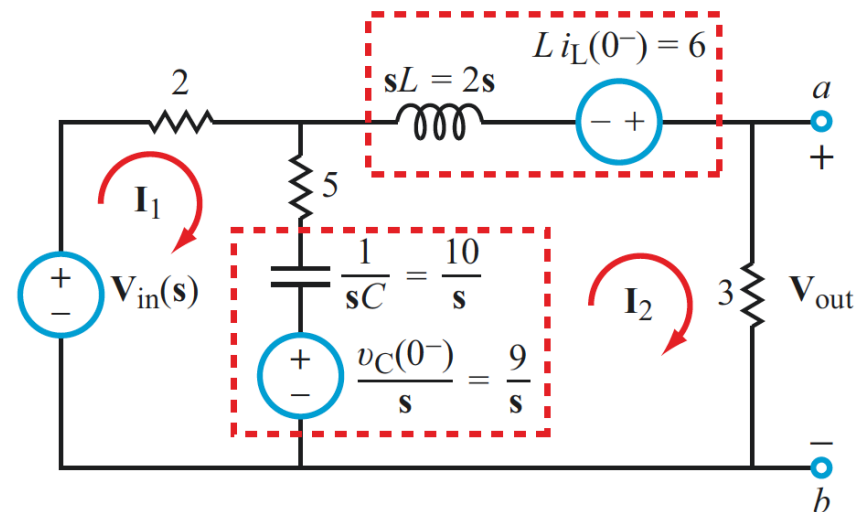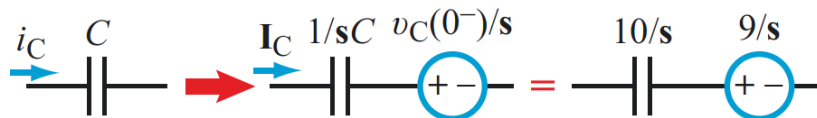

(e) s-domain
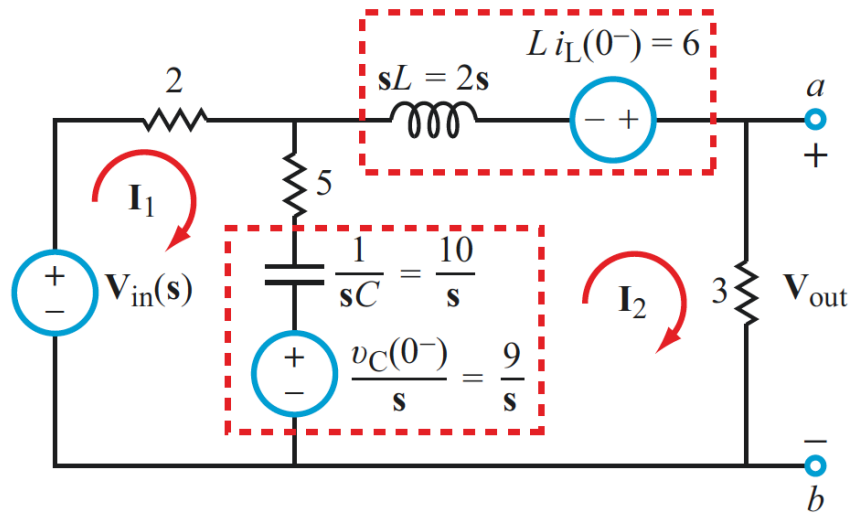
# Example 4-1: Interrupted Voltage Source



(e) s-domain

By inspection, the mesh-current equations for loops 1 and 2 are given by

$$\left(2 + 5 + \frac{10}{s}\right) \mathbf{I}_1 - \left(5 + \frac{10}{s}\right) \mathbf{I}_2 = \mathbf{V}_{\text{in}} - \frac{9}{s} \quad (4.13)$$

and

$$-\left(5 + \frac{10}{s}\right) \mathbf{I}_1 + \left(3 + 5 + 2s + \frac{10}{s}\right) \mathbf{I}_2 = \frac{9}{s} + 6. \quad (4.14)$$


**Simultaneous solution leads to:**

$$\mathbf{V}_{\text{in}}(s) = \frac{15}{s} - \frac{15}{s+2}$$

$$\begin{aligned} \mathbf{I}_2 &= \frac{42s^3 + 162s^2 + 306s + 300}{s(s+2)(14s^2 + 51s + 50)} \\ &= \frac{42s^3 + 162s^2 + 306s + 300}{14s(s+2)(s^2 + 51s/14 + 50/14)} \end{aligned}$$


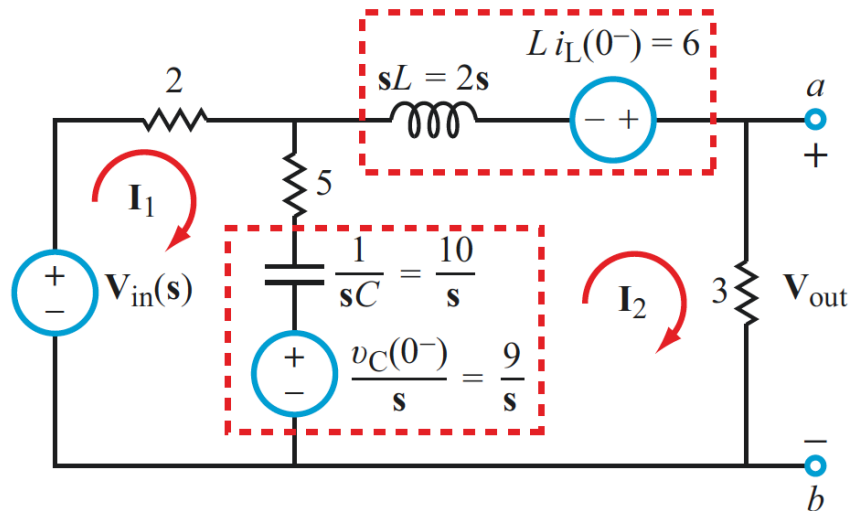
# Example 4-1: Interrupted Voltage Source



(e) s-domain

$$\begin{aligned}
 \mathbf{I}_2 &= \frac{42s^3 + 162s^2 + 306s + 300}{s(s+2)(14s^2 + 51s + 50)} \\
 &= \frac{42s^3 + 162s^2 + 306s + 300}{14s(s+2)(s^2 + 51s/14 + 50/14)} \\
 &= \frac{42s^3 + 162s^2 + 306s + 300}{14s(s+2)(s + 1.82 + j0.5)(s + 1.82 - j0.5)}
 \end{aligned}$$

Partial fraction expansion:

$$\mathbf{I}_2 = \frac{3}{s} + \frac{5.32e^{-j90^\circ}}{s + 1.82 + j0.5} + \frac{5.32e^{j90^\circ}}{s + 1.82 - j0.5}$$

Laplace Transform pairs:

$$\frac{3}{s} \longleftrightarrow 3u(t),$$

and from property #3 of Table 3-3, we have


$$\frac{Ae^{j\theta}}{s + a + jb} + \frac{Ae^{-j\theta}}{s + a - jb} \longleftrightarrow 2Ae^{-at} \cos(bt - \theta) u(t).$$

Time-domain current:


$$\begin{aligned}
 i_2(t) &= [3 + 10.64e^{-1.82t} \cos(0.5t + 90^\circ)] u(t) \\
 &= [3 - 10.64e^{-1.82t} \sin 0.5t] u(t) \text{ A},
 \end{aligned}$$



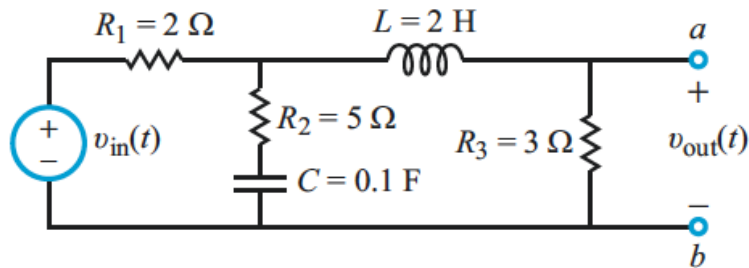
# Example 4-1: Interrupted Voltage Source



(a) Time domain

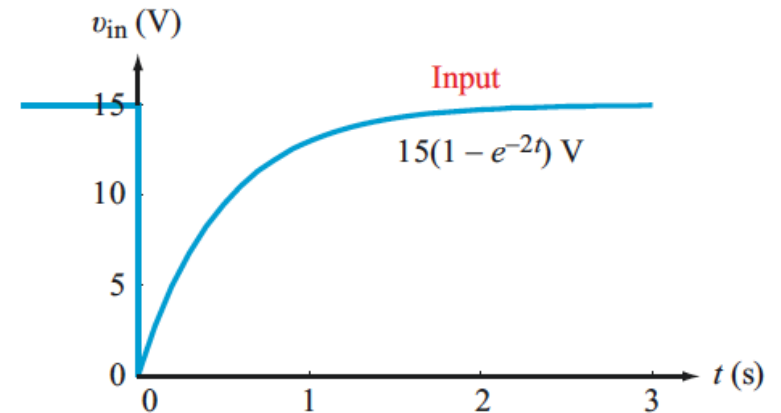

(b) Waveform of  $v_{in}(t)$

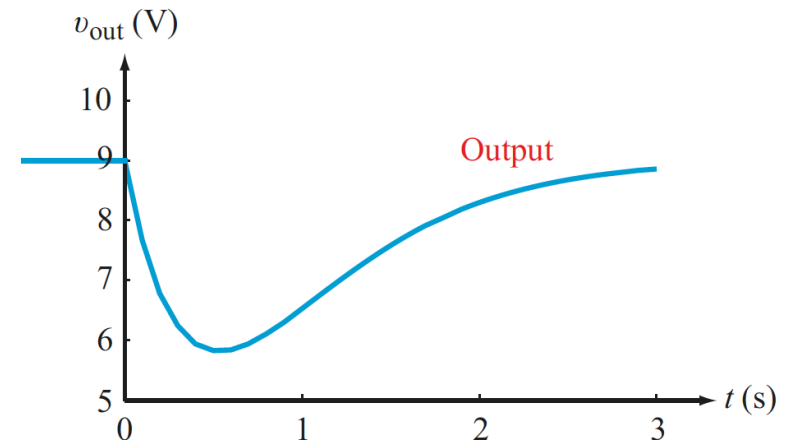

(c) Waveform of  $v_{out}(t)$


$$\begin{aligned} v_{out}(t) &= 3i_2(t) \\ &= [9 - 31.92e^{-1.82t} \sin 0.5t] u(t) \text{ V.} \end{aligned}$$

## Example 4-4: Lowpass Filter Response to a Rectangular Pulse

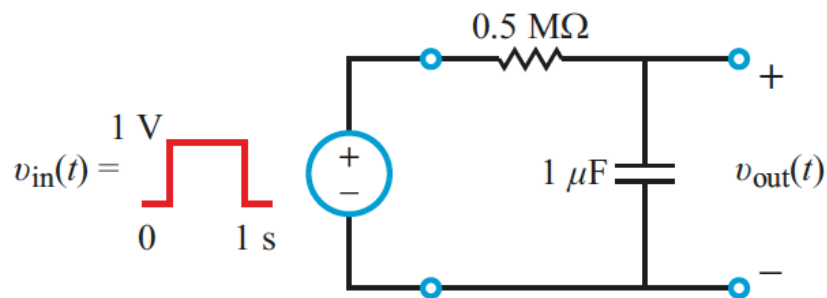
### Solution:

With  $R = 0.5 \text{ M}\Omega$  and  $C = 1 \text{ }\mu\text{F}$ , the product is  $RC = 0.5 \text{ s}$ . Voltage division in the s-domain (Fig. 4-4(b)) leads to

$$\mathbf{H}(s) = \frac{\mathbf{V}_{\text{out}}(s)}{\mathbf{V}_{\text{in}}(s)} = \frac{1/sC}{R + 1/sC} = \frac{1/RC}{s + 1/RC} = \frac{2}{s + 2}. \quad (4.43)$$



(a) RC lowpass filter

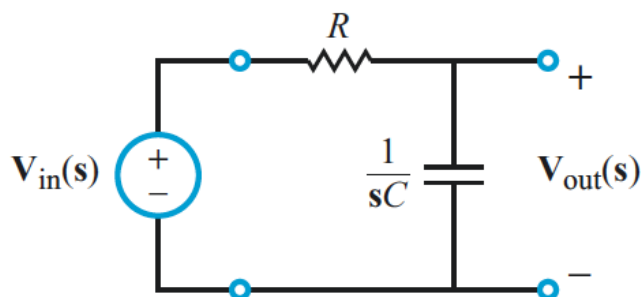

(b) s-domain

The rectangular pulse is given by

$$v_{\text{in}}(t) = [u(t) - u(t - 1)] \text{ V},$$

and with the help of Table 3-2, its s-domain counterpart


$$\mathbf{V}_{\text{in}}(s) = \left[ \frac{1}{s} - \frac{1}{s} e^{-s} \right] \text{ V}.$$

Hence,

$$\begin{aligned} \mathbf{V}_{\text{out}}(s) &= \mathbf{H}(s) \mathbf{V}_{\text{in}}(s) \\ &= 2(1 - e^{-s}) \left[ \frac{1}{s(s + 2)} \right]. \end{aligned}$$



$$\mathbf{V}_{\text{out}}(s) = \frac{1}{s} - \frac{1}{s + 2} - \frac{1}{s} e^{-s} + \frac{1}{s + 2} e^{-s}.$$
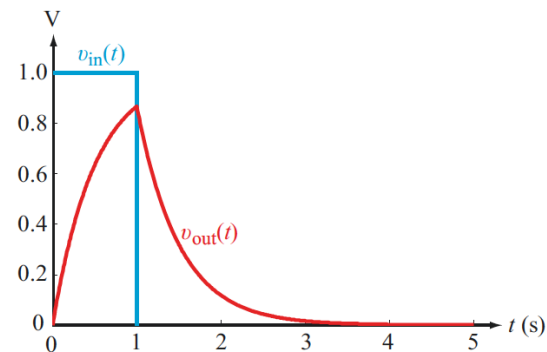
$$v_{\text{out}}(t) = \left[ [1 - e^{-2t}] u(t) - [1 - e^{-2(t-1)}] u(t - 1) \right] \text{ V}.$$




(c) Output response


# Electromechanical Analog

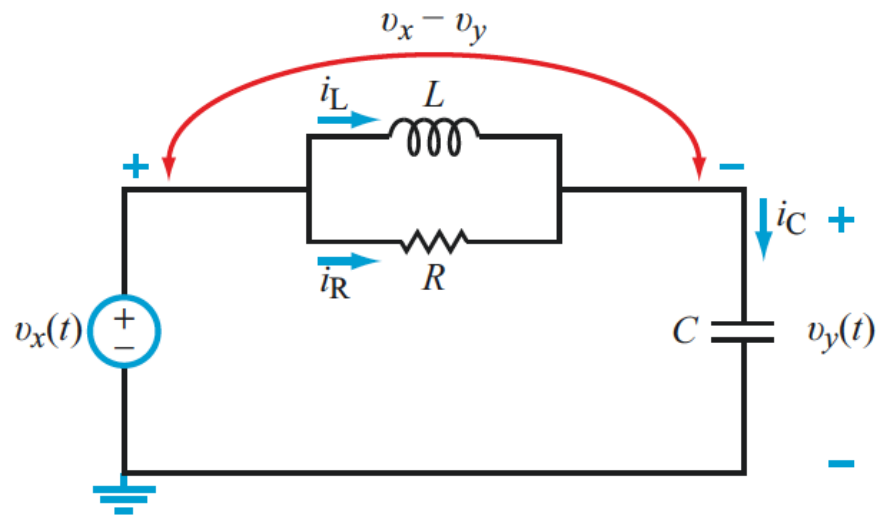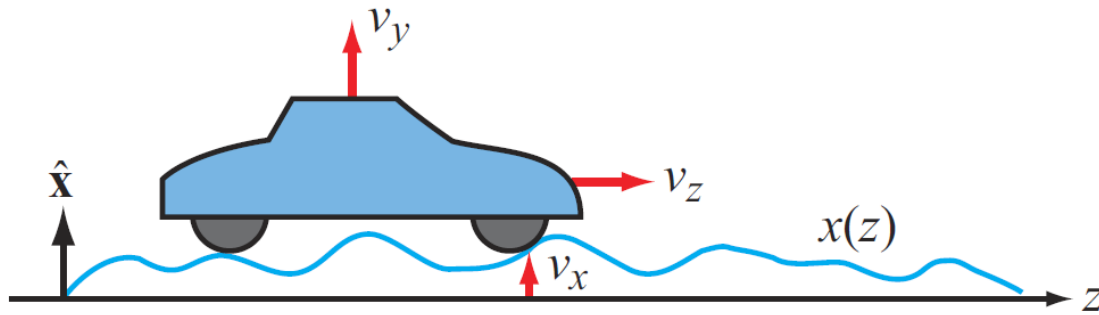

(b) Electrical system

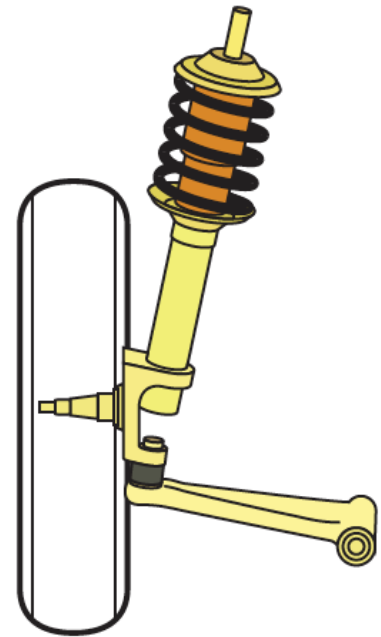

(a) Damping system

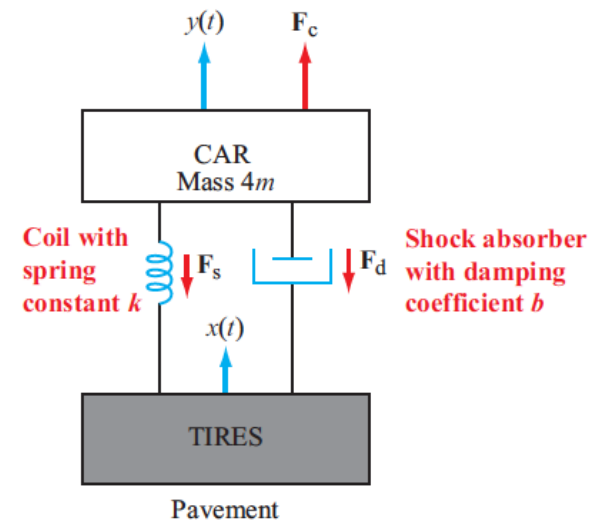

(b) Model

Figure 2-26: Car suspension system model.

**Table 4-2:** Mechanical-electrical analogue.

Mechanical		Electrical
<ul style="list-style-type: none"> <li>Force <math>\mathbf{F}</math> <math>\mathbf{F}</math> is positive when pointing upwards</li> </ul>	$\longleftrightarrow$	Current $i$ $i$ is positive when entering positive voltage terminal of device
<ul style="list-style-type: none"> <li>Vertical velocity <math>v</math> <math>v</math> is positive when car or tire is moving upwards</li> </ul>	$\longleftrightarrow$	Voltage $v$ $v$ 's positive terminal is where $i$ enters device
<ul style="list-style-type: none"> <li>Mass <math>m</math> (1/4 of car's mass) <math>F_c = m \frac{dv_y}{dt}</math></li> </ul>	$\longleftrightarrow$	Capacitance $C$ $i_C = C \frac{dv_y}{dt}$
<ul style="list-style-type: none"> <li>Spring constant <math>k</math> <math>F_s = k \int_0^t (v_x - v_y) d\tau</math></li> </ul>	$\longleftrightarrow$	1/ $L$ : Inverse of inductance $i_L = \frac{1}{L} \int_0^t (v_x - v_y) d\tau$
<ul style="list-style-type: none"> <li>Damping coefficient <math>b</math> <math>F_d = b(v_x - v_y)</math></li> </ul>	$\longleftrightarrow$	1/ $R$ : Inverse of resistance (conductance) $i_R = \frac{1}{R} (v_x - v_y)$
<ul style="list-style-type: none"> <li><math>F_c = F_s + F_d</math></li> </ul>	$\longleftrightarrow$	$i_C = i_L + i_R$

### SMD-RLC Analysis Procedure

**Step 1: Replace each mass with a capacitor** with one terminal connected to a node and the other to ground.

**Step 2: Replace each spring with an inductor** with  $L = 1/k$ , where  $k$  is the spring's stiffness coefficient.

- If the spring connects two masses, its equivalent inductor connects to their equivalent capacitors at their non-ground terminals.
- If the spring connects a mass to a stationary surface, its equivalent inductor should be connected between the capacitor's non-ground terminal and ground.
- If one end of the spring connects to a moving surface,

the corresponding terminal of its equivalent inductor should be connected to a voltage source.


**Step 3: Replace each damper with a resistor** with  $R = 1/b$ . Connection rules are the same as for springs.

**Step 4: Analyze the RLC circuit** using the s-domain technique described in Section 4-2.

The solution of the RLC circuit provides expressions for the voltages across capacitors, corresponding to the velocities of their counterpart masses in the mechanical system. Displacement of a mass or its acceleration can be obtained by integrating or differentiating its velocity  $v(t)$ , respectively.
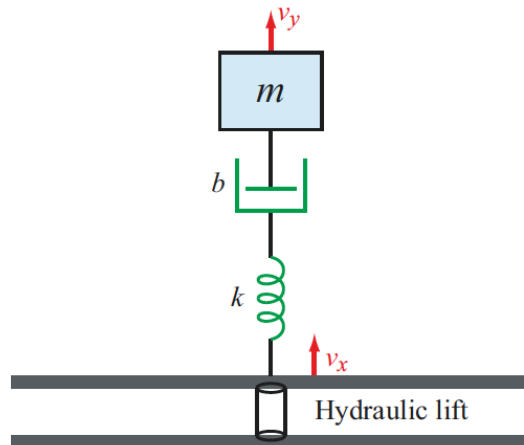
# Hydraulic Lift Example

The lift was used to raise the platform by 4 m at a constant speed of 0.5 m/s. Determine the corresponding vertical speed and displacement of the mass  $m$ , given that  $m = 150$  kg,  $k = 1200$  N/m, and  $b = 200$  N·s/m.




(a) Series system

0.5 m/s over a distance of 4 m, which corresponds to a travel time of  $4/0.5 = 8$  s,  $v_x(t)$  is a rectangle waveform given by


$$v_x(t) = 0.5[u(t) - u(t - 8)] \text{ m/s.} \quad (4.60)$$

Using entries #2 and #2a in Table 3-2, the Laplace transform of  $v_x(t)$  is
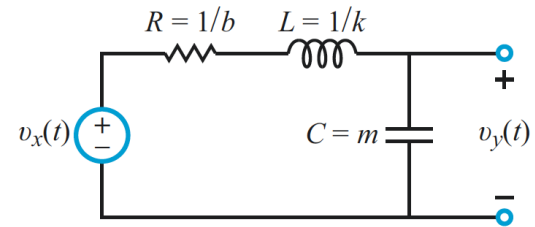
$$\mathbf{V}_x = \frac{0.5}{s} - \frac{0.5}{s} e^{-8s}. \quad (4.61)$$



(b) Equivalent circuit

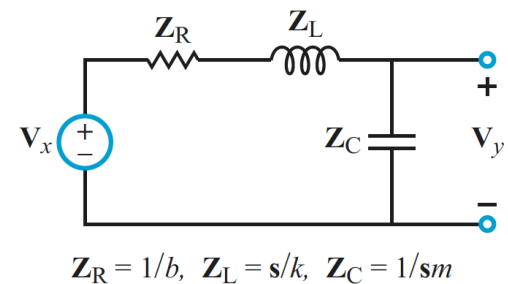

(c) s-domain circuit

$$\begin{aligned} \mathbf{V}_y &= \frac{\mathbf{V}_x \mathbf{Z}_C}{\mathbf{Z}_R + \mathbf{Z}_L + \mathbf{Z}_C} = \frac{1/sm}{\frac{1}{b} + \frac{s}{k} + \frac{1}{sm}} \mathbf{V}_x \\ &= \frac{k/m}{s^2 + \frac{k}{b}s + \frac{k}{m}} \mathbf{V}_x \\ &= \frac{8}{s^2 + 6s + 8} \mathbf{V}_x. \end{aligned}$$

# Hydraulic Lift Example

The lift was used to raise the platform by 4 m at a constant speed of 0.5 m/s. Determine the corresponding vertical speed and displacement of the mass  $m$ , given that  $m = 150$  kg,  $k = 1200$  N/m, and  $b = 200$  N·s/m.


$$\begin{aligned} V_y &= \frac{4}{s(s^2 + 6s + 8)} - \frac{4e^{-8s}}{s(s^2 + 6s + 8)} \\ &= \frac{4}{s(s+2)(s+4)} - \frac{4e^{-8s}}{s(s+2)(s+4)} \end{aligned}$$

$$v_{y1}(t) = [0.5 - e^{-2t} + 0.5e^{-4t}] u(t)$$


$$v_{y2}(t) = -[0.5 - e^{-2(t-8)} + 0.5e^{-4(t-8)}] u(t-8),$$

$$v_y(t) = v_{y1}(t) + v_{y2}(t).$$


$$y(t) = \int_0^t v_y(\tau) d\tau.$$

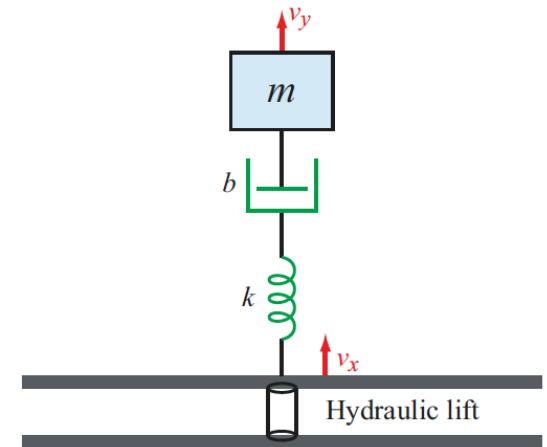

(a) Series system

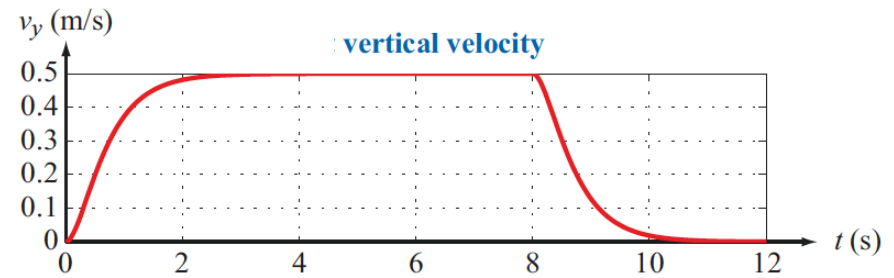


(d) Vertical velocity  $v_y(t)$

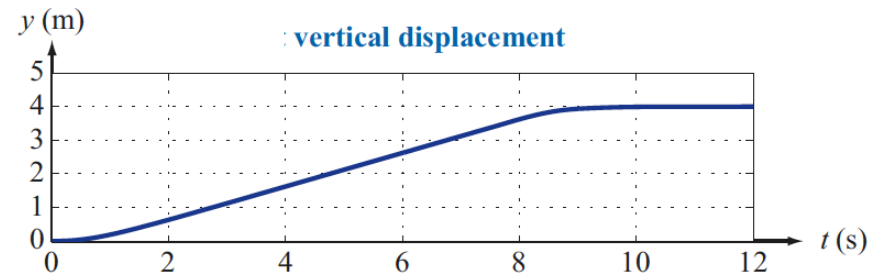


(e) Vertical displacement  $y(t)$




# System Configurations

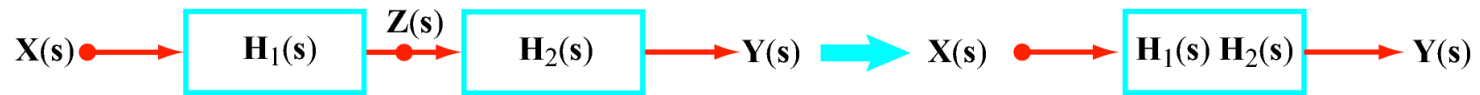

(a) **Two cascaded systems**

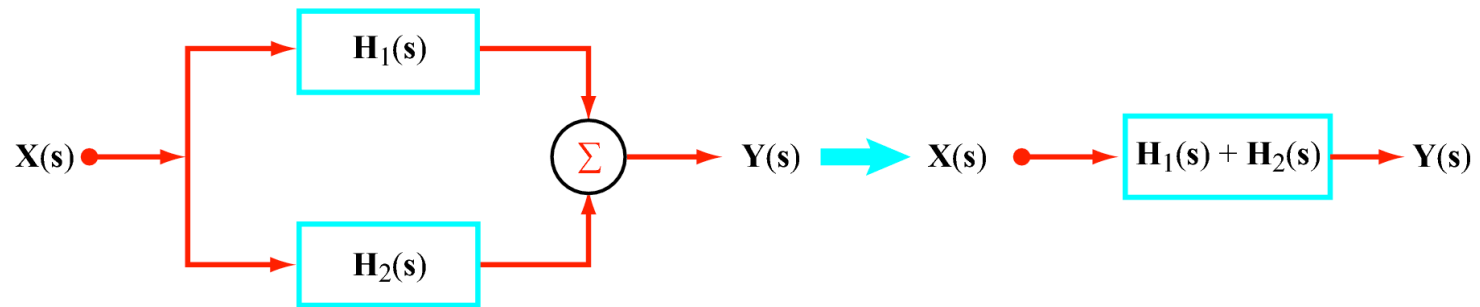

(b) **Two parallel systems**

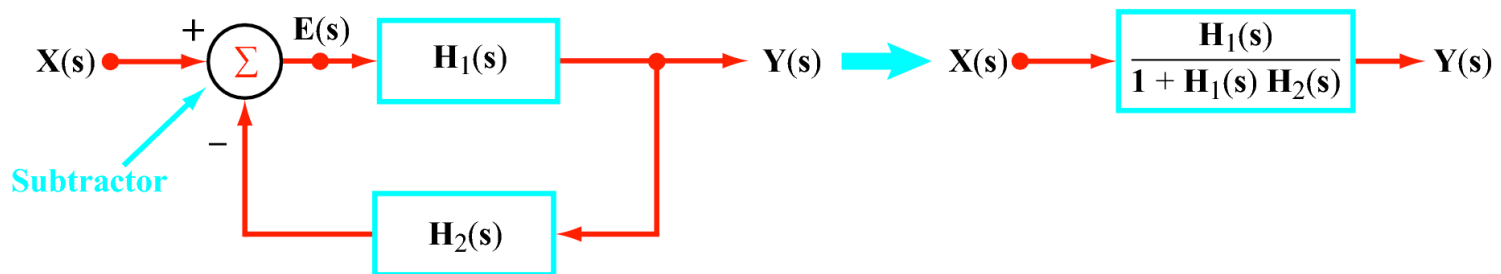

(c) **Negative feedback system**

# System Synthesis— Direct Forms I & II Topologies

Given:

$$\mathbf{H}(s) = \frac{b_0 s^3 + b_1 s^2 + b_2 s}{s^3 + a_1 s^2 + a_2 s + a_3}$$

procedure entails rewriting the expression in terms of inverse powers of  $s$ :


$$\begin{aligned} \mathbf{H}(s) &= \frac{b_0 s^3 + b_1 s^2 + b_2 s}{s^3 + a_1 s^2 + a_2 s + a_3} \cdot \frac{1/s^3}{1/s^3} \\ &= \left( b_0 + \frac{b_1}{s} + \frac{b_2}{s^2} \right) \left( \frac{1}{1 + \frac{a_1}{s} + \frac{a_2}{s^2} + \frac{a_3}{s^3}} \right) \\ &= \mathbf{H}_1(s) \mathbf{H}_2(s), \end{aligned} \quad (4.89)$$

with


$$\mathbf{H}_1(s) = b_0 + \frac{b_1}{s} + \frac{b_2}{s^2} \quad (4.90a)$$

and
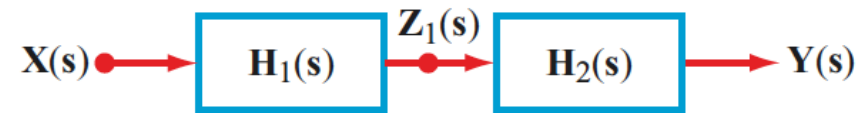
$$\mathbf{H}_2(s) = \left( 1 + \frac{a_1}{s} + \frac{a_2}{s^2} + \frac{a_3}{s^3} \right)^{-1}. \quad (4.90b)$$




(a) **DFI** realization topology

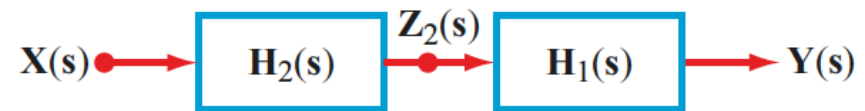

(b) **DFII** realization topology


**Figure 4-19:** In the DFI process,  $\mathbf{H}_1(s)$  is realized ahead of  $\mathbf{H}_2(s)$ , whereas the reverse is the case for the DFII process.

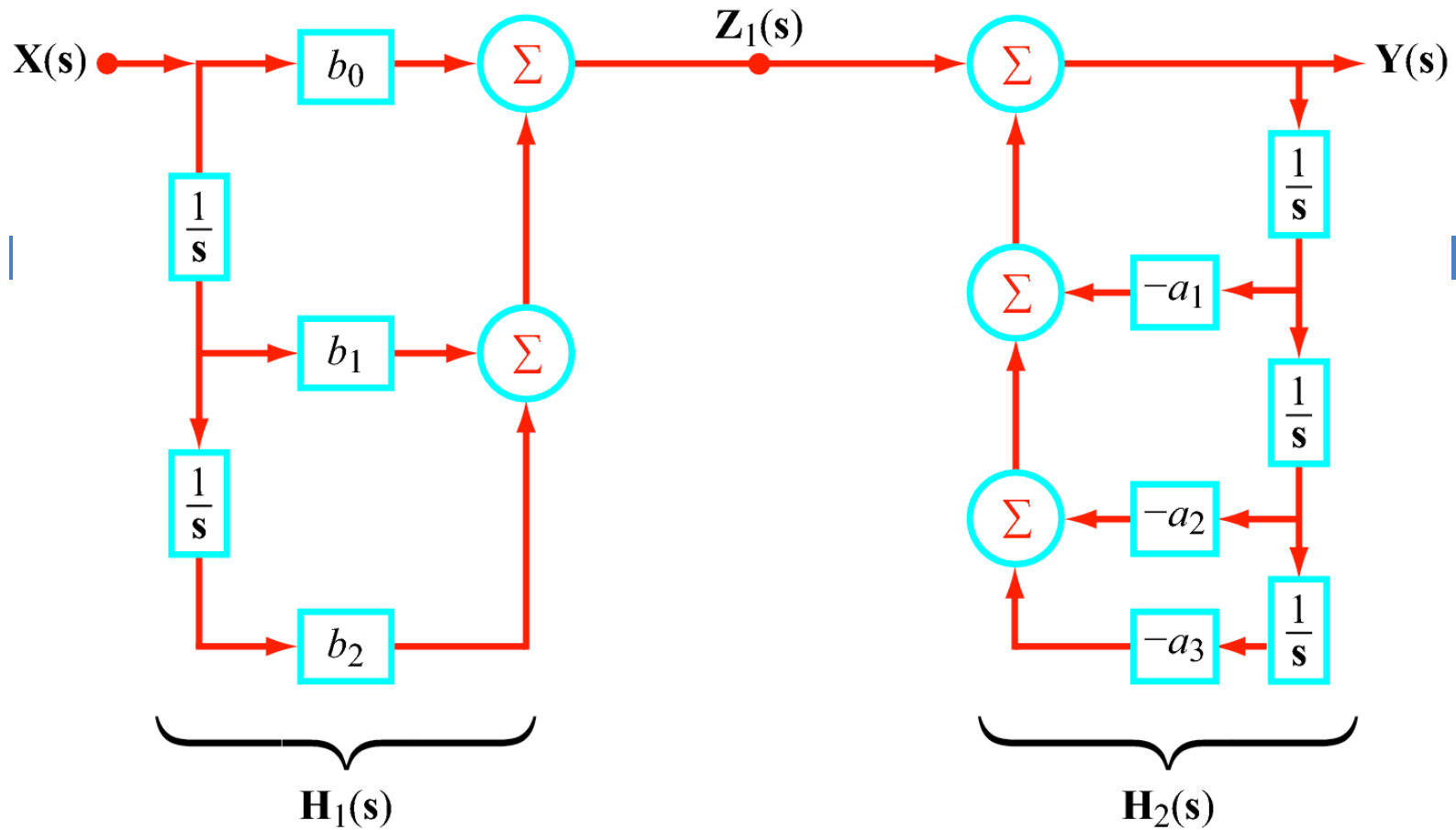


$$H_1(s) = b_0 + \frac{b_1}{s} + \frac{b_2}{s^2}$$

Direct Form I Topology
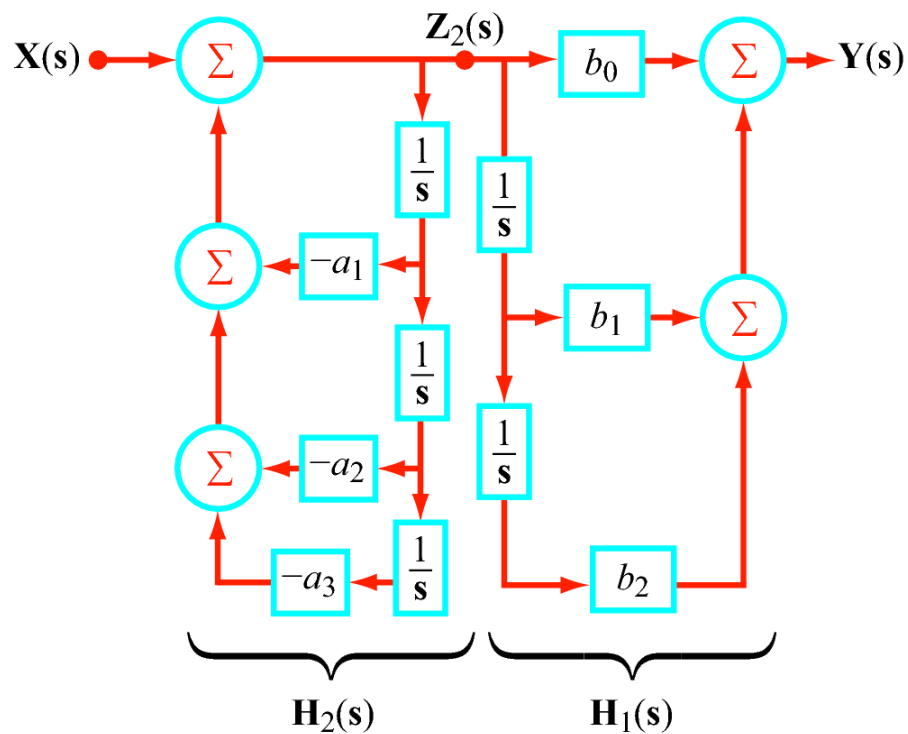
$$H_2(s) = \left(1 + \frac{a_1}{s} + \frac{a_2}{s^2} + \frac{a_3}{s^3}\right)^{-1}$$



(a) **Separate integrators**

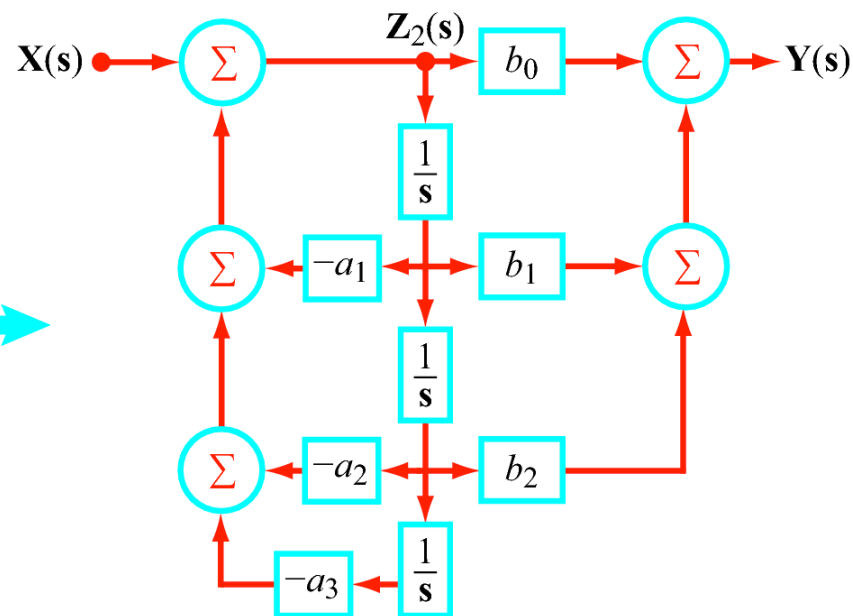

(b) **Common integrators**

$$\mathbf{H}_1(s) = b_0 + \frac{b_1}{s} + \frac{b_2}{s^2}$$


## Direct Form II Topology

$$\mathbf{H}_2(s) = \left(1 + \frac{a_1}{s} + \frac{a_2}{s^2} + \frac{a_3}{s^3}\right)^{-1}$$

DFII topology requires fewer operations to implement than DFI

# Control Theory

## Temperature Control Example

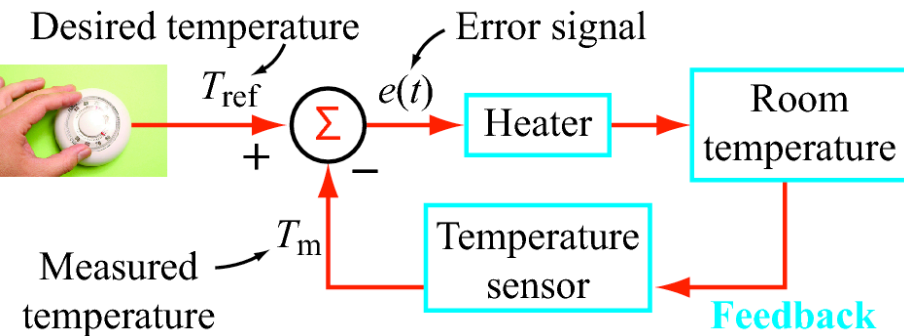



$$\begin{aligned} Y(s) &= H(s) E(s) \\ &= H(s)[X(s) - G(s) Y(s)], \end{aligned}$$

which leads to


$$Y(s) = \frac{H(s) X(s)}{1 + G(s) H(s)}. \quad (4.100)$$

The output-to-input ratio of the closed-loop system is called the *closed-loop transfer function*  $Q(s)$ . From Eq. (4.100), we obtain
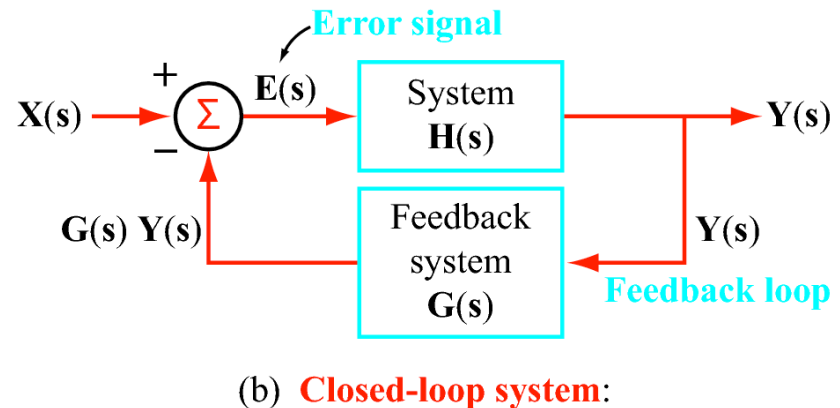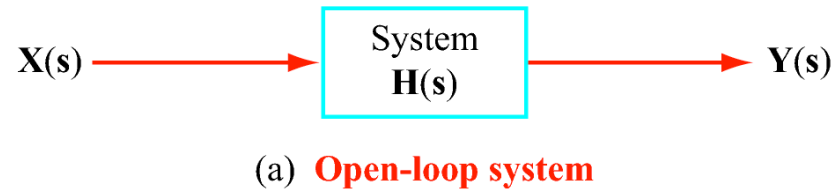
$$Q(s) = \frac{Y(s)}{X(s)} = \frac{H(s)}{1 + G(s) H(s)}. \quad (4.101)$$



# System Stabilization

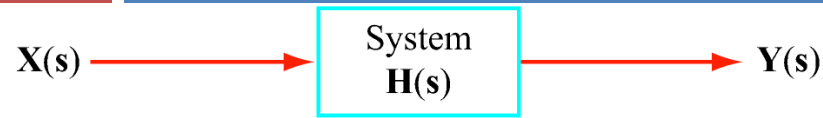


(a) **Open-loop system**

Let's introduce Proportional Feedback with:

$$G(s) = \hat{K}$$

Hence:
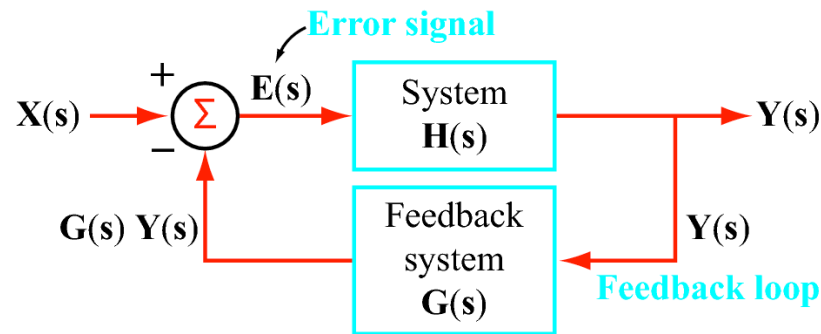
$$\begin{aligned} Q(s) &= \frac{H(s)}{1 + G(s) H(s)} \\ &= \frac{A/(s - p_1)}{1 + \frac{KA}{s - p_1}} = \frac{A}{s - p_1 + KA} \end{aligned}$$



(b) **Closed-loop system:**

Consider the first-order system:

$$H(s) = \frac{A}{s - p_1} \quad \text{with } p_1 > 0. \quad (4.106)$$

The open-loop transfer function  $H(s)$  has a single pole at  $s = p_1$ , and since  $p_1 > 0$ , the pole resides in the RHP

Hence, the system is unstable.

The pole of  $Q(s)$  is at  $p_1 - KA$ . By choosing  $KA > p_1$ , the pole location moves to the OLHP, thereby converting the unstable open-loop system into a stable closed-loop system.