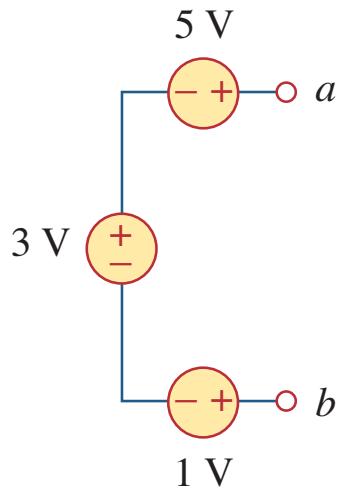



There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

1. Find V_{ab}




$$V_{ab} = 5 + 3 - 1 = 7 \text{ V}$$

2. Find I_T

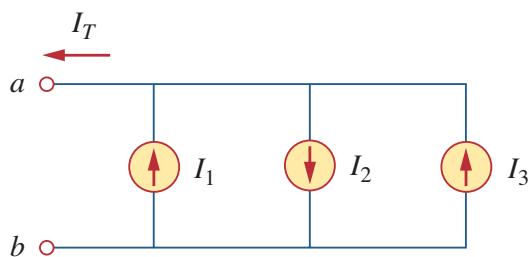


$$I_T = I_1 - I_2 + I_3$$

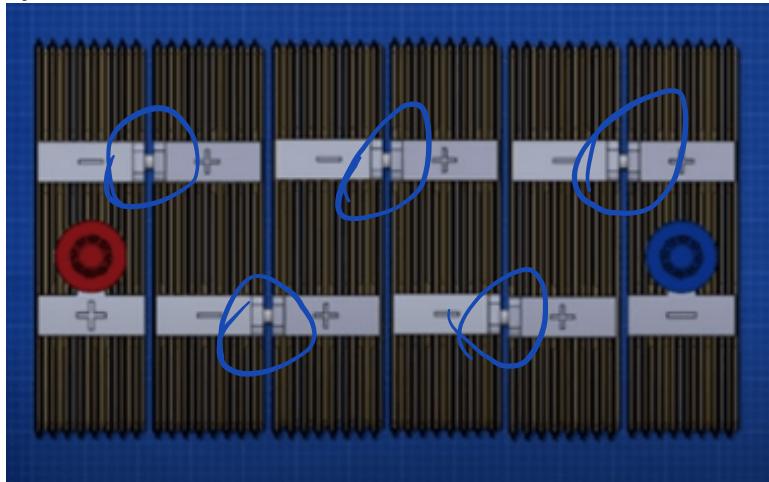3. A common 12V lead-acid car battery is composed of 6 cells. Highlight the inter-cell connections and verify that these individual cells are in "series." What is the nominal voltage produced by each cell?



2 V/cell

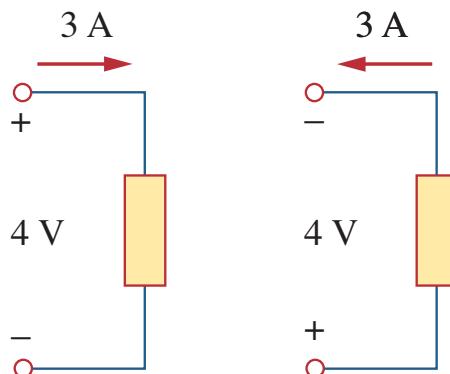4. Find the power absorbed by the element on the right and by the element on the left:



Which of these conforms to the passive sign convention?

Right

$$P = 3\text{ A} \cdot 4\text{ V} = 12\text{ W}$$


Left

2

$$P = 3\text{ A} \cdot 4\text{ V} = 12\text{ W}$$


There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

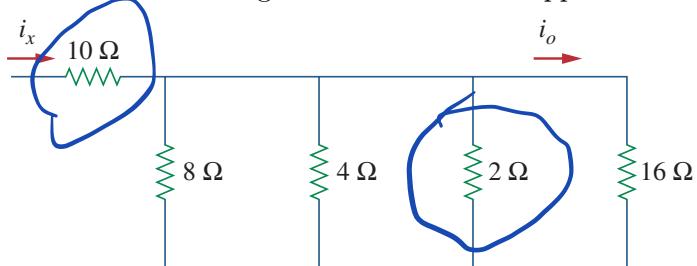1. Estimate reasonable integer-valued lower and upper bounds for the equivalent resistance.



$$10 < R < 12$$

2. Find the equivalent resistance

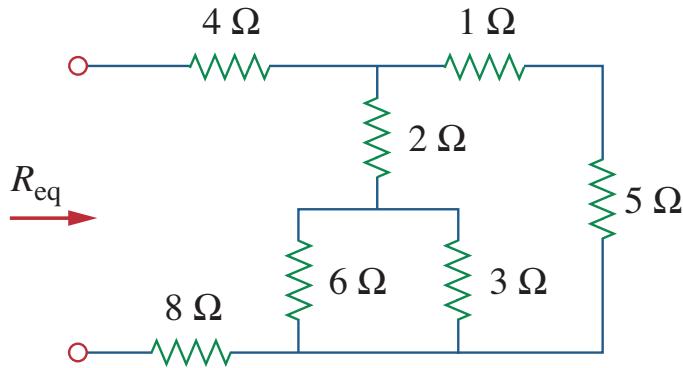


$$4 + 2 \cdot 4 + 8 = 14.4 \Omega$$

4 Ω

Score: _____/20


3. Find v_1 and v_2

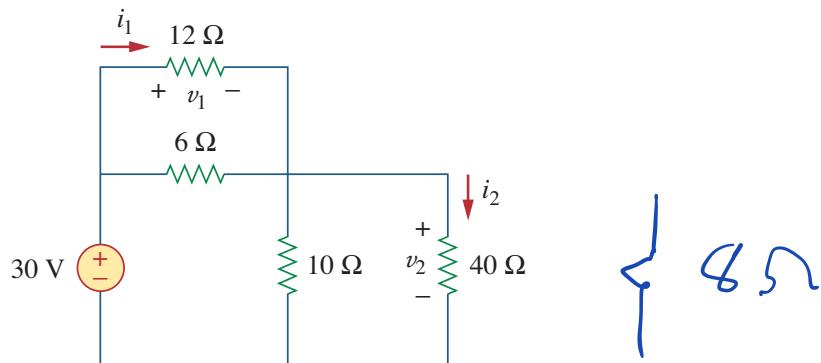

$$v_1 = \frac{30 \cdot 4}{12} = 10 \text{ V}$$

$$v_2 = \frac{30 \cdot 8}{12} = 20 \text{ V}$$

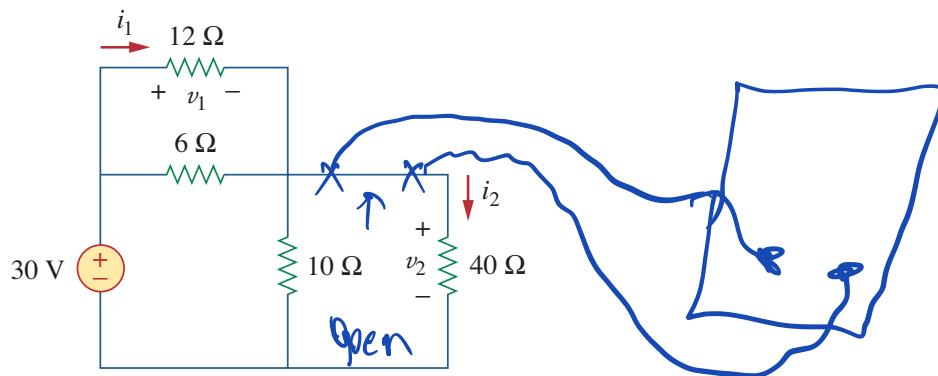4. Sketch a multimeter with leads and illustrate the connection to measure i_2




What is the appropriate multimeter dial setting to measure i_2 ?

10 A


EE 2010 Circuit Analysis: Quiz 3 Name (Last, First): _____

There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

The circuit below is in DC steady state.

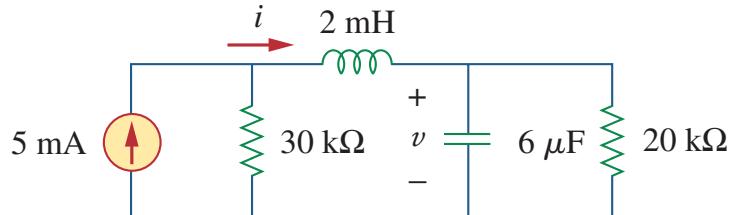

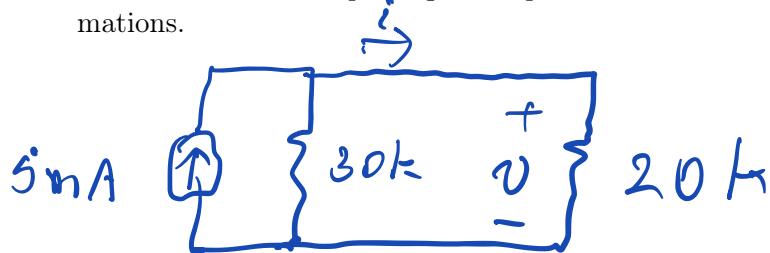1. Redraw the circuit replacing the capacitor and inductor with their DC steady state approximations.




2. Next, find i (the current through the $20k\ \Omega$ resistor) for the DC steady state approximation circuit.

$$i_{20k} = \frac{5 \text{ mA} \cdot 30k}{30k + 20k} = 3 \text{ mA}$$

3. Which of the dynamic components we have considered stores energy in the form of a *magnetic field*?

Inductor

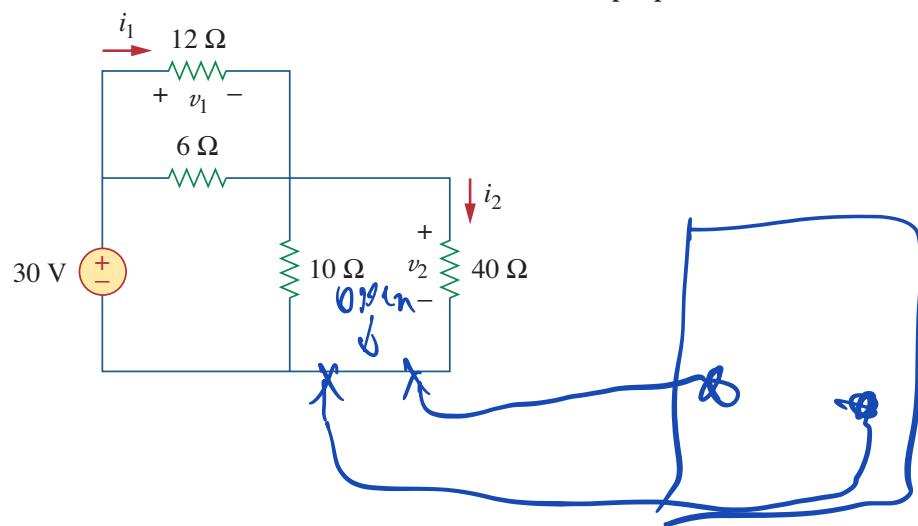
4. Sketch a multimeter with leads and illustrate the proper connection to measure the current i_2



EE 2010 Circuit Analysis: Quiz 4 Name (Last, First): _____

There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

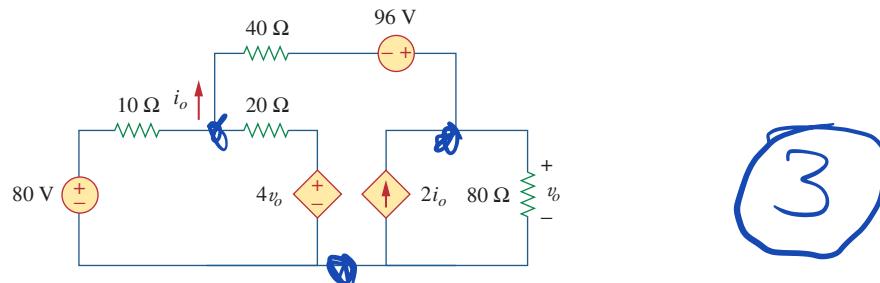
1. Find the number of essential nodes: (0,1,2,3,4)



2. For the circuit above, find the minimum number of equations (node plus otherwise) needed to describe this circuit: (0,1,2,3,4)


3

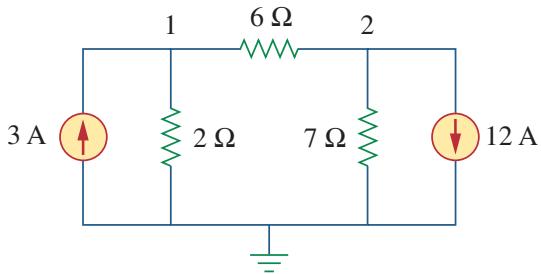3. Write a node equation at "1" denoting the voltage there as v_1 .



$$\frac{v_1}{2} - 3 + \frac{(v_1 - v_2)}{6} = 0$$

4. Write a node equation at v_3 .

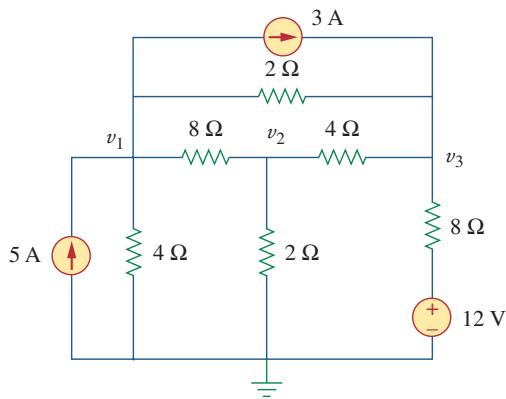


$$\frac{(v_3 - 12)}{8} + \frac{(v_3 - v_2)}{4} + \frac{(v_3 - v_1)}{2} - 3 = 0$$

EE 2010 Circuit Analysis: Quiz 5 Name (Last, First): _____


There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

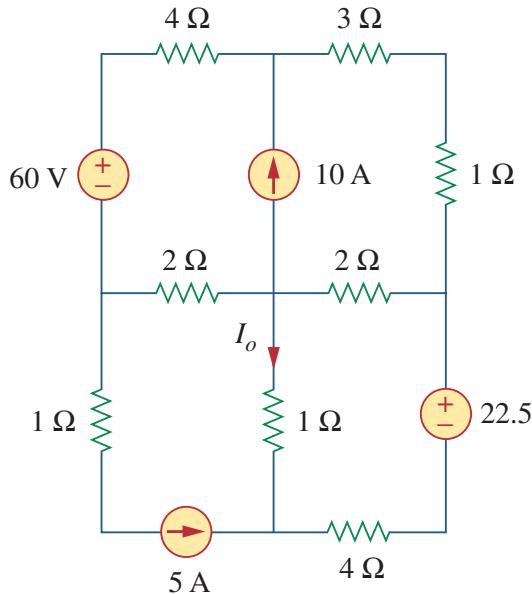1. How many essential nodes in the circuit below? (Your answer should be a positive integer.)




5

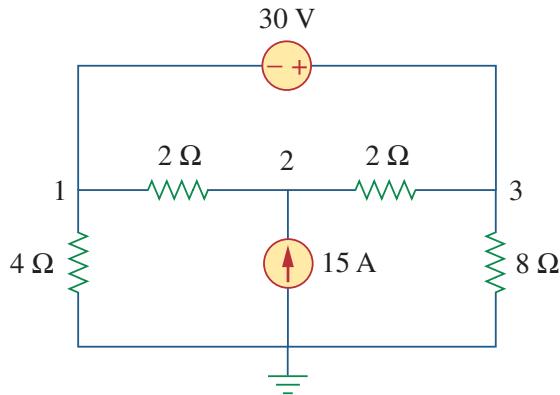2. What is the *minimum* number of equations *necessary* to find the relevant voltages in this circuit? (Your answer should be a positive integer.)




2

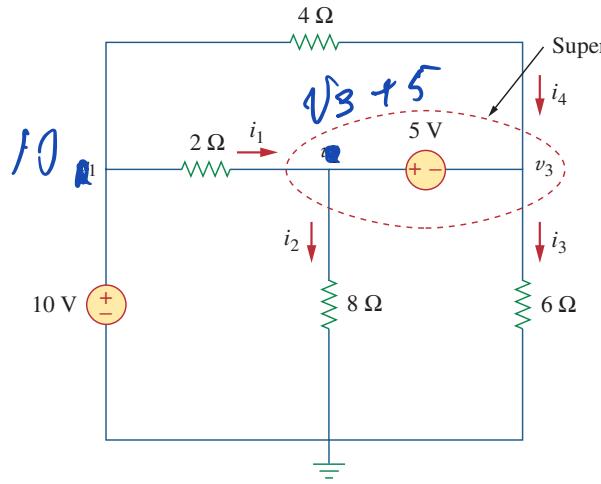3. Write a linked-node equation accounting for the currents leaving the region surrounding the 5V source. Please ignore the authors silly current labels. Do not write any other equations.



$$\frac{v_3}{6} + \frac{(v_3 - 10)}{4} + \frac{(v_3 + 5)}{8} + \frac{(v_3 + 5 - 10)}{2} = 0$$

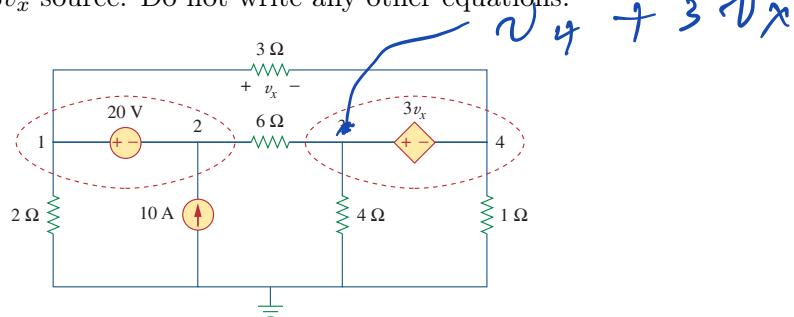
4. Write a linked-node equation accounting for the currents leaving the region surrounding the $3v_x$ source. Do not write any other equations.



$$\frac{v_4}{1} + \frac{(v_4 - v_1)}{3} + \frac{(v_4 + 3v_x)}{4} + \frac{(v_4 + 3v_x - v_2)}{6} = 0$$


There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

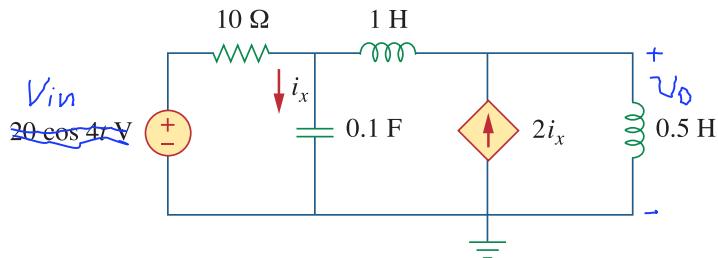1. How many distinct energy storage devices (dynamic elements) are in the circuit below? (Your answer should be a positive integer.)




3

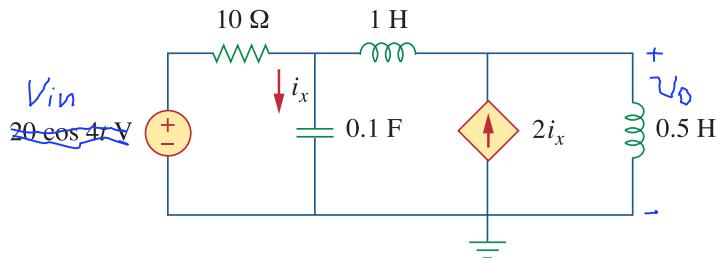2. We would expect the transfer function of this system $H_{vo}(s) = \frac{v_o}{V_{in}}$ to have denominator polynomial of order 3? (Fill in the blank. Your answer should be a positive integer.)




3

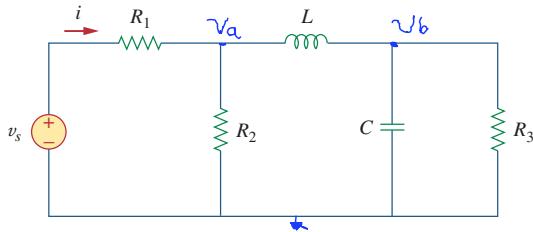3. Write a node equation at v_b . Please ignore other nodes. Do not write any other equations.



$$\frac{v_b}{R_3} + v_b \cdot C s + \frac{(v_b - v_a)}{L s} = 0$$

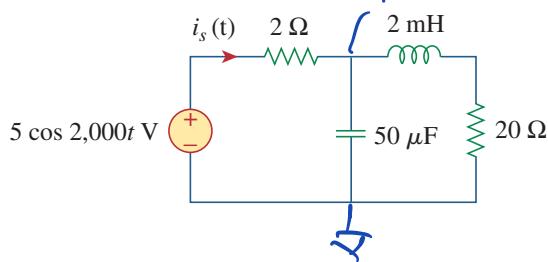
4. Write a node equation describing ~~the~~ circuit. Do not write any other equations. Do not solve.



$$v_a \cdot 50 e^{-6} s + \frac{(v_u - v_{in})}{2} + \frac{v_u}{2e^{-3} s + 20} = 0$$

There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

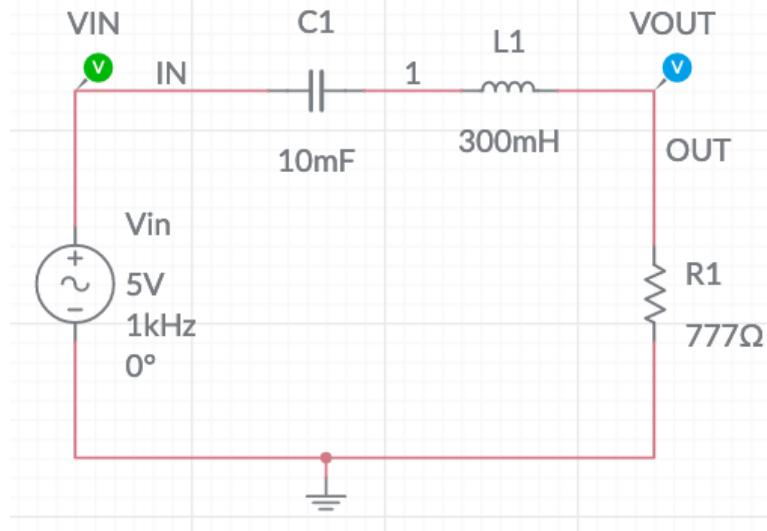1. Find the transfer function $H(s) = \frac{V_{OUT}}{V_{in}}$. Do not simplify or compute.



$$H(s) = \frac{777}{777 + 300e^{-3}s + \frac{1}{10e^{-3}s}}$$

2. An analysis of a certain circuit yields transfer function $H(s) = \frac{v_o}{V_{in}}$. If

$$V_{in}(t) = 20 \cos(100t + 0.3)$$


and

$$H(j * 100) = 0.6 \angle 0.2$$


Find $v_o(t) =$

$$v_o(t) = 20 \cdot 0.6 \cos(100t + 0.3 + 0.2)$$

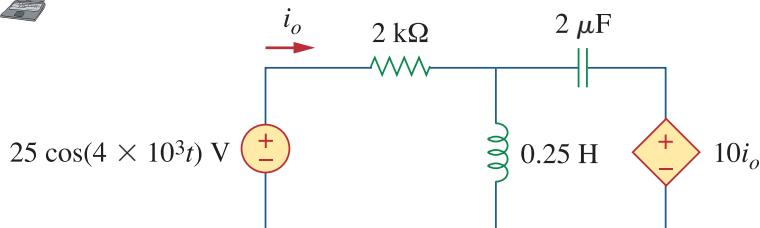
3. Draw the phasor-domain equivalent circuit for the circuit below.


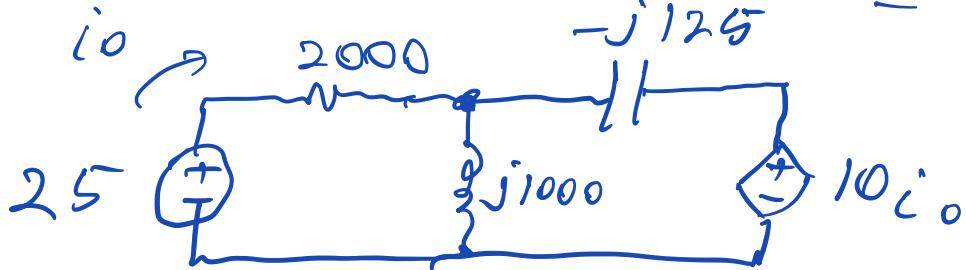
$$\frac{-j}{4000 \cdot 2 \times 10^{-6}} = -\frac{5000}{8}$$



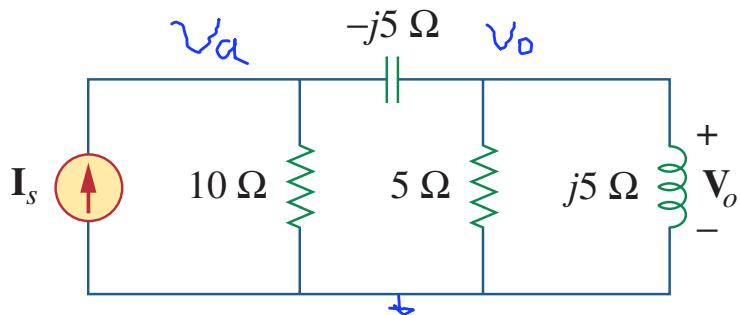4. Write a node equation at v_o . Do not write any other equations. Do not solve.




$$\frac{V_o}{5} + \frac{V_o}{j5} + \frac{(V_o - V_a)}{-j5} = 0$$

Sorry about the 5's.

There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

1. Find v due only to the 6V source.

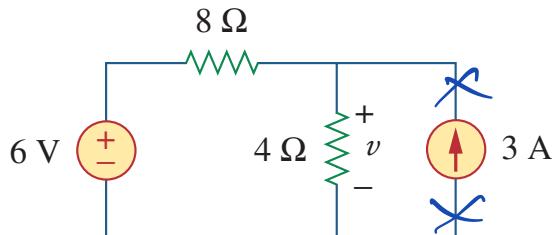

$$v = \frac{6 \cdot 4}{4 + 8} = 2 \text{ V}$$

2. The analysis of a certain circuit yields

$$v_o = \frac{11}{5} I_{in} + \frac{13}{5} V_{in}$$


Execution of the code below:

```
vx5A = eval(subs(vx, [Iin, Vin], [0, 10]))
```

yields what result?


$$\begin{aligned} v_o &= \frac{11}{5} \cdot 0 + \frac{13}{5} \cdot 10 \\ &= 26 \text{ V} \end{aligned}$$

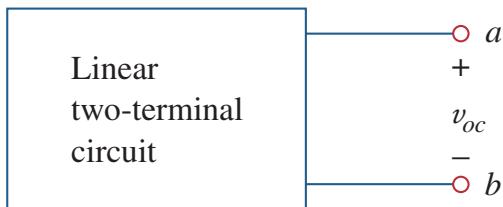3. For the system shown, it is found that $v_{oc} = 12V$.




$$V_{Th} = v_{oc}$$

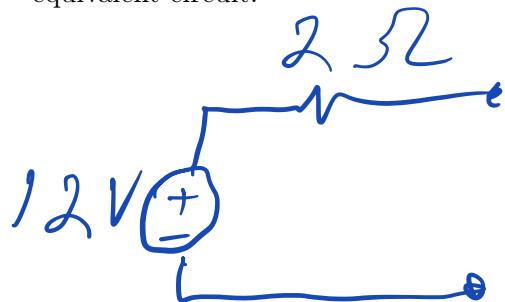When a 4Ω load is connected to $\{a, b\}$, v_{ab} is found to be 8V. Find and sketch the Thevenin equivalent circuit.



$$\frac{12 - 6}{4/4} = 2$$

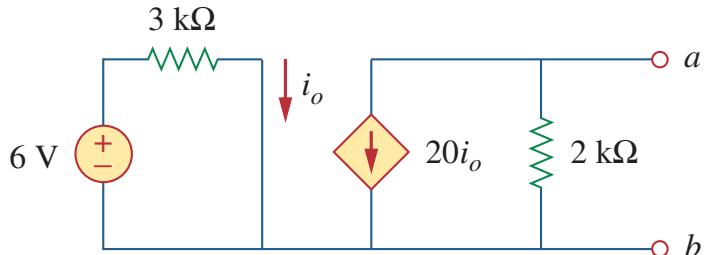4. Find the Thevenin voltage for the circuit below:



$$V_{Th} = -80 V$$

$$i_o = \frac{6 V}{3000} = 2 \text{ mA}$$


$$20i_o = 40 \text{ mA}$$

$$v_{ab} = -40 \text{ mA} \cdot 2000$$

$$= -80$$


There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

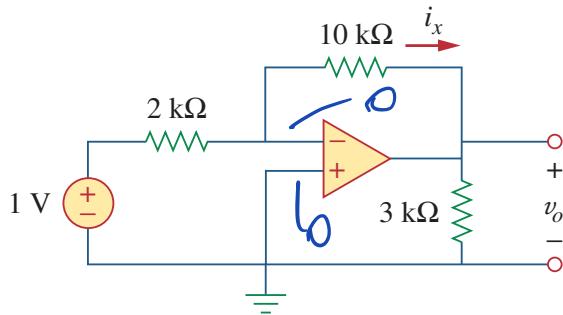1. Write a node equation you would use to find v_o .



$$\frac{0 - 1}{2000} + \frac{0 - v_o}{10000} = 0$$

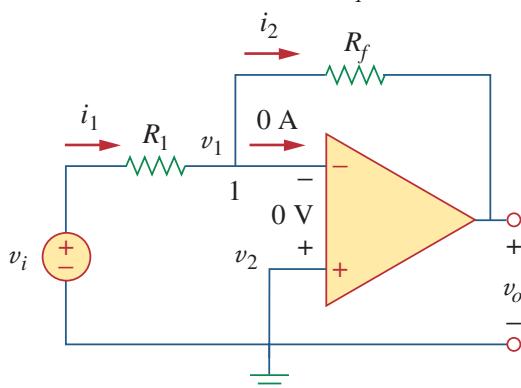
2. Find the transfer function, $\frac{v_o}{v_i} =$



$$v_o = v_i \left(-\frac{R_f}{R_1} \right)$$

$$H(s) = -\frac{R_f}{R_1}$$

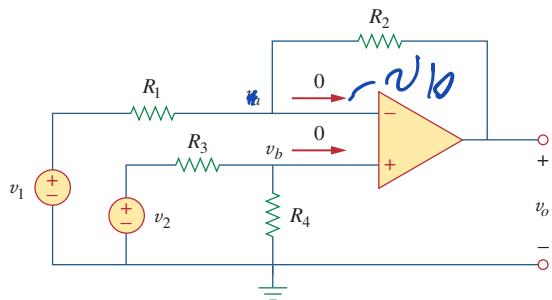
3. Write a node equation you would use to find v_o . Include any conveniently-labeled voltages. Do not simplify or solve.



$$\frac{(v_b - v_1)}{R_1} + \frac{(v_b - v_o)}{R_2} = 0$$

$$v_b = \frac{v_2 \cdot R_4}{R_3 + R_4}$$

4. Find $v_o =$. Do not simplify.

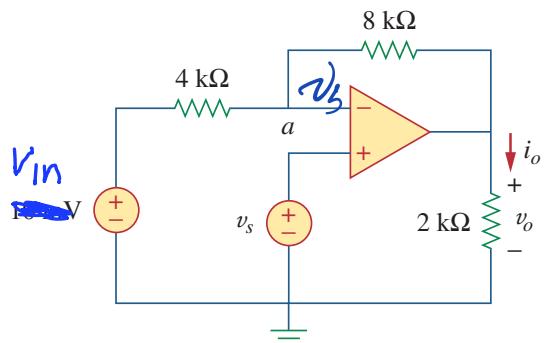


$$\frac{v_s - v_{in}}{4k} + \frac{v_s - v_o}{8k} = 0$$

$$v_o = v_s + \frac{(v_s - v_{in})}{4k}, 8k$$

$$v_o = 3v_s - 2v_{in}$$


There are 4 problems. Please address each question with a boxed, short, neatly-written answer.

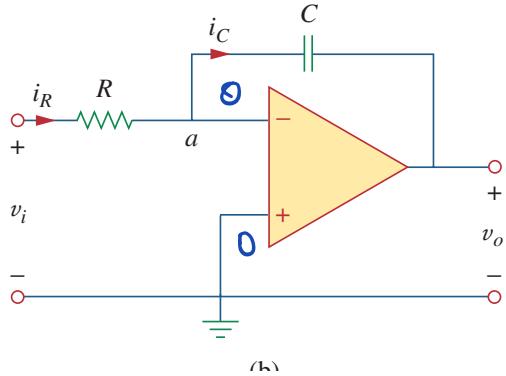1. Write a node equation you would use to find v_o . Ignore the authors current labels. Do not simplify or solve.



$$\left(\frac{v_o - v_i}{R} \right) + (0 - v_o) \cdot Cs = 0$$

2. Find the transfer function, $H(s)$.

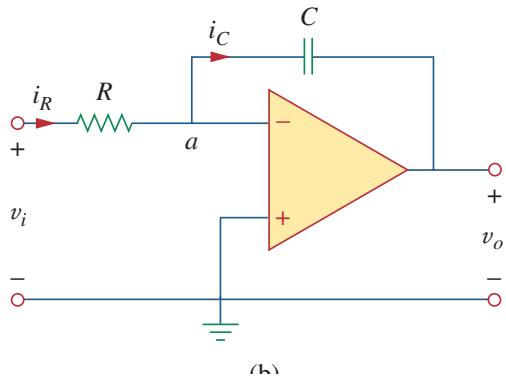


$$v_o = -\frac{v_i}{RCs}$$


$$H(s) = \frac{-1}{RCs}$$

Score: _____/20

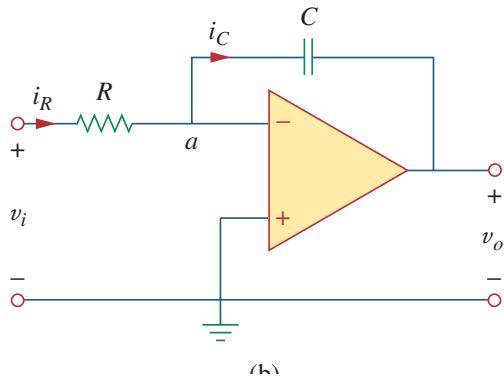3. This circuit is a realization of (choose one): a) High-pass filter, b) Low-pass filter, c) Band-pass filter.



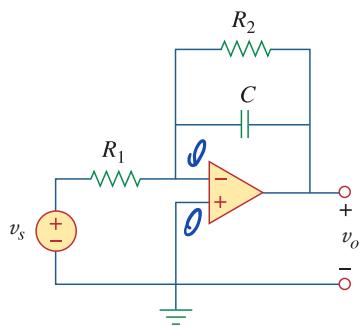4. Write a node equation you would use to find v_o . Do not simplify or solve.



$$\frac{(0 - v_s)}{R_1} + \frac{(0 - v_o)}{R_2} + (0 - v_o) \cdot C_s = 0$$