

## EE 3310L/5310L • Electronic Devices and Circuits Laboratory


### Lab 6: NPN Cascode Amplifier

#### Purpose

The purpose of this lab is to construct and test an NPN cascode amplifier using 2N3904 transistors and compare its performance to the basic common-emitter amplifier analyzed in Lab 5. The cascode configuration offers the high gain and relatively high input resistance of the common-emitter amplifier plus the wide bandwidth of the common-base amplifier due to the virtual elimination of Miller Effect input capacitance.

#### Procedure

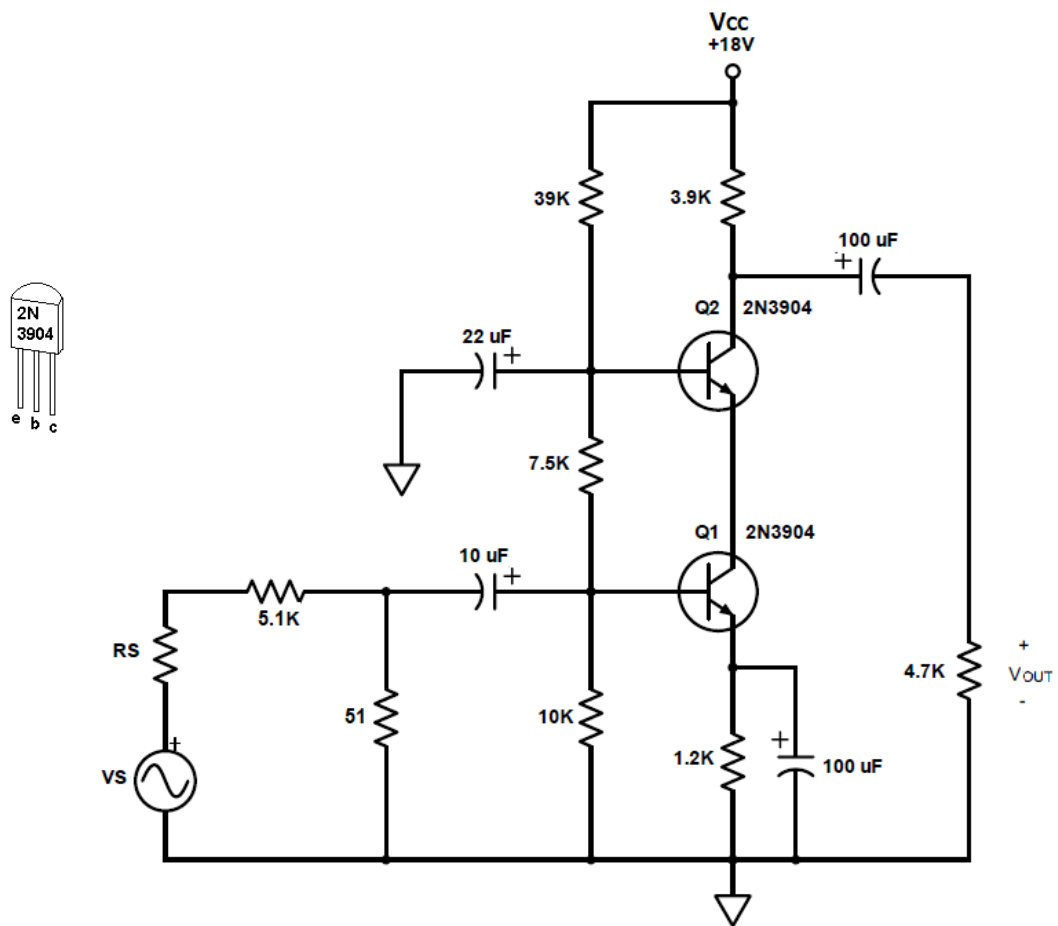- 1) Select two 2N3904 NPN transistors and use your DMM to measure and record their  $h_{FE}$ . Discard any transistor whose value is less than 100.
- 2) Build the following circuit. Measure and record all transistor DC voltages before applying an AC signal. For reference, you should measure approximately 2.5 V at the emitter of the input transistor if the circuit is built properly, for a quiescent emitter current of about 2 mA.



- 3) Connect channel 1 of the oscilloscope to the function generator and channel 2 to the output of the amplifier ( $V_{OUT}$ ).
- 4) Set the signal generator to 1 V<sub>p-p</sub>, 1 kHz sine and verify this amplitude on the oscilloscope. Display both channels simultaneously; **the output waveform should be an inverted sine wave.**
- 5) **Measure and record the peak-to-peak output voltage shown on the oscilloscope. Use it to calculate the 1-kHz gain of the amplifier by  $A_V = (V_{OUT}/V_S)$ . Also compute  $A_V(\text{dB})$ . Don't forget to divide  $V_S$  by 100, as this is the effective signal amplitude at the input of the amplifier due to the 40-dB input pad!**
- 6) Increase the frequency of the signal generator until the output has decreased 3 dB (i.e., the peak-to-peak voltage times 0.707). **Record the frequency; this is the upper cutoff frequency,  $f_H$ .**
- 7) Now decrease the frequency of the signal generator (below 1 kHz) until the output drops by 3 dB. **Record the frequency; this is the lower cutoff frequency,  $f_L$ .**
- 8) Return the signal generator to 1 kHz. **Increase the amplitude until the output waveform is visibly clipped; record the maximum peak-to-peak output voltage at clipping.**

#### Postlab

- 1) **Analytically determine all DC and AC parameters using equations we derived in class for the cascode configuration.** Show all work!
- 2) Simulate the circuit using Multisim; determine the DC values, midband gain, and high- and low-frequency cutoffs.
- 3) Compare simulated, experimental, and analytical values.