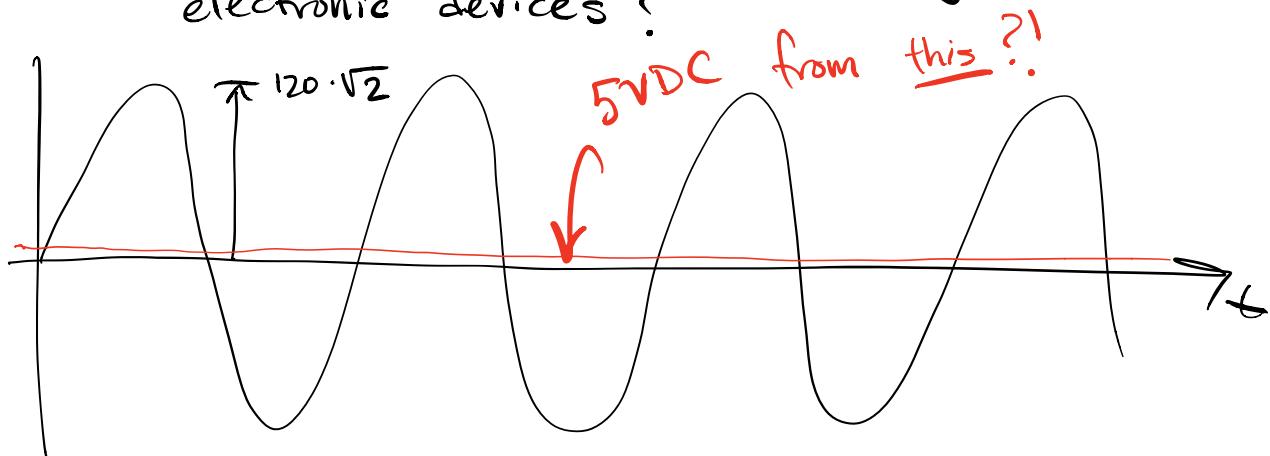


Rectification and Power Supplies

- linear power supply; not switching!
- how do you turn $120 \text{ V}_{\text{RMS}}$ @ 60 Hz (sine) into, say, 5 VDC for powering small electronic devices?




- 1.) use stepdown transformer to scale magnitude of AC voltage into more reasonable range
- 2.) use rectifier to make sine wave all positive [for now]
 - still not D.C.!

- 3.) Use capacitors and/or inductors to "smooth" the waveform into something much closer to D.C.
 - 4.) electronic voltage regulation will set precise voltage and make it almost perfect D.C.
-
- in power supplies, transformers are specified with primary and secondary voltages, not turns or turns ratio!
 - secondary voltage specified at rated load current.

rectifiers


- used to convert AC sine wave into one-direction (positive) waveform

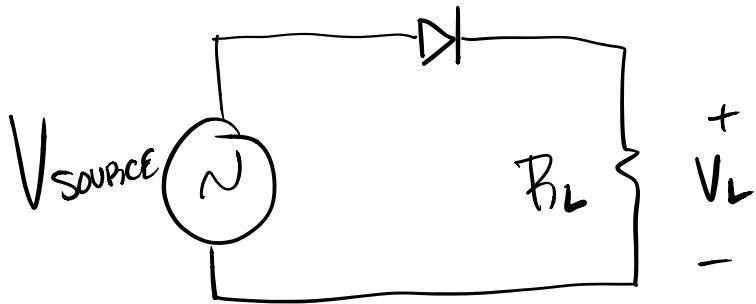half-wave rectifier : simplest, requires no transformer



- diode becomes forward biased only when $V_{SOURCE} > \sim 0.7V$

[Si diode]

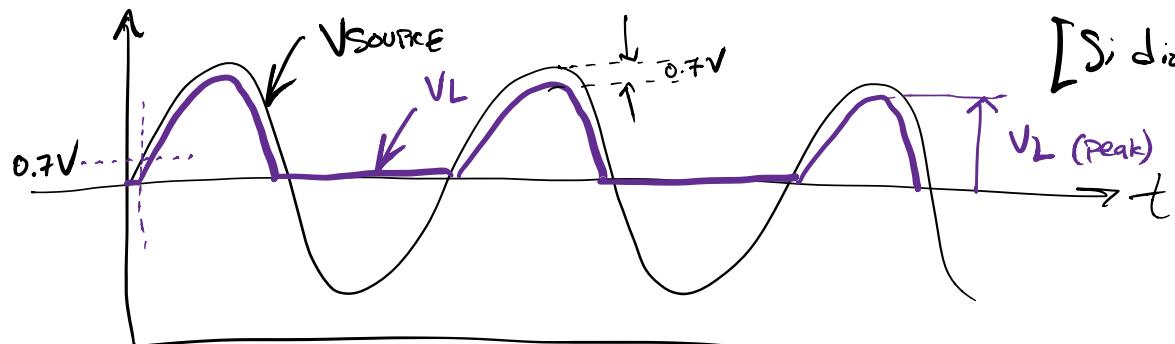


$$V_L(\text{peak}) = V_{\text{SOURCE(RMS)}} \cdot \sqrt{2} - 0.7$$

- one disadvantage of half-wave rectifier;
negative peaks simply ignored

- we need a more efficient circuit!

Center-tapped rectifier

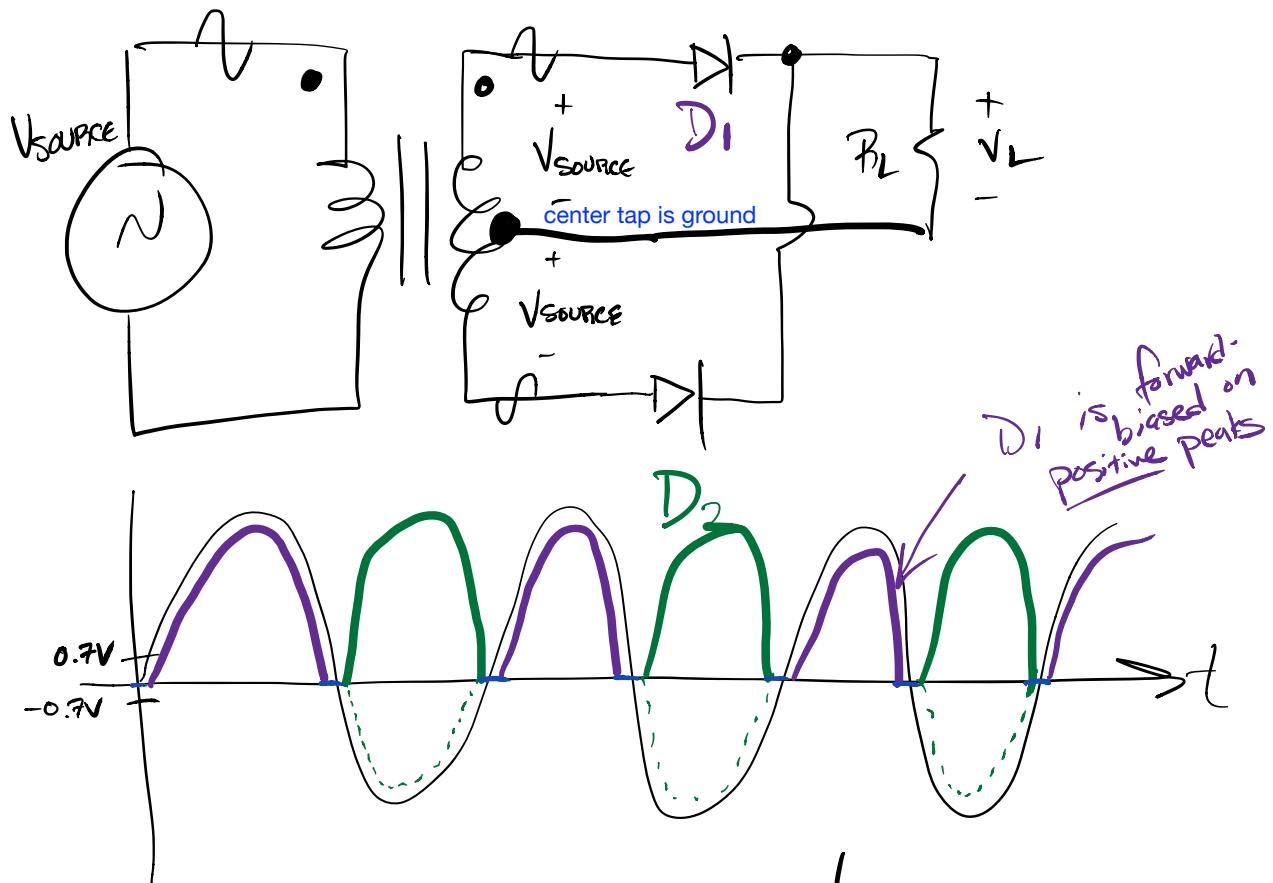- requires transformer secondary w/ center tap.



- full-wave rectification

$$V_L(\text{peak}) = V_{\text{SOURCE(rms)}} \sqrt{2} - 0.7$$

one half
of transformer
secondary.

assuming si diode


- Some transformer manufacturers will state secondary voltage as, for example:


12 - 0 - 12 V_{RMS} @ 2A

- Most would state "24 VCT" for the same secondary "center-tap"


- regular secondary w/ no center tap: "24 VAC"

full-wave bridge rectifier

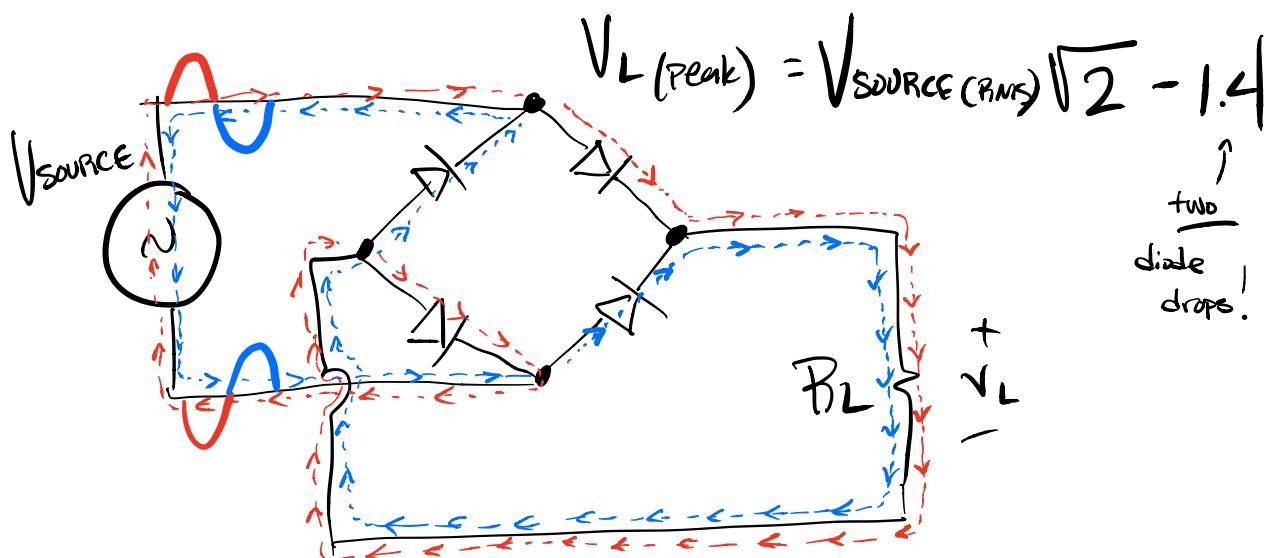

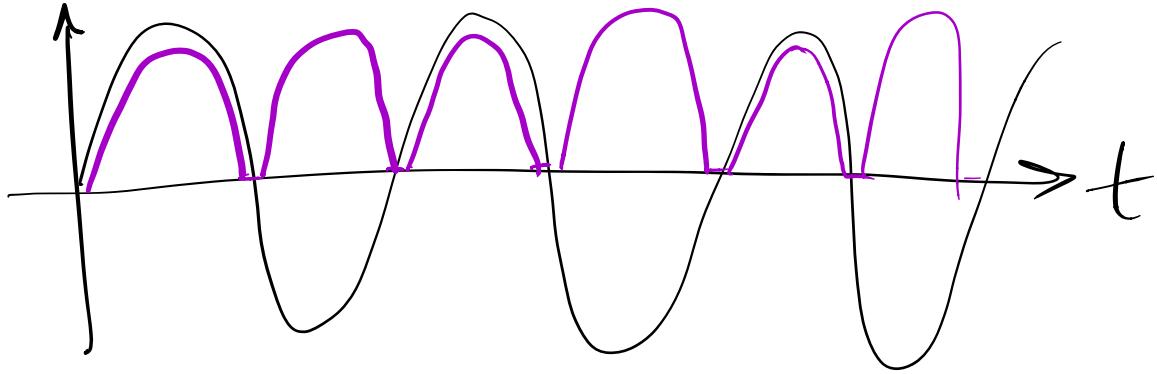


Voltage doubler :

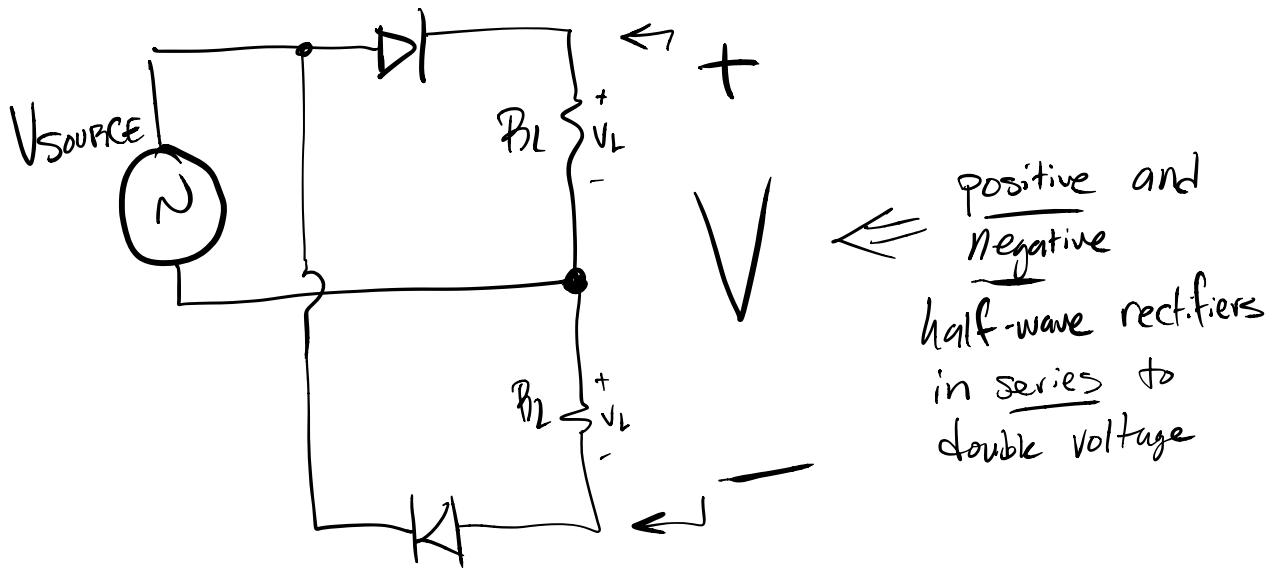

$$V_{\text{peak}} = 2 \cdot V_{\text{SOURCE(RMS)}} - \underbrace{2 \cdot 0.7}_{1.4V} \quad (\text{two diode voltage drops})$$


- a full-wave rectified sine wave is equivalent to the absolute value of a sine wave

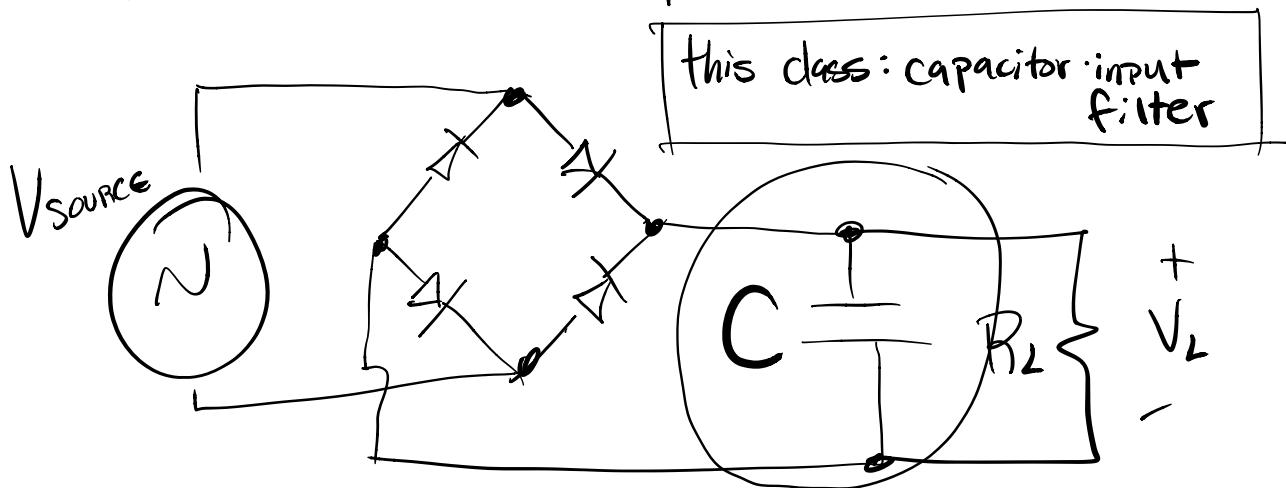- how do we turn it into D.C.?
- we must "smooth" those peaks with low-pass filter; leave D.C. component $f=0$, get rid of A.C. component



· purpose of capacitor is to store charge and attempt to hold V_L steady between rectified pulses

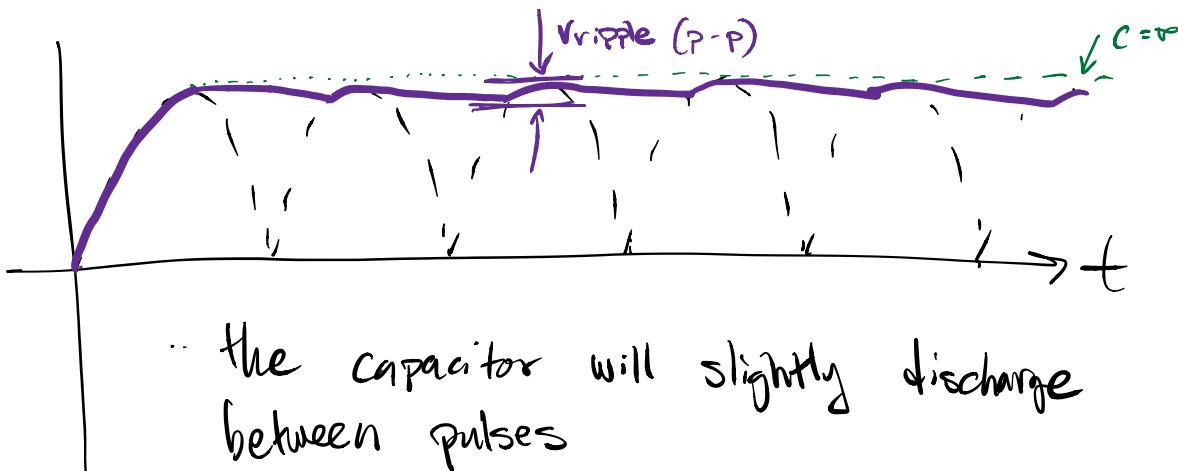· called "filter capacitor" or "reservoir capacitor" due to its dual functionality!



- the capacitor will slightly discharge between pulses
- these variations are called ripple
- if $C = \infty$ or $R_L = \infty$ (and thus no load current to discharge C), there would be zero ripple; perfect D.C.!
- ripple is measured in V_{P-P} ; typically we subtract half from peak rectified voltage to get an "average" V_L .