
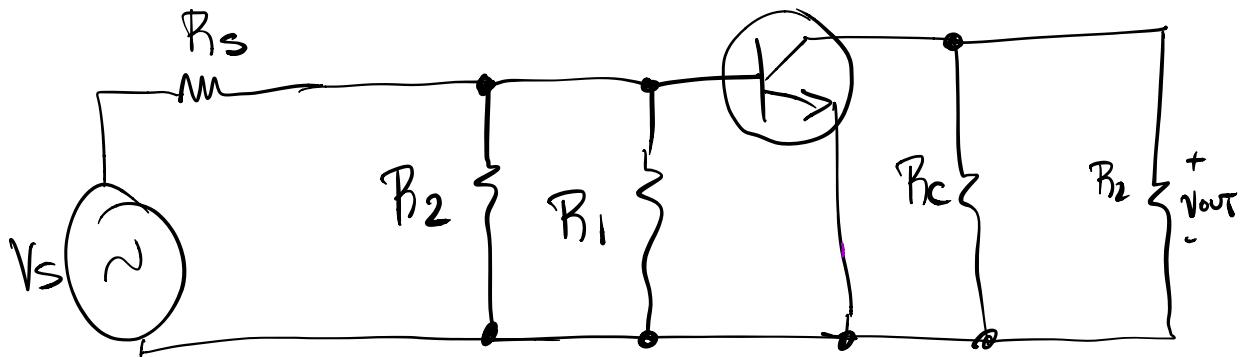


last time : mid-frequency AC Circuit


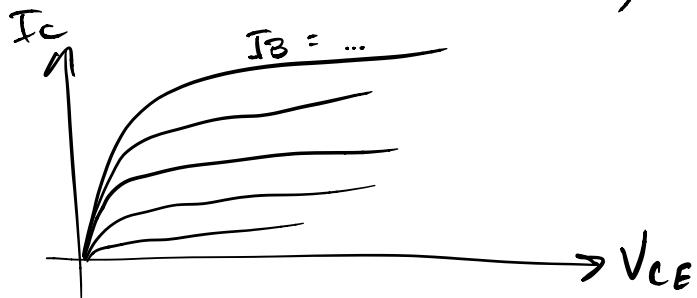


- how do we compute the gain of this amplifier?

- all active devices are non-linear;



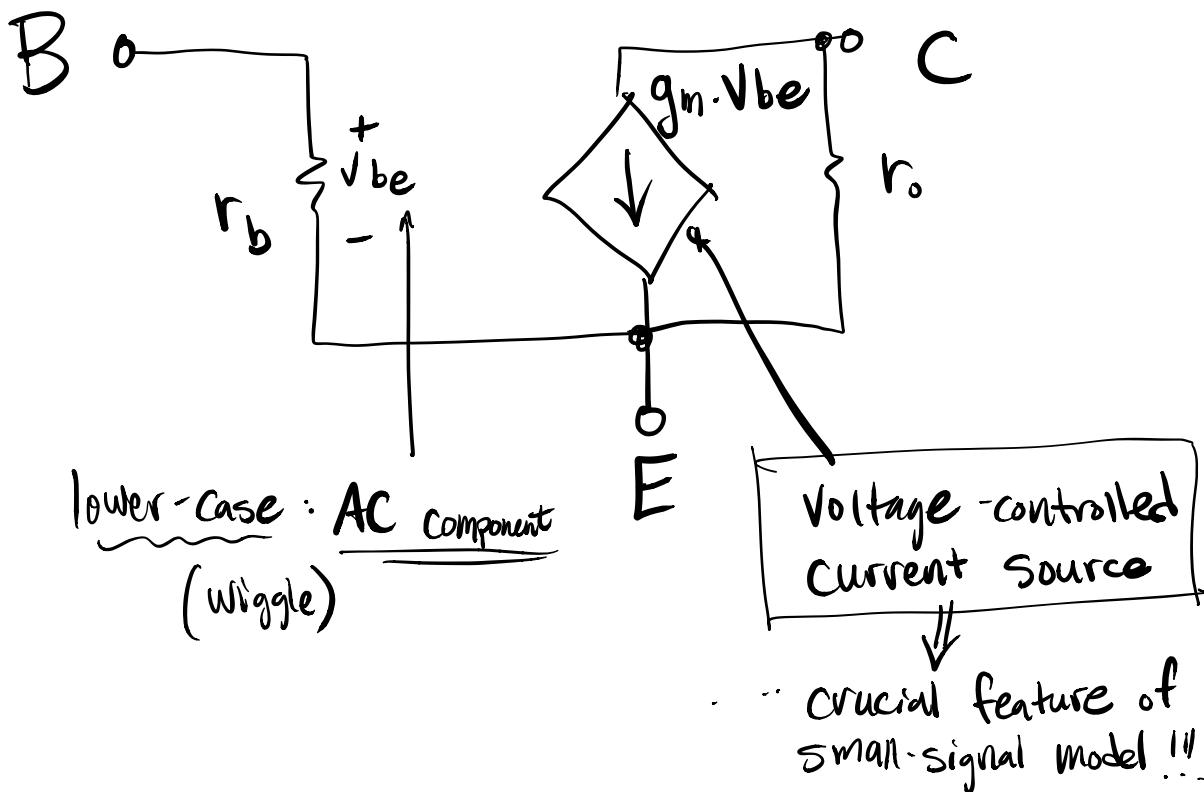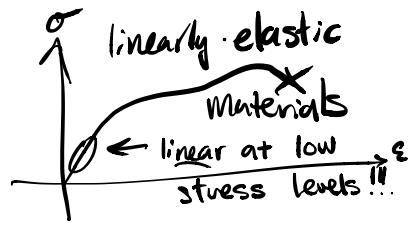- however, at small signal amplitudes we may use a linear model for the transistor!



- the small-signal AC voltage between base and emitter ( $V_{be}$ ) controls AC collector current by a parameter called mutual conductance,

$\text{g}_m$  (a/k/a transconductance)  
unit:  $\text{A/V}$ , or  $\text{mA/V}$  ... not siemens!  
... not mho or  $\Omega^{-1}$  !!!

- for Si transistors ①  $I_c < 100 \text{ mA}$ ,

$$g_m \approx 35 I_c$$

... where  $I_c$  is the DC collector current

[Fbers / Moll Equation]

- now we see why we do DC analysis first!!
- there are also a couple resistances in the model we need to deal with :


$r_b$  : small-signal resistance between base and emitter

$$r_b = \frac{\beta}{g_m}$$

$r_o$  : small-signal resistance in parallel w/  
current source


$$r_o = \frac{|V_A|}{I_C}$$

...  $V_A$  is called the Early voltage

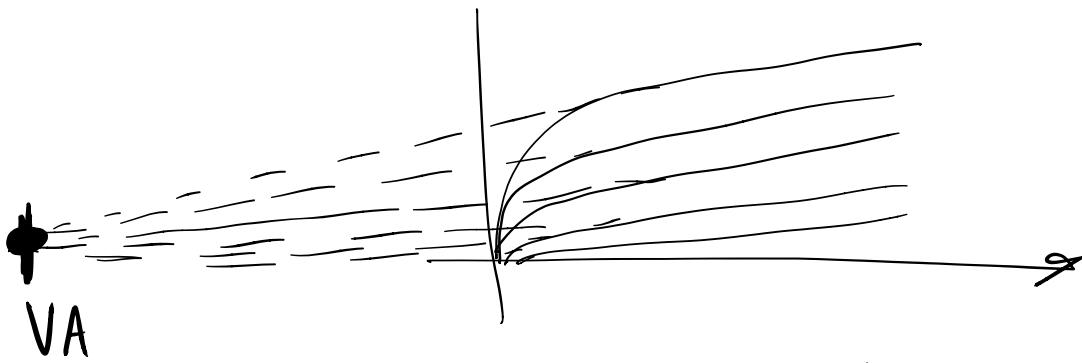

... Well use  $V_A = 100V$  in this class!

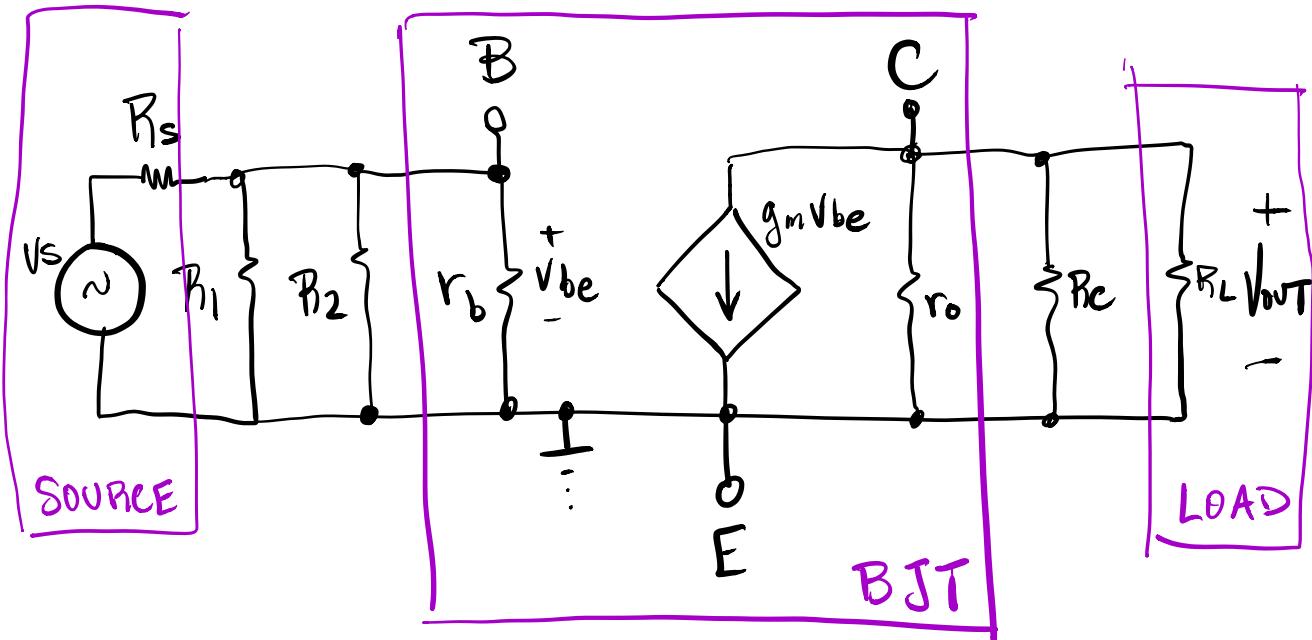.. We have enough information to draw a complete  
mid-frequency AC model of the  
common-emitter voltage amplifier :



• note:  $R_E$  is not in the model, because it is shorted by  $C_E$  at mid frequencies!

• We want to determine  $\frac{V_{out}}{V_S}$ .


That's the gain.

• We do this in two parts:

input stuff

and output stuff

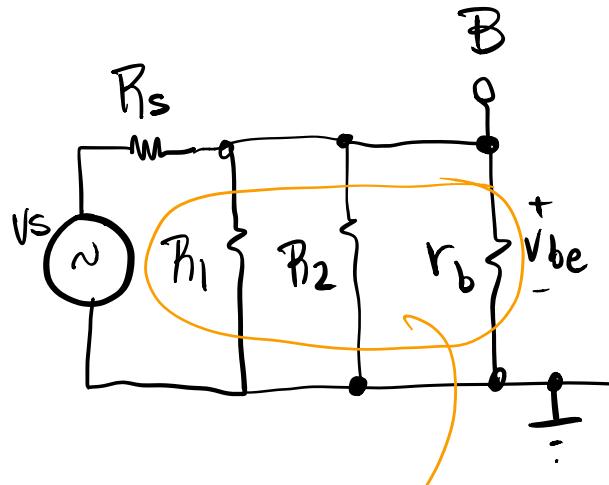- input stuff ( $A_{V_1}$ ) tells us the relationship between  $V_s$  and  $V_{be}$ ;  $\underbrace{A_{V_1} = \frac{V_{be}}{V_s}}$
- output stuff ( $A_{V_2}$ ) tell us the relationship between  $V_{be}$  and  $V_{out}$ ;  $\underbrace{A_{V_2} = \frac{V_{out}}{V_{be}}}$
- let's do  $A_{V_1}$  first.



- just voltage division !!!
- define  $R_{b'} = R_1 \parallel R_2 \parallel r_b$

then  $V_{be} = V_s \left[ \frac{R_b'}{R_s + R_b'} \right]$

need small-signal resistances and mutual conductance.

$$g_m = 35 I_c$$

$$= 35 \cdot 2.63$$

$$g_m = 92.05 \text{ mA/V}$$

$$r_b = \frac{\beta}{g_m} = \frac{200}{92.05} \rightarrow 2N3904$$

$$r_b = 2.173 \text{ k}\Omega$$

$$r_o = \frac{|V_A|}{I_C} = \frac{100}{2.63}$$

$$r_o = 38.02 \text{ k}\Omega$$

original circuit!

$$R_{b'} = R_1 \parallel R_2 \parallel r_b = \overbrace{62k \parallel 10k \parallel 2.173k}^{\text{!}}$$


$$R_{b'} = 1.735 \text{ k}\Omega$$

then  $A_{V_1} = \frac{V_{be}}{V_s} = \frac{R_{b'}}{R_{b'} + R_S} = \frac{1.735k}{1.735k + 50}$

↑  
Signal  
generator  
impedance  
in lab!

$A_{V_1} = 0.97$

now, output stuff

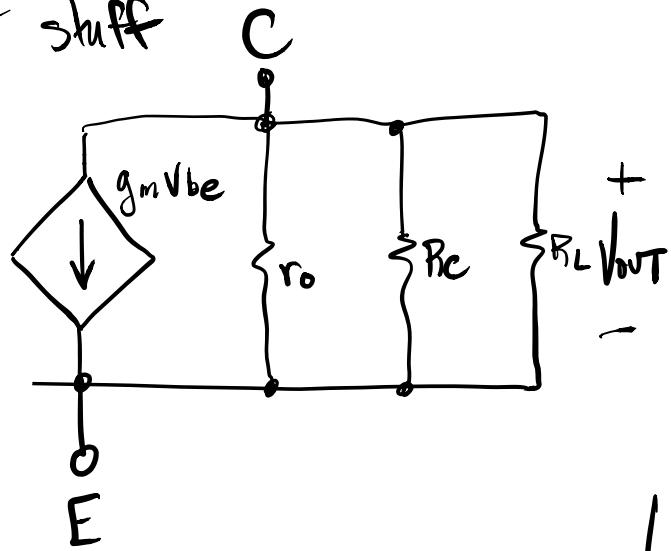

just current w/ parallel resistance

$$V_{\text{OUT}} = -g_m V_{\text{be}} (R'_c)$$

↓ direction of current source    .. important !!!!

Where  $R'_c = r_o \parallel R_c \parallel R_L$

$$= 38.02k \parallel 4.7k \parallel 10k$$

$$\underbrace{R'_c = 2.949 \text{ k}\Omega}$$

$$A_{V2} = \frac{V_{out}}{V_{be}} = -g_m \cdot R_C'$$

$$= 92.05 \cdot 2.949$$

~~$\times 10^3$~~   ~~$\frac{V}{A}$~~

$$\underline{A_{V2} = -271.5}$$

- final gain:  $\frac{V_{out}}{V_s} = A_{V1} \cdot A_{V2}$

$$= 0.97 \cdot \underline{-271.5}$$

$$\boxed{A_V = -263.3}$$

or 48.4 dB, inverting

- why does this amplifier invert?

positive change in  $V_s$


→ positive change in  $V_{BE}$

→ .. .. in  $I_c$

→ more drop across  $R_C$


... subtracts from  $V_{cc}$  more!!!

→ negative change in  $V_C$

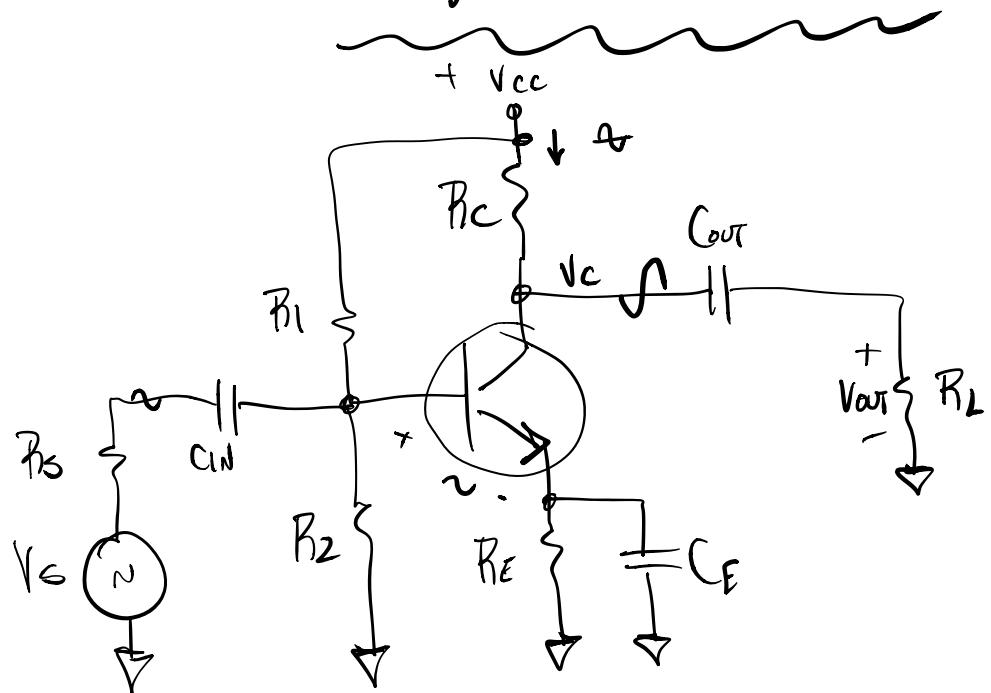


ex: 10 mV p-p sine @ MF  $\leftarrow 1 \text{ kHz}$

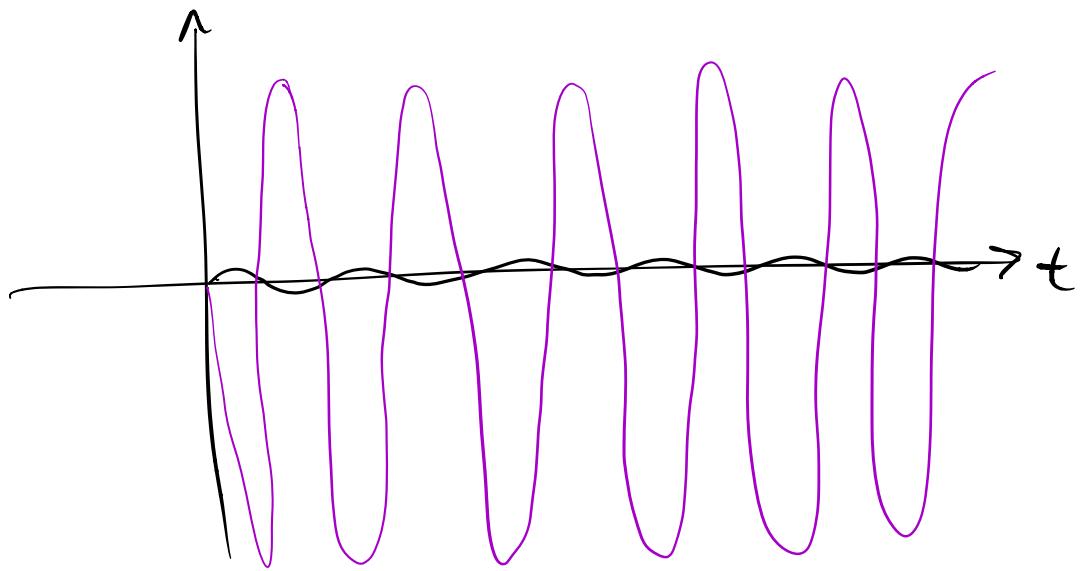
∴  $V_{out}$  will be  $.010 - .263.3 = -2.633 \text{ V}_{\text{p-p}}$



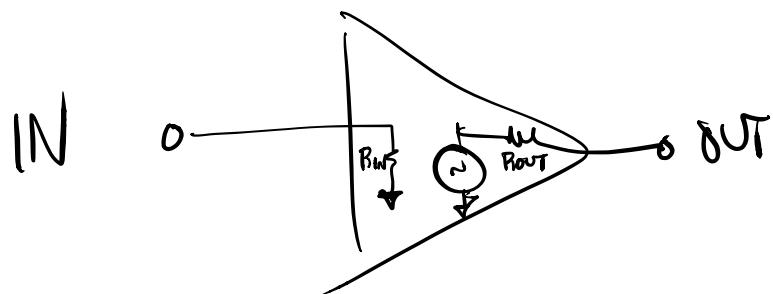- "linear model" implies perfect output sine wave with no added harmonic components
- just as important as mid-frequency gain are the input and output resistances,  
i.e., how does this amplifier look to the outside world?



- go back to input and output circuits!

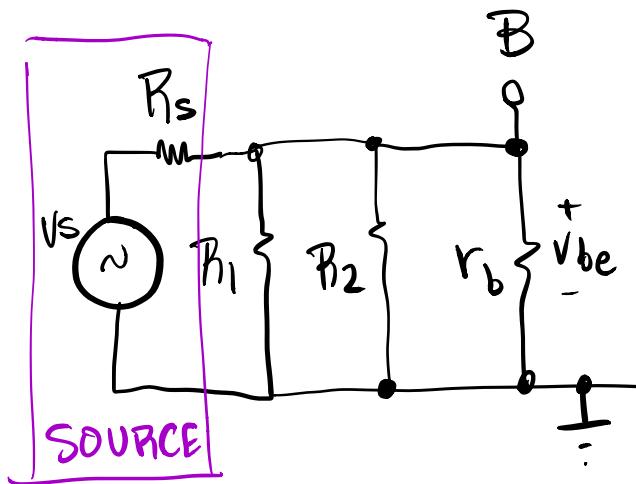


- from the source's perspective

$$R_{IN} = R_1 \parallel R_2 \parallel r_b = \underbrace{r_b}_1$$

$$\therefore R_{IN} = 1.735 \text{ k}\Omega$$

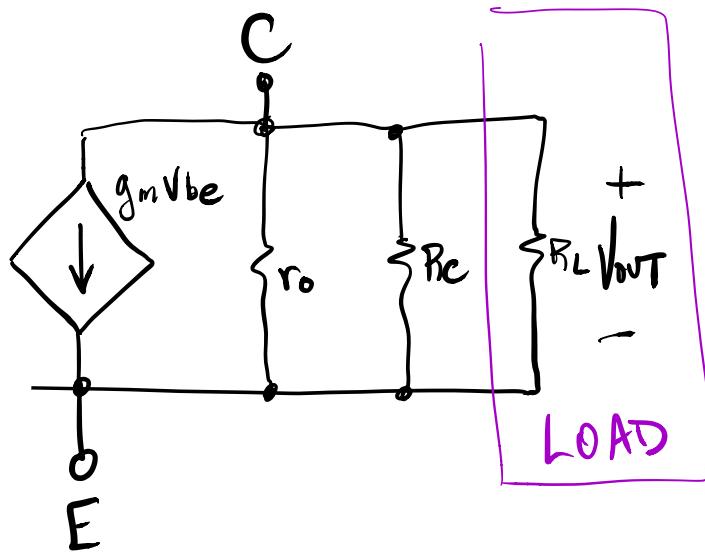- terrible compared to op-amps ( $M\Omega$  range)



- from the load's perspective:

$$\begin{aligned}
 R_{\text{OUT}} &= r_o \parallel R_c \\
 &= 38.02 \text{ k} \parallel 4.7 \text{ k}
 \end{aligned}$$

$$\underbrace{R_{\text{OUT}} = 4.185 \text{ k}\Omega}_{}$$

- again, compared to op-amp output  $Z$  of tens of ohms, terrible - (We can fix both!)