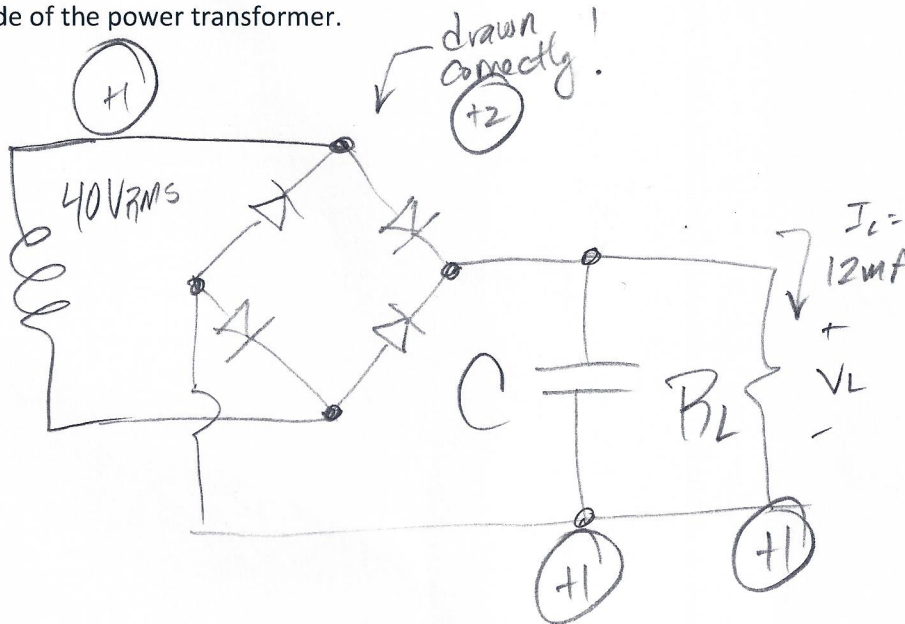


A transformer secondary voltage of **40 V_{RMS}** is connected to a full-wave bridge rectifier and capacitor-input filter. Determine the value of capacitor that will achieve **less than 1% ripple** at a load current of **12 mA**, and choose the nearest commercially-available part. Also determine the voltage ratings of the capacitor and diodes, and choose a 1N400X-series diode. Finally, draw the circuit and determine the final output voltage. You do not need to show the primary side of the power transformer.



$$\begin{aligned}
 \text{Final } V_L &= V_{\text{peak}} - \frac{1}{2} V_{\text{ripple}} \\
 &= 55.16 - \frac{1}{2} \cdot 0.5516 \\
 &= 54.88 \text{ V}
 \end{aligned}$$

$$V_{\text{peak}} = V_{\text{secondary}} \sqrt{2} - 2 \cdot 0.7 = 40\sqrt{2} - 1.4 = 55.16 \text{ V}$$

$$V_{\text{ripple}} \approx \frac{I_L}{2fC} \rightarrow C = \frac{I_L}{2fV_{\text{ripple}}}$$

$$V_{\text{ripple}} = 55.16 \times 0.01 = 0.5516 \text{ V}$$

$$\therefore C = \frac{0.012}{2 \cdot 60 \cdot 0.5516} = 1.813 \times 10^{-4} \text{ or } 181.3 \mu\text{F}$$


Use 220 μF

Cap Voltage should be 63V (standard value)

$$\text{PIV} > \sqrt{2} V_s = \sqrt{2} \cdot 40 = 56.57 \text{ V use } 100 \text{ V diode}$$

1N4002

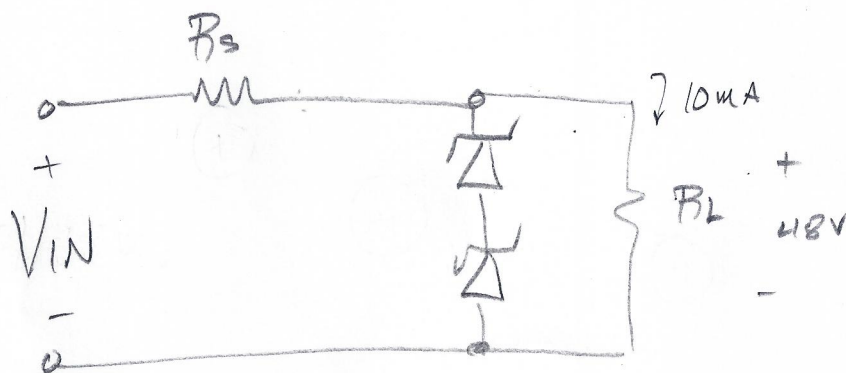Design a Zener regulator for the above power supply that achieves a final output voltage of **48 V @ 10 mA load current**.
 Set minimum Zener current to 2 mA. Choose an E24 value for R_s , and determine the power in each component. Note: 48 V is not an E24 value, so use two 24V Zener diodes in series (yes, this works, and each one only has to handle half the power!).



$$\therefore V_{IN(\min)} = V_{\text{peak}} - V_{\text{ripple}} = 55.16 - 0.5516 \\ = \underline{54.61 \text{ V}} \quad (+2)$$

$$\therefore R_s = \frac{V_{IN(\min)} - 48}{I_L + I_{Z(\min)}} = \frac{54.61 - 48}{0.010 + 0.002} \\ = \underline{550.8 \Omega} \quad (+2) \quad \left(\begin{array}{l} \text{usually round down} \\ \text{to ensure min. } I_Z, \\ \text{but close enough} \end{array} \right)$$

$$\text{Use } \underline{R_s = 560 \Omega} \quad (+1) \quad (\text{E24})$$

$$P_{R_s} = I^2 R = (0.010 + 0.002)^2 \cdot 560 = 0.08064 \text{ W}$$

$$[\text{use anything; } 1/4 \text{ W etc.}] \quad (+2)$$

$$P_{Z_{\max}} = I_{Z_{\max}} V_Z = 0.012 \cdot 24 = \underline{0.288 \text{ W}} \quad (+2) \\ \quad \quad \quad \uparrow \\ \quad \quad \text{each} \quad \left(\frac{1}{2} \text{ W Zeners will be fine} \right)$$

Design a relay circuit that will energize the 120V primary of the power supply you just designed from a **24VAC source located far away**. Show the primary circuitry, and assume the relay has both N/C and N/O contacts available. Include a snubber network and fuse in your circuit.

