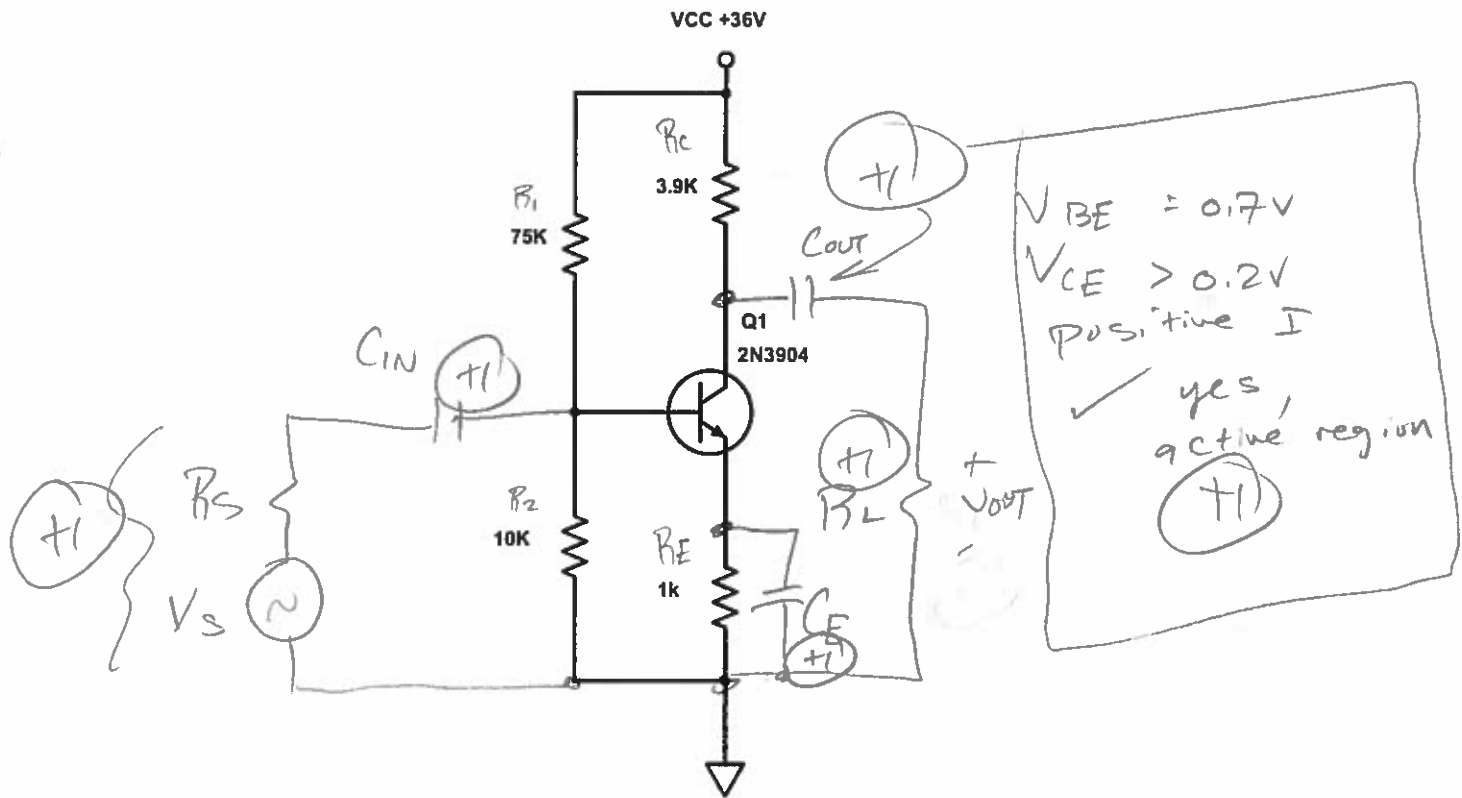


Determine the D.C. operating point of the following circuit (I_C and V_{CE}) if base current may be assumed negligible. Check P_{diss} and verify that the transistor is operating in the active region. Draw additional components on the circuit to create a common-emitter voltage amplifier with a source resistance of $600\ \Omega$ and a load resistance of $25\ \text{k}\Omega$. Don't worry about the actual values of added capacitors yet; just draw them correctly.



$$V_B = V_{CC} \left[\frac{R_2}{R_1 + R_2} \right] = 36 \left[\frac{10k}{10k + 75k} \right] = 4.235 \text{ V} \quad (+1)$$

$$V_{BE} = 0.7 \text{ V (Si NPN)} \quad (+1)$$

$$V_E = 4.235 - 0.7 = 3.535 \text{ V} \quad (+1)$$

$$I_E = \frac{3.535}{1k} = 3.535 \text{ mA} \quad (+1)$$

$$\text{high-}\beta \rightarrow I_C = 3.535 \text{ mA} \quad (+1)$$

$$V_C = V_{CC} - I_C R_C = 36 - 3.535 \cdot 3.9 = 22.21 \text{ V} \quad (+1)$$


$$V_{CE} = V_C - V_E = 22.21 - 3.535$$

$$V_{CE} = 18.68 \text{ V}$$

$$P_{diss} = I_C \cdot V_{CE} = 3.535 \cdot 18.68 = 66.02 \text{ mW} \quad (+1)$$

Draw the mid-frequency AC small-signal model of the amplifier. Calculate the parameters g_m , r_b , and r_o if $\beta = 250$. and $|V_A| = 50V$. Include a unit with each answer.

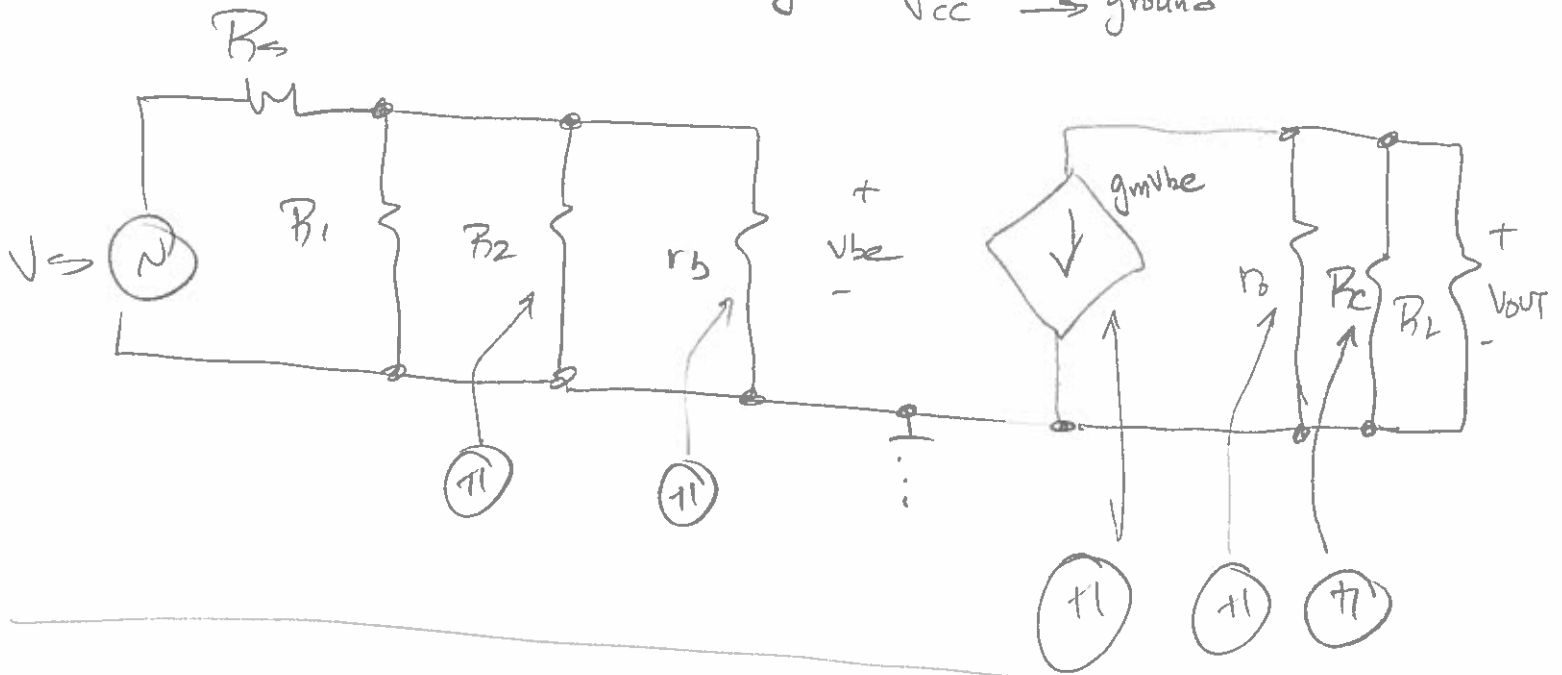mid-frequency : capacitors \rightarrow shorts
 $V_{CC} \rightarrow$ ground



$$g_m = 35 I_C \text{ (Ebers/Moll)} \quad (+1) \text{ eqn}$$

$$= 35 \cdot 3.535$$

$$g_m = 123.7 \text{ mA/V}$$

(+1) unit

$$r_b = \frac{\beta}{g_m} = \frac{250}{123.7} = 2.021 \text{ k}\Omega$$

(+1) unit

$$r_o = \frac{|V_A|}{I_C} \quad (+1) \text{ eqn}$$

$$= \frac{50}{3.535}$$

$$= 14.14 \text{ k}\Omega$$

(+1) unit

Determine the mid-frequency gain A_v and $A_v(\text{dB})$. ~~Also calculate the approximate $A_v(\text{dB})$ with C_E removed.~~

input network :

$$R_b' = R_1 \parallel R_2 \parallel r_b = 10k \parallel 75k \parallel 2.021k = 1.644k \quad (+1)$$

$$V_{be} = V_s \left[\frac{R_b'}{R_b' + R_{in}} \right] = V_s \left[\frac{1.644}{0.6 + 1.644} \right] = 0.7327 V_s \quad (+1)$$

output network :

$$R_c' = r_o \parallel R_c \parallel R_L = 14.14k \parallel 3.9k \parallel 25k = 2.724k \quad (+1)$$

$$V_{out} = -g_m V_{be} \cdot R_c' \quad (+1)$$


$$= -123.7 \cdot 0.7327 V_s \cdot 2.724$$

$$V_{out} = -246.9 V_s$$

$$A_v = -246.9 \quad (+1) \quad \text{or} \quad +47.85 \text{ dB, inverting} \quad (+1)$$

Draw the low-frequency small-signal model including C_E . You do not have to compute anything because you don't know the capacitor values.

AC circuit.

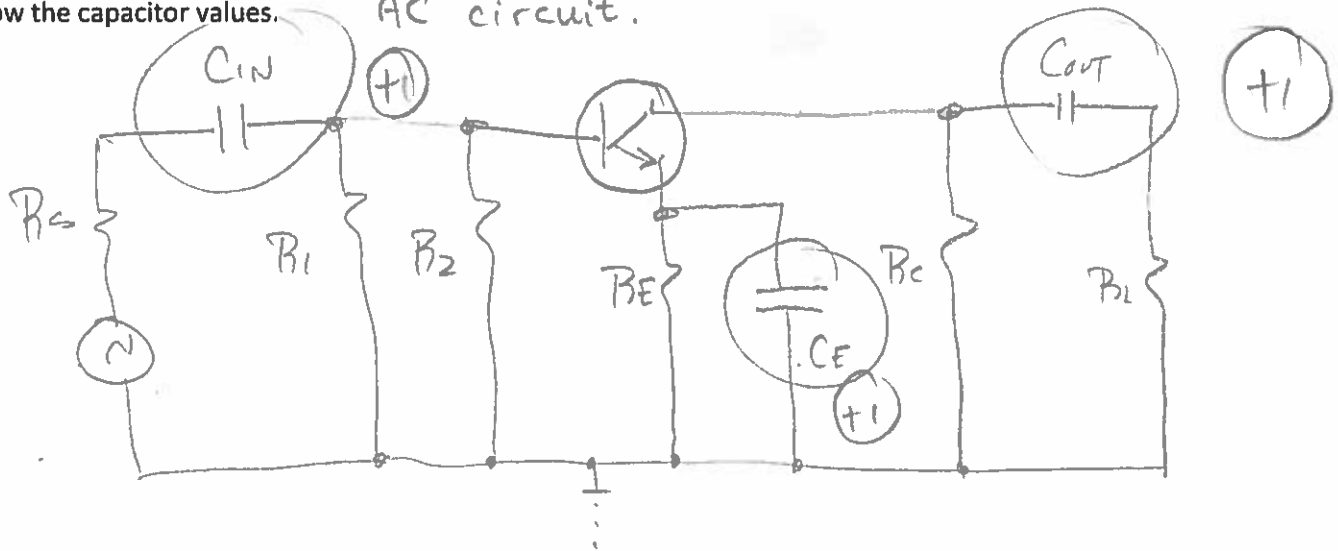

Determine the high-frequency input and output capacitances using Miller's Theorem if $C_{BC} = 6 \text{ pF}$ and $C_{BE} = 22 \text{ pF}$.

Compute the input and output HF cutoff frequencies and the approximate overall high-frequency cutoff, f_H .

~~Assume the following circuit configuration~~

$$\begin{aligned} C_{BC(IN)} &= C_{BC} (1 - A_V) \quad (+1) \text{ eqn} \\ &= 6 \cdot (1 - -246.9) \\ &= \underline{1487 \text{ pF}} \quad (+1) \end{aligned}$$

$$\begin{aligned} C_{BC(OUT)} &= C_{BC} \left(1 - \frac{1}{A_V}\right) \approx C_{BC} \\ &= \underline{6 \text{ pF}} \quad (+1) \end{aligned}$$

$$\begin{aligned} C_{IN(HF)} &= C_{BC(IN)} + C_{BE} \\ &= 1487 + 22 \\ &= \underline{1509 \text{ pF}} \quad (+1) \end{aligned}$$

$$\rightarrow f_{H(IN)} = \frac{1}{2\pi \cdot C_{IN} \cdot (R_b \parallel R_s)} = \frac{1}{2\pi \cdot 1509 \times 10^{-12} \cdot (1.644 \text{ k} \parallel 600)} = 240 \text{ kHz} \quad (+1)$$

$\uparrow = 440 \Omega$

$$C_{OUT(HF)} = \underline{6 \text{ pF}} \quad (+1)$$

$$f_{H(OUT)} = \frac{1}{2\pi \cdot C_{OUT} \cdot (R_{out} \parallel R_L)} = \frac{1}{2\pi \cdot 6 \times 10^{-12} \cdot 2.724 \text{ k}} = 9.7 \text{ MHz} \quad (+1)$$

$$\underline{f_H \approx 240 \text{ kHz}} \quad (+1) \quad (\text{dominant pole; } \rightarrow \text{ s/s separation})$$