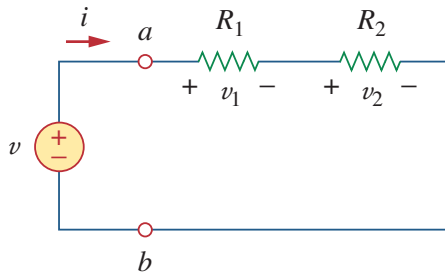


These notes are drawn from *Alexander and Sadiku*, 2013, *O'Malley*, 2011, and other sources. They are intended to offer a summary of topics to guide you in focused studies. You should augment this handout with notes taken in class, reading textbook(s), and working additional example problems.

**Definition:** *Resistors in Series:*



**Figure 2.29**


A single-loop circuit with two resistors in series.

Notice that KVL implies:  $v = v_1 + v_2$  or  $v = i(R_1 + R_2)$  so that  $i = \frac{v}{(R_1 + R_2)}$ . From this result, we can find  $v_1$  as a *voltage division*

$$v_1 = iR_1 = \frac{vR_1}{(R_1 + R_2)}$$

Also notice that the *electrically-equivalent* element is


$$R_{eq} = R_1 + R_2$$

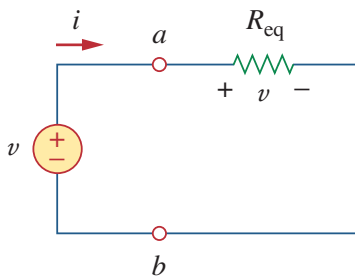

**Figure 2.30**

Equivalent circuit of the Fig. 2.29 circuit.

**Definition:** *Resistors in Parallel:*

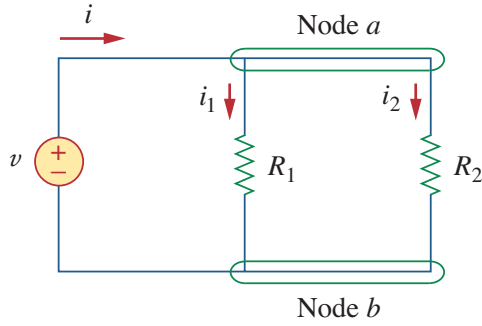

**Figure 2.31**

Two resistors in parallel.

Ohm's law and KCL implies:  $i_1 = \frac{v}{R_1}$ ,  $i_2 = \frac{v}{R_2}$ , and  $i = i_1 + i_2$ . The total current can be rewritten as

$$i = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2} = v \frac{R_1 + R_2}{R_1 R_2} = \frac{v}{R_{eq}}$$

where the *electrically-equivalent* element is

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

or more generally:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Now, since  $v = i R_{eq} = i \frac{R_1 R_2}{R_1 + R_2}$  and  $i_1 = \frac{v}{R_1}$ , we can find  $i_1$  as a *current division*, as

$$i_1 = i \frac{R_2}{R_1 + R_2}$$

## Impedance Element Combinations

We will soon include the consideration of *dynamic* elements, i.e., capacitors and inductors. These are modeled as more general *impedances*. In particular, for resistors with value  $R$ , capacitors with value  $C$ , and inductors with value  $L$ , these are given, respectively, as

$$Z_R = R, \quad Z_C = \frac{1}{C \cdot s}, \quad Z_L = L \cdot s$$

where  $s$  is the *Laplace Transform* variable. Nonetheless, the impedance combination rules reflect those for resistors as:

*Impedances in Series:*


$$Z_{eq} = Z_1 + Z_2 + Z_3 + \cdots$$

*Impedances in Parallel:*

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \cdots$$




Examples:

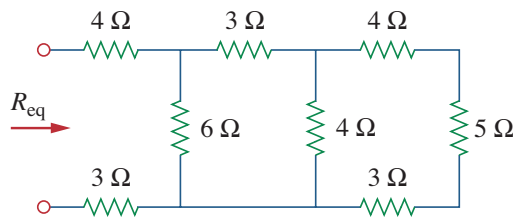


**Figure 2.36**

For Practice Prob. 2.9.

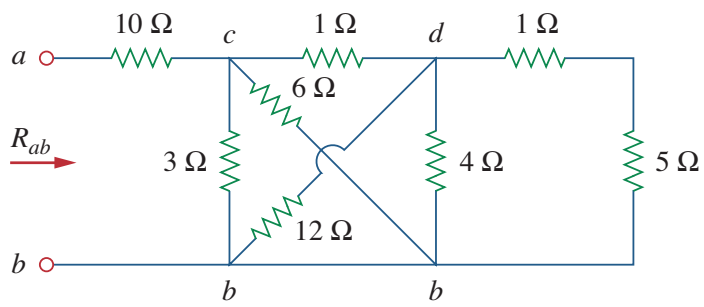


**Figure 2.37**  
For Example 2.10.

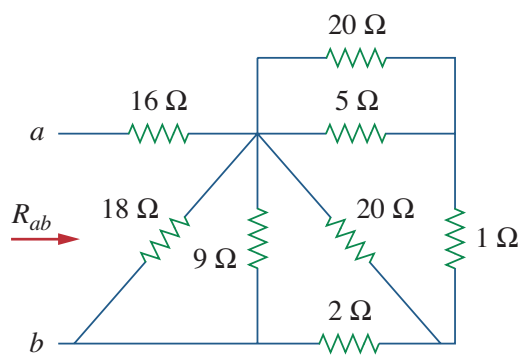

**Figure 2.39**

For Practice Prob. 2.10.

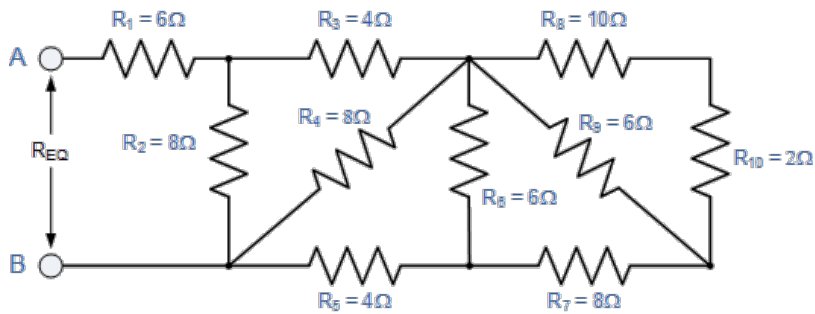Numerical computation packages can be useful in quickly solving otherwise tedious tasks. For example:



```
>> SeriesParallelExample1
Req =
    10
>>
```

where the script, `SeriesParallelExample1.m` is given by

#### %% Example in notes


```
% For the circuit shown, we can move from right to left and simply dictate
% the resistor connections with + representing series and the function
% parallel() (which is Latin for parallel) representing parallel.
% Note: I could not use the function name "parallel" since Matlab already
% has a function of this name, but not for circuit analysis.
```

```
Req = 6+parallel(8,4+parallel(8,4+parallel(6,8+parallel(6,10+2))))
```

```
% Here's the function definition:
```

```
function requivalent = parallel(varargin)
    nargs = length(varargin);
    admittance = 0;
    for k = 1:nargs % add the admittances (the 1/R's)
        admittance = admittance + 1/varargin{k};
    end
    requivalent = 1/admittance; % do the inverse
end
```

```
% results in: Req = 10
```

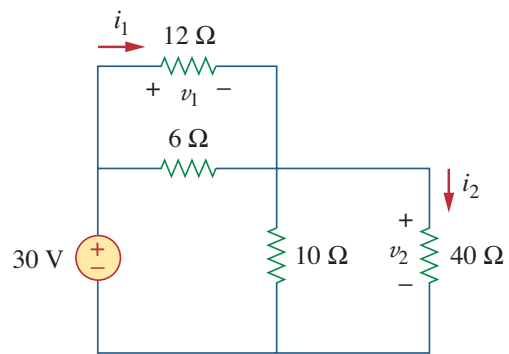


**Figure 2.43**  
For Practice Prob. 2.12.



**Homework 04:** Chapter 2 # 23, 26, 27, 30, 31, 34, 35, 37, 38, 39, 42, 43




- 2.23** In the circuit shown in Fig. 2.87, determine  $v_x$  and the power absorbed by the  $12\text{-}\Omega$  resistor.

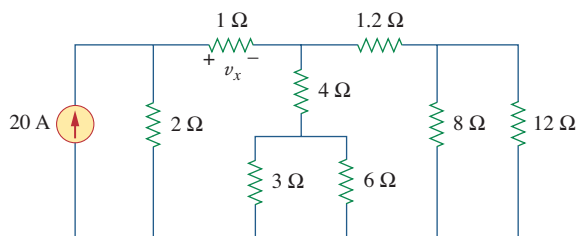

**Figure 2.87**

For Prob. 2.23.


- 2.24** For the circuit in Fig. 2.88, find  $V_o/V_s$  in terms of  $\alpha$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$ . If  $R_1 = R_2 = R_3 = R_4$ , what value of  $\alpha$  will produce  $|V_o/V_s| = 10$ ?

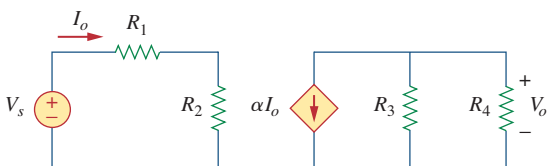

**Figure 2.88**

For Prob. 2.24.

- 2.25** For the network in Fig. 2.89, find the current, voltage, and power associated with the  $20\text{-k}\Omega$  resistor.

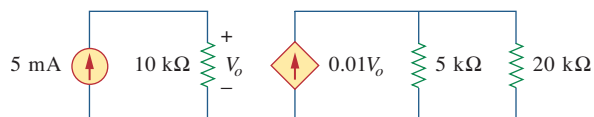


**Figure 2.89**

For Prob. 2.25.

### Sections 2.5 and 2.6 Series and Parallel Resistors


- 2.26** For the circuit in Fig. 2.90,  $i_o = 3\text{ A}$ . Calculate  $i_x$  and the total power absorbed by the entire circuit.

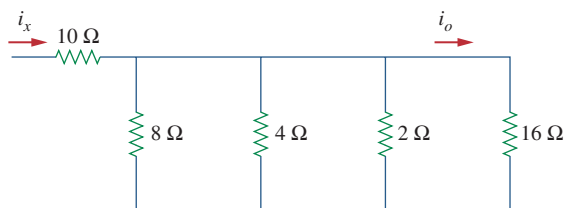

**Figure 2.90**

For Prob. 2.26.


- 2.27** Calculate  $I_o$  in the circuit of Fig. 2.91.

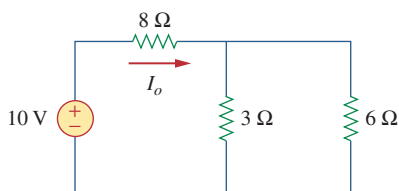

**Figure 2.91**

For Prob. 2.27.


- 2.28** Design a problem, using Fig. 2.92, to help other students better understand series and parallel circuits.

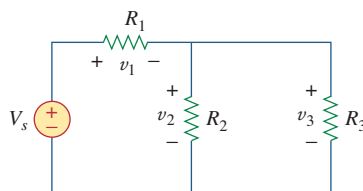

**Figure 2.92**

For Prob. 2.28.


- 2.29** All resistors in Fig. 2.93 are  $5\text{ }\Omega$  each. Find  $R_{eq}$ .

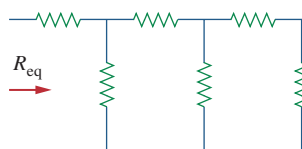

**Figure 2.93**

For Prob. 2.29.


- 2.30** Find  $R_{eq}$  for the circuit in Fig. 2.94.

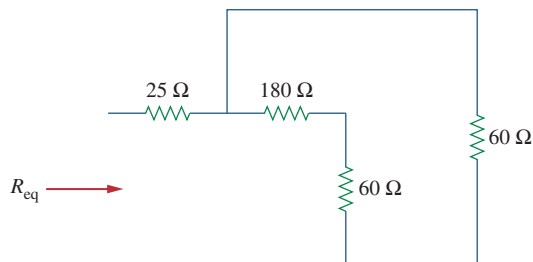

**Figure 2.94**

For Prob. 2.30.


2.31 For the circuit in Fig. 2.95, determine  $i_1$  to  $i_5$ .

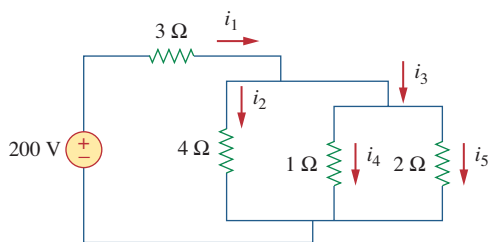

**Figure 2.95**

For Prob. 2.31.


2.32 Find  $i_1$  through  $i_4$  in the circuit in Fig. 2.96.

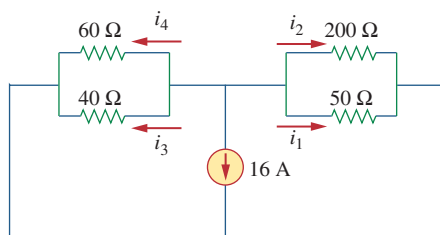

**Figure 2.96**

For Prob. 2.32.


2.33 Obtain  $v$  and  $i$  in the circuit in Fig. 2.97.

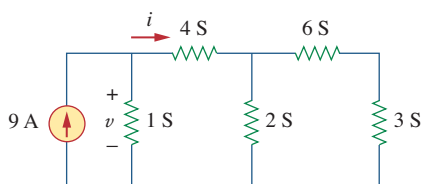

**Figure 2.97**

For Prob. 2.33.


2.34 Using series/parallel resistance combination, find the equivalent resistance seen by the source in the circuit of Fig. 2.98. Find the overall absorbed power by the resistor network.

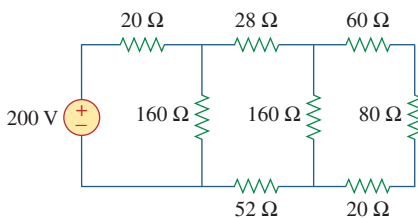

**Figure 2.98**

For Prob. 2.34.


2.35 Calculate  $V_o$  and  $I_o$  in the circuit of Fig. 2.99.

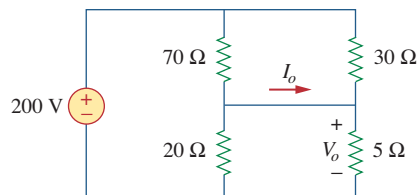

**Figure 2.99**

For Prob. 2.35.


2.36 Find  $i$  and  $V_o$  in the circuit of Fig. 2.100.

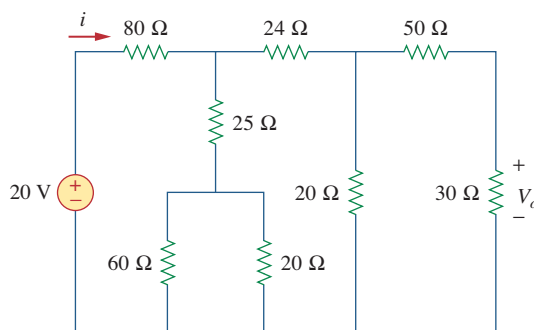

**Figure 2.100**

For Prob. 2.36.


2.37 Find  $R$  for the circuit in Fig. 2.101.

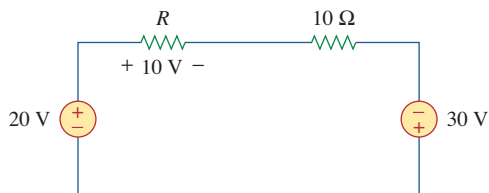

**Figure 2.101**

For Prob. 2.37.


2.38 Find  $R_{eq}$  and  $i_o$  in the circuit of Fig. 2.102.

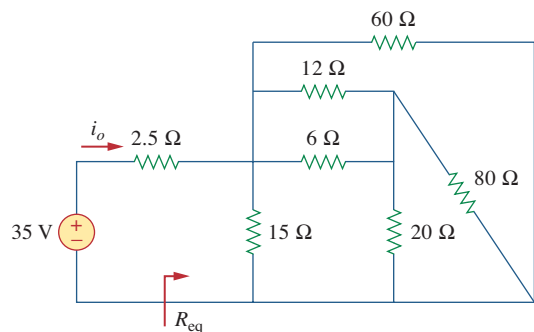

**Figure 2.102**


For Prob. 2.38.

**2.39** Evaluate  $R_{eq}$  for each of the circuits shown in Fig. 2.103.

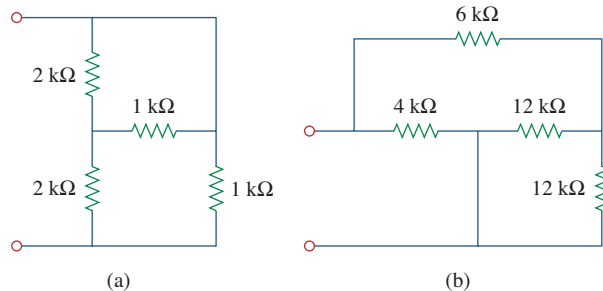


**Figure 2.103**  
For Prob. 2.39.

**2.40** For the ladder network in Fig. 2.104, find  $I$  and  $R_{eq}$ .

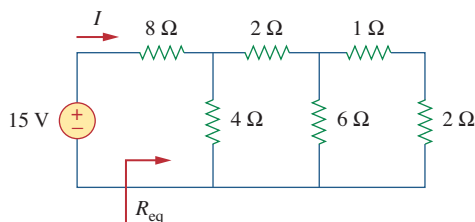



**Figure 2.104**  
For Prob. 2.40.

**2.41** If  $R_{eq} = 50 \Omega$  in the circuit of Fig. 2.105, find  $R$ .

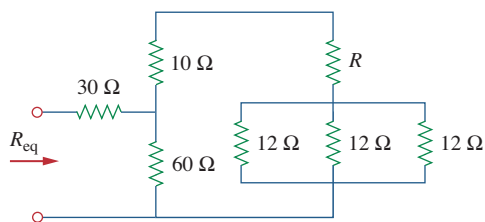



**Figure 2.105**  
For Prob. 2.41.

**2.42** Reduce each of the circuits in Fig. 2.106 to a single resistor at terminals  $a-b$ .

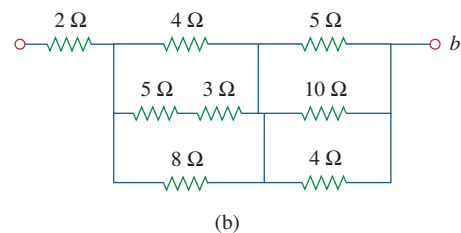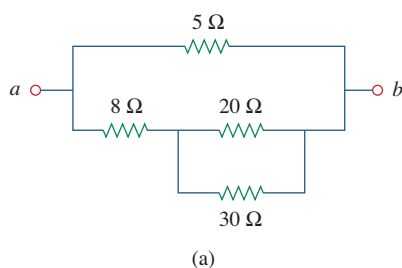


**Figure 2.106**  
For Prob. 2.42.

**2.43** Calculate the equivalent resistance  $R_{ab}$  at terminals  $a-b$  for each of the circuits in Fig. 2.107.

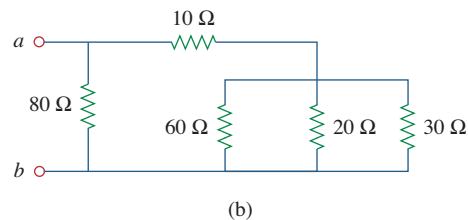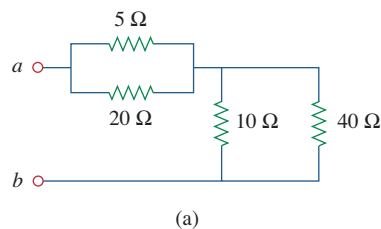



**Figure 2.107**  
For Prob. 2.43.

**2.44** For the circuits in Fig. 2.108, obtain the equivalent resistance at terminals  $a-b$ .

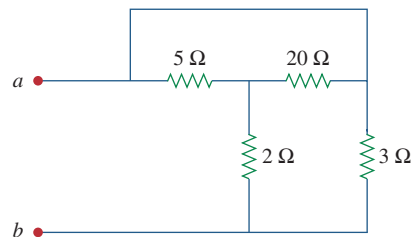

**Figure 2.108**  
For Prob. 2.44.


**2.45** Find the equivalent resistance at terminals  $a$ - $b$  of each circuit in Fig. 2.109.

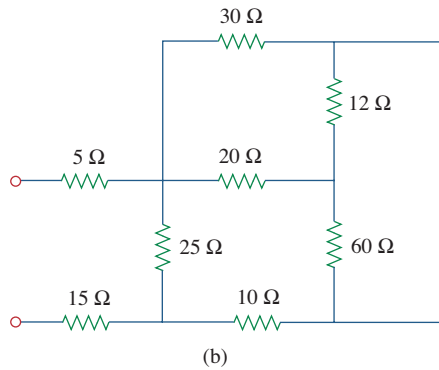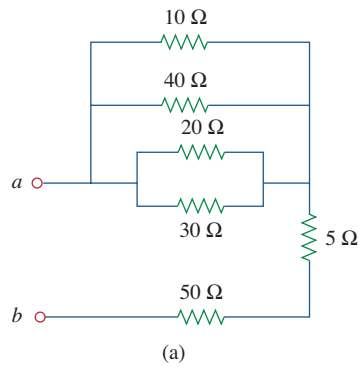

**Figure 2.109**

For Prob. 2.45.


**2.46** Find  $I$  in the circuit of Fig. 2.110.

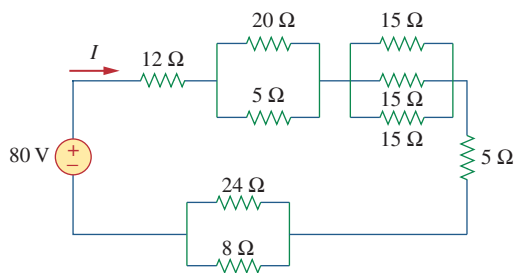

**Figure 2.110**

For Prob. 2.46.

**2.47** Find the equivalent resistance  $R_{ab}$  in the circuit of Fig. 2.111.

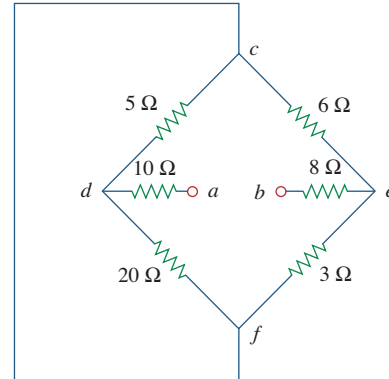


**Figure 2.111**

For Prob. 2.47.

## Section 2.7 Wye-Delta Transformations


**2.48** Convert the circuits in Fig. 2.112 from Y to  $\Delta$ .

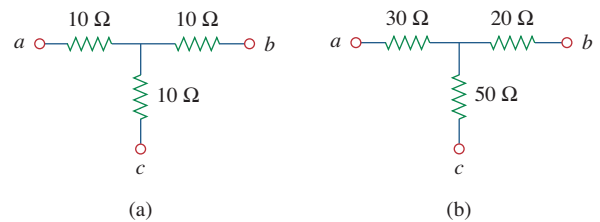

**Figure 2.112**

For Prob. 2.48.


**2.49** Transform the circuits in Fig. 2.113 from  $\Delta$  to Y.

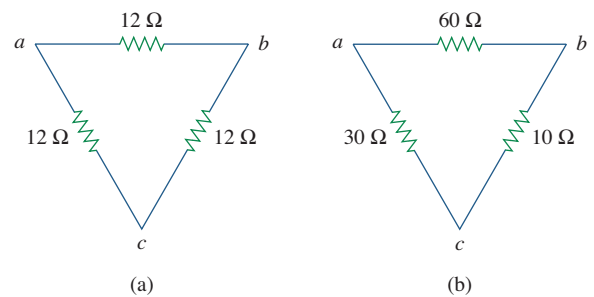

**Figure 2.113**

For Prob. 2.49.


- 2.50** Design a problem to help other students better understand wye-delta transformations using Fig. 2.114.

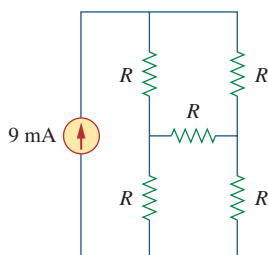


**Figure 2.114**

For Prob. 2.50.

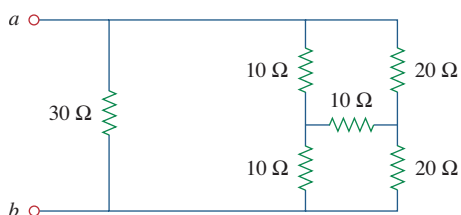- 2.51** Obtain the equivalent resistance at the terminals  $a$ - $b$  for each of the circuits in Fig. 2.115.



(a)

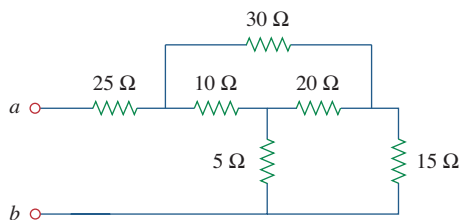


(b)

**Figure 2.115**

For Prob. 2.51.

- \*2.52** For the circuit shown in Fig. 2.116, find the equivalent resistance. All resistors are  $3\ \Omega$ .

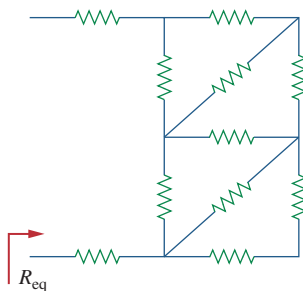


**Figure 2.116**

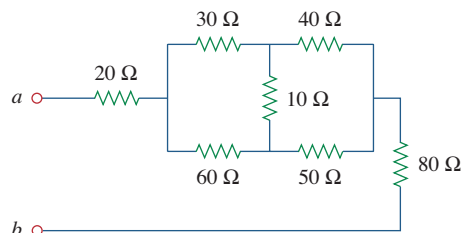
For Prob. 2.52.

\* An asterisk indicates a challenging problem.

- \*2.53** Obtain the equivalent resistance  $R_{ab}$  in each of the circuits of Fig. 2.117. In (b), all resistors have a value of  $30\ \Omega$ .



(a)

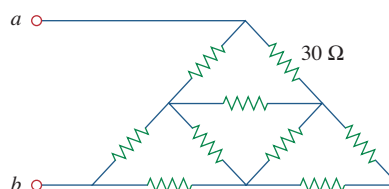


(b)

**Figure 2.117**

For Prob. 2.53.


- 2.54** Consider the circuit in Fig. 2.118. Find the equivalent resistance at terminals: (a)  $a$ - $b$ , (b)  $c$ - $d$ .

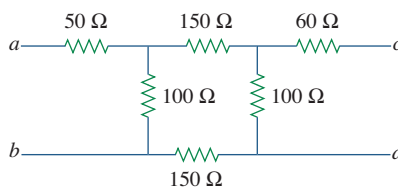

**Figure 2.118**

For Prob. 2.54.


- 2.55** Calculate  $I_o$  in the circuit of Fig. 2.119.

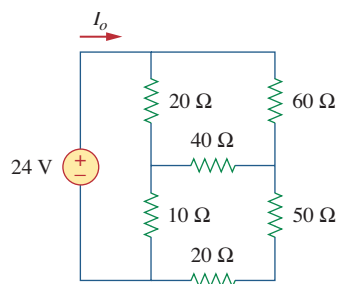

**Figure 2.119**

For Prob. 2.55.


**2.56** Determine  $V$  in the circuit of Fig. 2.120.

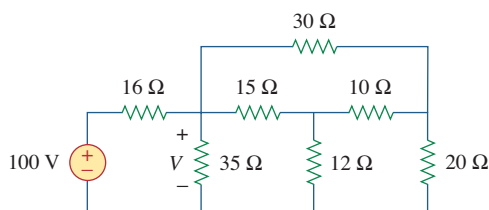

**Figure 2.120**

For Prob. 2.56.

**\*2.57** Find  $R_{eq}$  and  $I$  in the circuit of Fig. 2.121.

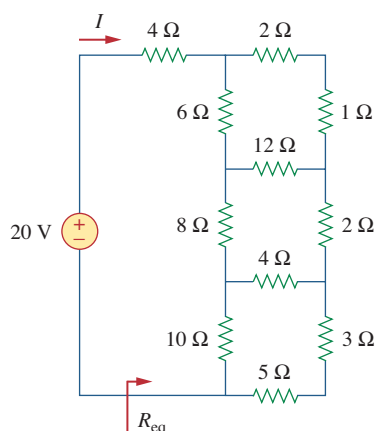


**Figure 2.121**

For Prob. 2.57.

## Section 2.8 Applications


**2.58** The 60 W light bulb in Fig. 2.122 is rated at 120 volts. Calculate  $V_s$  to make the light bulb operate at the rated conditions.

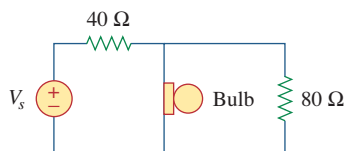

**Figure 2.122**

For Prob. 2.58.

**2.59** Three light bulbs are connected in series to a 120-V source as shown in Fig. 2.123. Find the current  $I$  through the bulbs. Each bulb is rated at 120 volts. How much power is each bulb absorbing? Do they generate much light?

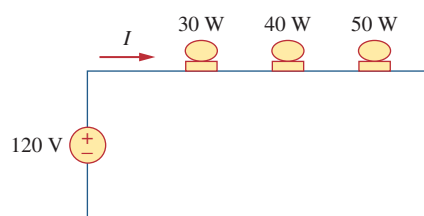

**Figure 2.123**


For Prob. 2.59.

**2.60** If the three bulbs of Prob. 2.59 are connected in parallel to the 120-V source, calculate the current through each bulb.

**2.61** As a design engineer, you are asked to design a lighting system consisting of a 70-W power supply and two light bulbs as shown in Fig. 2.124. You must select the two bulbs from the following three available bulbs.

- $R_1 = 80 \Omega$ , cost = \$0.60 (standard size)
- $R_2 = 90 \Omega$ , cost = \$0.90 (standard size)
- $R_3 = 100 \Omega$ , cost = \$0.75 (nonstandard size)


The system should be designed for minimum cost such that lies within the range  $I = 1.2 \text{ A} \pm 5 \text{ percent}$ .

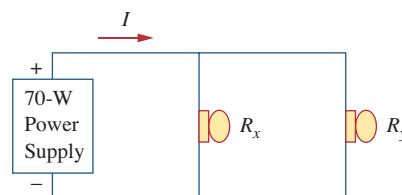

**Figure 2.124**

For Prob. 2.61.

**2.62** A three-wire system supplies two loads  $A$  and  $B$  as shown in Fig. 2.125. Load  $A$  consists of a motor drawing a current of 8 A, while load  $B$  is a PC drawing 2 A. Assuming 10 h/day of use for 365 days and 6 cents/kWh, calculate the annual energy cost of the system.

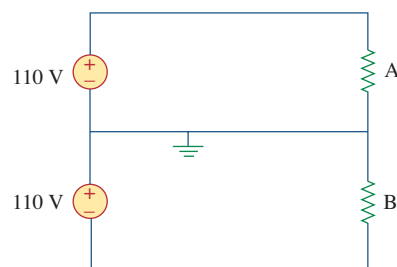


**Figure 2.125**

For Prob. 2.62.

**2.63** If an ammeter with an internal resistance of  $100 \Omega$  and a current capacity of 2 mA is to measure 5 A, determine the value of the resistance needed.

Calculate the power dissipated in the shunt resistor.

- 2.64** The potentiometer (adjustable resistor)  $R_x$  in Fig. 2.126 is to be designed to adjust current  $i_x$  from 1 A to 10 A. Calculate the values of  $R$  and  $R_x$  to achieve this.

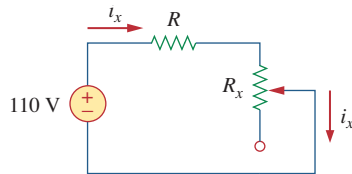

**Figure 2.126**

For Prob. 2.64.

- 2.65** A d'Arsonval meter with an internal resistance of  $1\text{ k}\Omega$  requires 10 mA to produce full-scale deflection. Calculate the value of a series resistance needed to measure 50 V of full scale.


- 2.66** A  $20\text{-k}\Omega/\text{V}$  voltmeter reads 10 V full scale.

- What series resistance is required to make the meter read 50 V full scale?
- What power will the series resistor dissipate when the meter reads full scale?

- 2.67** (a) Obtain the voltage  $V_o$  in the circuit of Fig. 2.127(a).  
 (b) Determine the voltage  $V'_o$  measured when a voltmeter with  $6\text{-k}\Omega$  internal resistance is connected as shown in Fig. 2.127(b).  
 (c) The finite resistance of the meter introduces an error into the measurement. Calculate the percent error as

$$\left| \frac{V_o - V'_o}{V_o} \right| \times 100\%$$

- Find the percent error if the internal resistance were  $36\text{ k}\Omega$ .

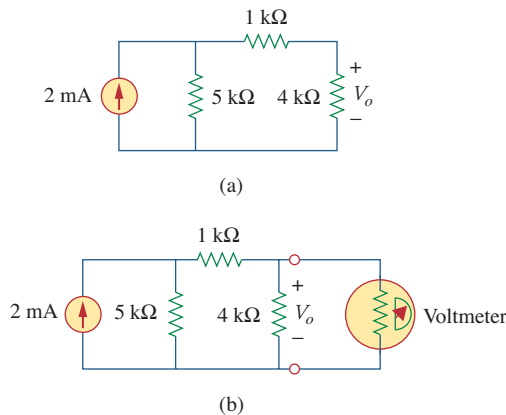

**Figure 2.127**


For Prob. 2.67.

- 2.68** (a) Find the current  $I$  in the circuit of Fig. 2.128(a).

- An ammeter with an internal resistance of  $1\text{ }\Omega$  is inserted in the network to measure  $I'$  as shown in Fig. 2.128(b). What is  $I'$ ?

- Calculate the percent error introduced by the meter as

$$\left| \frac{I - I'}{I} \right| \times 100\%$$

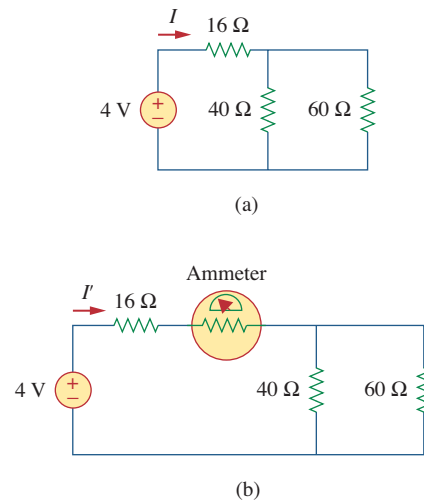


**Figure 2.128**

For Prob. 2.68.

- 2.69** A voltmeter is used to measure  $V_o$  in the circuit in Fig. 2.129. The voltmeter model consists of an ideal voltmeter in parallel with a  $100\text{-k}\Omega$  resistor. Let  $V_s = 40\text{ V}$ ,  $R_s = 10\text{ k}\Omega$ , and  $R_1 = 20\text{ k}\Omega$ . Calculate  $V_o$  with and without the voltmeter when


- $R_2 = 1\text{ k}\Omega$
- $R_2 = 10\text{ k}\Omega$
- $R_2 = 100\text{ k}\Omega$

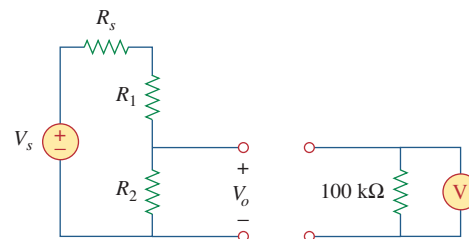

**Figure 2.129**

For Prob. 2.69.


- 2.70** (a) Consider the Wheatstone bridge shown in Fig. 2.130. Calculate  $v_a$ ,  $v_b$ , and  $v_{ab}$ .  
 (b) Rework part (a) if the ground is placed at  $a$  instead of  $o$ .

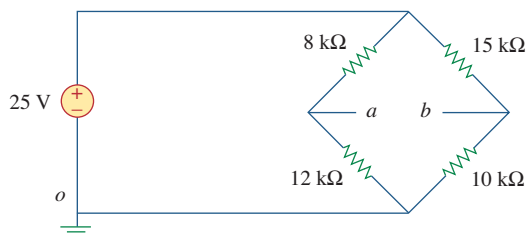

**Figure 2.130**

For Prob. 2.70.


- 2.71** Figure 2.131 represents a model of a solar photovoltaic panel. Given that  $V_s = 30$  V,  $R_1 = 20$   $\Omega$ , and  $i_L = 1$  A, find  $R_L$ .

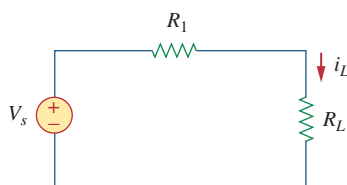

**Figure 2.131**

For Prob. 2.71.


- 2.72** Find  $V_o$  in the two-way power divider circuit in Fig. 2.132.

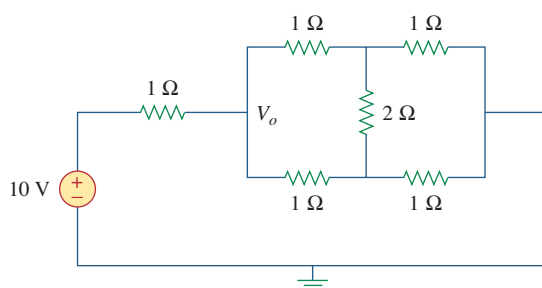

**Figure 2.132**

For Prob. 2.72.


- 2.73** An ammeter model consists of an ideal ammeter in series with a 20- $\Omega$  resistor. It is connected with a current source and an unknown resistor  $R_x$  as shown in Fig. 2.133. The ammeter reading is noted. When a potentiometer  $R$  is added and adjusted until the ammeter reading drops to one half its previous reading, then  $R = 65$   $\Omega$ . What is the value of  $R_x$ ?

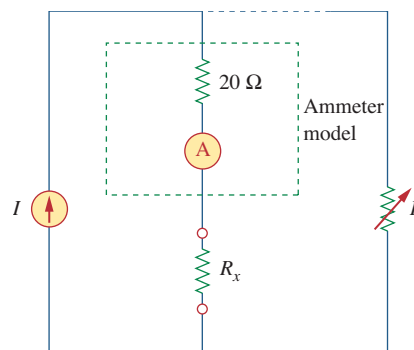

**Figure 2.133**

For Prob. 2.73.


- 2.74** The circuit in Fig. 2.134 is to control the speed of a motor such that the motor draws currents 5 A, 3 A, and 1 A when the switch is at high, medium, and low positions, respectively. The motor can be modeled as a load resistance of 20 m $\Omega$ . Determine the series dropping resistances  $R_1$ ,  $R_2$ , and  $R_3$ .

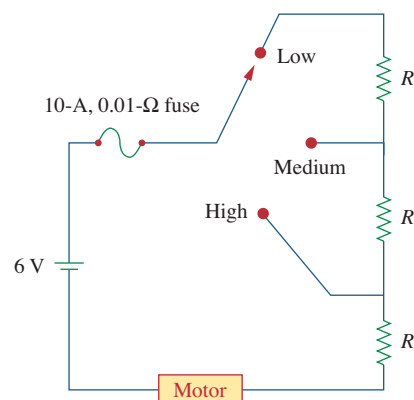

**Figure 2.134**

For Prob. 2.74.

- 2.75** Find  $R_{ab}$  in the four-way power divider circuit in Fig. 2.135. Assume each element is 1  $\Omega$ .

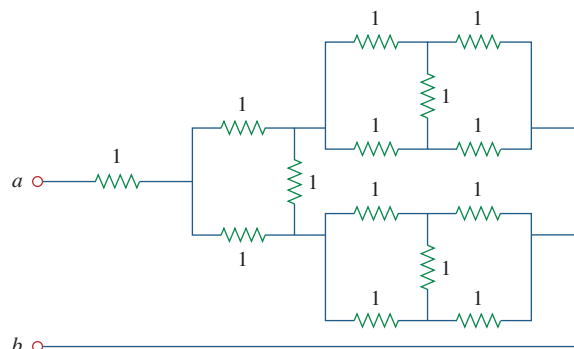


**Figure 2.135**

For Prob. 2.75.



## Comprehensive Problems

**2.76** Repeat Prob. 2.75 for the eight-way divider shown in Fig. 2.136.

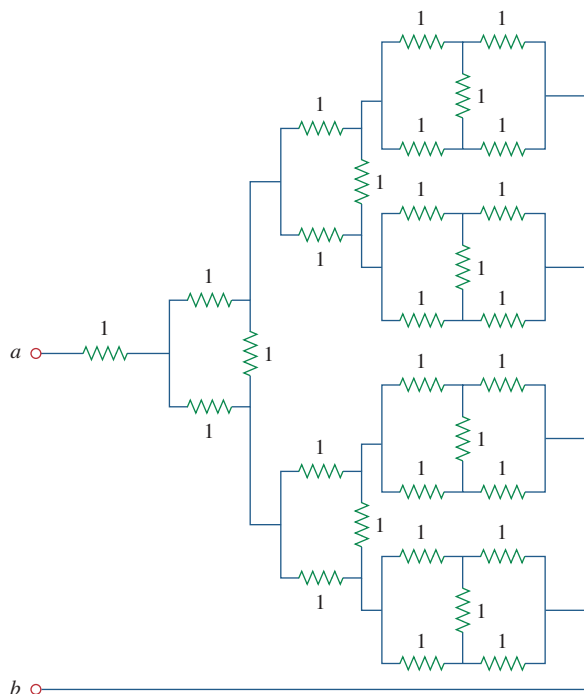

**Figure 2.136**

For Prob. 2.76.


**2.77** Suppose your circuit laboratory has the following standard commercially available resistors in large quantities:

1.8  $\Omega$     20  $\Omega$     300  $\Omega$     24 k $\Omega$     56 k $\Omega$

Using series and parallel combinations and a minimum number of available resistors, how would you obtain the following resistances for an electronic circuit design?

- (a) 5  $\Omega$     (b) 311.8  $\Omega$   
 (c) 40 k $\Omega$     (d) 52.32 k $\Omega$


**2.78** In the circuit in Fig. 2.137, the wiper divides the potentiometer resistance between  $\alpha R$  and  $(1 - \alpha)R$ ,  $0 \leq \alpha \leq 1$ . Find  $v_o/v_s$ .

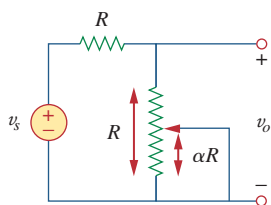

**Figure 2.137**

For Prob. 2.78.

**2.79** An electric pencil sharpener rated 240 mW, 6 V is connected to a 9-V battery as shown in Fig. 2.138. Calculate the value of the series-dropping resistor  $R_x$  needed to power the sharpener.

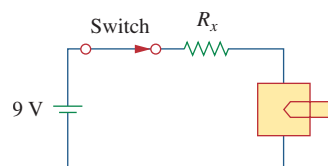

**Figure 2.138**

For Prob. 2.79.

**2.80** A loudspeaker is connected to an amplifier as shown in Fig. 2.139. If a 10- $\Omega$  loudspeaker draws the maximum power of 12 W from the amplifier, determine the maximum power a 4- $\Omega$  loudspeaker will draw.




**Figure 2.139**

For Prob. 2.80.

**2.81** In a certain application, the circuit in Fig. 2.140 must be designed to meet these two criteria:

- (a)  $V_o/V_s = 0.05$     (b)  $R_{eq} = 40$  k $\Omega$

If the load resistor 5 k $\Omega$  is fixed, find  $R_1$  and  $R_2$  to meet the criteria.

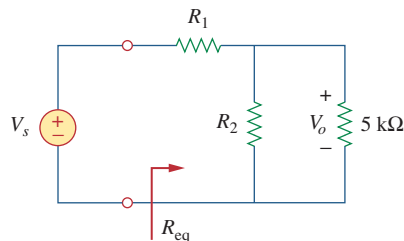


**Figure 2.140**

For Prob. 2.81.

**2.82** The pin diagram of a resistance array is shown in Fig. 2.141. Find the equivalent resistance between the following:


- (a) 1 and 2
- (b) 1 and 3
- (c) 1 and 4

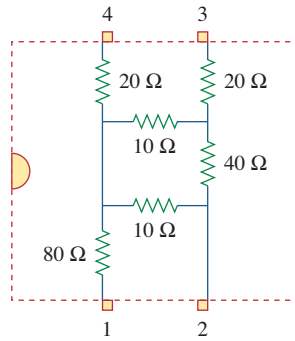

**Figure 2.141**

For Prob. 2.82.

**2.83** Two delicate devices are rated as shown in Fig. 2.142. Find the values of the resistors  $R_1$  and  $R_2$  needed to power the devices using a 24-V battery.

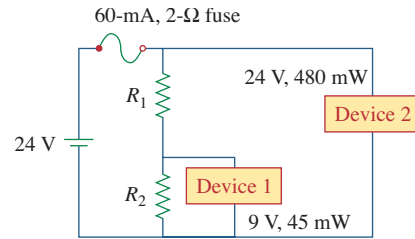

**Figure 2.142**

For Prob. 2.83.