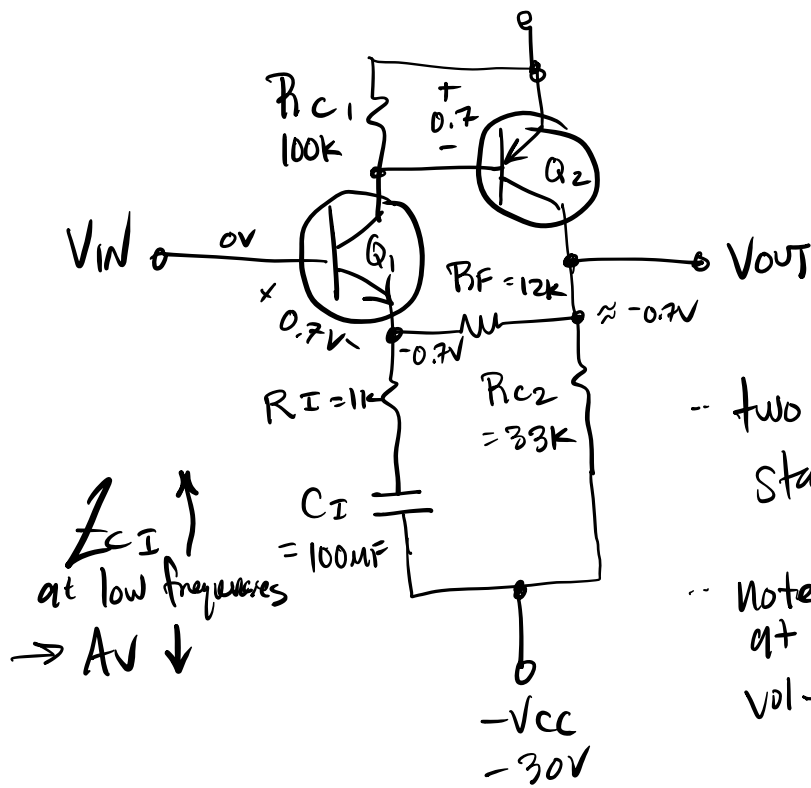


Multistage Feedback Amplifiers

- we know from the feedback equation that if βA_{vo} is a sufficiently high value, then the closed-loop gain of a feedback amplifier becomes $\frac{1}{\beta}$; strictly determined by the feedback network!
- thus, we would like higher open-loop gain A_{vo}
- one way to do this is to use two or more stages of amplification
- we need more than one stage anyway if we want a non-inverting amplifier with gain
- this configuration was very popular in the 60s, which uses an NPN CE direct-coupled to a PNP CE, with direct-coupled negative feedback:

$$+V_{CC} = 30V$$



-- two inverting gain stages (net non-inverting)

-- note that V_{out} rests at a DC collector voltage of $\approx -0.7V$

-- $\therefore V_{out}$ can swing close to $\pm V_{CC}$

-- also note that C_1 introduces a high-pass filter into the circuit; more importantly, $Z_{CI}|_{DC} = \infty$;

\therefore there is 100% D.C. negative feedback, which stabilizes the operating point

-- another important point: note the use of a PNP transistor for Q_2 with negative V_{CE2} intentionally shifts V_{C2} ($=V_{out}$) back towards 0V.

-- thus, Q_2 is both a CE amplifier and level shifter

.. moving towards an all-DC-coupled amplifier!

.. this is a shunt-derived, series-applied feedback network whose β value is a voltage division of V_{out} caused by R_F and R_I

$$\beta = \frac{R_I}{R_F + R_I}$$

.. plugging this into our feedback equation :

$$A_v = \frac{A_{vo}}{1 + \beta A_{vo}}$$
$$= \frac{A_{vo}}{1 + \frac{R_I}{R_F + R_I} A_{vo}}$$

.. and if the loop gain βA_{vo} is high, then

$$A_v \approx \frac{\cancel{A_{vo}}}{\frac{R_F}{R_F + R_I} \cancel{A_{vo}}} = \frac{R_F + R_I}{R_I}$$

$$A_v \approx 1 + \frac{R_F}{R_I}$$

look familiar ???


.. there is only one low-frequency pole, located at

$$f_{LP} = \frac{1}{2\pi \cdot C_I \cdot R_I} \text{ (user-selected)}$$

... and one zero located at


$$f_{LZ} = \frac{1}{2\pi \cdot C_I (R_I + R_F)}$$

.. thus, the low-frequency response is :

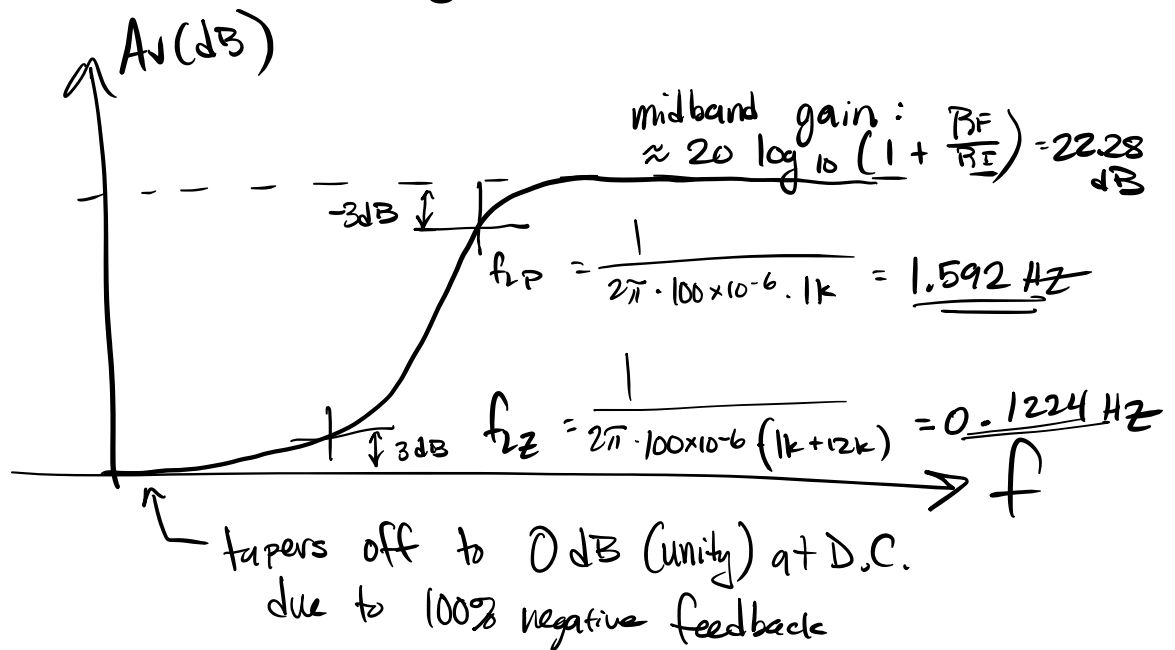


Three-Transistor Op-Amp

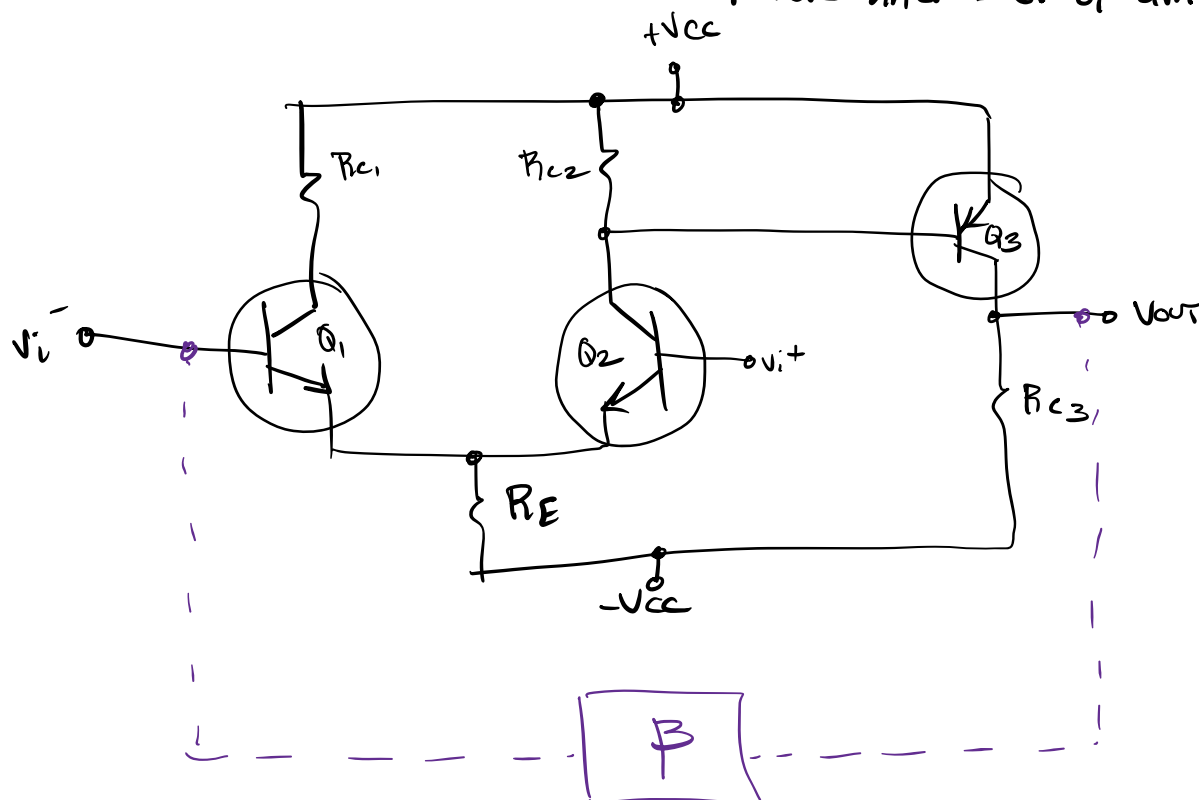- .. this is truly the missing link between discrete one- or two-transistor amplifiers and I.C. op-amps!



- .. a differential pair direct-coupled to a complementary CE / level shifter
- .. diff pair provides gain, differential input for negative feedback, and common-mode rejection.
- .. second stage provides gain and level-shifts Vout so we can have an all D.C. coupled amplifier.

ex: inverting amplifier

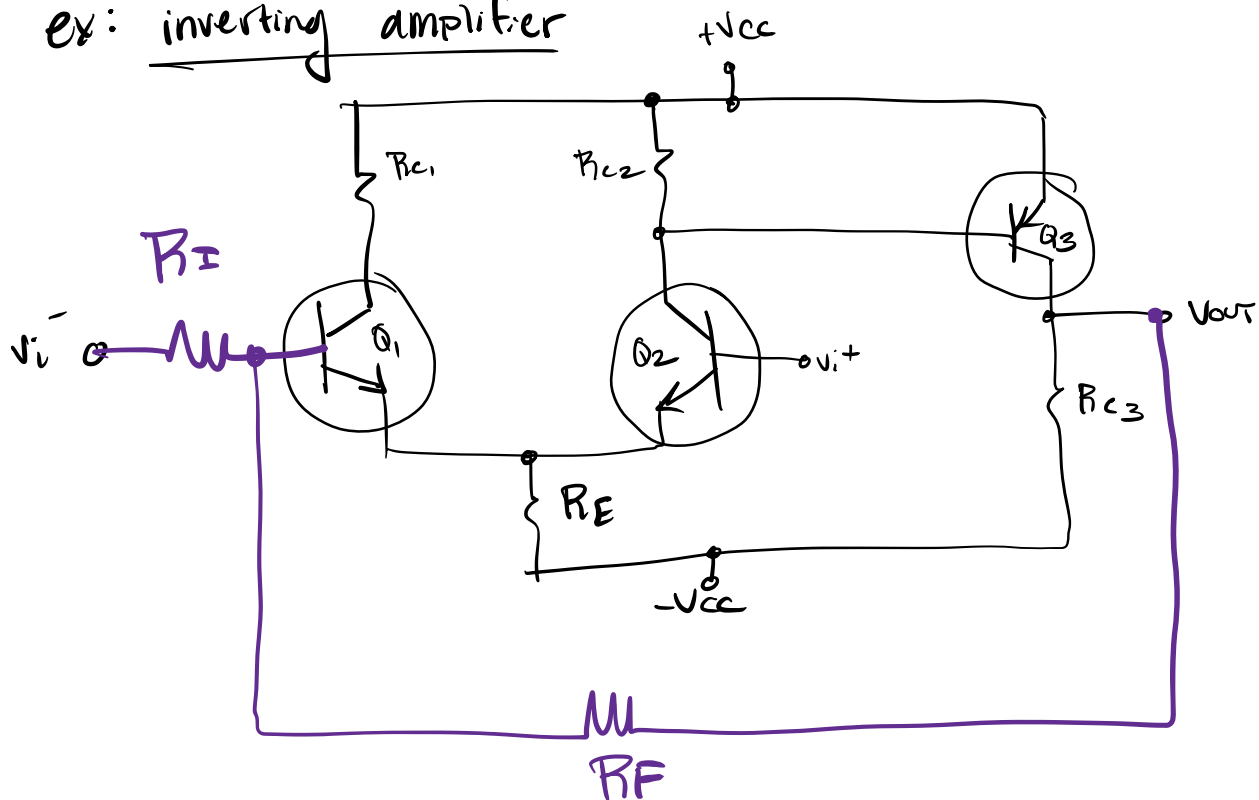

.. assuming high A_{vo} , $A_v \approx \frac{-R_F}{R_I}$

.. No capacitors @ LF; Works at D.C. !!!


.. with three amplifying stages inside the feedback loop, there is potential for high-frequency instability due to multiple HF poles .. but we can address this!

.. how do we improve on the three-transistor op-amp?

.. replace resistors with active loads / current sinks


.. more gain, better CMRR, advantages in I.C. fabrication

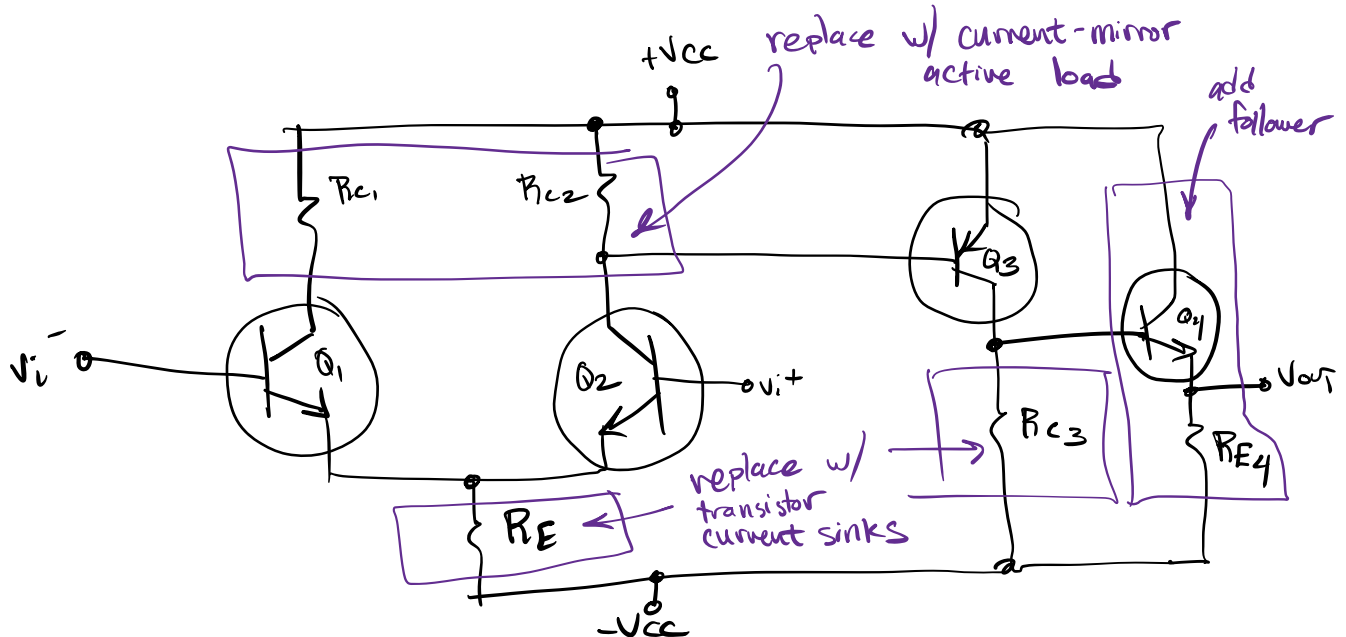.. add output emitter follower in order to drive a variety of loads



.. so far, all of our amplifiers have been Class-A; that is, we bias the transistor such that current and voltage "wiggle" above and below some carefully-chosen mid value

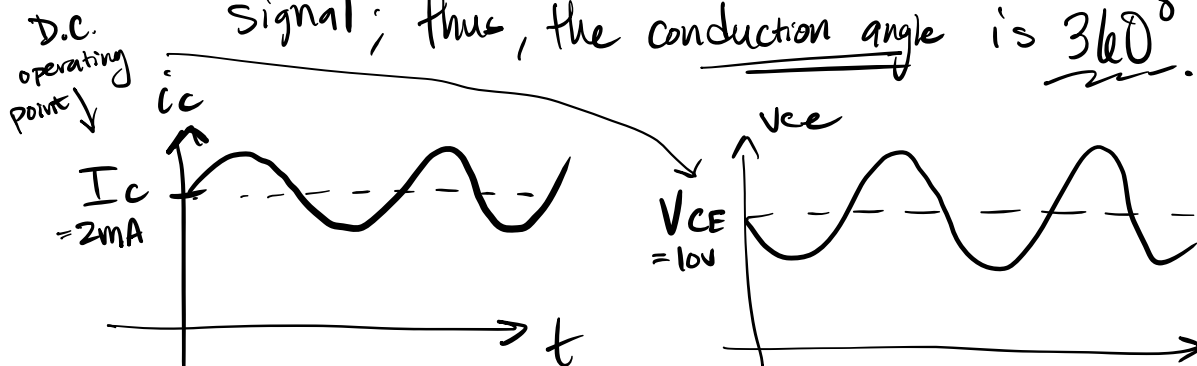.. the transistor is always ON, even when there's no signal; thus, the conduction angle is 360° .




- .. the transistor dissipates power continuously, even when there's no signal present; thus, it is inefficient.

→ max. Class-A efficiency is 25%

.. we can do better!


Class-B Push/Pull Power Amplifier

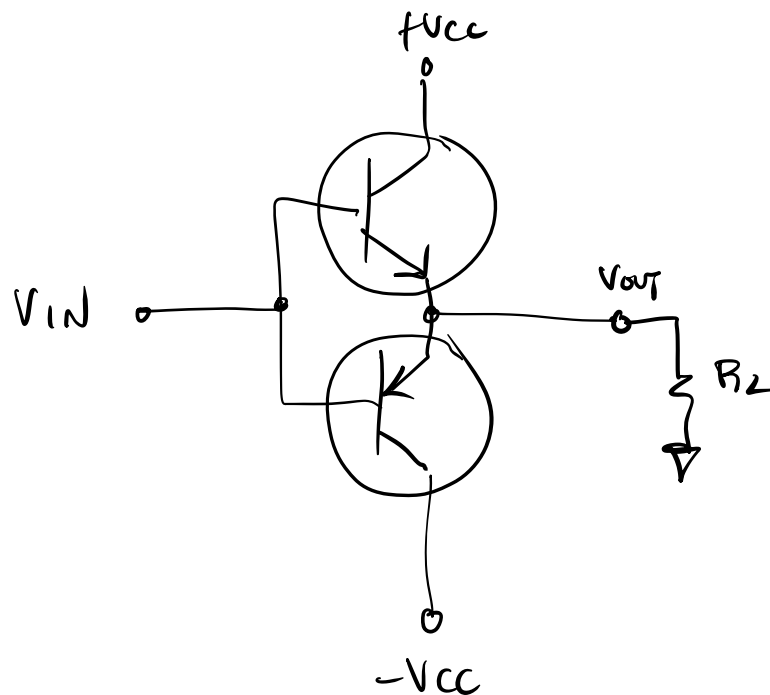

- .. when $V_{IN} = 0$ (Zero signal), both transistors are OFF
- .. when $V_{IN} > +0.7V$, Q_1 turns ON and becomes a NPN emitter follower with $V_{OUT} \approx V_{IN}$

When $V_{IN} < -0.7V$, Q_2 turns ON and becomes a PNP emitter follower with $V_{OUT} \approx V_{IN}$

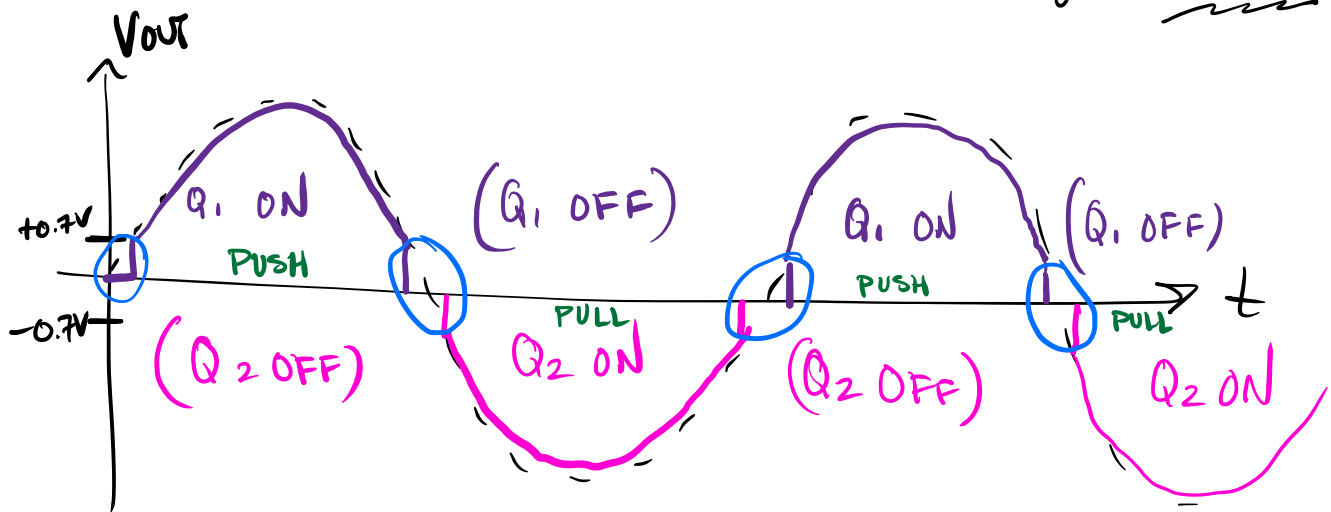thus, each transistor has a conduction angle of 180°



Max. efficiency is 78.5% (much better)


there is, naturally, a problem: Crossover distortion caused by dead zones when $|V_{IN}| < 0.7V$

how do we fix this?

1) include the Class-B push/pull amplifier inside negative feedback loop

regions where V_{OUT} starts to turn off are equivalent to lower open-loop gain; thus, closed-loop gain will change less, but will eventually run out!

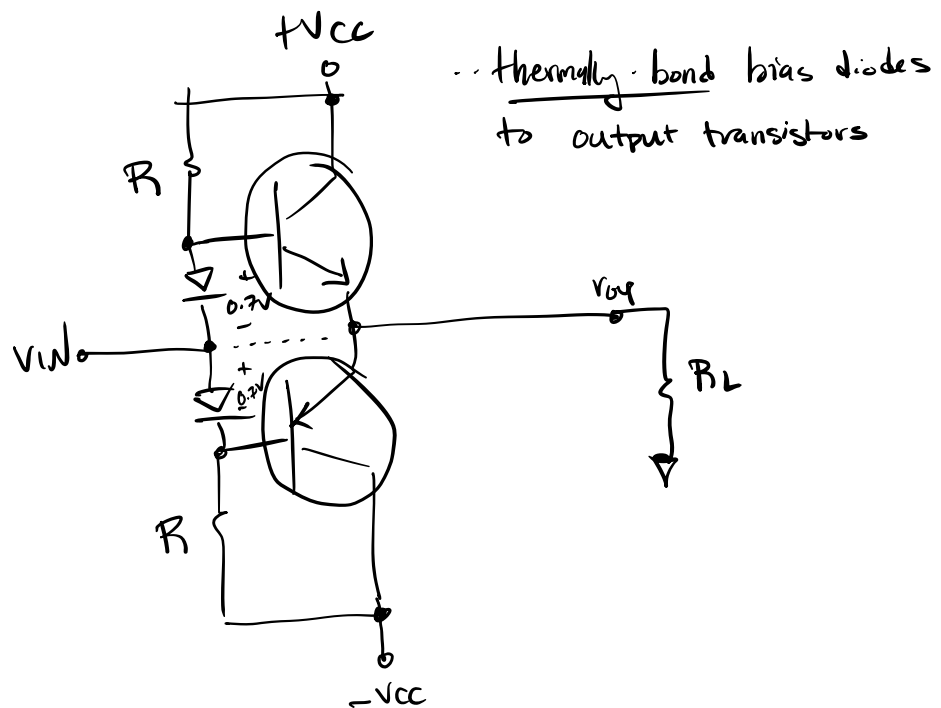2) bias the stage such that Q_1 and Q_2 are barely turned ON all the time; this is called Class AB operation



.. next lecture: we tie this all together into a true operational amplifier