
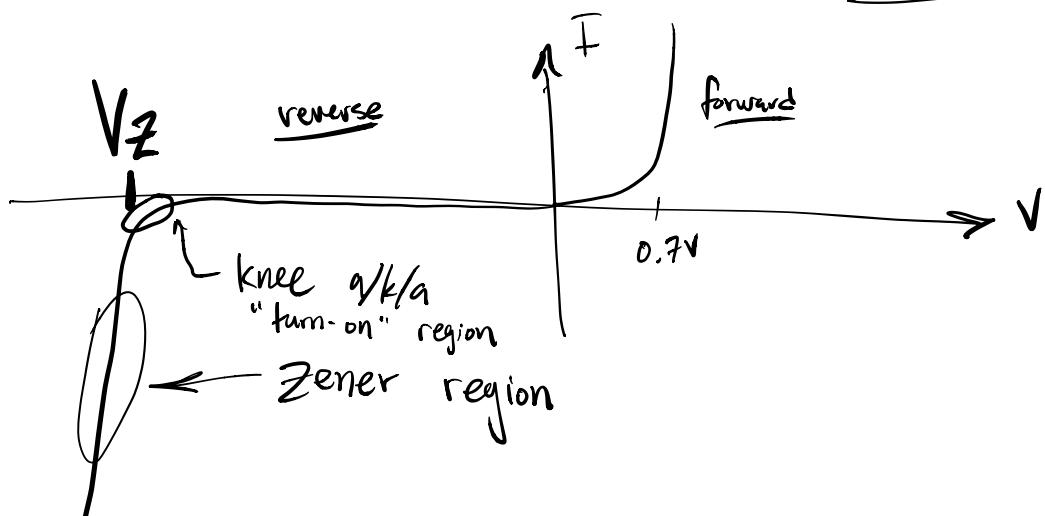


Zener Diodes

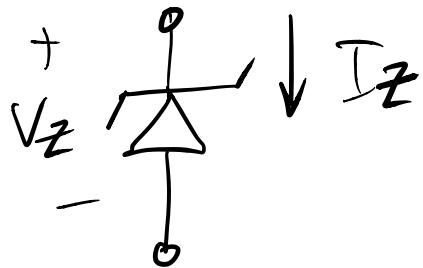- intentionally used in reverse-breakdown mode!
- forward characteristics are similar to any Si diode; constant drop around 0.7V
- reverse characteristics are carefully controlled by doping chemistry to have specific breakdown voltage, called Zener voltage.




- once past the "knee" region ($> 1-2 \text{ mA}$), very constant voltage drop V_Z
- we can use this phenomenon to regulate the output voltage of a power supply when I_L changes



- Note that I_Z is intentionally drawn cathode-to-anode instead of anode-to-cathode \hookrightarrow regular diode
- likewise, V_Z is drawn cathode-positive, instead of cathode negative
- because Zeners are used in reverse-breakdown, no need to have negative quantities all the time
- Zeners are available in E24 values of voltage
 - i.e., 10V, 11V, 12V, 13V, 15V, 18V etc.
 - up into hundreds of volts, down to at least $1.2V$
- V_Z is given by manufacturer at specific test current $I_Z(\text{test})$
- for our purposes: constant drop V_Z past knee region $> 1.2 \text{ mA}$

application: Shunt Voltage Regulator

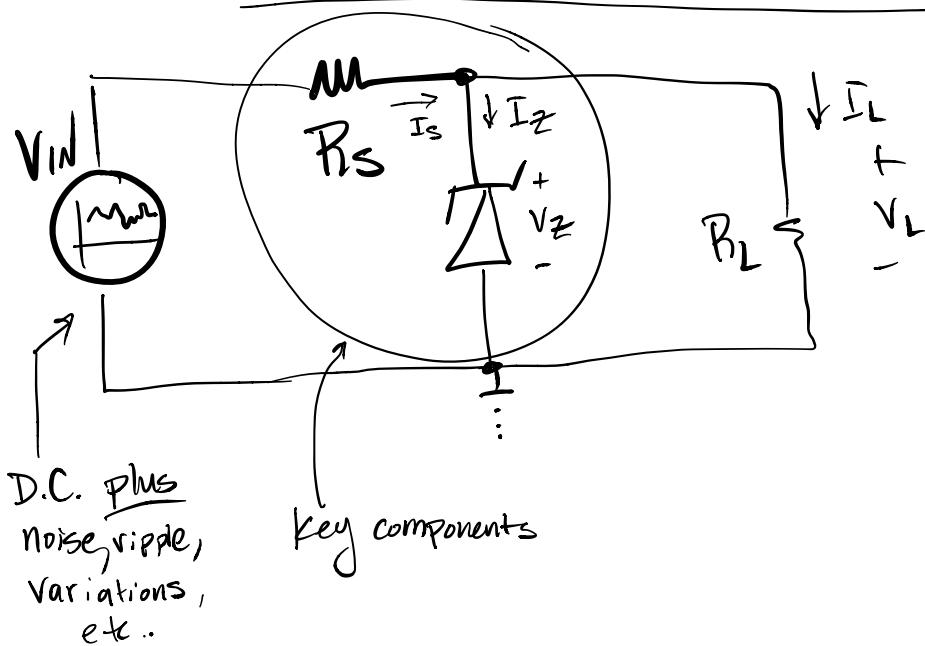

- two main features:


\Rightarrow 1.) V_L is kept relatively constant $\approx V_Z$
 load regulation \Leftarrow When I_L varies due to different loads being switched on and off etc..

\Rightarrow 2.) reduces variations in V_L when V_{IN} varies due to line fluctuations, ripple etc..
 line regulation \Leftarrow

ex: "raw" power supply whose output voltage varies between 15 and 18V; various reasons

- you need a constant 12V and load current varies from 0 to 50 mA

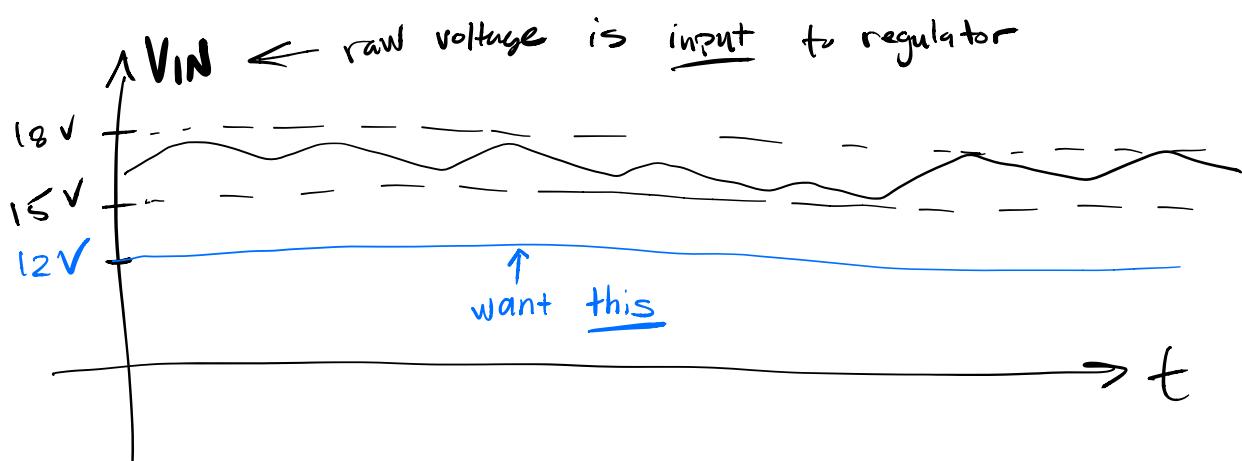- design shunt regulator to achieve this;
specify actual components



- We automatically know that we need a 12V Zener diode; $V_Z = V_L$

- Zener must have enough current at all times to stay in Zener region

"assume 2mA is sufficient

- minimum Zener current happens when V_{IN} is low
and I_L is high

$\sqrt{50\text{mA}}$

$$\text{by KCL : } I_S = I_Z + I_L$$

$$I_s = 2 + 50 = 52 \text{ mA}$$

∴ We can now calculate R_s !

$$R_s = \frac{V_{IN} - V_L}{I_s} = \frac{15 - 12}{0.052}$$

$$R_s = 57.69 \Omega$$

Use

$$R_s = 56 \Omega$$

↑
E24 value;
round down to
keep sufficient I_s
and thus I_Z

∴ Need to check power in each component

∴ Max. power in R_s occurs when V_{IN} is high

$$I_{s(\max)} = \frac{V_{IN(\max)} - V_L}{R_s} = \frac{18 - 12}{56} = 0.1071 A$$

or 107.1 mA

$$P_{R_s} = I^2 R = 0.1071^2 \cdot 56 = 0.64 W$$

use 1W resistor
minimum (2W!)

- Max. power in Zener diode occurs when V_{IN} is high

and I_L is low

↳ why? Because $I_S = I_Z + I_L$

- I_S is constant (given V_{IN} , because
 V_L is held at V_Z)

$$\therefore I_Z = I_S - I_L$$

\downarrow
constant

- Zener has to take all of I_S when I_L is zero!

$$I_Z(\max) = I_S(\max) - I_L(\min)$$

\downarrow
from original specification


$$= 0.1071 - 0 = \underline{\underline{0.1071}}$$

$$P_Z(\max) = V_Z \cdot I_Z(\max) = 12 \cdot 0.1071 \quad \text{dusp!}$$
$$= \underline{\underline{1.285 \text{ W}}}$$

- Use at least 2W zener diode;

12V 5W
IN5349B

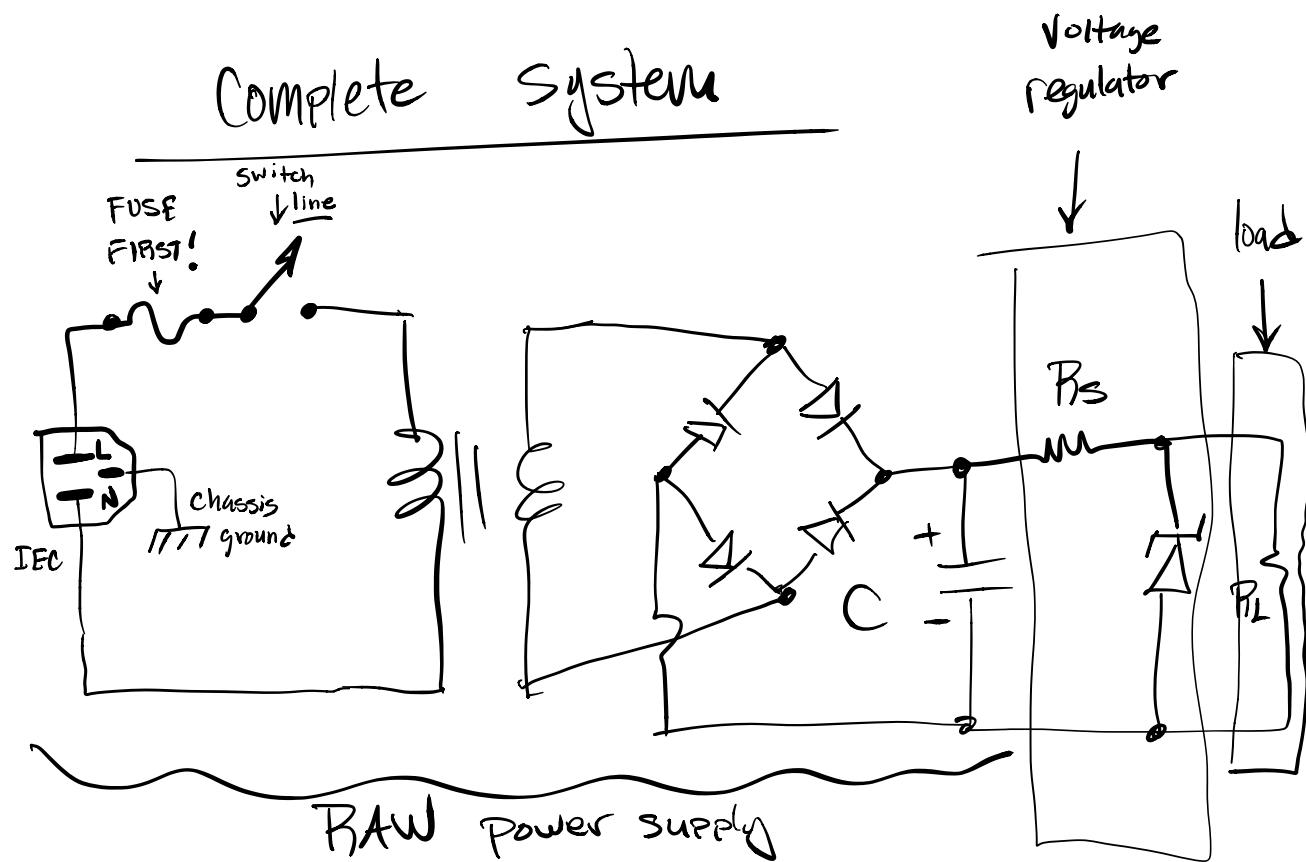Midwest Surplus Electronics in Fairborn
talk to Roger and Dave!



Homework: design Voltage regulator [P_S and zener, w/ power ratings]

to take voltage from center-tapped 350·0·350 power supply and produce V_L = 300V

① $I_L = 0 - 30 \text{ mA}$