

**EE 2010 Circuit Analysis**  
**Lab 13: Transient Response**

**Lab Section:**

**Printed Name (Last, First):**

---

**Learning Objectives:**

- Understand the concept of Transient Responses
- Simulate the transient response using a unit-step excitation
- Observe the transient response in lab using a square-wave excitation

**Transient Response:**

From WIKIPEDIA: “In electrical engineering and mechanical engineering, a *transient response* or natural response is the *response* of a system *to a change* from an equilibrium or a steady state. The transient response is not necessarily tied to “on/off” events but to any event that affects the equilibrium of the system. The *impulse response* and *step response* are transient responses to a specific input.”

**A. Before coming to lab:**

**1. Background:**


1.1 Read this [WIKIPEDIA overview of transient responses](#).

1.2 View this [Youtube video](#) on Interview Questions about transient responses.

In this lab, we examine the output due to a unit-step excitation by via a Multisim simulation.

**2. Step Response of an RC Circuit:**

Find  $v_o(t)$  for a unit-step input:

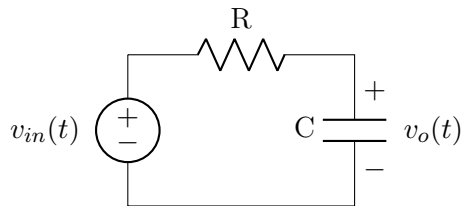

2.1 Construct the circuit above with  $R = 100\Omega$  and  $C = 1mF$ .

2.2 Place a 5V Step-Voltage source as shown. Note: This is NOT a 5V DC source.

2.3 Set the Step Time at 5mS (so the step occurs a bit AFTER  $t=0$ ).


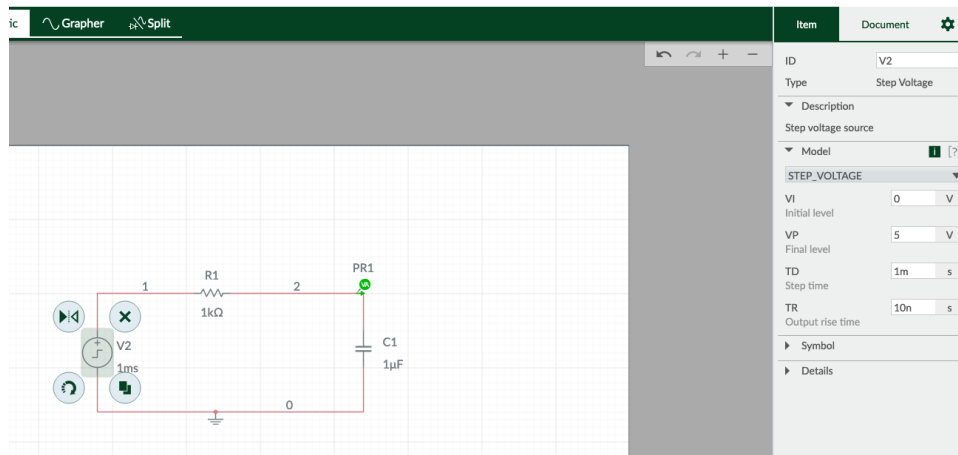


Figure 1: Unit-step input settings

2.4 Measure the output waveform with a voltage probe.

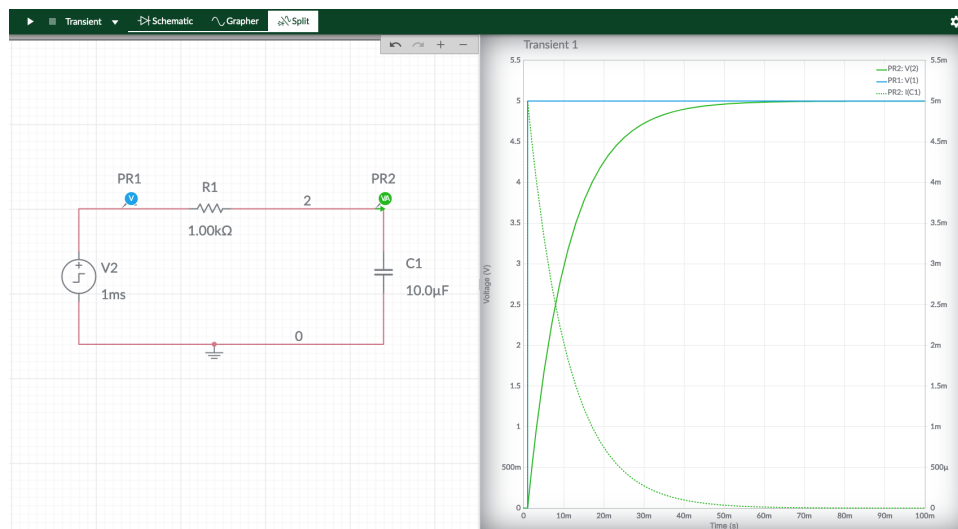2.5 The result should approximate the figure below.




2.6 Compare the simulation result to a Matlab symbolic prediction of  $v_o(t)$  for a unit-step input.

2.7 Screen capture into a document to upload to dropbox.

### 3. Step Response of an RL Circuit:

Find  $v_o(t)$  for a unit-step input:

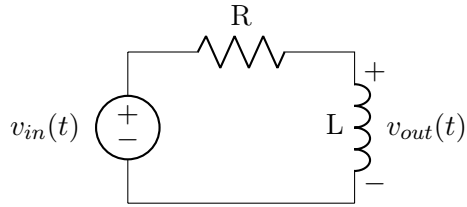

3.1 Construct the circuit above with  $R = 100\Omega$  and  $L = 10H$ .

3.2 Place a 5V Step-Voltage source as shown. Note: This is NOT a 5V DC source.

3.3 Set the Step Time at 5mS (so the step occurs a bit AFTER  $t=0$ ).


3.4 Measure the output waveform with a voltage probe.

3.5 Compare the simulation result to a Matlab symbolic prediction of  $v_o(t)$  for a unit-step input.

3.6 Screen capture into a document to upload to dropbox.

### 4. Step Response of an RLC Circuit:

Find  $v_o(t)$  for a unit-step input:

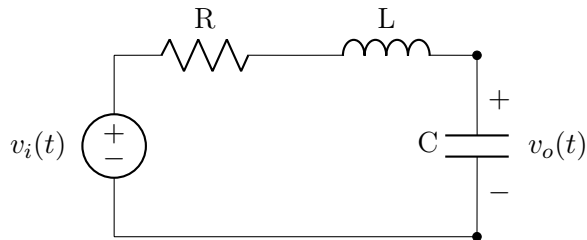

4.1 Construct the circuit above with  $R = 20\Omega$  and  $L = 1H$  and  $C = 0.1mF$ .



4.2 Place a 5V Step-Voltage source as shown. Note: This is NOT a 5V DC source.



4.3 Set the Step Time at 5mS (so the step occurs a bit AFTER  $t=0$ ).



4.4 Measure the output waveform with a voltage probe.

4.5 Compare the simulation result to a Matlab symbolic prediction of  $v_o(t)$  for a unit-step input.

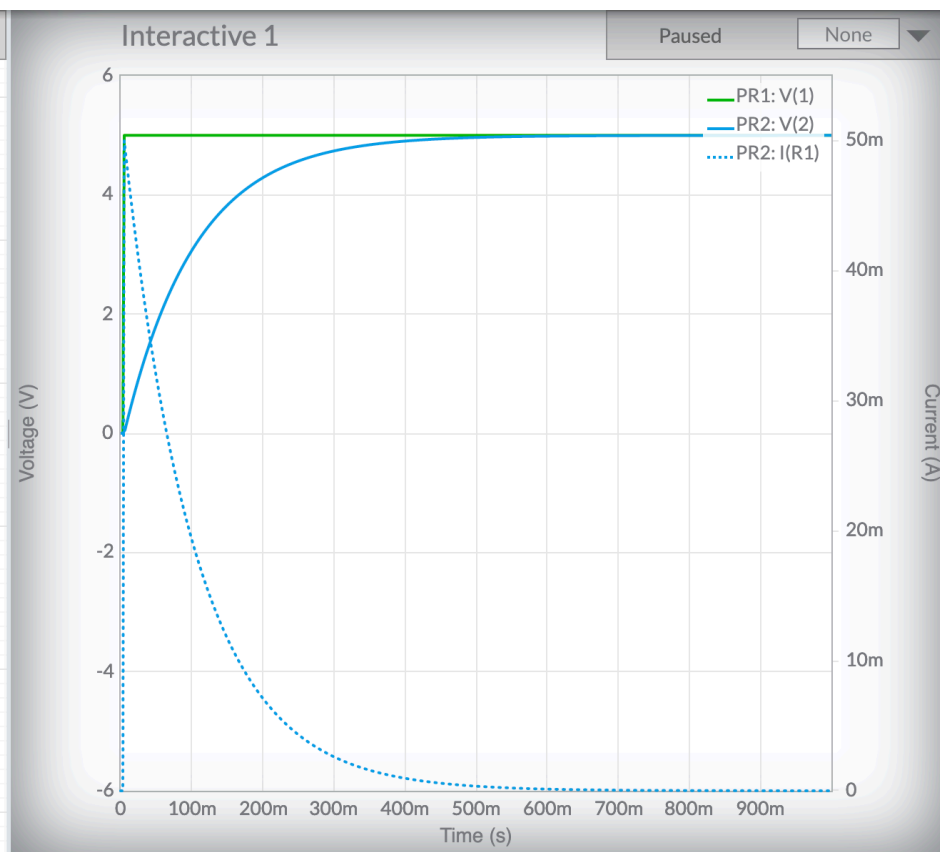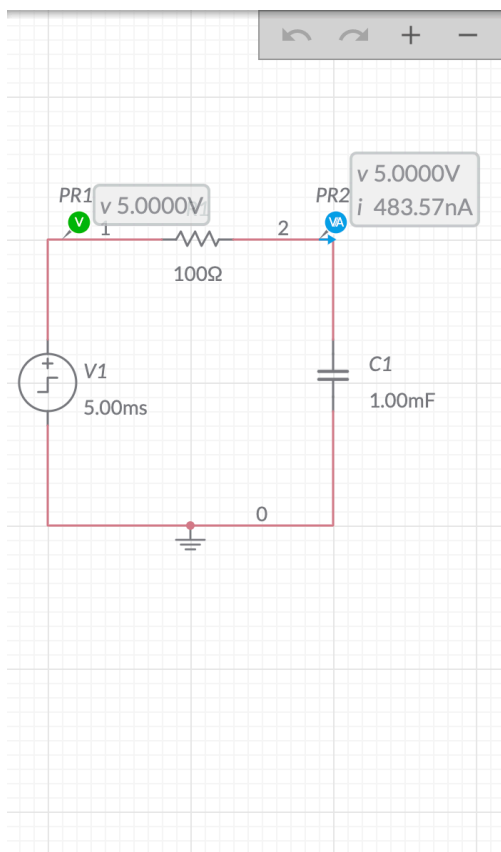4.6 Screen capture into a document to upload to dropbox.



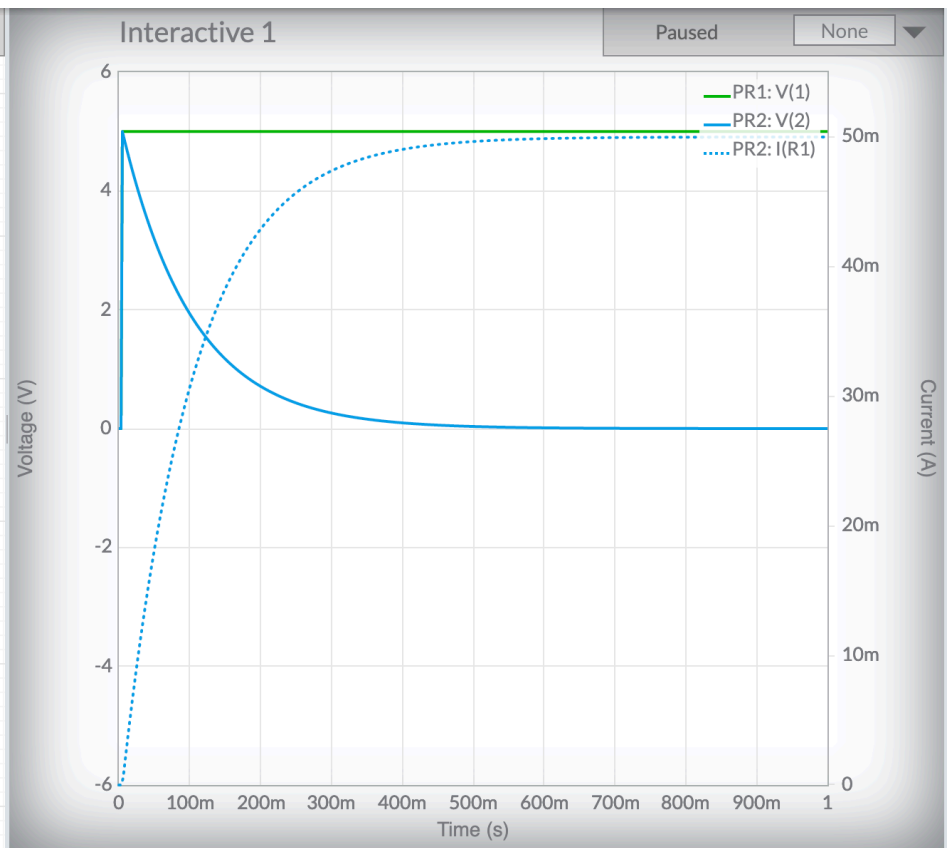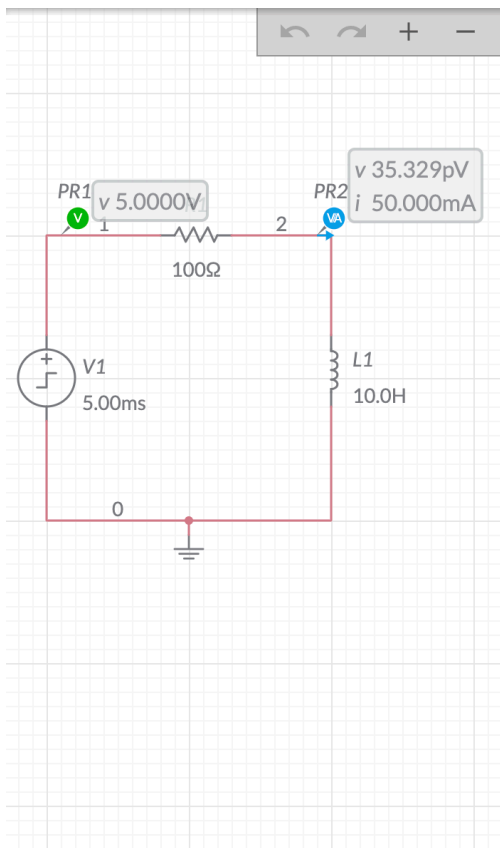


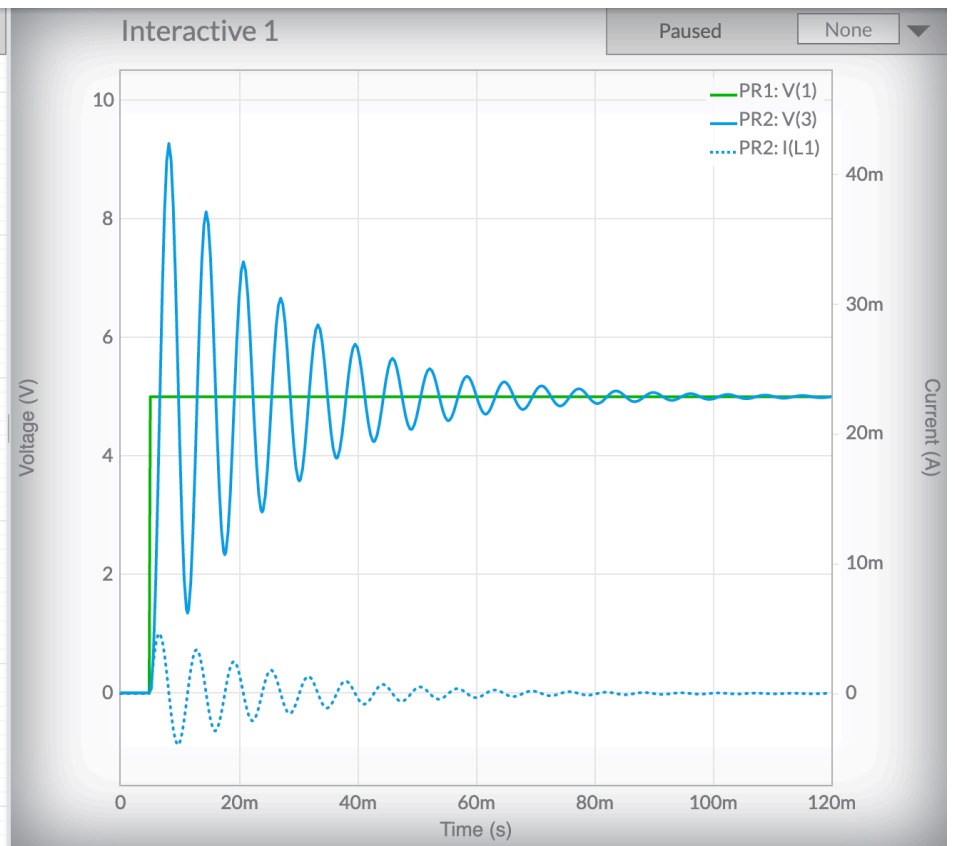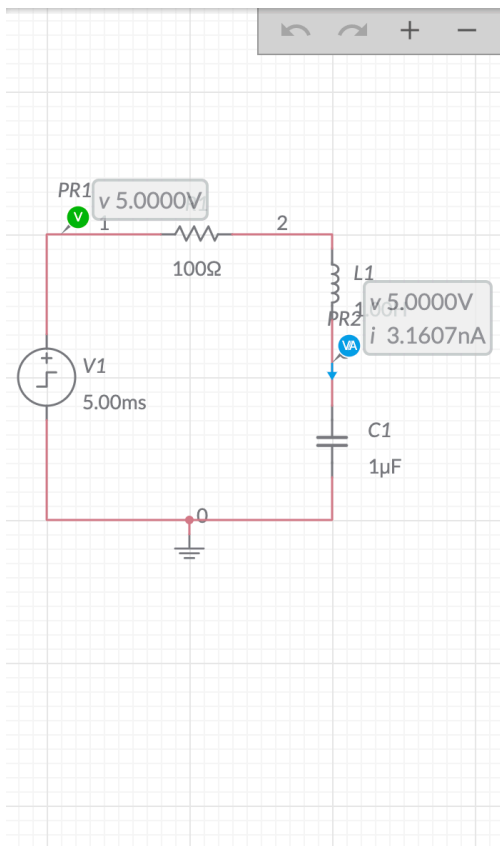

## B. In-Lab Procedures

### 1. Step Response of an RLC Circuit:

Find  $v_o(t)$  for a square-wave input:

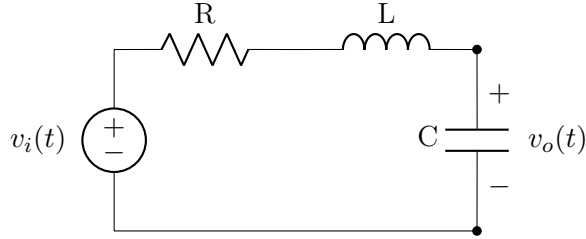

- 1.1 Construct the circuit above with  $R = 20\Omega$  and  $L = 1H$  and  $C = 0.1mF$ .
  - 1.2 Place a 5V *rectangular-pulse* from the function generator source as shown.
  - 1.3 Adjust the *frequency* to be about 2 Hz so that the *period* of the square wave is about 500mS.
  - 1.4 Measure the output waveform with the oscilloscope. **overdamped**
  - 1.5 Adjust the period of the square wave and the time-scale of the oscilloscope to obtain an aesthetically-pleasing display of the transient response.
  - 1.6 Show the transient response waveform to your TA.
- 

## C. Takeaways:

- Transient responses are the result of disturbances to dynamic systems.
- The characteristics of transient responses provide great insight to system dynamics.
- Step responses are an observable characterization of transient responses.
- Every physical system exhibits transient behaviors. It is important for engineers to understand their causes and behaviors.