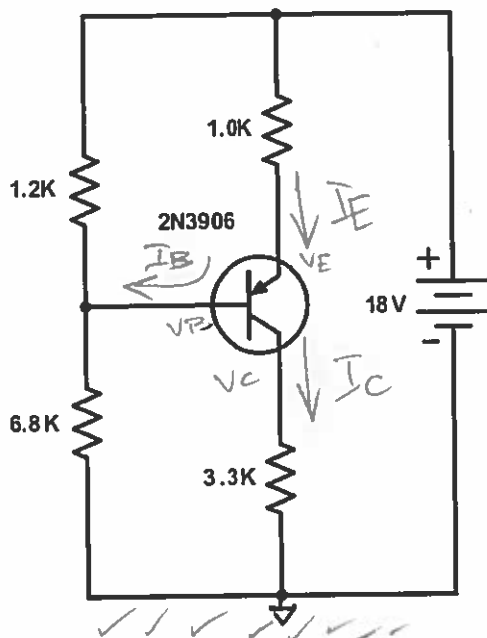


1) Refer to the following circuit:



Compute  $V_B$ ,  $V_C$ ,  $V_E$ ,  $V_{BE}$ ,  $V_{CE}$ ,  $I_B$ ,  $I_C$ ,  $I_E$ , and  $P_{diss}$  if  $\beta = 250$ . Compute  $V_B$  assuming base current is small compared to the current in the biasing resistors. Also verify that the transistor is operating in the active region.

$$V_B = 18 \left[ \frac{6.8}{1.2 + 6.8} \right] = \underline{15.3 \text{ V}} \quad (+2)$$

$$V_{BE(ON)} = -0.7 \text{ V (PNP)} \quad (+1)$$

$$\begin{aligned} V_E &= V_B - V_{BE} \quad (+1) \\ &= 15.3 - -0.7 = \underline{16 \text{ V}} \quad (+1) \end{aligned}$$

$$I_E = \frac{18 - V_E}{1 \text{ k}} = \frac{18 - 16}{1 \text{ k}} = \underline{2 \text{ mA}} \quad (+1)$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{2 \text{ mA}}{250 + 1} = 0.008 \text{ mA} \quad (+1)$$

or 8  $\mu$ A

$$I_C \approx I_E \quad (+1)$$


$$V_C = I_C \cdot 3.3 \text{ k} = \underline{6.6 \text{ V}} \quad (+2)$$

ok to compute from  $I_C$  instead

$$\begin{aligned} V_{CE} &= V_C - V_E = 6.6 - 16 = \underline{-9.4 \text{ V}} \quad (+2) \\ P_{diss} &= V_{CE} \cdot I_C = -9.4 \cdot 2 = \underline{18.8 \text{ mW}} \quad (+2) \end{aligned}$$

yes, active region (+1)


2) What amplifier configuration is this?

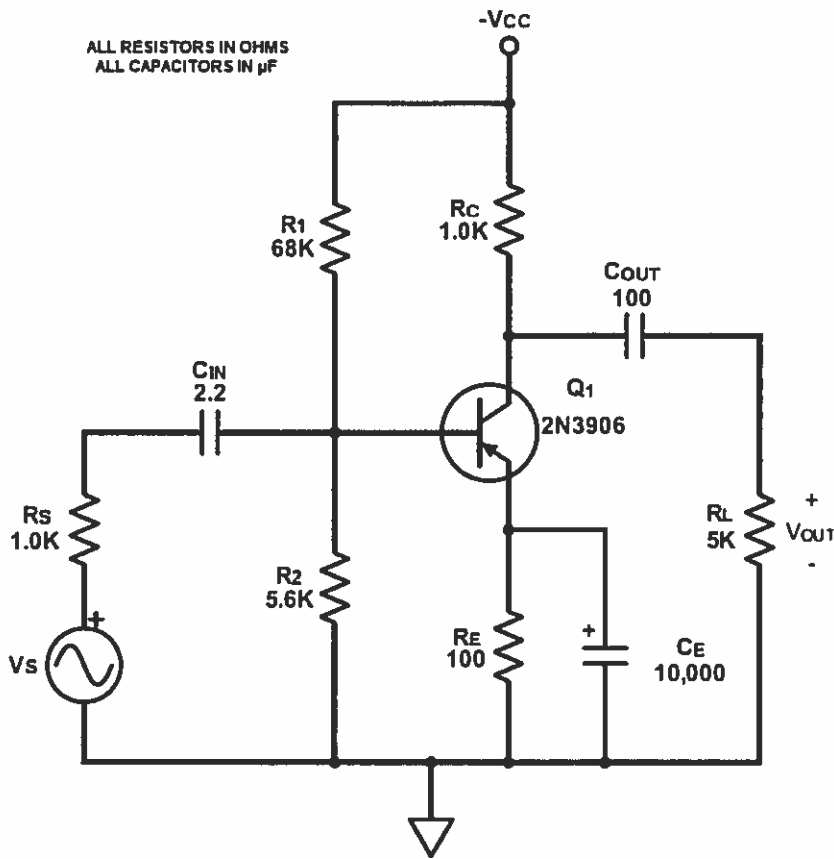

common-emitter (+1)

Draw the mid-frequency small-signal model. Calculate the dynamic parameters  $g_m$ ,  $r_b$ , and  $r_o$  if  $I_C = 8 \text{ mA}$  and  $|V_A| = 80 \text{ V}$ . Include a unit with each answer.

$\beta = 250$

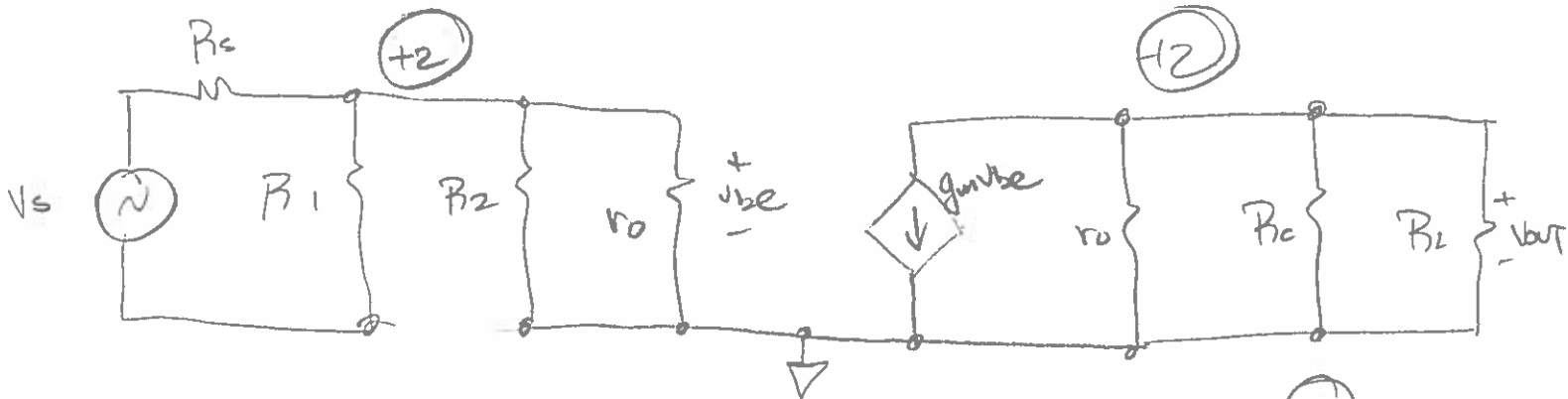

$$g_m = 35 I_C = 35 \cdot 8 = \underline{280 \text{ mA/V}} \quad (+1) \text{ unit}$$

(+1) eqn.

$$r_b = \frac{\beta}{g_m} = \frac{250}{280} = \underline{0.893 \text{ k}\Omega} \quad (+1) \text{ unit}$$

(+1) eqn.

$$r_o = \frac{|V_A|}{I_C} = \frac{80}{8} = \underline{10 \text{ k}\Omega} \quad (+1) \text{ eqn.}$$

$$= 68k \parallel 5.6k \parallel 0.893k = 0.762 k\Omega$$

Determine the mid-frequency gain  $A_v$ .

$$r_o = 10k \parallel 1k \parallel 5k = 0.769 k\Omega \quad (+)$$

$$V_{OUT} = -g_m V_{be} [r_o \parallel R_c \parallel R_2] \quad (+)$$

$$V_{OUT} = -280 \cdot V_{be} \cdot .769 = -215.32 V_{be} \quad (+)$$

$$V_{be} = V_s \frac{R_1 \parallel R_2 \parallel r_o}{R_1 \parallel R_2 \parallel r_o + R_s} \quad (+)$$

$$V_{be} = V_s \frac{.762}{.762 + 1} = 0.432 V_s \quad (+)$$

~~Draw the high-frequency small-signal model. Determine the input and output capacitances using Miller's Theorem if  $C_{BC} = 6 \text{ pF}$  and  $C_{BE} = 22 \text{ pF}$ .~~


$$V_{OUT} = -215.32 \cdot .432 V_s$$

$$\therefore A_v = \frac{V_{OUT}}{V_s} = -93.1 \quad (+)$$

OR 39 dB investing  
(+)

~~Compute the input and output HF cutoff frequencies and the approximate overall high-frequency cutoff,  $f_H$ .~~

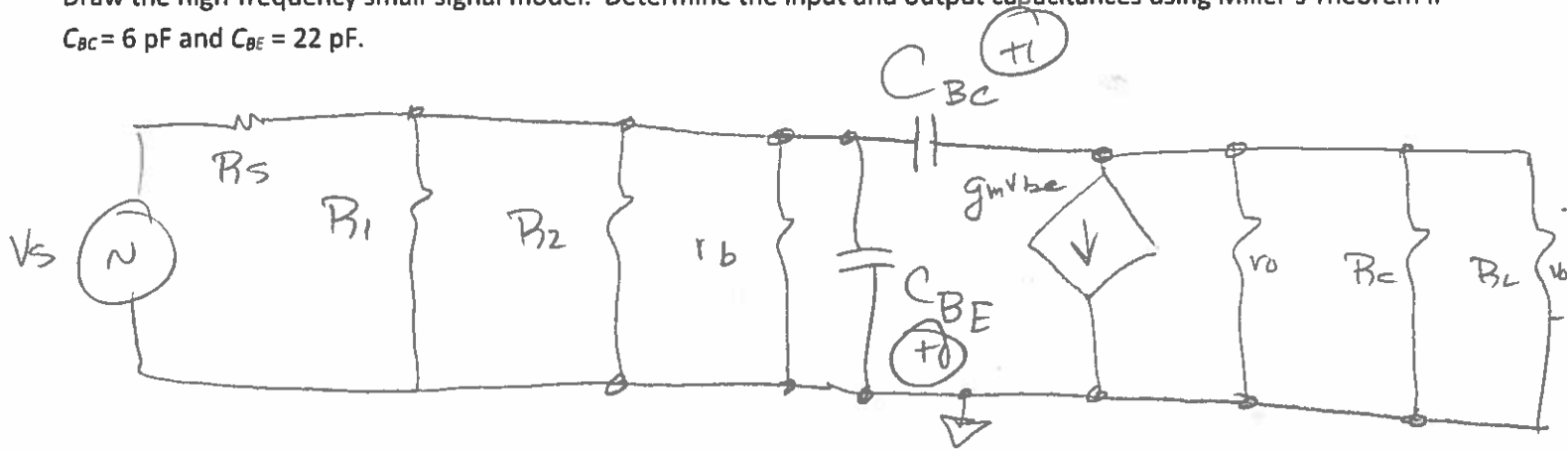Draw the high-frequency small-signal model. Determine the input and output capacitances using Miller's Theorem if  $C_{BC} = 6 \text{ pF}$  and  $C_{BE} = 22 \text{ pF}$ .



$$C_{BC(IN)} = C_{BC} (1 - A_V) = 6 \cdot (1 - 93) = \underline{\underline{564 \text{ pF}}} \quad (+1)$$

$$\therefore C_{IN} = C_{BC(IN)} + C_{BE} = 564 + 22 = \underline{\underline{586 \text{ pF}}} \quad (+1)$$

$$C_{OUT} = C_{BC(OUT)} = C_{BC} \left(1 - \frac{1}{A_V}\right) \approx \underline{\underline{6 \text{ pF}}} \quad (+1)$$

Compute the input and output HF cutoff frequencies and the approximate overall high-frequency cutoff,  $f_H$ .

$$f_{H(IN)} = \frac{1}{2\pi \cdot C_{IN} (R_S \parallel B_1 \parallel B_2 \parallel r_b)} \quad (+1)$$

$$= \frac{1}{2\pi \cdot 586 \times 10^{-12} \cdot 432} \rightarrow \begin{aligned} &= .762 \text{ k} \parallel 1 \text{ k} \\ &= \underline{\underline{432 \Omega}} \quad (+1) \end{aligned}$$

$$f_{H(IN)} = \underline{\underline{628.7 \text{ kHz}}} \quad (+1)$$

$$f_{H(OUT)} = \frac{1}{2\pi \cdot C_{OUT} (r_o \parallel R_C \parallel R_L)} \quad (+1)$$

$$f_{H(OUT)} = \frac{1}{2\pi \cdot 6 \times 10^{-12} \cdot .762 \text{ k}}$$

$$f_{H(OUT)} = \underline{\underline{34.8 \text{ MHz}}} \quad (+1)$$

$$f_{H(IN)} \ll f_{H(OUT)}$$

$$\therefore f_{H(IN)} \text{ dominates} \quad (+1)$$

$$f_H \approx \underline{\underline{628.7 \text{ kHz}}} \quad (+1)$$