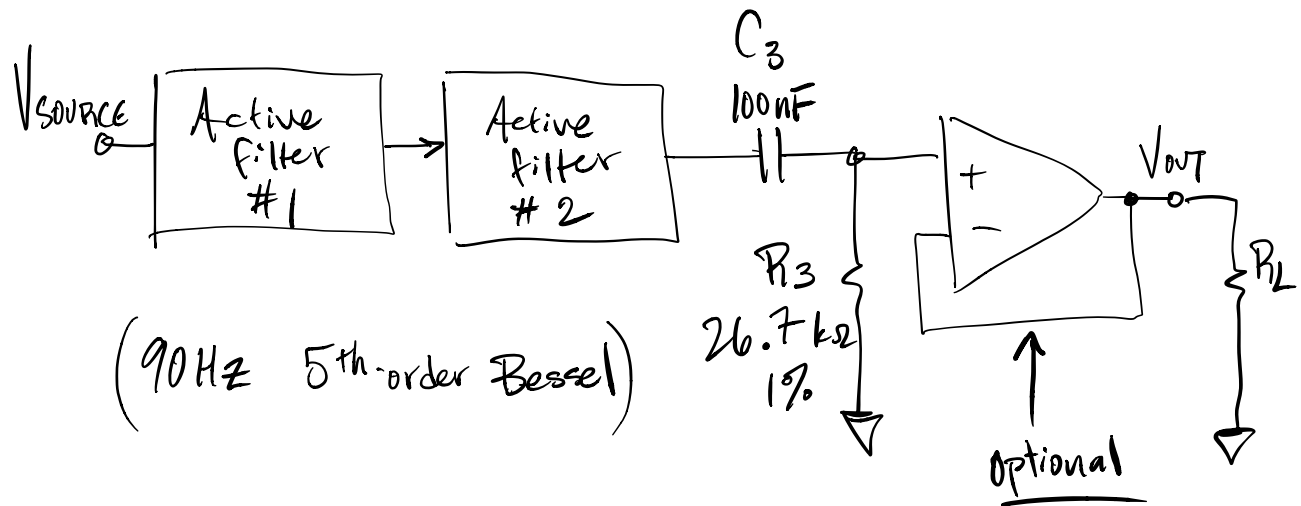



homework solution (refer to uploaded document) :



reality: these filters will be driving some external load, R_L

.. for the active filter sections, no problem;
as long as the op-amp can drive the load
($\text{k}\Omega$ - range)

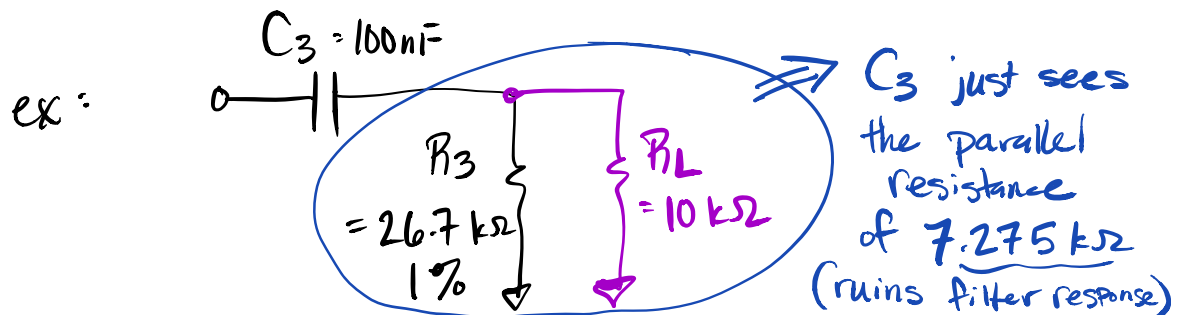.. but for the passive section (and all passive filters!)
need to consider the effects of R_L .




.. we could try to calculate C_3 for an expected load, if we're sure it'll never change

.. in this case, awkward value, possibly not available!

.. we could try to calculate some R_3 such that $R_3 \parallel R_L$ gives the right value
etc. etc. etc.




.. better : buffer it!

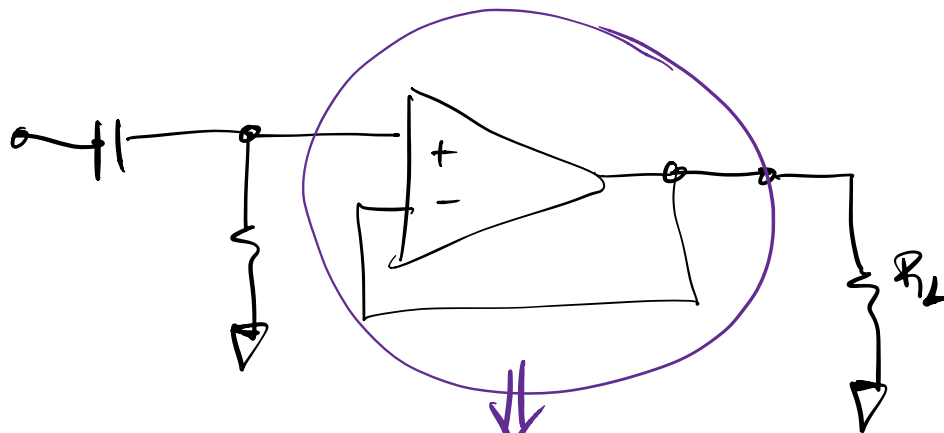

unity gain buffer!

.. doesn't change frequency response nor passband gain, but isolates R_L from $R_3 : C_3$!

Sallen-Key Equal-Component Band-Pass

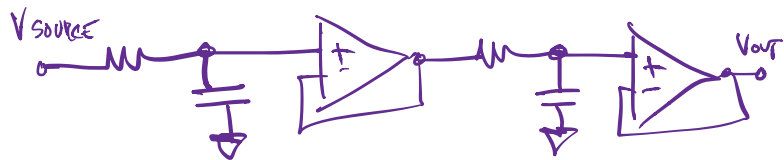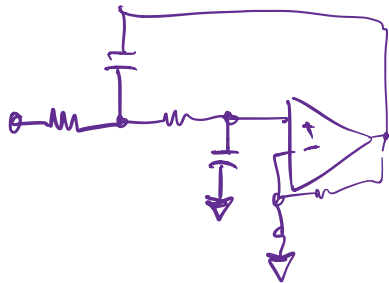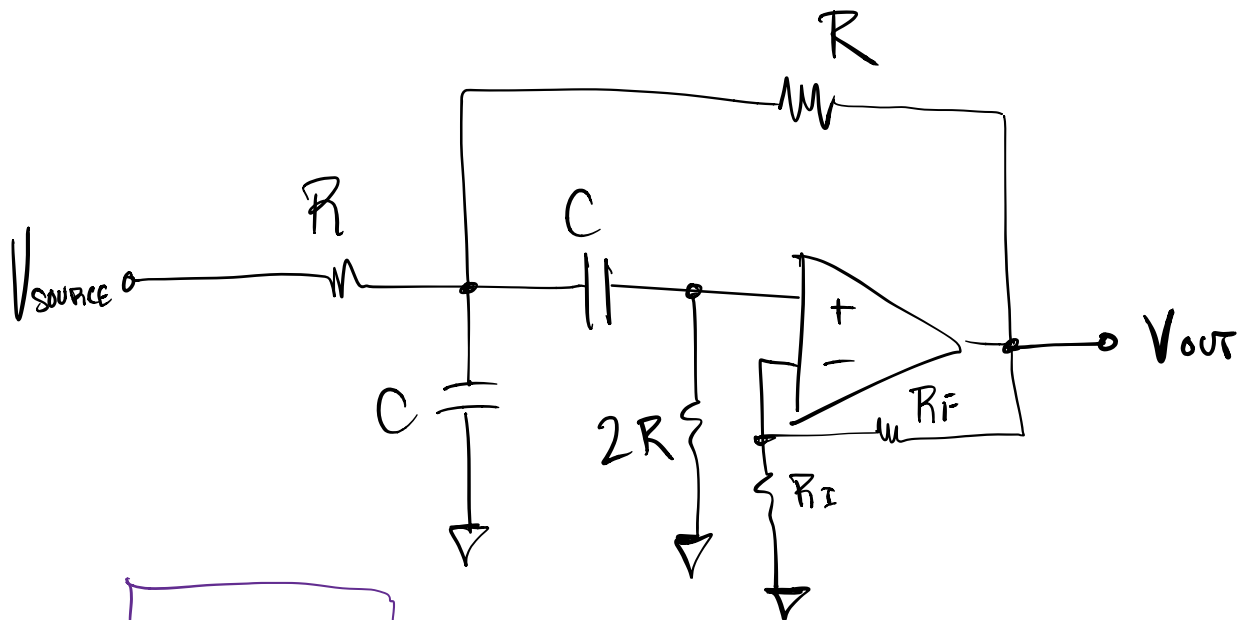

- .. two first-order low-pass filters in cascade \rightarrow max. Q of 0.5!
- .. positive feedback impedance is what underdamps (raises Q) the response!
- .. Same design procedure as other active S.K. E.C. filters; but notice 2R term.

1.) pick C

$$2.) R = \frac{1}{2\pi f_0 C}$$

$$3.) A_v = 3 - \frac{1}{Q}$$

$$\text{ex: } f_0 = 500 \text{ Hz}$$

$$Q = 4$$

↑
pretty sharp!

$$\text{pick } C = 10 \text{ nF}$$

$$\text{then } R = 31831 \rightarrow \text{use } \underline{31.6 \text{ k}\Omega \text{ } 1\%}$$

$$2R = 63662 \rightarrow \text{use } \underline{63.4 \text{ k}\Omega \text{ } 1\%}$$

$$A_v = 3 - \frac{1}{Q} = 3 - \frac{1}{4} = \underline{2.75} = 1 + \frac{R_F}{R_I}$$

$$\frac{R_F}{R_I} = 1.75$$

$$\text{pick } R_F = 10 \text{ k}\Omega \text{ } 1\%$$

$$\text{then } R_I = 5714$$

$$\text{use } \underline{5.76 \text{ k}\Omega \text{ } 1\%}$$

.. for this configuration, passband gain is not simply A_v !!!

$$\underline{A_v(f_0) = A_v \cdot Q}$$

$$\therefore A_v(500 \text{ Hz}) = 4 \cdot 2.75 = \underline{11}$$

$$\text{or } \underline{20.83 \text{ dB}}$$

.. that's a lot of gain !!! Check for amplifier clipping/saturation; may need to attenuate signal level ahead of filter

$$Q = \frac{f_0}{f_H - f_L}$$

$$\therefore f_H - f_L = \frac{500}{4} = 125 \text{ Hz}$$

