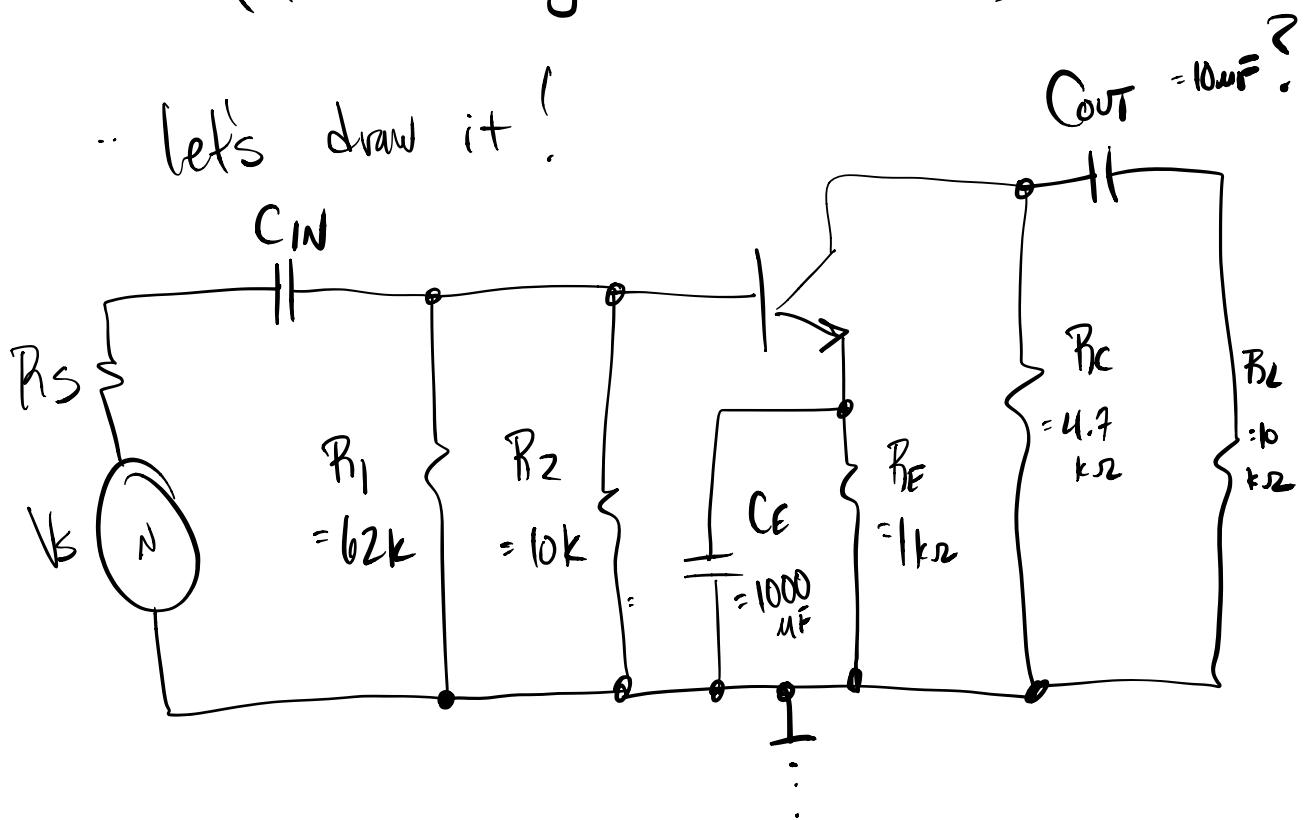


Low-Frequency AC Circuit


- at low frequencies, the impedances of the capacitors can no longer be considered non-zero /

(power supply is still "ground")

- let's draw it!




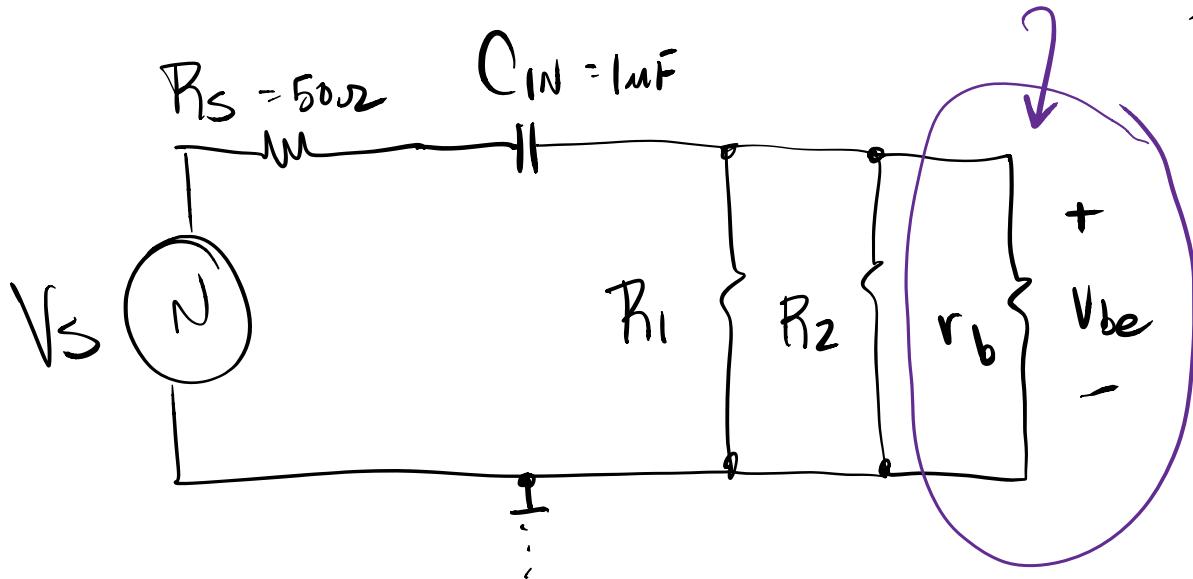C_{IN} : (back to small-signal BJT model!)



$$R_1 \parallel R_2 \parallel r_b = R_b' = 1.735 \text{ k}\Omega$$

.. slightly redraw circuit:

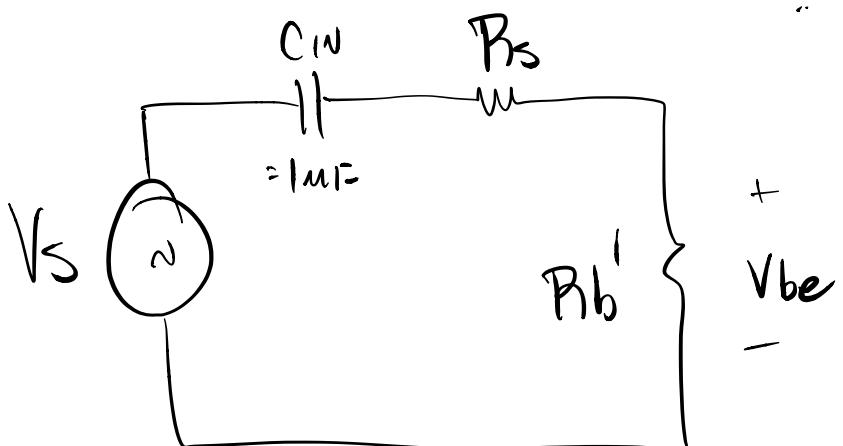

.. 1st-order HPF
w/ scaling factor!


$$= A_{V_1}$$

corner frequency of input HPF :


$$f_{CIN} = \frac{1}{2\pi C_{IN} (R_S + R_{lb}')} \\ = \frac{1}{2\pi \cdot 1 \times 10^{-6} (50 + 173S)}$$

$$\underline{f_{CIN} = 89.2 \text{ Hz}}$$

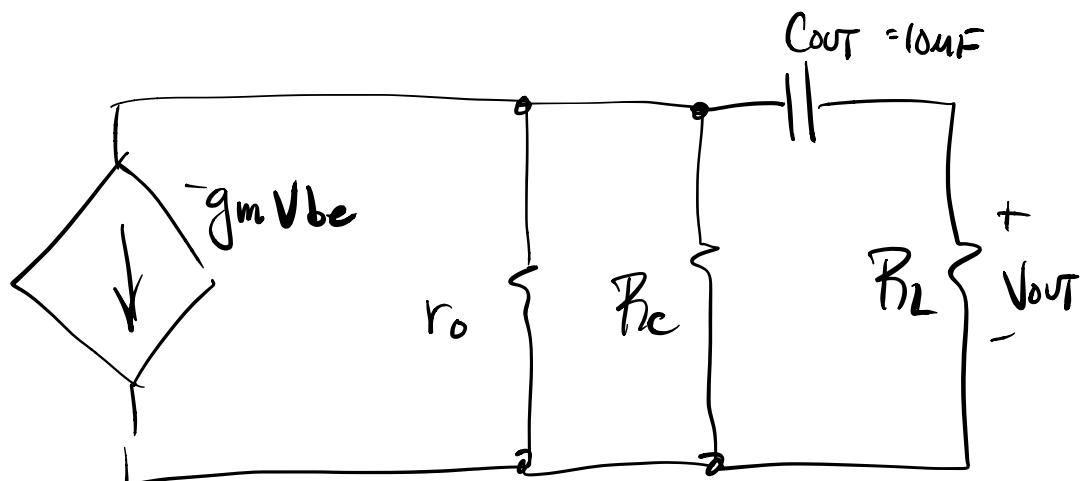
C_{OUT} : output half of small-signal model !



• One Source transformation:

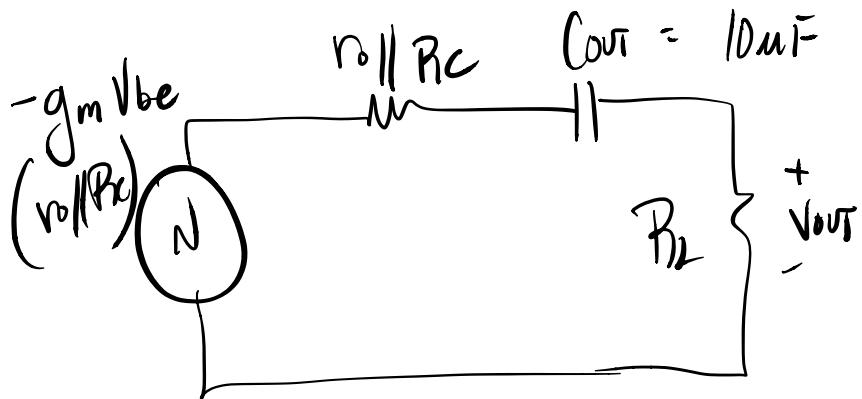

• Slight redraw:

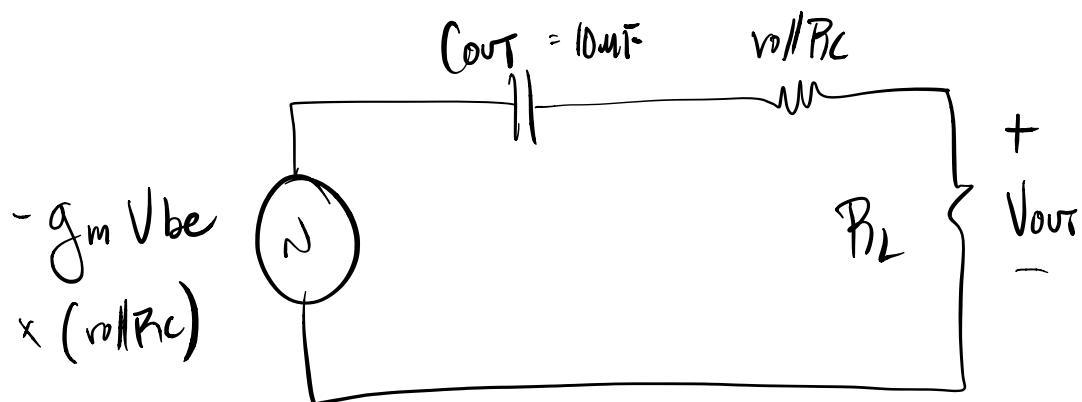

• Another HPF w/ scaling factor!

$$f_{c\text{ OUT}} = \frac{1}{2\pi C_{out} (r_o \parallel R_C + R_L)}$$

$$f_{C\text{ OUT}} = \frac{1}{2\pi \cdot 10 \times 10^{-6} (38.02k \parallel 4.7k + 10k)}$$

\Downarrow
 14.183 k

$$f_{C\text{ OUT}} = 1.12 \text{ Hz}$$


- now we deal w/ C_E
- it's complicated!
- beyond the scope of this course, the Thévenin resistance seen by C_E is

$$R_{CE} = \frac{1}{g_m} \parallel R_E$$

$$\frac{1}{g_m} = \frac{1}{92.05 \times 10^{-3}} = 10.952$$

... since $\frac{1}{g_m} \ll R_E$, ^{14!}

$$R_{CE} \approx \frac{1}{g_m}$$

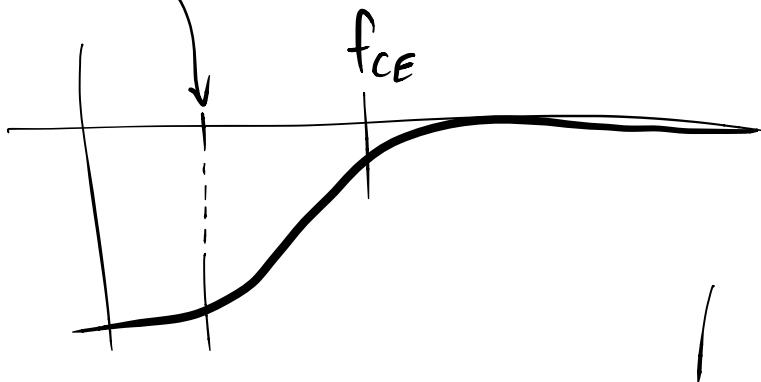

$$f_{CE} = \frac{1}{2\pi \cdot C_E \cdot R_{CE}}$$

$$= \frac{1}{2\pi \cdot 1000 \times 10^{-6} \cdot 10.9}$$

$$= \underbrace{14.6 \text{ Hz}}$$

... but then another thing happens that is a little less obvious.

- at some even lower frequency, $Z_{CE} \gg R_E$
and a shelf in the high-pass filter appears



- in this class : don't worry about it
- so we have three low-frequency cutoffs,
creating a third-order high-pass filter
(2nd if you include that shelf!)

third-order $\rightarrow 18 \text{ dB/oct}$

- because f_{CIN} , f_{COUT} , and f_{CE} are spaced
by a factor of ≈ 5 or better,
the approximate -3dB of the system is f_{CIN} !

- this concept is called a dominant pole.

- final -3dB LF point is $\approx f_{C_{IN}}$

$$f_L \approx 89.2 \text{ Hz}$$


High-Frequency AC Circuit

- at high frequencies, the impedances of C_{IN} , C_{OUT} , and C_E are sufficiently low that we treat them as shorts, just like at mid-frequencies

- so, what's the problem?

- now we have transistor capacitances to deal with (great!)

BJT High-Frequency Small-Signal Model

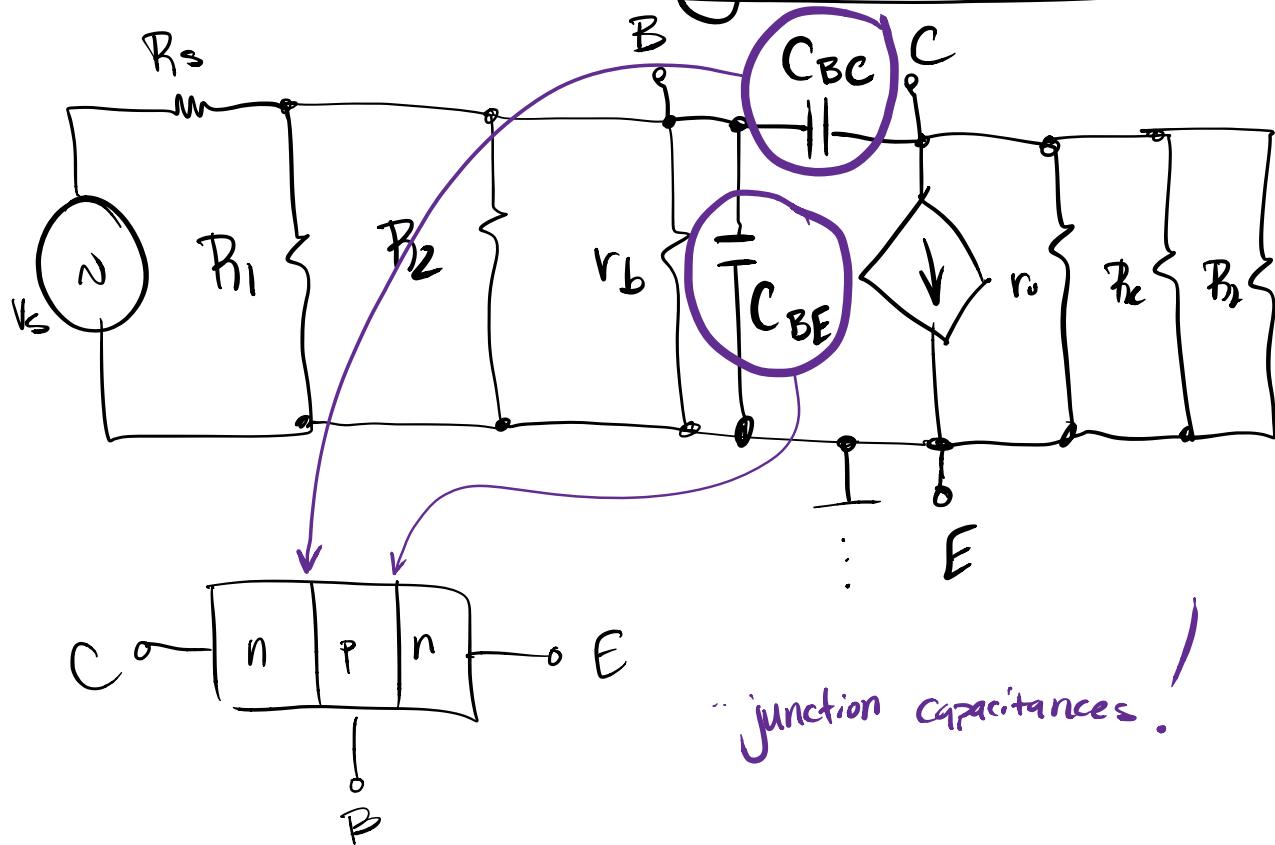

- Note : No significant capacitance between collector and emitter! So that's good!
- Slight issue : C_{BC} and C_{BE} change with quiescent operating point
(but we can approximate them)

from 2N3904 datasheet :

$$C_{BC0} = \underbrace{4 \text{ pF}}$$

① $I_E = 0$; actual value higher ② some I_E

$$C_{BEO} = \underbrace{18 \text{ pF}}$$



• C_{BE} looks like it would form a low-pass filter
w/ input resistances, but what about C_{BC} ?

• doesn't look like any filters we know !

• It's Miller Time



(Dr. Kazimierczuk !)

Miller's Theorem

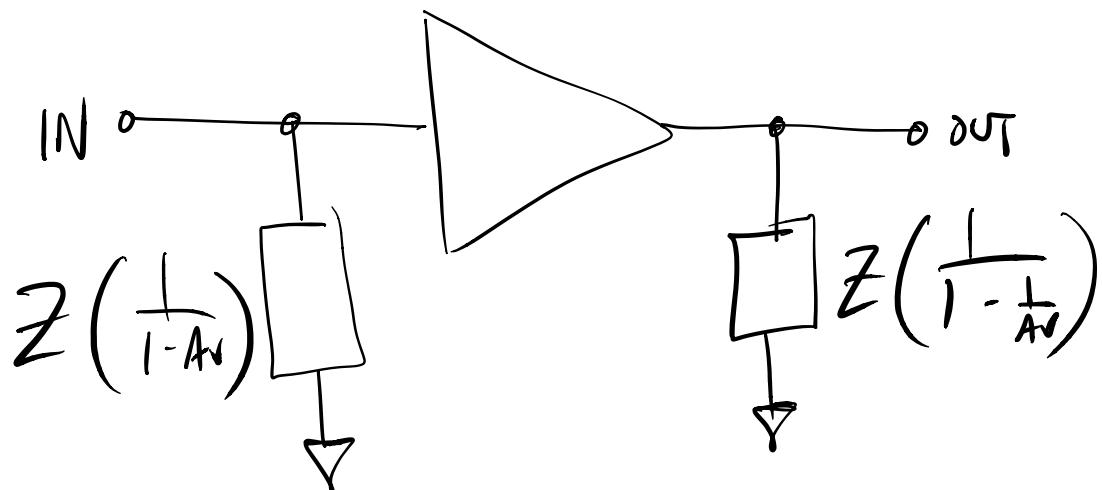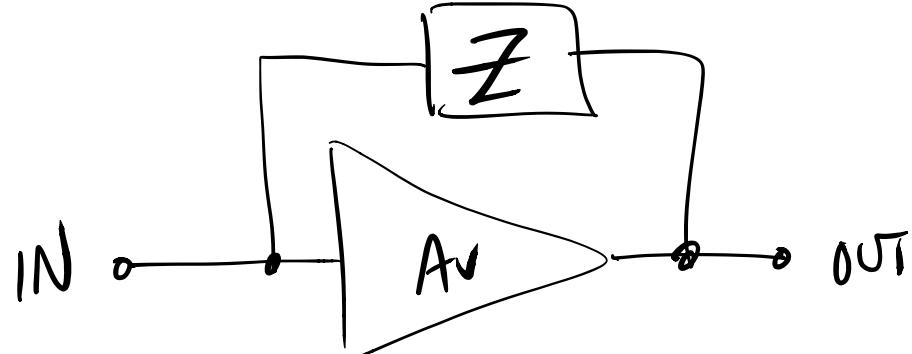

... now we're getting somewhere!

Since $Z_C = \frac{1}{j\omega C}$:

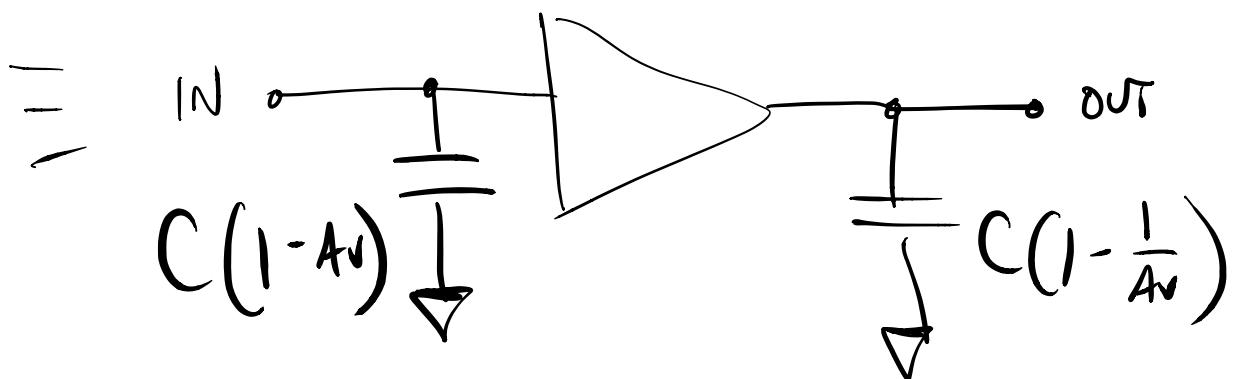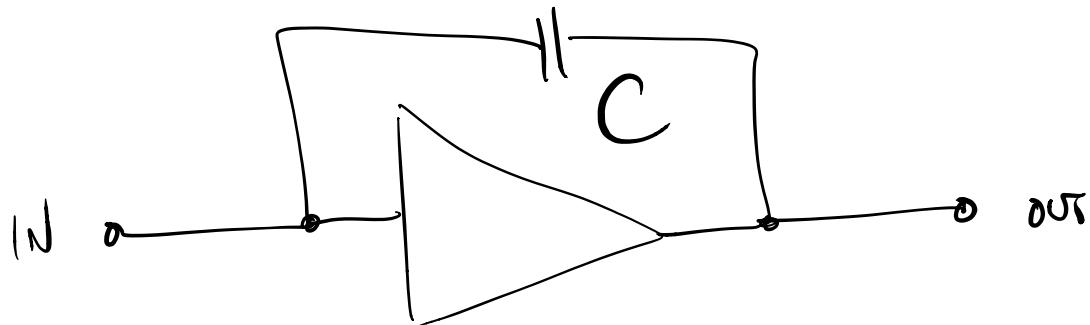

this means that C_{BC} , which is between the input and output of the circuit, may be split into two components:

$$C_{BC}(IN) = C_{BC} \left(1 - A_{V2} \right)$$


↓
gain between V_{be} and V_{out}

$$= 4 \left(1 - (-271) \right)$$



$$= \underbrace{1084 \text{ pF}}_{\dots} \quad ||||$$

$$C_{BC(\text{out})} = C_{BC} \left(1 - \frac{1}{A_V} \right) \approx \underbrace{4 \text{ pF}}_{\approx 1}$$

.. input half of HF SSM : $\approx R_b$

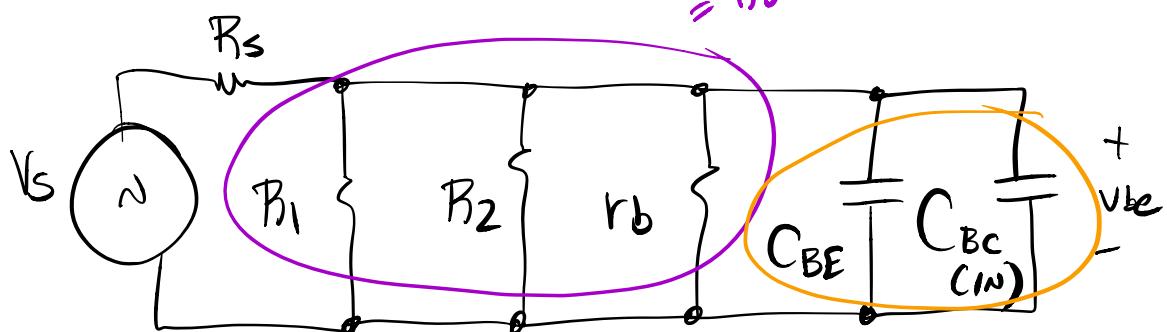

.. one source transformation :

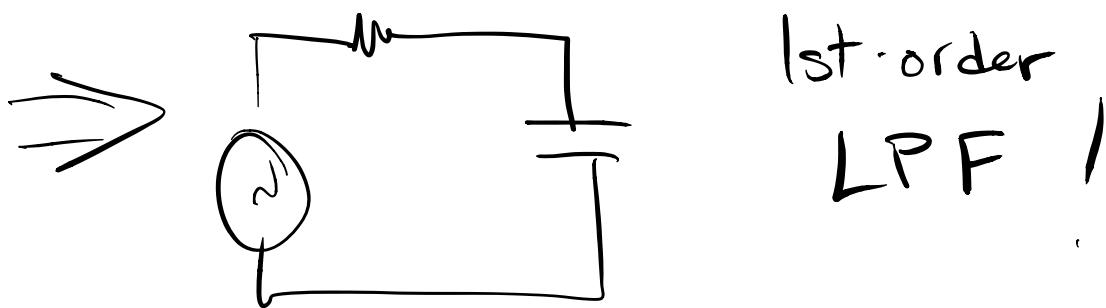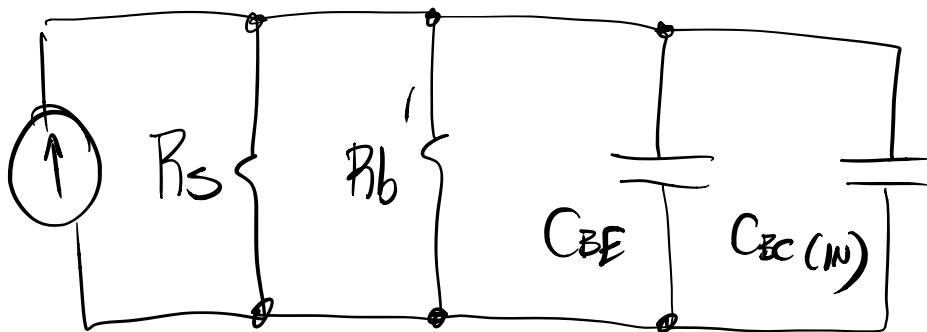

$$f_H(1N) = \frac{1}{2\pi} \left(C_{BE} + C_{BC}(1N) \right) \left(R_s \parallel R_{b'} \right)$$


$\stackrel{= 1084 + 18}{=} 1102 \text{ pF}$

Caps in parallel add!

$= 50 \parallel 1.735 \text{ k}$
 $= 48.6 \text{ Hz}$

$$f_H(1N) = 2.97 \text{ MHz}$$

- output half of HF SSM :

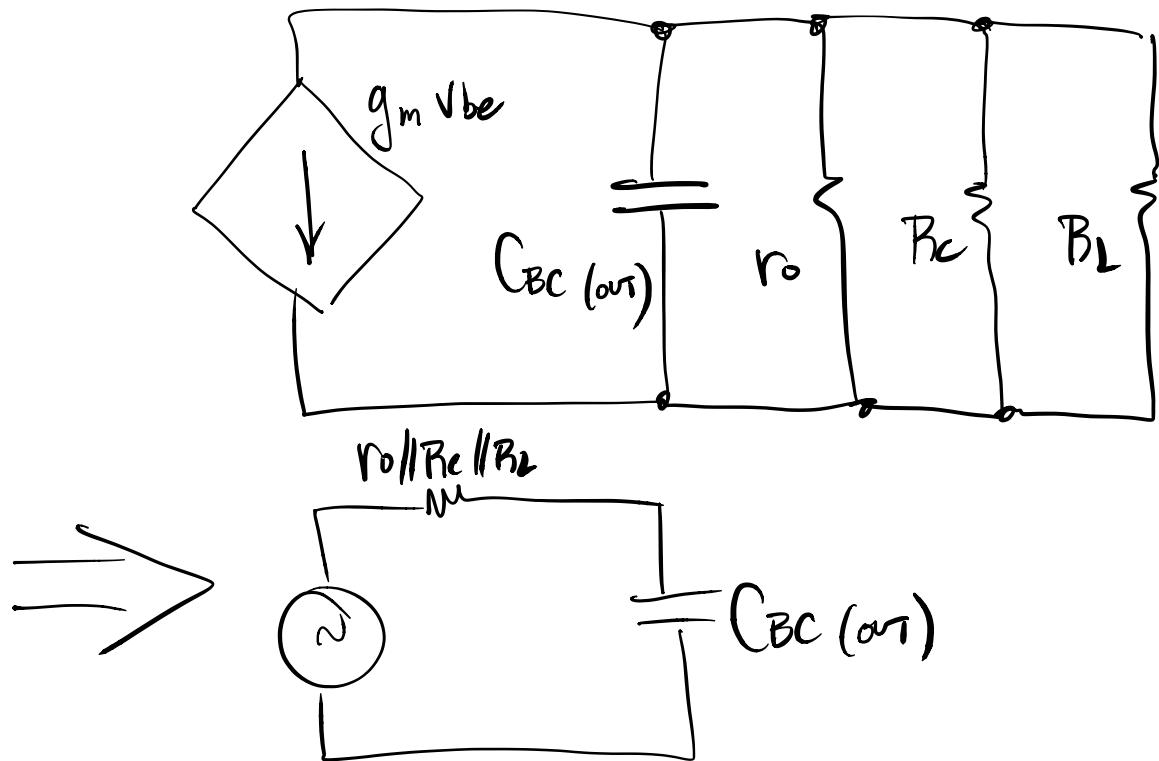

- another 1st-order LPF !

$$f_H(\text{out}) = \frac{1}{2\pi \cdot C_{BC}(\text{out}) (r_o \parallel R_C \parallel R_L)}$$

\Downarrow
 $\approx 4\text{pF}$ $\Rightarrow 38.02\text{k} \parallel 4.7\text{k} \parallel 10\text{k}$

$f_H(\text{out}) = 13.5 \text{ MHz}$

Since $f_H(\text{in}) \approx 4.5 f_H(\text{out})$,
it's the dominant pole

$\therefore f_H \approx 2.97 \text{ MHz}$

