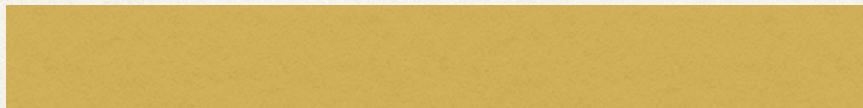


Capacitors



Capacitors

- ❖ Store Electrical Potential Energy AND Charge.

$$Q = CV$$

$$C = \epsilon_o \frac{A}{d}$$

$$\epsilon_o = 8.85 \times 10^{-12}$$

$$C = K \left(\epsilon_o \frac{A}{d} \right) = \epsilon \frac{A}{d}$$

$$\epsilon = K \epsilon_o$$

$$K = 1.000 \text{ ---} \rightarrow 300+$$

Capacitors

- ❖ What is the spacing between the plates of a 150 μF , if the plates are 20.0 cm x 30.0 cm

$$C = \epsilon_o \frac{A}{d}$$

$$d = \epsilon_o \frac{A}{C}$$

$$d = \left(8.85 \times 10^{-12}\right) \frac{(0.2\text{m} * 0.3\text{m})}{150 \times 10^{-6}} = 3.5 \times 10^{-9} \text{m}$$

Capacitors

- ❖ What is the charge stored on a 150 μF , if the plates are connected to a 5 V battery

$$Q = CV$$

$$Q = (150\mu\text{F})(5\text{V})$$

$$Q = 0.00075 \text{ Coulombs}$$

Capacitors: Energy

- ❖ What is the energy stored on capacitors

$$PE = \frac{1}{2}QV$$

$$PE = \frac{1}{2}CV^2$$

$$PE = \frac{1}{2}\frac{Q^2}{C}$$

Capacitors

- ❖ What is the energy stored on a 150 μF capacitor, if the plates are connected to a 5 V battery

$$PE = \frac{1}{2}CV^2$$

$$PE = \frac{1}{2}(150\mu\text{F})(5\text{V})^2$$

$$PE = 0.001875 \text{ J}$$

Capacitors

- ❖ What is the energy stored on a capacitor if the plates hold 0.00075 C of charged are connected to a 5 V battery

$$PE = \frac{1}{2}QV$$

$$PE = \frac{1}{2}(0.00075C)(5V)$$

$$PE = 0.001875 \text{ J}$$

Capacitors

- ❖ What is the energy stored on a 150 μF capacitor, if the plates hold 0.00075C of charge.

$$PE = \frac{1}{2} \frac{Q^2}{C}$$


$$PE = \frac{1}{2} \frac{(0.00075\text{C})^2}{(150\mu\text{F})}$$

$$PE = 0.001875 \text{ J}$$

Capacitors




Capacitors in series

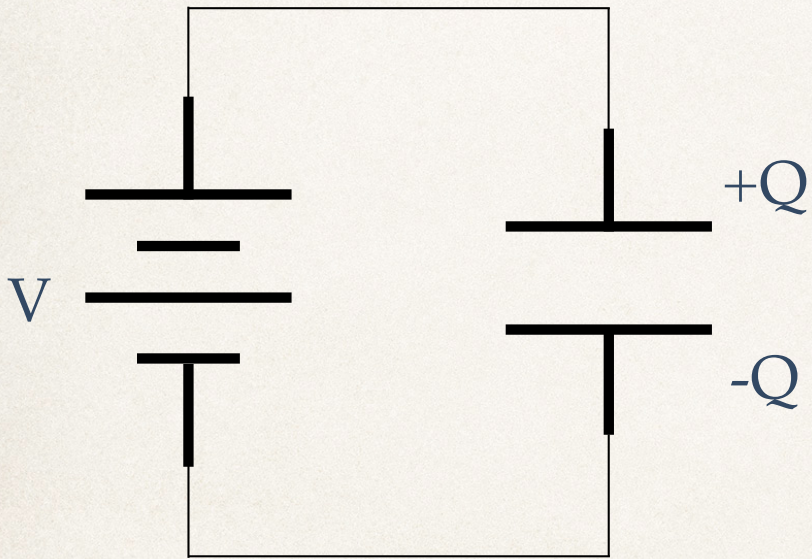


$$Q = CV$$

Capacitors in series

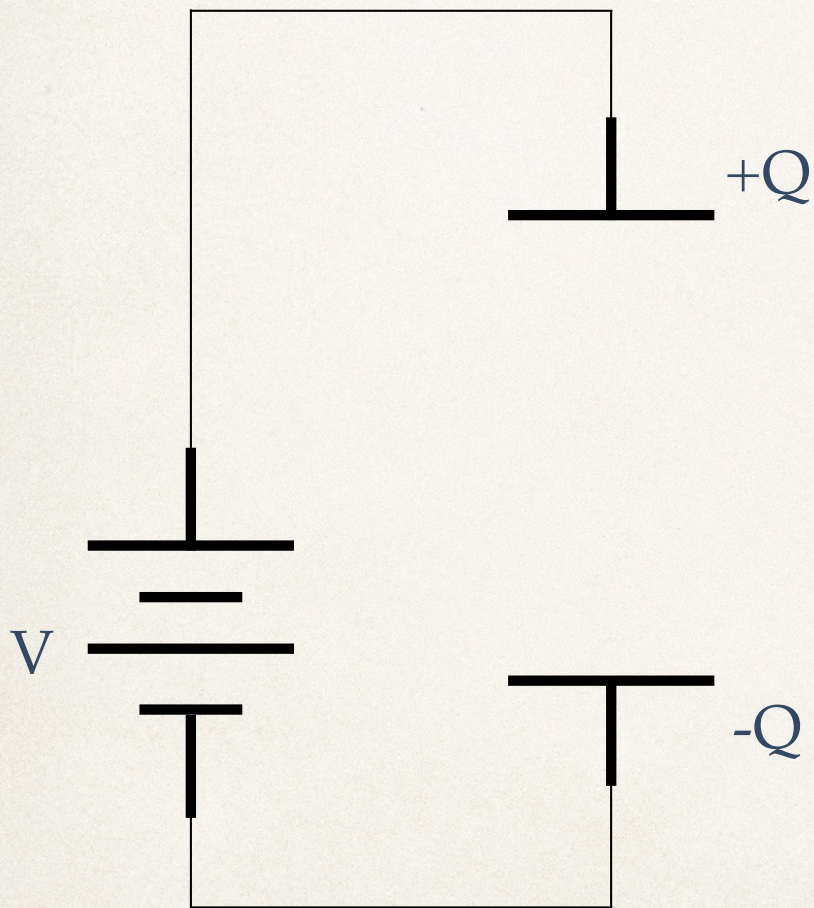

$$Q = CV$$

Capacitors in series

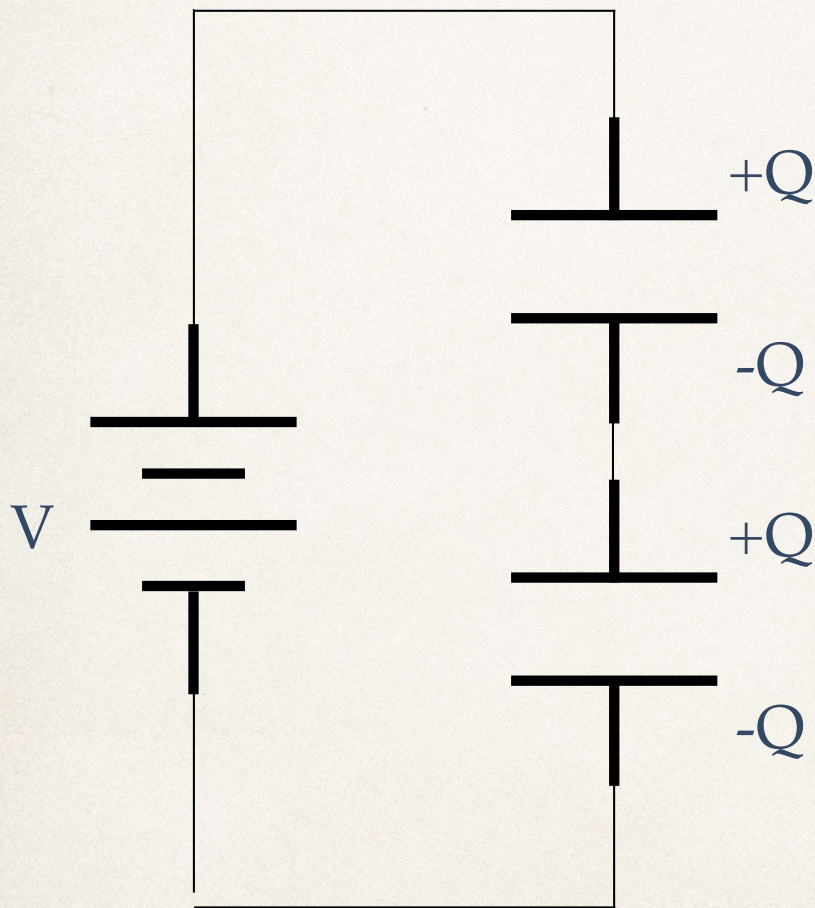


$$V = \frac{Q}{C}$$

$$V = V_1 + V_2$$

$$\frac{Q_{total}}{C_{total}} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

but... $Q_{total} = Q_1 = Q_2$

Capacitors in series

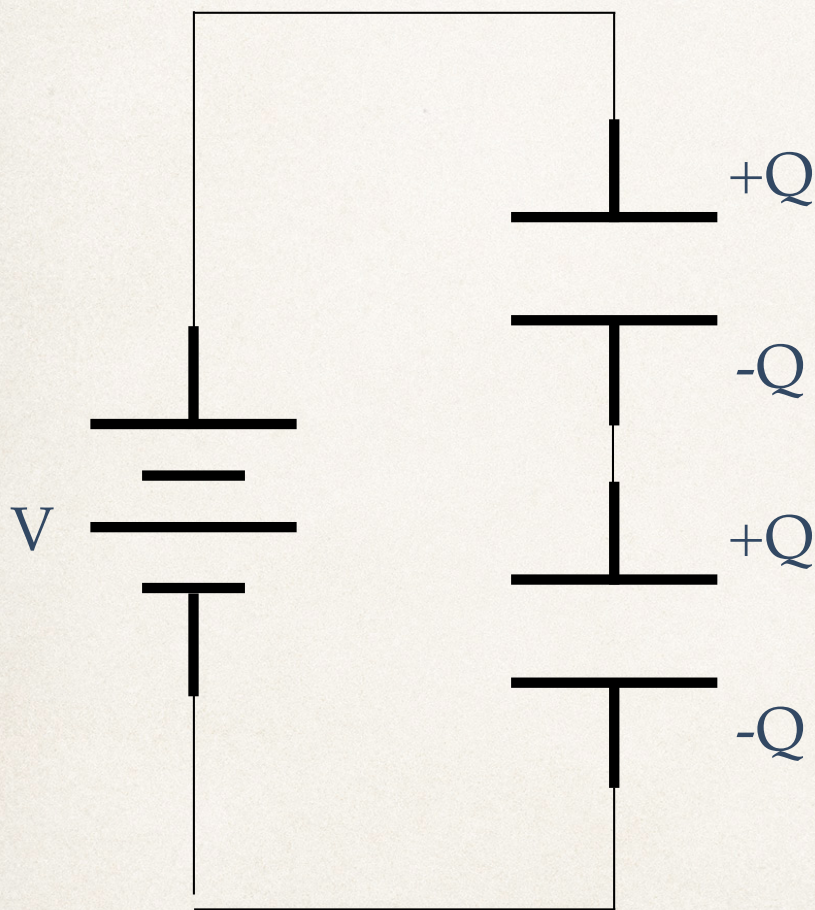

so...

$$\frac{Q}{C_{total}} = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$\boxed{\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}}$$

Series Capacitors

- ❖ What is the total capacitance of the following capacitors connected in series: 150 nF, 300 nF, 450 nF

$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{total}} = \frac{1}{150 \times 10^{-9} F} + \frac{1}{300 \times 10^{-9} F} + \frac{1}{450 \times 10^{-9} F}$$

$$\frac{1}{C_{total}} = 6.67 \times 10^7 \frac{1}{F} + 3.33 \times 10^7 \frac{1}{F} + 2.22 \times 10^7 \frac{1}{F}$$

Series Capacitors


- ❖ What is the total capacitance of the following capacitors connected in series: 150 nF, 300 nF, 450 nF

$$\frac{1}{C_{total}} = 12.22 \times 10^7 \frac{1}{F}$$

$$C_{total} = \frac{1}{12.22 \times 10^7 \frac{1}{F}}$$

$$C_{total} = 8.18 \times 10^{-9} F = 8.18 \text{ nF}$$


Capacitors in parallel

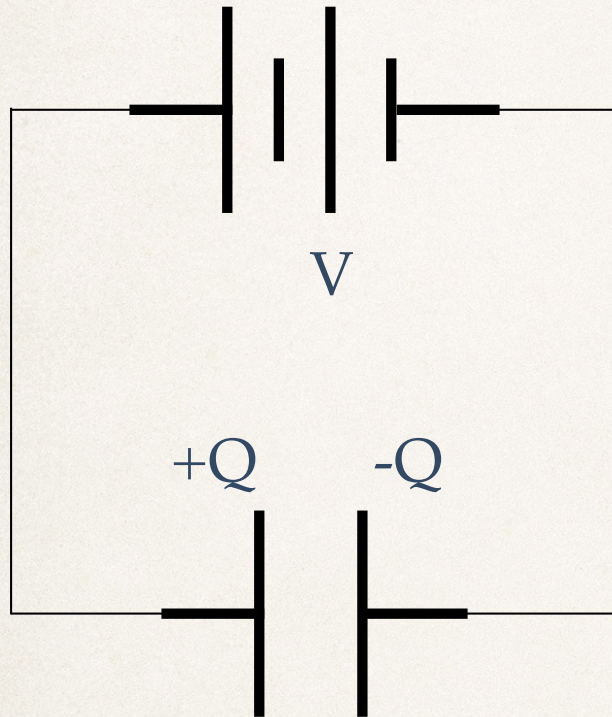

$$Q = CV$$

Capacitors in parallel

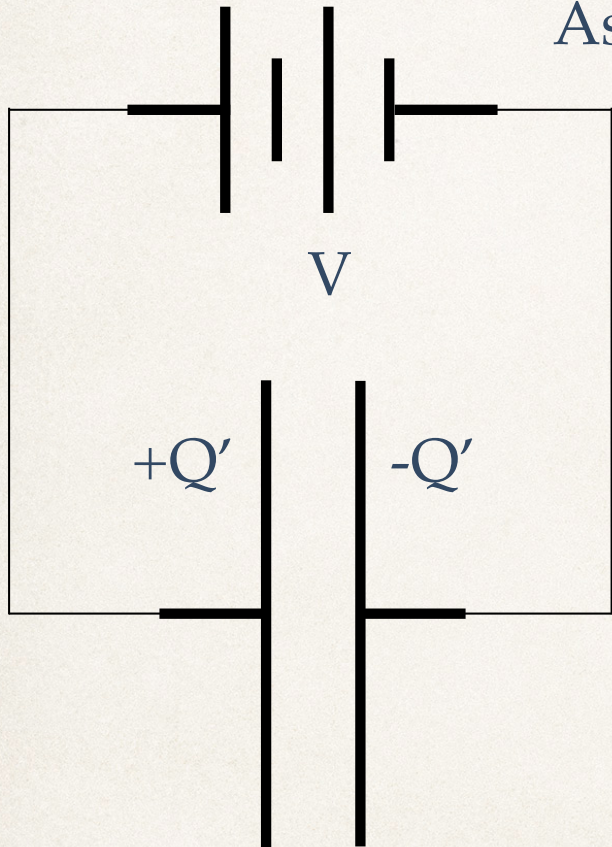Assume plates are twice as big as previous example



$$Q = \epsilon_o \frac{A}{d}$$


$$Q' = \epsilon_o \frac{A'}{d} \quad \text{but} \quad A' = 2A$$

$$Q' = \epsilon_o \frac{2A}{d} \quad Q' = 2 \left(\epsilon_o \frac{A}{d} \right)$$

\therefore

$$\boxed{Q' = 2Q}$$

Capacitors in parallel

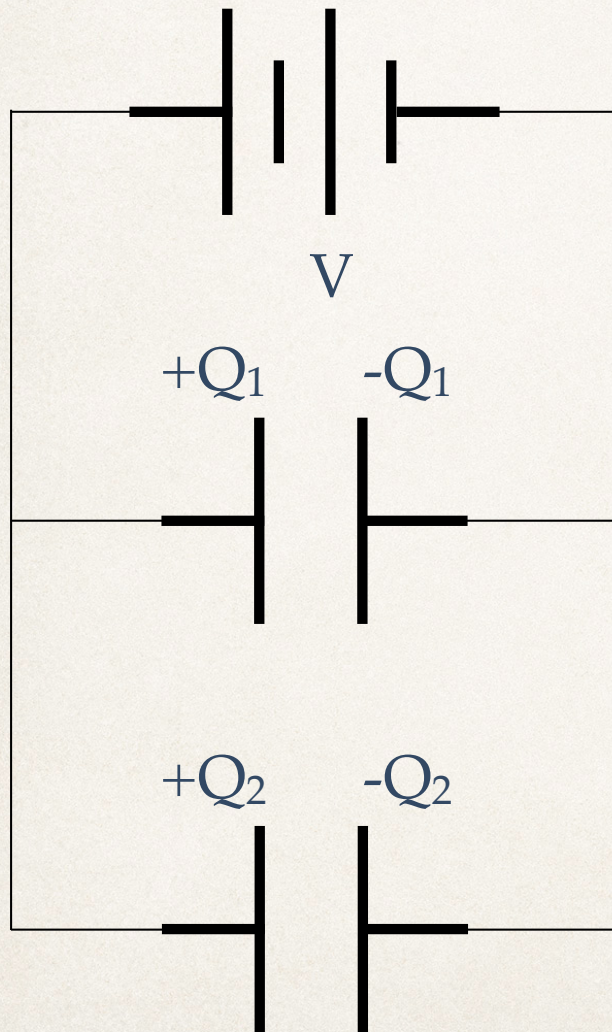

$$Q_{total} = Q_1 + Q_2$$

$$C_{total} V_{total} = C_1 V_1 + C_2 V_2$$

but... $V_{total} = V_1 + V_2$

so...

$$\boxed{C_{total} = C_1 + C_2}$$

Parallel Capacitors

- ❖ What is the total charge stored on the following capacitors connected in parallel, if connected to a 12V battery?: 150 nF, 300 nF, 450 nF

$$C_{total} = C_1 + C_2 + C_3$$

$$C_{total} = 150 \text{ nF} + 300 \text{ nF} + 450 \text{ nF}$$

$$C_{total} = 900 \text{ nF}$$

Parallel Capacitors


- ❖ What is the total charge stored on the following capacitors connected in parallel, if connected to a 12V battery?: 150 nF, 300 nF, 450 nF

$$Q = CV$$

$$Q = (900 \times 10^{-9} \text{ F})(12 \text{ V})$$


$$Q = 10.8 \mu\text{C}$$

Equivalent Capacitance

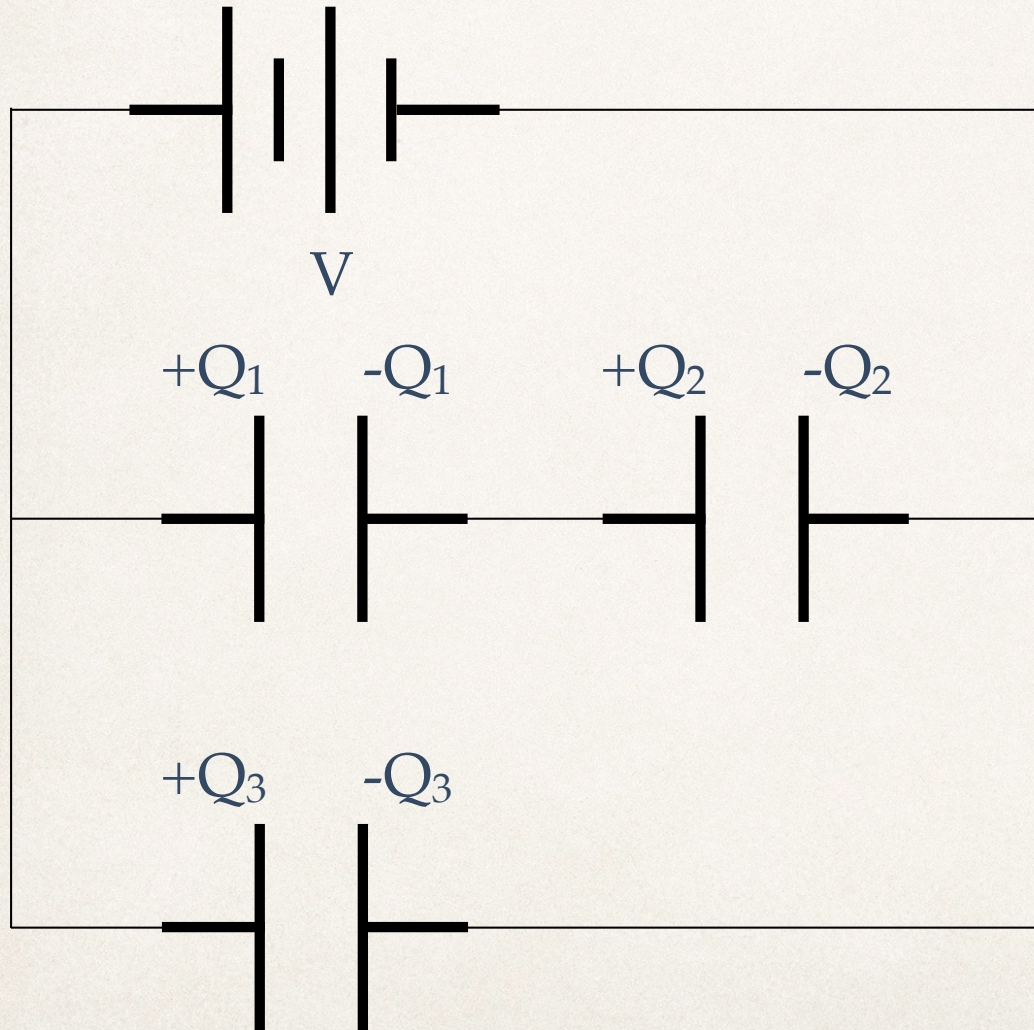

- ❖ What is the total charge stored on the following capacitors connected in parallel, if connected to a 12V battery?: $C_1=150$ nF, $C_2=300$ nF, $C_3=450$ nF


Equivalent Capacitance

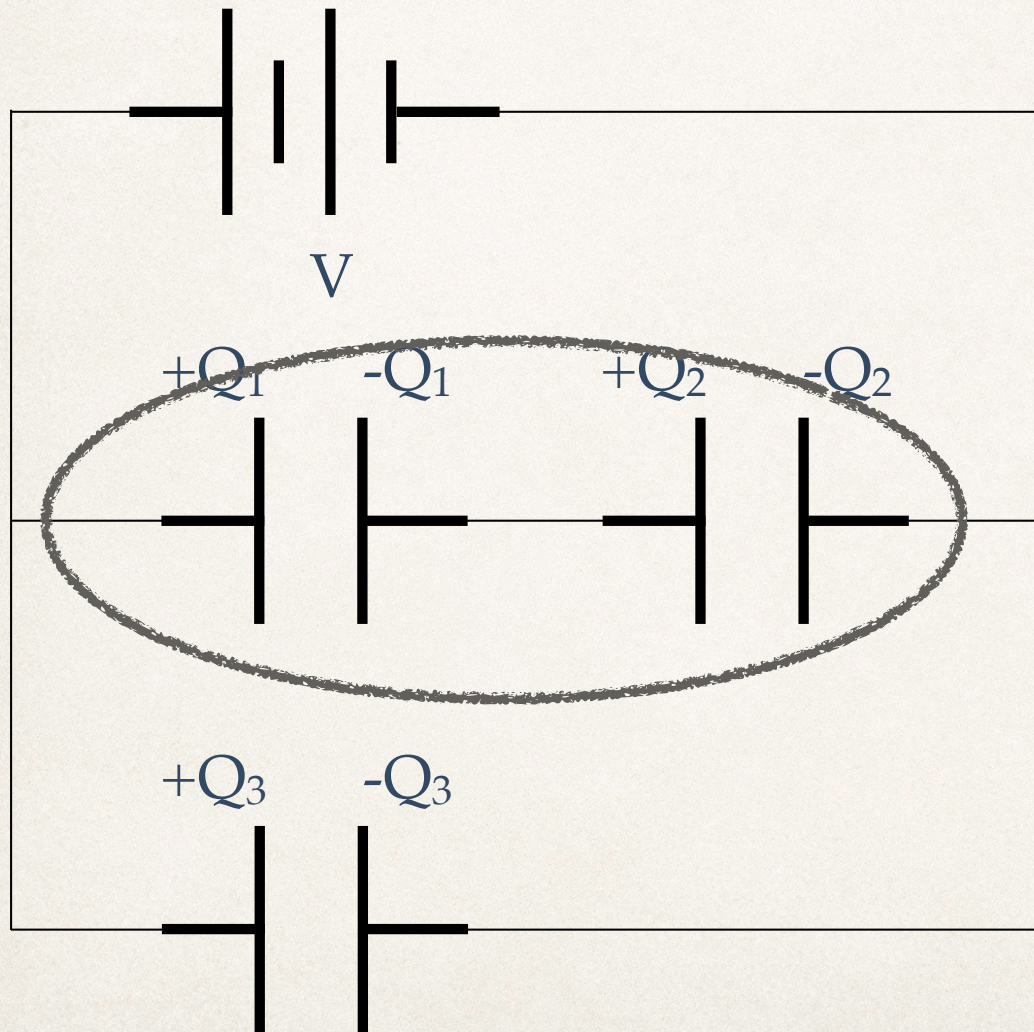

$$Q = ?$$

$$\frac{1}{C_{EQ_1}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Equivalent Capacitance

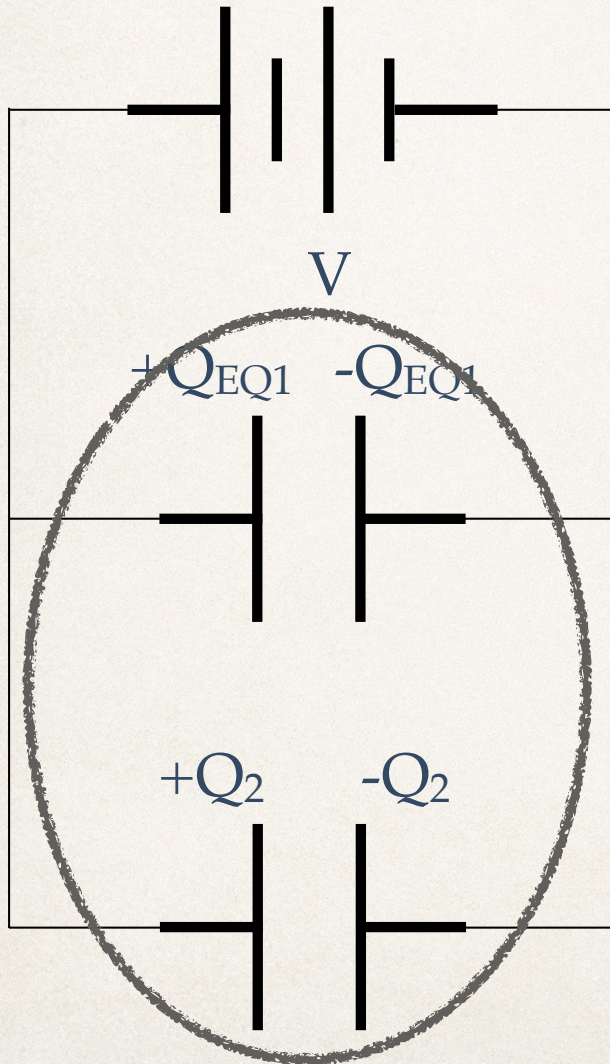

$$C_{EQ_2} = C_{EQ_1} + C_3$$

Equivalent Capacitance

