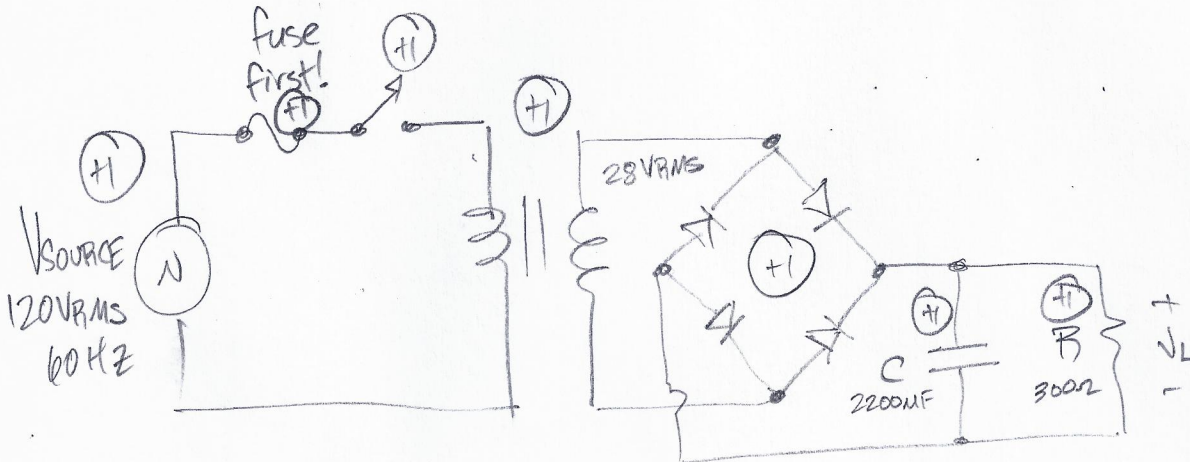


1) Draw a complete schematic for a linear power supply using the following components:

- 120-V_{RMS}, 60-Hz sinusoidal voltage source
- Line fuse and SPST on/off switch
- Ideal transformer with 28-V_{RMS} secondary voltage
- Full-wave bridge rectifier using silicon diodes
- 2,200-μF smoothing/filter capacitor
- 300-Ω load resistance



What is the turns ratio of this transformer? Is it a stepup or a stepdown?

$$\frac{V_P}{V_S} = \frac{120}{28} \approx 4.3 : 1 \quad (+1)$$

stepdown (+1)

What is the required PIV rating for the diodes in the bridge rectifier, and what 1N400X-series part will work?

$$PIV > \underline{V_{peak}} = 28\sqrt{2} \approx 39.6V \quad (+2)$$

∴ 1N4001 @ 50V is adequate (+1)

also use 50V capacitor (+1)

Determine the peak rectified voltage and approximate load current. (Don't calculate ripple yet.)

$$V_{\text{peak}} = V_s \sqrt{2} - 1.4 = 28\sqrt{2} - 1.4 = 38.20 \text{ V}$$

+2

$$I_L \approx \frac{V_{\text{peak}}}{R_L} = \frac{38.20}{300} = 0.1273$$

or 127.3 mA +2

Calculate the peak-to-peak ripple voltage and final average DC output voltage. What percentage of the DC voltage is the ripple, and is this "acceptable?"

$$V_{\text{ripple}} = \frac{I_L}{2fC} = \frac{0.1273}{2 \cdot 60 \cdot 2200 \times 10^{-6}}$$

$$= 0.4822$$

or 482.2 mV p.p +2


$$V_L = V_{\text{peak}} - \frac{1}{2} V_{\text{ripple}}$$

$$= 38.2 - \frac{1}{2} \cdot 0.4822 = \underline{37.96 \text{ V}} \quad +2$$

$$\frac{0.4822}{38.2} = 0.0126 \text{ or } \underline{1.26\%} \quad +1$$

(yes, acceptable)

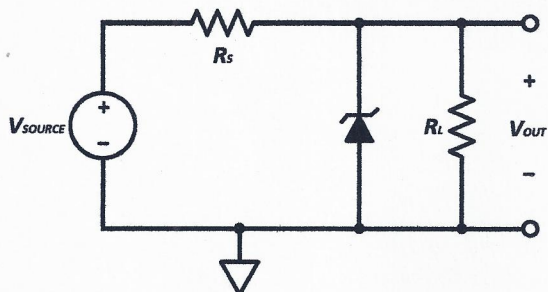2) What is this circuit called? What type of diode is used, and in what mode does it operate?



shunt voltage regulator

Zener diode (+1)

reverse-breakdown (+1)

V_{SOURCE} varies from 8.0 to 8.5 V, while R_L varies from $100\ \Omega$ to ∞ (open circuit). If the 1N5341B is rated at 6.2 V, calculate R_S such that the diode has a minimum current of 2 mA under all conditions. Choose the nearest E24 value and determine a suitable power rating.

lowest Zener current occurs when V_{SOURCE} is LOW
and I_L is HIGH

$$I_L(\max) = \frac{V_L}{R_{L(\min)}} = \frac{6.2}{100} = 0.062\text{ A} \quad (+2)$$

to keep 2mA in Zener, we therefore need

$$I_S = I_{L(\max)} + I_{Z(\min)} \\ = 0.062 + 0.002 = 0.064\text{ A} \quad (+2)$$

$$R_S = \frac{V_{SOURCE(\min)} - V_{OUT}}{I_S} = \frac{8 - 6.2}{0.064} = 28.125\ \Omega \quad (+2)$$

$$\text{Use } R_S = 27\ \Omega \quad (+1)$$

$$P_{RS(\max)} = \frac{(V_{SOURCE(\max)} - V_{OUT})^2}{R_S} = \frac{(8.5 - 6.2)^2}{27} = 0.1959 \quad (+2)$$

Is the 1N5341B's power rating of 5 W sufficient under all operating conditions?

max. power occurs @ $V_{SOURCE(\max)}$; $I_L(\min)$

$$I_{L(\min)} = \frac{6.2}{\infty} = 0$$

$$\therefore I_{Z(\max)} = \frac{8.5 - 6.2}{27} = 0.08519\text{ A} \quad (+2)$$

$$P_Z = 6.2 \cdot 0.08519 \\ = 0.5281\text{ W} \quad (+1)$$

ups 5W is ok!

Use $\frac{1}{4}\text{ W}$
or $\frac{1}{2}\text{ W}$
to be safe
(+1)