

EE 2010 Circuit Analysis

Module 21: Transient Response: Dynamic Circuits First-Order Problems

These notes are drawn from *Alexander and Sadiku*, 2013, *O'Malley*, 2011, and other sources. They are intended to offer a summary of topics to guide you in focused studies. You should augment this handout with notes taken in class, reading textbook(s), and working additional example problems.

Recall:

Every first-order linear differential equation with constant coefficients has exactly the same solution:

$$\text{quantity}(t) = \text{quantity}(\infty) + [\text{quantity}(t_0) - \text{quantity}(\infty)]e^{-\frac{(t-t_0)}{\tau}}, \quad t \geq t_0$$

where t_0 is the time we are initially interested in the system, and τ is the *time constant* of the system.

We're ready to solve problems.

Problem 7.5:

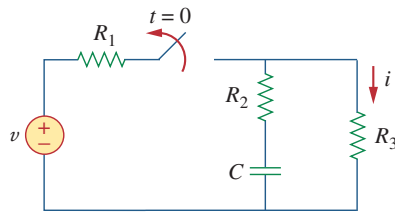


Figure 7.85


For Prob. 7.5.

We have $i(0) = \frac{v}{R_1 + R_3}$, $i(\infty) = 0$, $\tau = (R_2 + R_3)C$, so that:

$$i(t) = \frac{v}{R_1 + R_3} e^{-\frac{t}{(R_2 + R_3)C}}, \quad t \geq 0$$

Problem 7.7:

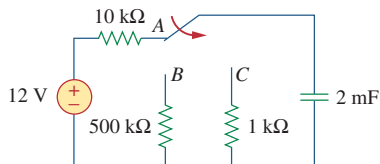7.7 Assuming that the switch in Fig. 7.87 has been in position A for a long time and is moved to position B at $t = 0$. Then at $t = 1$ second, the switch moves from B to C. Find $v_C(t)$ for $t \geq 0$.



This is called a sequential transient, where the final condition of the present epoch is the initial condition of the next epoch. Each of these is simple, just a matter of keeping track of time. So... for each time epoch, consider that circuit from its initial time to $t = \infty$.

For $0 \leq t \leq 1$: We have $v_C(0) = 12$, $v_C(\infty) = 0$, $\tau = RC = 500k\Omega \times 2mF = 1000$, so that:

$$v(t) = 12e^{-\frac{t}{1000}}, \quad 0 \leq t \leq 1$$

For $1 \leq t$: We have $v_C(1) = 12e^{-\frac{1}{1000}} \approx 11.988$, $v_C(\infty) = 0$, $\tau = RC = 1k\Omega \times 2mF = 2$, so that:

$$v(t) = 11.988e^{-\frac{(t-1)}{2}}, \quad 1 \leq t$$

... and we MUST have that $v(1)$ from the first part matches $v(1)$ from the second part. Check!
Hence:

$$v(t) = \begin{cases} 12e^{-\frac{t}{1000}}, & 0 \leq t \leq 1 \\ 11.988e^{-\frac{(t-1)}{2}}, & 1 \leq t \end{cases}$$

7.11 For the circuit in Fig. 7.91, find i_o for $t > 0$.

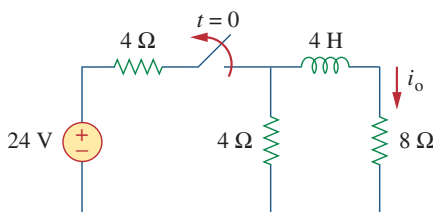


Figure 7.91

For Prob. 7.11.

We note, via a quick node equation that $v_o = 48/5$ so that $i_o(0) = 1.2$, $i_o(\infty) = 0$, $L = 4$ and $R_{eq} = 12$, so that:

$$i_o(t) = 1.2e^{-3t}, \quad t \geq 0$$

7.19 In the circuit of Fig. 7.99, find $i(t)$ for $t > 0$ if $i(0) = 6$ A.

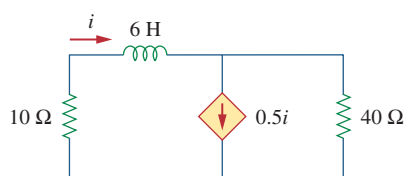


Figure 7.99

For Prob. 7.19.

We can't do 7.19. But if we knew the Thevenin equivalent of 7.19 as seen by the inductor, we could find $i(t)$ for the inductor driving the Thevenin equivalent. No independent sources, so $V_{th} = 0$. I would find R_{th} by removing the inductor and applying a 1Amp source so that $i = 1$. The voltage induced is $v = 0.5 \times 40 + 1 \times 10 = 30V$, so that $R_{th} = 30$.

So now we have that $i(0) = 6$, $i_o(\infty) = 0$, $L = 6$ and $R_{th} = 30$, so that:

$$i(t) = 6e^{-5t}, \quad t \geq 0$$

7.23 Consider the circuit in Fig. 7.103. Given that $v_o(0) = 10$ V, find v_o and v_x for $t > 0$.

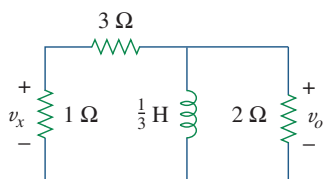


Figure 7.103

For Prob. 7.23.

Here, we could find the inductor current, and then do a current divider to find v_s and v_o . But, since every voltage and every current in the circuit has a first-order solution, let's just go directly to:

We have that $v_o(0) = 10$, $v_o(\infty) = 0$, $L = 1/3$ and $R_{eq} = 2 || 4 = 4/3$, so that:

$$v_o(t) = 10e^{-4t}, \quad t \geq 0$$

... and then by a voltage divider, $v_x(t) = v_o(t)/4$.

7.39 Calculate the capacitor voltage for $t < 0$ and $t > 0$ for each of the circuits in Fig. 7.106.

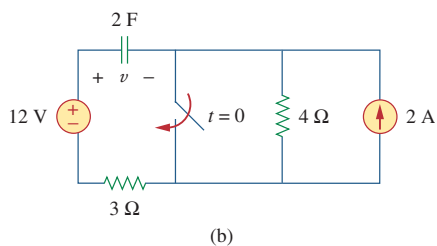
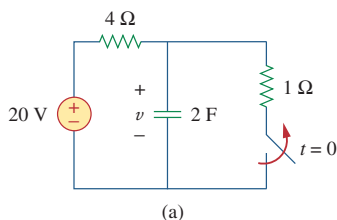


Figure 7.106

For Prob. 7.39.

We'll just ignore the $t < 0$ goofiness. We note, for part a) that $v(0) = 4$, $v(\infty) = 20$, $C = 2$ and $R = 4$, so that:

$$v(t) = 20 + (4 - 20)e^{-\frac{t}{8}}, \quad t \geq 0$$

For part b) we note that $v(0) = 12 - 8 = 4$, $v(\infty) = 12$, $C = 2$ and $R = 3$, so that:

$$v(t) = 12 + (4 - 12)e^{-\frac{t}{6}}, \quad t \geq 0$$

Problem 7.40:

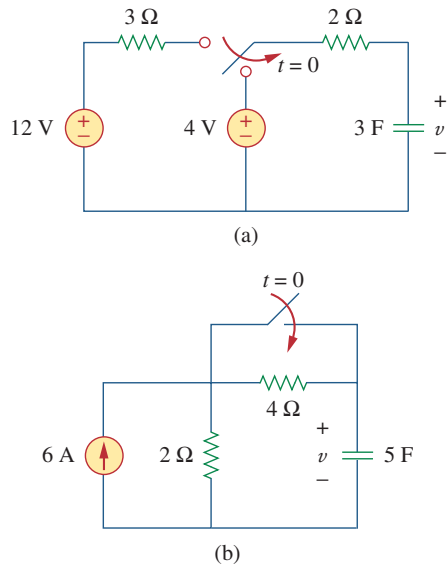


Figure 7.107

For Prob. 7.40.

We note, for part a) that $v(0) = 12$, $v(\infty) = 4$, $C = 3$ and $R = 2$, so that:


$$v(t) = 4 + (12 - 4)e^{-\frac{t}{6}}, \quad t \geq 0$$

For part b) we note that $v(0) = 12$, $v(\infty) = 12$, so that this is a really stupid problem since:

$$v(t) = 12$$

Problem 7.42:

Example: Find $v_o(t)$ for $t > 0$.

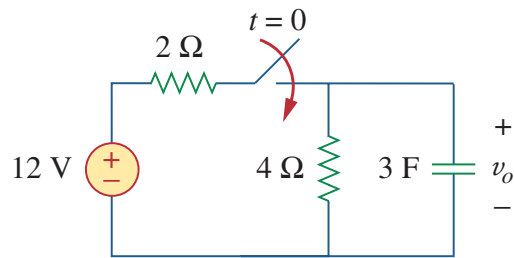
**The t -land approach:**

We observe that $v_o(0) = 0$, $v_o(\infty) = 8$, $C = 3$ and $R_{eq} = 4 \parallel 2 = 4/3$, so that:

$$v(t) = 8 - 8e^{-\frac{t}{4}}, \quad t \geq 0$$

Problem 7.42:

Example: Find $v_0(t)$ for $t > 0$.

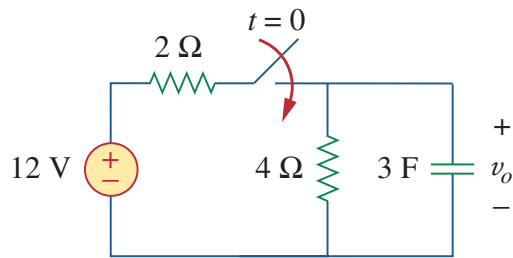

The s -land approach:

```
%% EE 2010 — Circuit Analysis
```

```
clear all
```

```
syms s t V0 v0
```

```
% Node equation
```

```
V0(s) = solve((V0-(12/s))/2 + V0/4 + 3*s*V0==0,V0)
```

```
% and the time-domain response
```

```
v0(t) = ilaplace(V0(s))
```


```
%
```

```
fplot(v0(t),[0,40]), grid
```

```
title('Capacitor voltage v0(t)'); xlabel('Time(seconds)'); ylabel('Voltage')
```

```
%%
```

and the result: $V0(s) = 8/(4s^2 + s)$, $v0(t) = 8 - 8\exp(-t/4)$

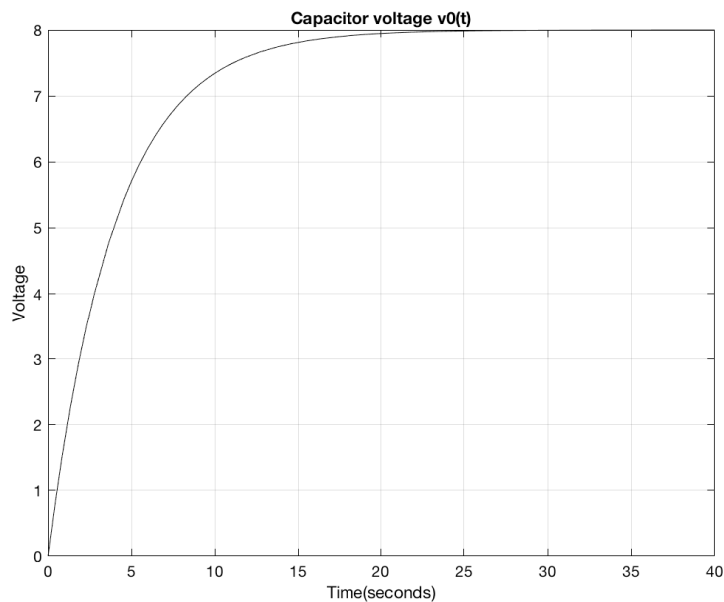

Problem 7.56:

7.56 For the network shown in Fig. 7.122, find $v(t)$ for $t > 0$.

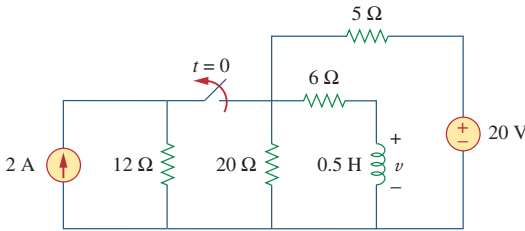


Figure 7.122

For Prob. 7.56.

This problem can be a bit confusing since one is inclined to jump to a first-order solution for $v(t)$ using the two steady-state values $v(0^-) = 0$ and $v(\infty) = 0$. But this is incorrect because while the inductor **current** cannot instantaneously change, the inductor **voltage** can indeed change instantaneously. That is, while $v(0^-) = 0$, $v(0^+) \neq 0$!

One could find the inductor **current** and then find the voltage as $v(t) = L di(t)/dt$, or one could find the inductor voltage directly. If we pursue the inductor current, we have a node equation before the switch opens:

%% Problem 7.56 a

% Node equation

clear all

syms va

va = solve(-2 + va/12 + va/20 + va/6 + (va-20)/5 ==0, va)

i = va/6

from which we obtain $i(0) = 2A$. Again, after the switch opens, we have

%% Problem 7.56 b

% Node equation

clear all

syms va

va = solve(va/20 + va/6 + (va-20)/5 ==0, va)

i = va/6

which yields $i(\infty) = 8/5 = 1.6A$. We then have (with $R = 6 + 20 \parallel 5 = 10$ so that $\tau = 0.05$):

$$i(t) = 1.6 + (2 - 1.6)e^{-20t}, \quad 0 \leq t$$

so that

$$v(t) = 0.5 \frac{di(t)}{dt} = -4e^{-20t}, \quad 0 \leq t$$

Problem 7.62:

7.62 For the circuit in Fig. 7.127, calculate $i(t)$ if $i(0) = 0$.

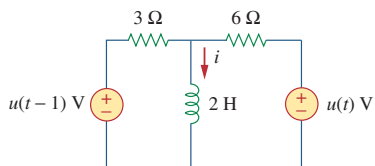


Figure 7.127

For Prob. 7.62.

Here is another sequential transient, where the final condition of the one epoch is the initial condition of the next epoch. Each of these is simple, just a matter of keeping track of time. So... for each time epoch, consider that circuit from it's initial time to $t = \infty$.

For $0 \leq t \leq 1$: We have $i(0) = 0$, $i(\infty) = 1/6$, $\tau = \frac{L}{R} = \frac{2}{6||3} = 1$, so that:

$$i(t) = 1/6 - 1/6e^{-t}, \quad 0 \leq t \leq 1$$

For $1 \leq t$: We have $i(1) = 1/6 - 1/6e^{-1} = 0.1054$, $i(\infty) = 1/6 + 1/3 = 1/2$, $\tau = \frac{L}{R} = \frac{2}{6||3} = 1$, so that:

$$i(t) = 0.1054e^{-(t-1)}, \quad 1 \leq t$$

... and we MUST have that $i(1)$ from the first part matches $i(1)$ from the second part. Check! Hence:

$$i(t) = \begin{cases} 1/6 - 1/6e^{-t}, & 0 \leq t \leq 1 \\ 0.1054e^{-(t-1)}, & 1 \leq t \end{cases}$$