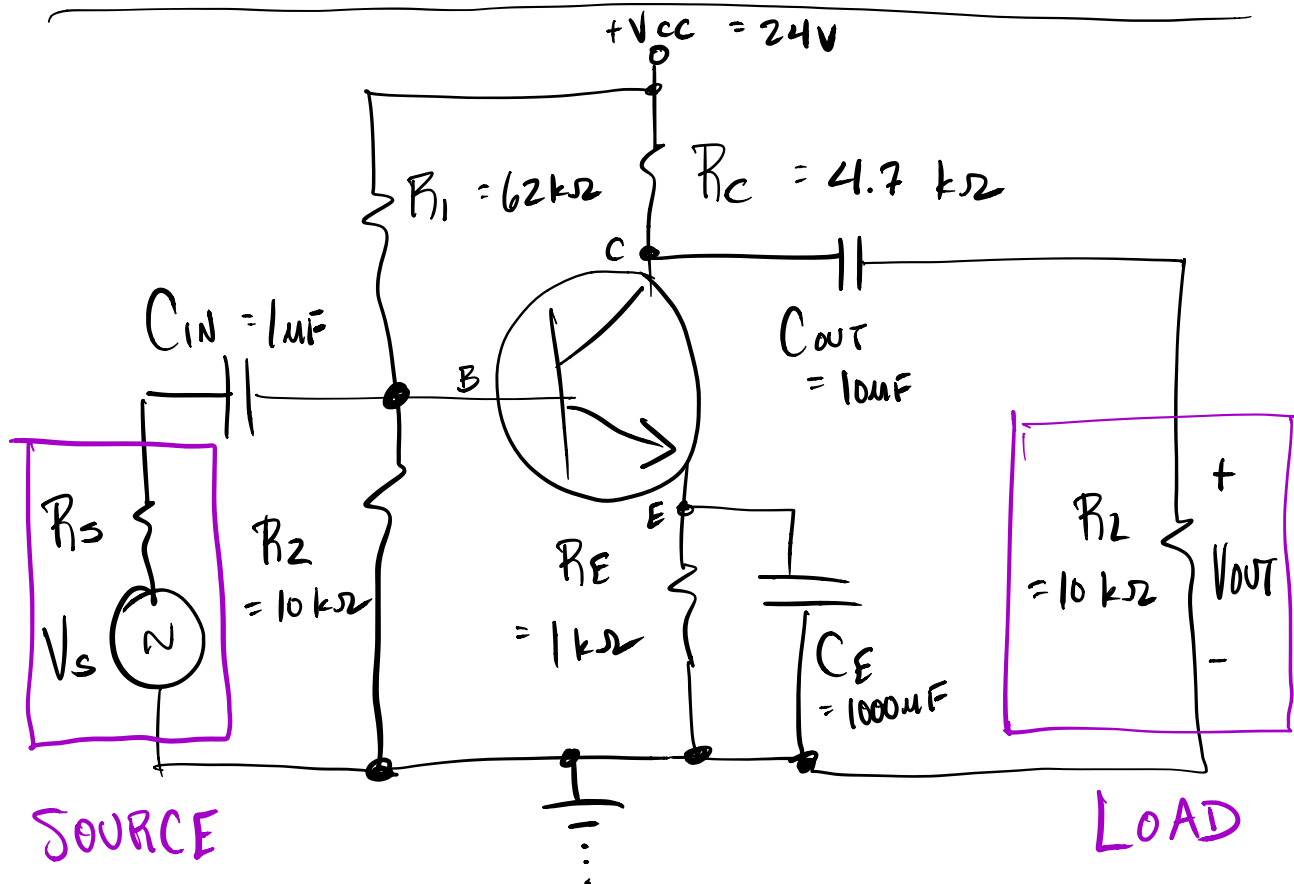


# Common - Emitter Voltage Amplifier




Common emitter : because the large capacitor  $C_E$  has a sufficiently low impedance at most frequencies that the emitter is effectively grounded for AC signals.

- .. input signal (source) is connected to the base (via.  $C_{in}$ ,  $R_1$ , &  $R_2$ )
- .. Output signal (load) emanates from the collector (via.  $R_c$  and  $C_{out}$ )
- .. analyze this circuit in stages.

DC Circuit       $Z_c = \frac{1}{j\omega c}$

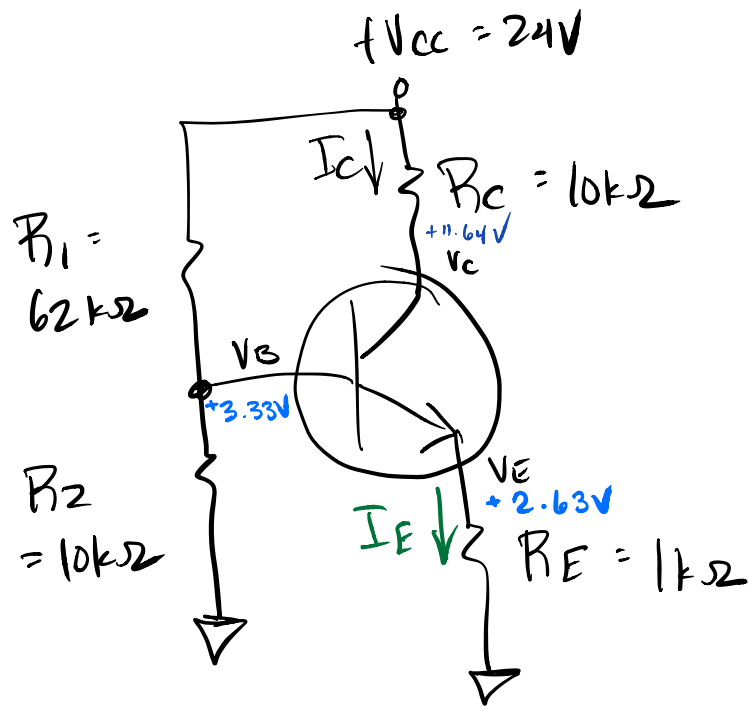- .. at D.C., all three capacitors have infinite  $Z$  and therefore disappear
- .. redraw!



.. assume  $\beta$  is "sufficiently high" that  $I_B \rightarrow 0$

$$\therefore V_B = V_{CC} \left[ \frac{R_2}{R_1 + R_2} \right]$$

$$= 24 \left[ \frac{10}{10 + 62} \right]$$

$$V_B = 3.33 \checkmark$$

.. for NPN Si transistor, ON and operating in active region:  $V_{BE} = 0.7 \text{ V}$

$$\therefore V_{BE} = V_B - V_E$$

$$\begin{aligned}\longrightarrow V_E &= V_B - 0.7 \\ &= 3.33 - 0.7 \\ V_E &= 2.63 \text{ V}\end{aligned}$$

$$\therefore \text{then } I_E = \frac{V_E}{R_E} = \frac{2.63}{1\text{k}} = \underline{2.63 \text{ mA}}$$

"high  $\beta$ " means  $I_C = I_E = \underline{2.63 \text{ mA}}$

$$\begin{aligned}V_C &= V_{CC} - I_C R_C \\ &= 24 - 2.63 \cancel{\text{mA}} \cdot 4.7 \cancel{\text{k}}\end{aligned}$$

$$\underline{V_C = 11.64 \text{ V}}$$

.. finally, we need  $V_{CE}$ ;

$$\begin{aligned} V_{CE} &= V_C - V_E \\ &= 11.64 - 2.63 \approx \underline{\underline{9V}} \end{aligned}$$


$$\begin{array}{l} I_C = 2.63 \text{ mA} \\ V_{CE} = 9V \end{array} \left. \vphantom{\begin{array}{l} I_C = 2.63 \text{ mA} \\ V_{CE} = 9V \end{array}} \right\} \begin{array}{l} \text{quiescent or operating point} \\ \downarrow \\ \text{"idle", meaning not 'wiggling' (yet)} \end{array}$$

.. to ensure "wiggle room" when applying the AC signal we wish to amplify,  $V_{CE}$  shouldn't be too close to either  $V_{CC}$  nor ground

.. also good to ensure  $R_{Ee} < \frac{1}{2} R_L$

.. Check "high- $\beta$ " assumption!

- current in input voltage divider :

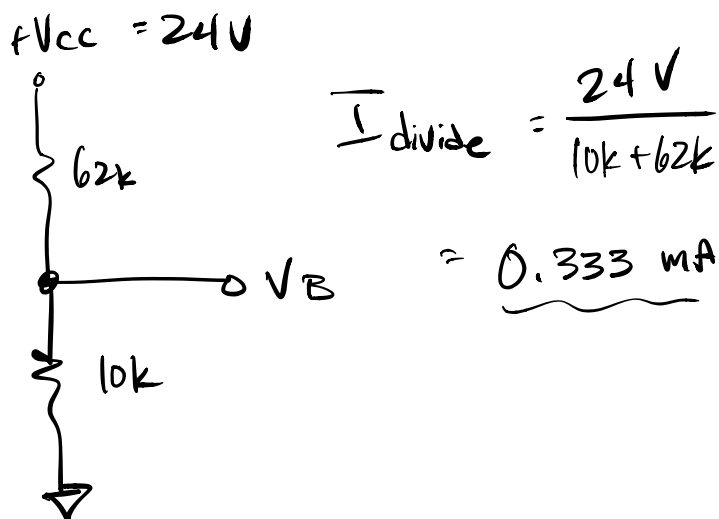

.. say  $\beta = 200$  ;

$$\text{then } I_B = \frac{I_C}{\beta} \approx \frac{2.63}{200} = 0.01315 \text{ mA}$$


$$I_{\text{divide}} > 25 I_B$$

∴ yes, we can ignore base current!

.. We're done w/ D.C. analysis, nothing new here!
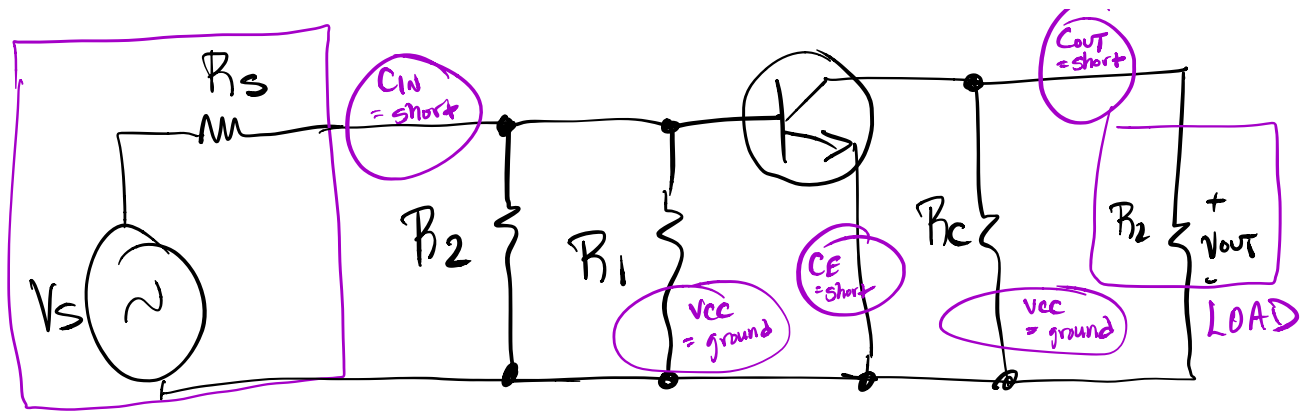
# Mid-Frequency AC Circuit

- .. the purpose of  $C_E$  is to "ground" the emitter at "most" frequencies
- .. the purpose of  $C_{IN}$  is to protect  $V_S$  from the  $3.3V$  needed at the base of the transistor to get it into the active region!
  - .. often called "bias" voltage
  - .. ... but still get "useful" frequencies through
- .. the purpose of  $C_{OUT}$  is to protect the load from the  $11.64V$  collector voltage, but get the "useful" frequencies into it
- .. a "perfect" power supply looks like "ground" for all AC signals !!! All DC, no wiggling allowed.!!!
- .. at "middle" frequencies, the circuit looks like this :



SOURCE

.. the next thing we want to know :  
the mid-frequency AC gain of the circuit