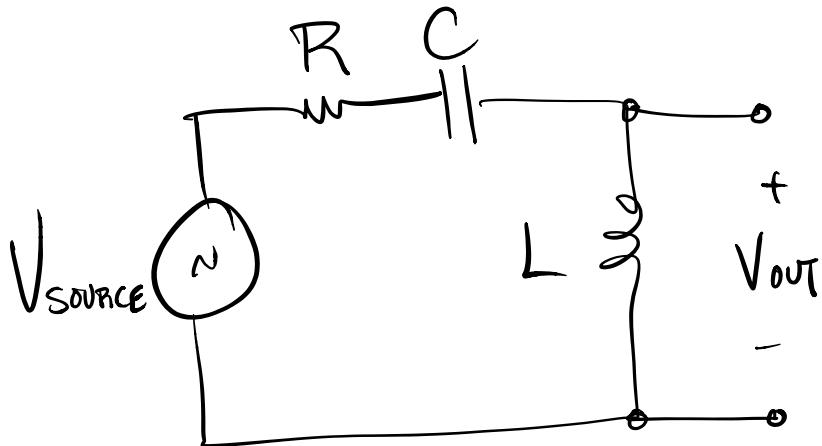


Series - RLC High-Pass Filter



$$H(\omega) = \frac{j\omega L}{j\omega L + R + \frac{1}{j\omega C}}$$



* top and bottom by $j\omega/L$

$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + j\omega R/L + 1/LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad Q_{\text{series}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$H(\omega) = \frac{(j\omega)^2}{(j\omega)^2 + j\omega \frac{\omega_0}{Q} + \omega_0^2}$$

as $\omega \rightarrow \infty$,

$$\begin{aligned} H(\omega) &\rightarrow \frac{(j \text{BIG})^2}{\omega_0^2 + j\omega \frac{\text{BIG}}{Q} + (j \text{BIG})^2} \\ &\approx \frac{(j \text{BIG})^2}{(j \text{BIG})^2} \rightarrow 1 \end{aligned}$$

.. high frequencies are indeed passed!

as $\omega \rightarrow 0$,

$$H(\omega) \rightarrow \frac{(j \text{SMALL})^2}{\omega_0^2 + j \text{SMALL} \frac{\omega_0}{Q} + (j \text{SMALL})^2}$$

$$\rightarrow \frac{(j \text{SMALL})^2}{\omega_0^2} \rightarrow \frac{1}{j^2 \text{SMALL}^2}$$


$$\rightarrow 0 \quad +180^\circ$$

.. low frequencies stopped,
phase $\rightarrow 180^\circ$


④ ω_0 ← Natural frequency


$$H(\omega) = \frac{(j\omega)^2}{\cancel{\omega_0^2 + j\omega_0 \frac{\omega_0}{Q} + (j\omega)^2}}$$
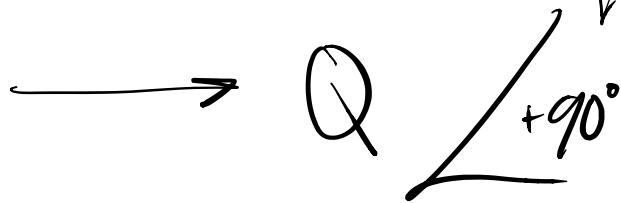
$$= \frac{j^2 \omega_0^2}{j \cancel{\omega_0^2/Q}} = jQ$$



again, Magnitude at ω_0 is Q !

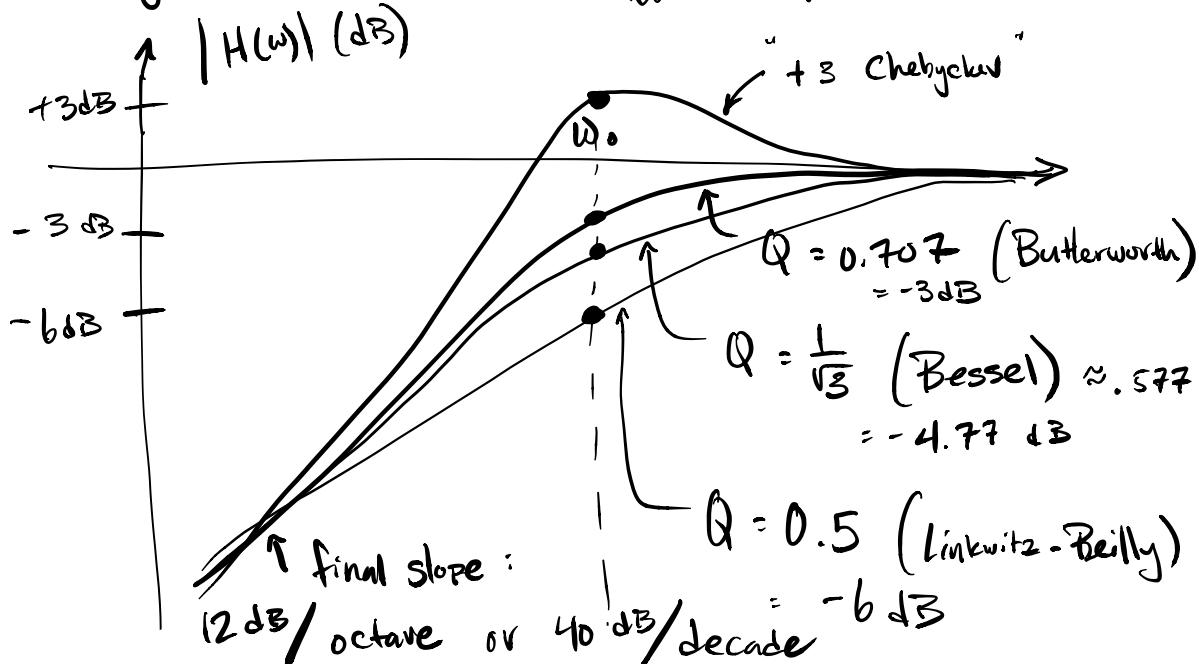

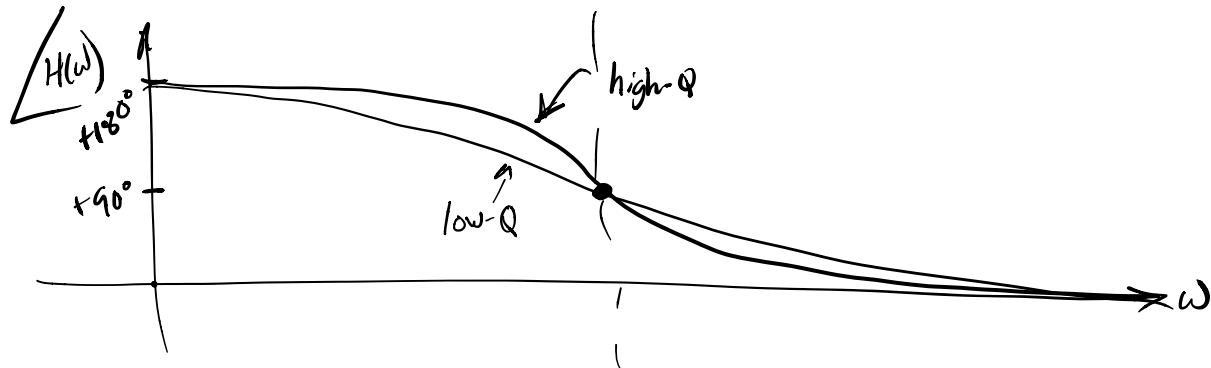

homework : BLC high-pass


$$L = 2.2 \text{ mH}$$

$$R = 16\Omega$$

$$C = 3.3 \mu\text{F}$$

- sketch circuit, determine ω_0 , f_0 , and Q ,
describe freq. response (i.e., Butterworth etc..),
describe transient response (i.e., overdamped, etc..),
determine $H(\omega_0)$, $H(2\omega_0)$, and $H(0.5\omega_0)$
(Mag. in dB and Phase),
Sketch $|H(\omega)|$ and $\angle H(\omega)$.

Series RLC Bandpass Filter

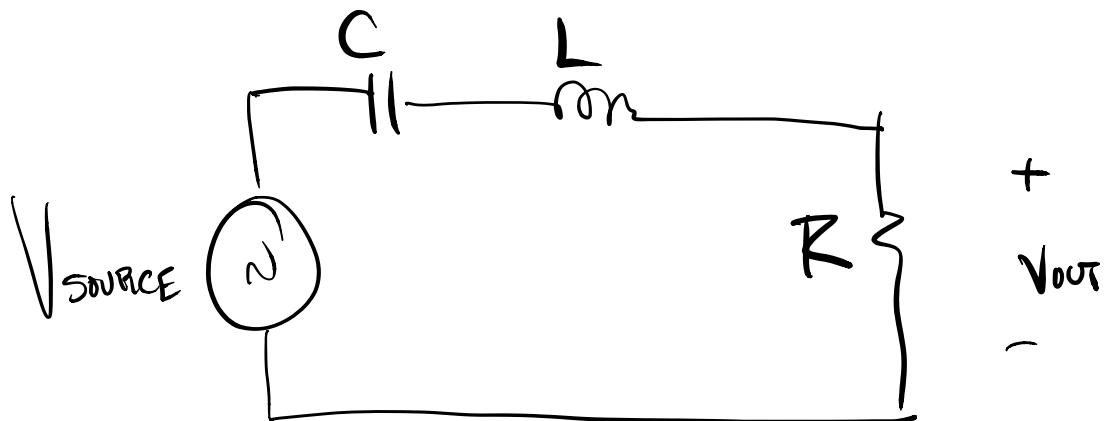

.. only passes frequencies in some range

$$H(\omega) = \frac{Z_R}{Z_R + Z_C + Z_L}$$

$$H(\omega) = \frac{R}{R + \frac{1}{j\omega C} + j\omega L}$$

$$H(\omega) = \frac{j\omega R}{(j\omega)^2 L + \frac{1}{C} + j\omega R}$$

$$H(\omega) = \frac{j\omega R/L}{(j\omega)^2 + \frac{1}{LC} + j\omega^2 R/L}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}, \quad Q_{\text{series}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

then $H(\omega) = \frac{j\omega \frac{\omega_0}{Q}}{(j\omega)^2 + j\omega \frac{\omega_0}{Q} + \omega_0^2}$



Same denominator !!!

- ω_0 is the center frequency of the filter

- Q has a special definition;


$$Q = \frac{f_0}{f_H - f_L}$$

- where $f_0 = \omega_0 / 2\pi$

- f_H : upper -3dB point

- f_L : lower -3dB point
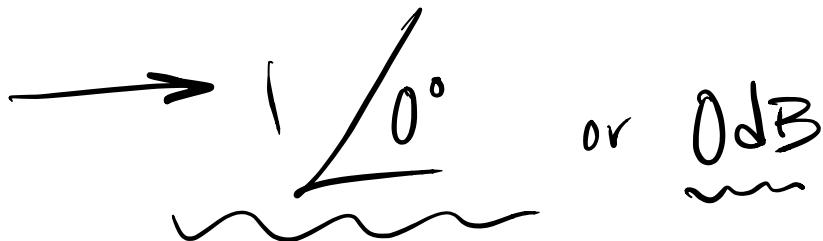
$$H(\omega) = \frac{j\omega_0 \frac{\omega_0}{Q}}{(j\omega_0 + j\omega_0 \frac{\omega_0}{Q} + \omega)^2} = \frac{j\omega_0^2/Q}{j\omega_0^2/Q}$$





• perfect, lossless bandpass filter; naturally, some R in L , etc..

high-Q filter \rightarrow small difference between
 - 3 dB points \rightarrow sharp
 (highly resonant @ ω_0)

low-Q filter \rightarrow large difference between

- 3 dB points \rightarrow broad

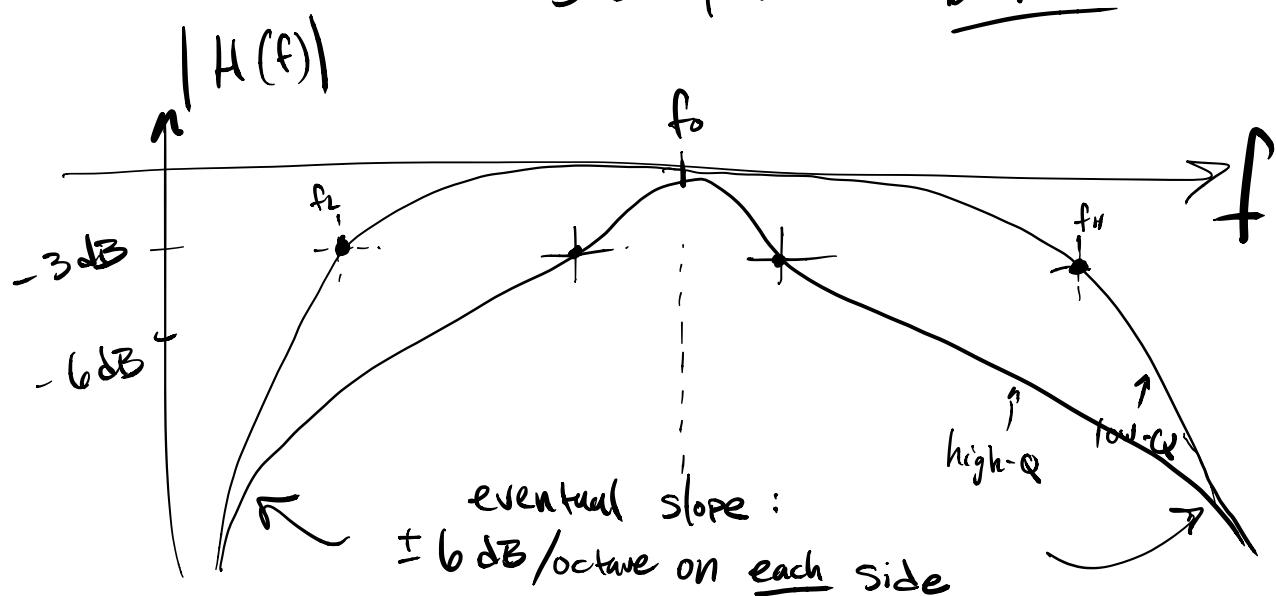

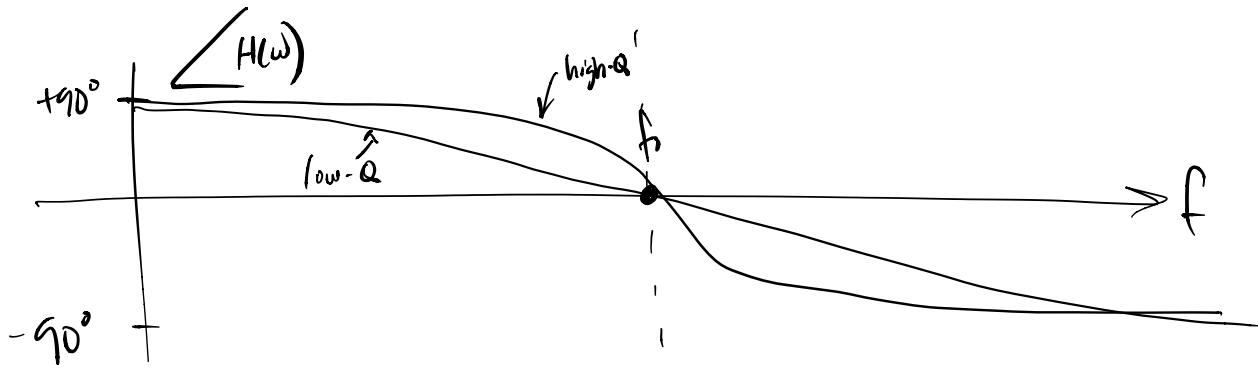


if f_H and f_L are known, then

$$f_0 = \sqrt{f_H f_L}$$

useful in design!

(geometric mean)

Series RLC Bandreject Filter

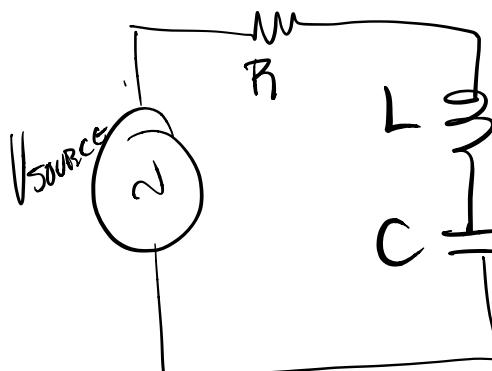

$$H(\omega) = \frac{Z_L + Z_C}{Z_L \cdot Z_C + R}$$

$$H(\omega) = \frac{\frac{1}{j\omega C} + j\omega L}{j\omega L + \frac{1}{j\omega C} + R}$$

$$= \frac{\frac{1}{C} + (j\omega)^2 L}{(j\omega)^2 L + \frac{1}{C} + j\omega R}$$

$$= \frac{\frac{1}{LC} + (j\omega)^2}{(j\omega)^2 + \frac{1}{LC} + j\omega \frac{R}{L}}$$

$$H(\omega) = \frac{\omega_0^2 + (j\omega)^2}{(j\omega)^2 + j\omega \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q_{\text{series}} = \frac{1}{P} \sqrt{\frac{L}{C}}$$

↓
again!

ω_0 : center frequency

Q : sharpness of rejection

high Q bandreject is also called a notch filter.


again: $Q = \frac{f_0}{f_H - f_L}$


$$f_0 = \sqrt{f_H f_L}$$

$$H(\omega) = \frac{\omega_0^2 + (j\omega)^2}{(j\omega)^2 + j\frac{\omega_0^2}{Q} + \omega_0^2}$$

$\rightarrow 0 \angle 0^\circ$


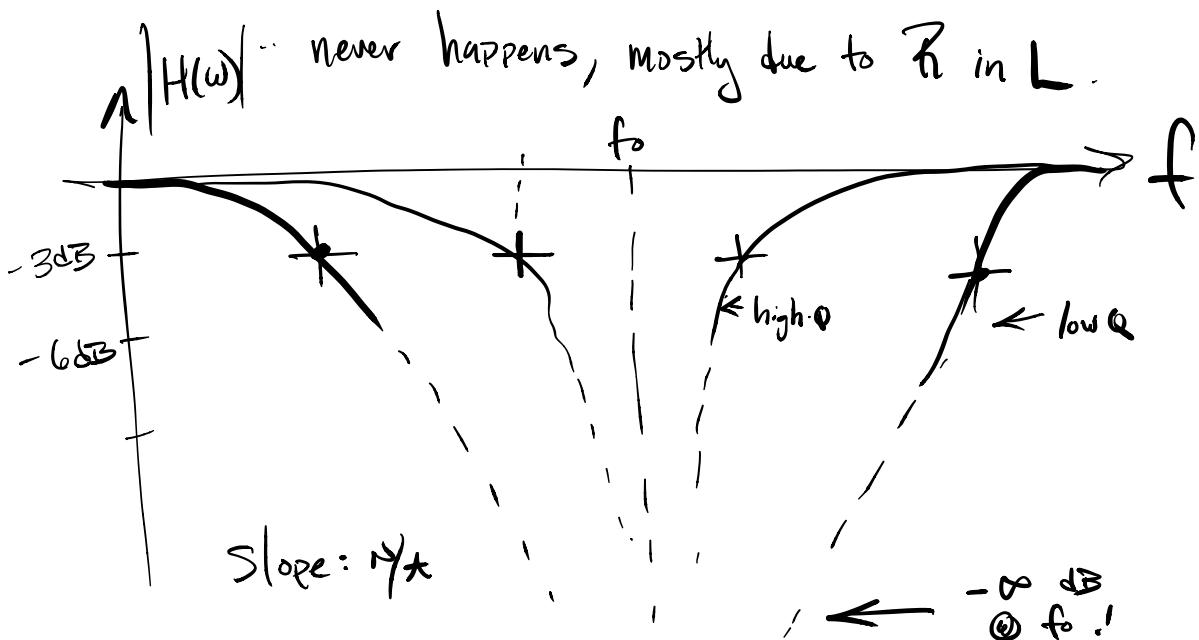
\therefore zero output $\oplus \omega_0$ for perfect bandreject filter!



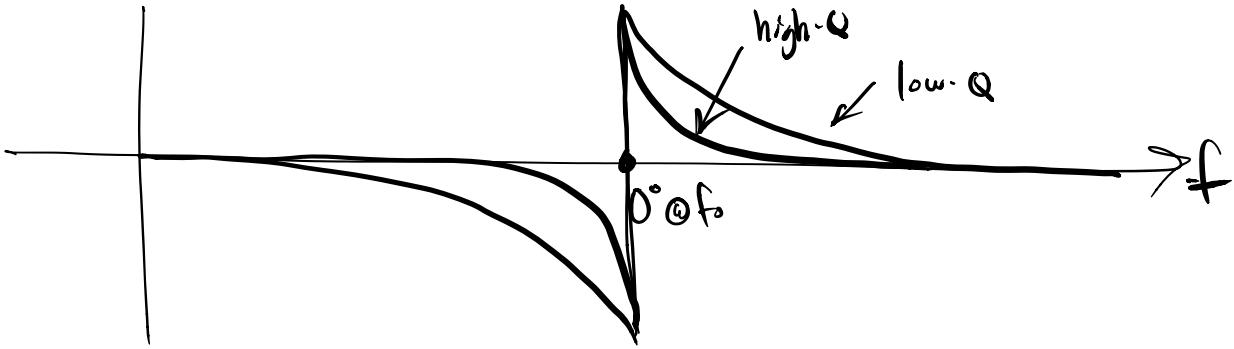


- What about Parallel RLC filters?

- just like

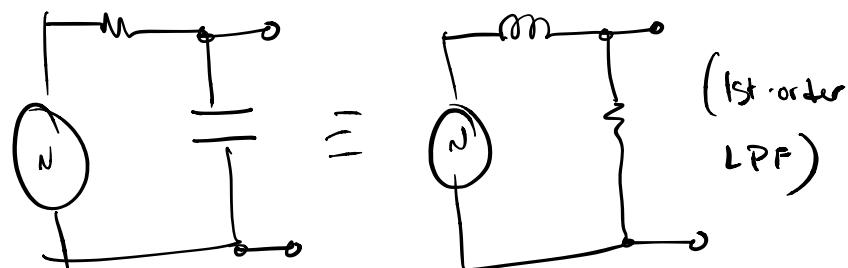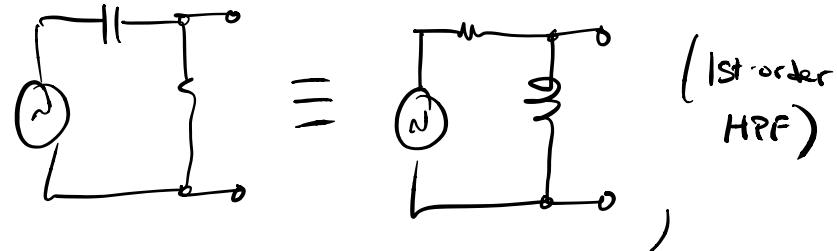

- ... we can build bandpass and bandreject filters w/ parallel LC combination,
same transfer function as series version!


bandpass :

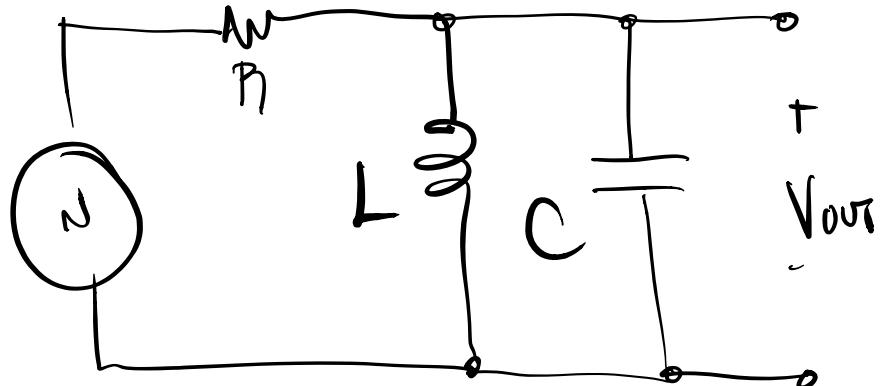

.. same ω_0 , but $Q_{\text{parallel}} = R \sqrt{\frac{C}{L}}$



bandreject :

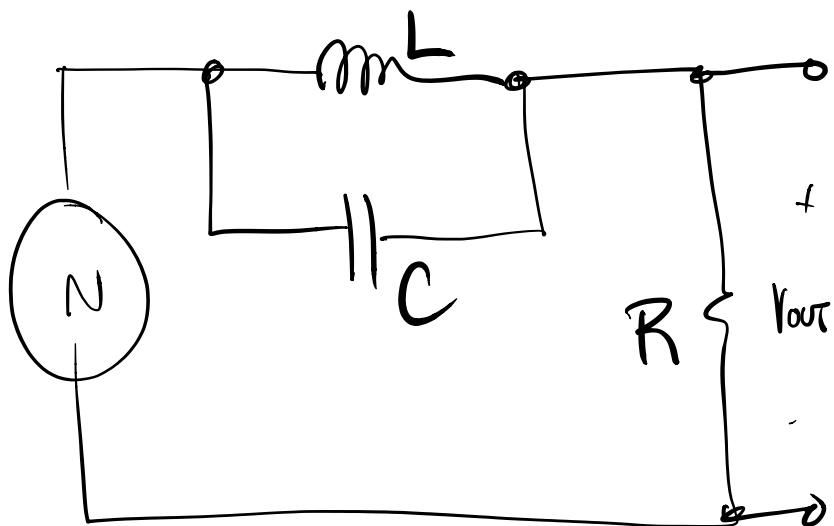

Homework: Sketch parallel RLC bandpass filter

$$L = 2.2 \text{ H}, C = 2.0 \text{ nF}, R = 47 \text{ k}\Omega$$

- .. determine ω_0 , f_r , Q , characterize frequency and transient response, sketch mag. and phase
 - .. determine f_H and f_L
- .. Simulate both homework problems in
LTSPICE !