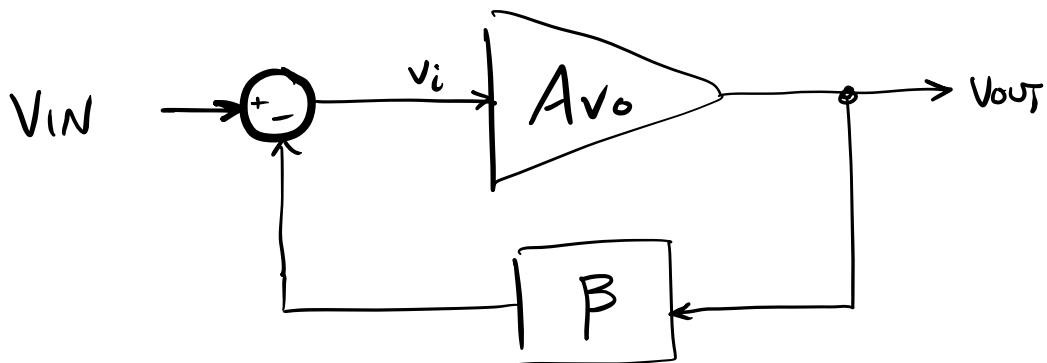


# Negative Feedback

- real-world amplifiers almost always use some type of negative feedback; you almost never see a basic transistor amplifier by itself, for any application!
- discovered by Harold Black at Bell Labs in August 1927, the essential mechanism of negative feedback is subtracting a portion of the output of an amplifier from its input, to correct errors in amplification, at the expense of gain.
  - unbelievably huge development!!!
  - reduces non-linear distortion, corrects frequency response, improves input and output impedances, reduces noise, and a host of related benefits

# System block diagram; Voltage amplifier example



$A_{vo}$ : open-loop gain of amplifier (i.e., with no feedback)

$\beta$ : feedback factor ( $a/k/a$  feedback fraction)

- $V_{OUT}$  with no feedback applied is

$$V_{OUT} = \underbrace{V_i \cdot A_{vo}}_{\substack{\text{input to amplifier} \\ \text{open-loop gain}}}$$

- $V_i$  comprises the system  $V_{IN}$ , minus a fraction of  $V_{OUT}$ ,

$$V_i = V_{IN} - V_{OUT} \cdot \beta$$

$$\therefore V_{OUT} = (V_{IN} - V_{OUT} \cdot \beta) A_{vo}$$

$$V_{OUT} = V_{IN} \cdot A_{vo} - V_{OUT} \cdot \beta \cdot A_{vo}$$

$$V_{OUT} (1 + \beta A_{vo}) = V_{IN} \cdot A_{vo}$$

- define closed-loop system gain; i.e., the final gain of the system with negative feedback

$$A_v = \frac{V_{out}}{V_{in}} ;$$

then

$$A_v = \frac{A_v}{1 + \beta A_v}$$

- magical negative feedback equation!
- impossible to overestimate the importance of this!
- there are four principal methods of applying a negative feedback loop to an amplifier:

- 1.) shunt-derived / series-applied
  - feedback network is connected in parallel w/ output and in series with input
  - this tends to lower output impedance of an amplifier (closer to ideal voltage source) and raise input impedance (ideally infinite like an ideal voltmeter)

## 2.) shunt-derived / shunt-applied

- feedback network in parallel w/ output  
and in parallel w/ input
- this tends to lower both input and output impedances; so voltage-source output and current input (remember, ideal ammeter is a short)

less common:

## 3.) series-derived / series-applied


- feedback network is in series with amplifier output, which samples output current rather than voltage, raising output impedance, and in series with the input, raising input impedance

## 4.) Series-derived / shunt-applied

- network samples current, raising output impedance, and shunts the input, lowering input impedance  
∴ current amplifier

- Well start with a mechanism that can be implemented on an amplifier with which we're already familiar:  
local feedback caused by an unbypassed emitter or source resistor in a common-emitter or common-source amplifier

## CE amplifier w/ bypassed $R_E$ :

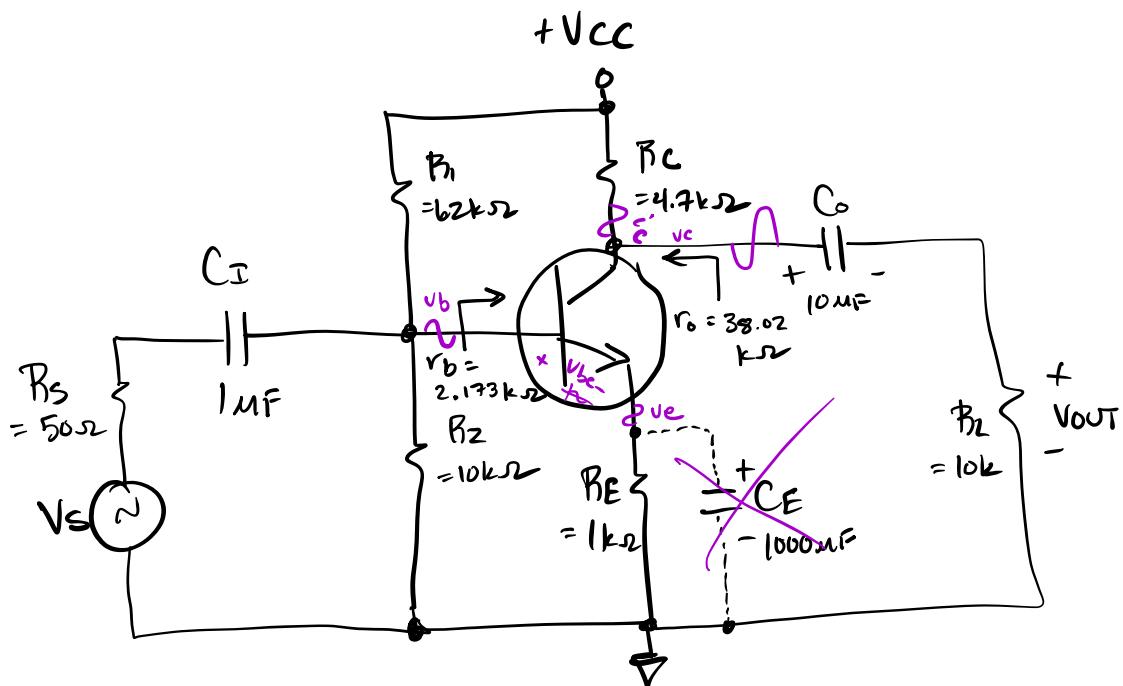

- We already performed small-signal analysis on this amplifier with  $C_E$  in place:

$$A_v = -263.3 \quad \text{or } 48.4 \text{ dB, inverting}$$

- now let's investigate how removing  $C_E$  creates a Series-derived / series-applied negative feedback loop
  - AC collector current  $[g_m V_{be}]$ , which also flows through  $R_E$ , is now allowed to drop a small-signal voltage  $v_e$
  - Since the transistor amplifies the small-signal base-to-emitter voltage  $V_{be}$ , this  $v_e$  subtracts from the input signal  $v_b$ , self-creating negative feedback!
    - hence, local feedback
  - Since it's output current that is sampled (AC collector current =  $\frac{V_{out}}{R_c \parallel r_o \parallel R_L}$ ), it is series-derived ↑ small-signal model!
  - Since this same current develops an AC emitter voltage that subtracts from the input voltage, it is series-applied.

$$v_e = \text{AC collector current} \cdot R_E$$

$$\therefore v_e = \frac{V_{out}}{R_c \parallel r_o \parallel R_L} \cdot R_E$$

- therefore, for this feedback mechanism, the feedback factor  $\beta$  is:

$$\boxed{\beta = \frac{R_E}{R_C \parallel r_{out} \parallel R_L}}$$

- we can show that for a field-effect transistor common-source amplifier,

$$\boxed{\beta = \frac{R_S}{R_D \parallel r_{out} \parallel R_L}}$$

- let's plug some numbers into the feedback equation

$$R_C \parallel r_{out} \parallel R_L = 4.7k \parallel 38.02k \parallel 10k = \underline{2.949k \Omega}$$

$$\beta = \frac{R_E}{R_C \parallel r_{out} \parallel R_L} = \frac{1k}{2.949k}$$

$$\underbrace{\beta = 0.3391}_{\text{open-loop gain}}$$

$$A_V = \frac{A_{VO}}{1 + \beta A_{VO}} = \frac{263.3}{1 + 0.3391 \cdot 263.3}$$

$$\underline{A_V = 2.916 \text{ or } 9.3 \text{ dB}} \quad [\text{still inverting of course}]$$

-- So the gain has been reduced by  $1 + \beta A_{vo}$   
or  $1 + 0.3391 \cdot 263.3$   
 $= 90.29$  or  $39.1 \text{ dB}$

check:  $\frac{\text{open-loop gain}}{\text{negative feedback}} = \frac{48.4 \text{ dB}}{39.1 \text{ dB}} = \underline{9.3 \text{ dB}}$   
closed-loop gain

-- note that if  $\beta A_{vo}$  is sufficiently high,  
 $1 + \beta A_{vo} \approx \beta A_{vo}$  (true here!)

-- then  $A_v \approx \frac{A_{vo}}{\beta A_{vo}}$

$$A_v \approx \frac{1}{\beta}$$

-- remember,  $\beta = \frac{R_E}{R_C \parallel r_o \parallel R_L}$

$$\therefore A_v \approx \frac{R_C \parallel r_o \parallel R_L}{R_E}$$

-- and if we can also assume  $r_o \gg R_C \parallel R_L$ ,

$$A_v \approx \frac{R_C \parallel R_L}{R_E}$$

-- unreliable transistor characteristics have been removed from the equation!

· gain set by resistors!

check:  $\frac{4.7\text{k} \parallel 10\text{k}}{1\text{k}} = \underline{\underline{3.197}}$

or 10.1 dB;

off by 0.8 dB

(probably not a problem!)

· because this feedback loop is series-derived  
series applied, we expect a 39.1 dB improvement in the following areas:

1.) increase in internal output impedance;

thus,  $r_o' = r_o (1 + \beta A_{vo})$

=  $38.02\text{k} \cdot 90.29$

= 3433 k $\Omega$  ← truly can be neglected compared to  $R_C$  and  $R_L$ !

· note:  $R_C$  is outside the negative feedback loop,  
so its effect on  $R_{out}$  is unchanged

thus,  $R_{out}' = R_C \parallel r_o'$   $\rightarrow$  huge!

$R_{out}' \approx R_C = 4.7\text{k}\Omega$

[slightly higher than  $R_{out} = 4.7k \parallel 38.02k = 4.183k$ ]

-- again, removes unreliable transistor  $r_o$  from  $R_{out}$

2.) increases internal input impedance;

$$\text{thus, } r_b' = r_b (1 + \beta A_{vo})$$

$$r_b' = 2.173k \cdot 90.29 = \underline{\underline{196.2k\Omega}}$$

-- since  $R_{in}$  is dominated by  $r_b$   $[R_{in} = R_b \parallel R_1 \parallel R_2]$ , this constitutes a significant improvement!

$$R_{in}' = r_b' \parallel \boxed{R_1 \parallel R_2}$$

$\uparrow$  outside feedback loop;  
thus unchanged!

-- Now  $r_b' \gg R_1 \parallel R_2$ ; thus,

$$\underbrace{R_{in}' \approx R_1 \parallel R_2}_{= \frac{1}{62k} \parallel \frac{1}{10k}} = \frac{1}{62k} \parallel \frac{1}{10k} = \underline{\underline{8.611k\Omega}}$$

-- Compared to  $R_{in} = 2.173k \parallel 62k \parallel 10k = 1.735k$ , this is way better; and removes unreliable BJT parameter  $r_b$ !

3.) increase in  $f_H$  caused by internal mechanisms

- we found a dominant input pole of

$$f_{H(in)} \approx 2.97 \text{ MHz} \quad \text{open-loop}$$

- thus, we expect a 90.29-fold increase to:

$$\begin{aligned} f_{H(out)} &= f_{H(in)}(1 + \beta A_{vo}) = 2.97 \cdot 90.29 \\ &= 268.2 \text{ MHz} \end{aligned}$$

- in reality, this now makes the output pole of 13.5 MHz dominant, which will be unchanged because it mostly involves  $R_C \parallel R_L$

4.) decrease in  $f_L$  caused by internal mechanisms

- for starters, we simply remove  $f_{LCE}$   $\hookrightarrow$  gone!
- $f_{L(in)}$  will decrease due to increased  $r_b'$ , but since external  $R_1 \parallel R_2$  are still in place, it won't be by the full  $1 + \beta A_{vo}$ !

$$f_L(\text{IN})' = \frac{1}{2\pi C_{IN} (R_1 \parallel R_2)}$$

$$= \frac{1}{2\pi \cdot 1 \times 10^{-6} (8.6 \parallel k)} = \underline{\underline{18.48 \text{ Hz}}}$$

- a lot better than  $f_L(\text{IN}) = 89.2 \text{ Hz}$  before!
- $f_L(\text{out}) = 1.12 \text{ Hz}$  won't change much because  $r_o$  wasn't a significant factor; thus,  $f_L(\text{IN})$  still dominates and  $f_L \approx 18.48 \text{ Hz}$ .

5.) 39.1 dB decrease in distortion of small signals!

- much more linear amplification, up until we get close to clipping
- Negative feedback is amazing and there are many more ways to implement it!