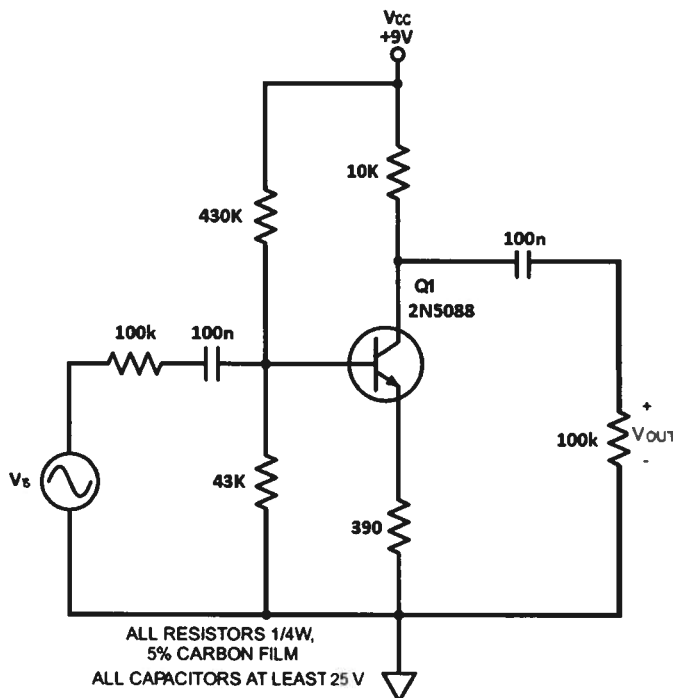


The Electro-Harmonix LPB-1 is an electronic device used to increase the signal level of an electric guitar before feeding an amplifier. It was introduced in 1968 and is still manufactured today in NYC. Thus, it is older than your mom, but most *unlike* your mom it is still valid.



First, perform DC analysis. Determine  $V_B$ ,  $V_E$ ,  $I_C$ ,  $V_C$ , and  $V_{CE}$  if 2N5088 is silicon and base current may be assumed negligible due to high  $\beta$ . Check  $P_{diss}$  and verify that the transistor is operating in the active region.

$$V_B = 9 \left( \frac{43}{43 + 430} \right) = 0.8182 \text{ V} \quad (+1)$$

$$V_E = V_B - 0.7 \text{ V} = 0.1182 \text{ V} \quad (+1)$$

$$I_E = \frac{V_E}{R_E} = \frac{0.1182}{390} = 0.000303 \text{ or } 0.303 \text{ mA} \quad (+1)$$

$$I_C \approx I_E = 0.303 \text{ mA} \quad (+1)$$

$$V_C = V_{CC} - I_C R_C = 9 - 0.303 \cdot 10 = 5.97 \text{ V} \quad (+1)$$

$$V_{CE} = V_C - V_E = 5.97 - 0.1182 = 5.851 \text{ V} \quad (+1)$$

yes, active

$$P_{diss} = V_{CE} \cdot I_C = 5.851 \cdot 0.303 = 1.773 \text{ mW} \quad (+1)$$

Calculate the parameters  $g_m$  and  $r_b'$  if  $\beta = 350$ . Also compute  $R_{IN}'$  and  $R_{OUT}'$ . Note that the emitter is unbypassed. Include a unit with each answer. You may neglect  $r_o$ .

$$g_m = 35 I_C = 35 \cdot .303$$

$$g_m = 10.605 \text{ mA/V} \quad (+2)$$

$$r_b' = \beta R_E = 350 \cdot 390 = 136500$$

$$\text{or } 136.5 \text{ k}\Omega \quad (+2)$$

$$R_{IN}' = R_1 \parallel R_2 \parallel r_b' = 430\text{k} \parallel 43\text{k} \parallel 136.5\text{k} = 30.39 \text{ k}\Omega \quad (+2)$$

$$R_{OUT}' = R_C = 10\text{k} \quad (+1)$$

Compute the input and output transfers  $A_{V1}$  and  $A_{V2}$  and use them to determine the overall mid-frequency gain  $A_V$  (dB).

$$A_{V1} = \frac{R_{IN}'}{R_S + R_{IN}'} = \frac{30.39}{30.39 + 100} = 0.2331 \quad (+2)$$

$$= 9.091\% \quad (+1)$$

$$A_{V2} = \frac{-R_C \parallel R_L}{R_E} = \frac{-10\text{k} \parallel 100\text{k}}{390} = -23.31 \quad (+2)$$

$$\therefore A_V = A_{V1} \cdot A_{V2} = 0.2331 \cdot -23.31$$

$$A_V = -5.434 \quad (+1)$$

$$\text{or } 14.7 \text{ dB inverting} \quad (+2)$$

Determine the high-frequency input capacitance using Miller's Theorem if  $C_{BC} = 4.0 \text{ pF}$  and  $C_{BE} = 10 \text{ pF}$ . Use it to compute the input HF cutoff frequency. You do not have to compute the output capacitance or cutoff frequency.

$$C_{BC(1N)'} = C_{BC} (1 - A_{V2})$$

$$= 4 (1 - -23.31) = 97.24 \text{ pF} \quad (+2)$$

$$\therefore f_H = \frac{1}{2\pi \cdot C_{BC(1N)'} \cdot (R_S \parallel R_{IN}')} = \frac{1}{2\pi \cdot 97.24 \text{ pF} \cdot (100\text{k} \parallel 30.39\text{k})}$$

$$= 23.3 \text{ k} \quad (+1)$$

$$f_H = 70.25 \text{ kHz} \quad (+2)$$

Compute the LF cutoff frequencies due to the input and output capacitors.

$$f_{C_{IN}'} = \frac{1}{2\pi C_{IN} (R_S + R_{IN}')} = \frac{1}{2\pi \cdot 100\text{n} (100\text{k} + 30.39\text{k})}$$

$$f_{C_{IN}'} = 12.2 \text{ Hz} \quad (+2)$$

$$f_{C_{OUT}'} = \frac{1}{2\pi C_{OUT} (R_C + R_L)} = \frac{1}{2\pi \cdot 100\text{n} (10\text{k} + 100\text{k})}$$

$$f_{C_{OUT}'} = 14.47 \text{ Hz} \quad (+2)$$

Finally, determine the approximate overall cutoff frequency  $f_L$  and sketch the overall magnitude response of the Electro Harmonix LPB-1.

$$f_L \approx \sqrt{12.2^2 + 14.47^2}$$

$$= 18.93 \text{ Hz}$$

(+1)

