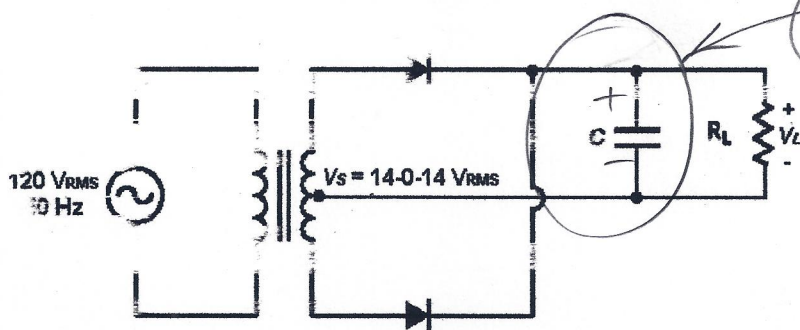


What type of rectifier is seen here? Is it half-wave or full-wave?



Center-tap

full-wave

If  $C = 470 \mu\text{F}$  and  $R_L = 240 \Omega$ , determine the ripple voltage in  $V_{P-P}$  and the approximate final  $V_L$ , assuming silicon diodes with the constant-drop model.

$$V_{\text{peak (center-tap)}} = V_s \sqrt{2} - V_D = 14\sqrt{2} - 0.7 = 19.10 \text{ V}$$

-- assume  $V_{\text{ripple}} \ll V_{\text{peak}}$ ; then  $I_L \approx \frac{19.10 \text{ V}}{240 \Omega} = 0.07958$

or  $79.58 \text{ mA}$

$$V_{\text{ripple}} \approx \frac{I_L}{2fC} = \frac{0.07958}{2 \cdot 60 \cdot 470 \times 10^{-6}} = 1.411 \text{ V}_{P-P}$$

$$V_L = V_{\text{peak}} - \frac{1}{2} V_{\text{ripple}} = 19.10 - \frac{1}{2} \cdot 1.411 = 18.39 \text{ V}$$

[plugging this back into  $I_L$ ,  $V_{\text{ripple}}$ , and  $V_L$  eqns. only changes final answer 0.16%]

Determine the required voltage rating of the capacitor and indicate the correct polarity on the schematic. Also choose a suitable 1N400X-series diode.

cap voltage must exceed 19.10V; 25V is standard

Center tap:  $PIV > 2\sqrt{2} V_s (\text{RMS})$

$$PIV > 2\sqrt{2} \cdot 14$$

$$PIV > 39.6 \text{ V}$$

1N4001 @ 50V  
will be fine

2) The headlamp switch in your car simultaneously turns on your headlamps and dashboard light. Design a relay circuit that accomplishes this task, given the following specs:


Headlamps:  
12 VDC, 55 W ea.  
(two lamps)

Dashboard Light:  
12 VDC, 640 mA

Relay:  
12 VDC, supplied from same system as lamps  
72-Ω coil w/ flyback diode  
SPDT, N/O and N/C contacts

Draw the complete circuit. Determine the current in the switch wiring and the current in the relay contacts. What relay contact voltage and current ratings do we need?

dashboard ! headlamps in parallel

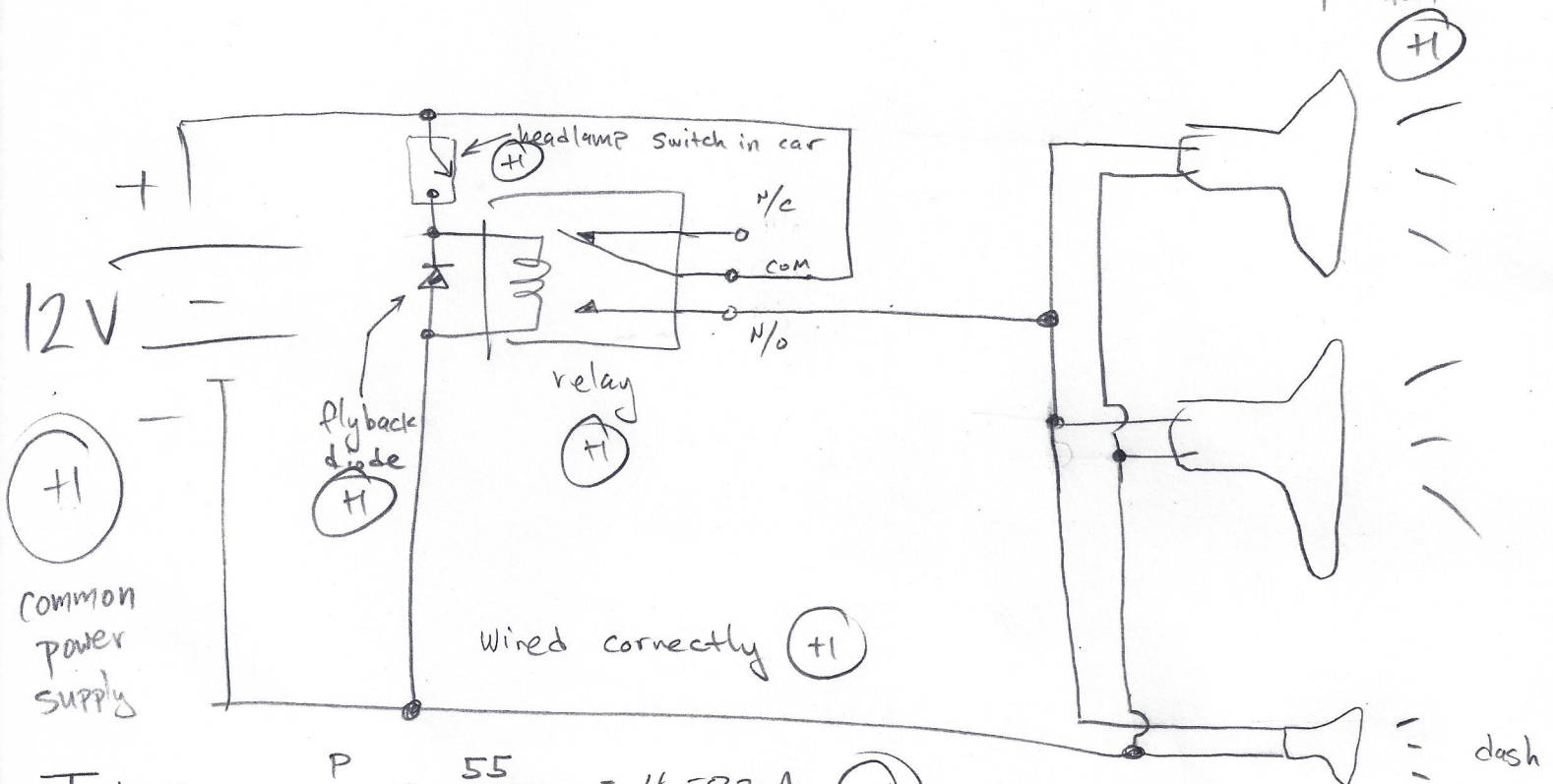

$$I_{\text{headlamp}} = \frac{P}{V} = \frac{55}{12} = 4.583 \text{ A} \quad (+1)$$

$$I_{\text{relay contacts}} = 4.583 \times 2 + 0.640 = 9.8 \text{ A} \quad (+2)$$

$$I_{\text{relay coil}} = \frac{V}{R} = \frac{12}{72} = 0.1667 \text{ A} \quad (+1)$$

Use at least 12V, 10A relay (+2)

Does the dashboard light really need to be switched with a relay, or could we possibly get away with switching it directly with the headlamp switch? Explain your answer.

Since  $I_{\text{dash}} \ll I_{\text{headlamp}}$ , and it's in the hundreds of mA range like relay coil, we could probably switch directly if close by.

(+2)

3) A hysteresis-synchronous motor used in a precision tape transport has 12 poles. Compute the resulting RPM of this motor when connected to the designed line frequency of 50 Hz at the correct voltage.

two-pole motor : one revolution per Hz

$$\therefore 50 \text{ rev/s} \cdot \frac{60 \text{ s}}{\text{min}} = 3000 \text{ RPM}$$

12-pole motor is then  $\frac{12}{2} = 6$  times slower

$$\therefore \frac{3000}{6} = 500 \text{ RPM}$$

(+3)

If the motor is a European model designed to run on 50 Hz and the owner unwittingly uses it in the USA at 60 Hz, compute the speed error in percent.

$$\frac{60}{50} = 1.2$$

20% faster

(+1)