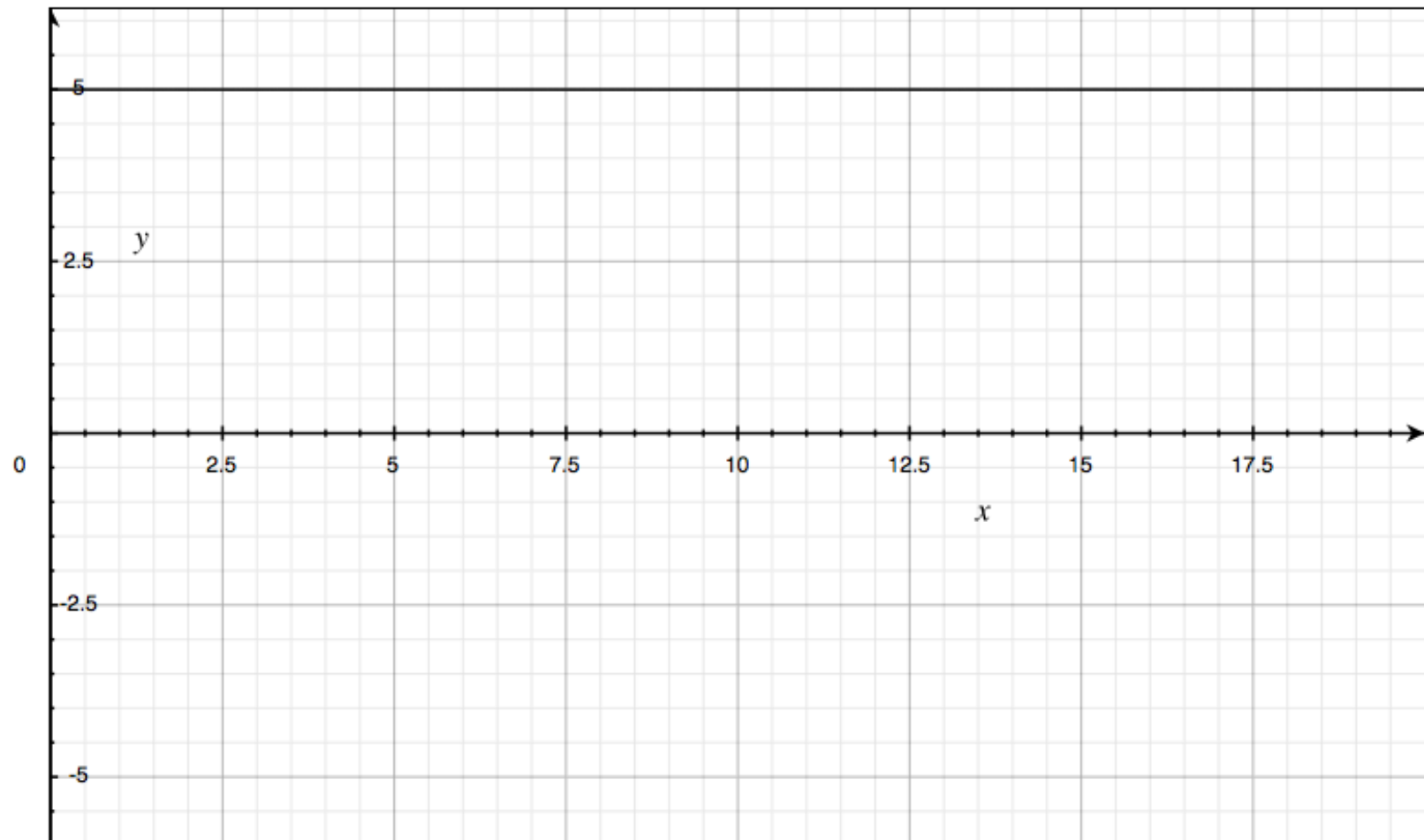


# DC - Direct Current

---





# DC - Direct Current

---

- ❖ What is the current through a  $72\ \Omega$  resistor if connected to a  $3.6\ \text{V}$  battery?

$$V = IR$$


$$I = \frac{V}{R} = \frac{3.6\ \text{V}}{72\ \Omega}$$

$$I = 0.05\ \text{A (or)}\ 50\ \text{mA}$$




# AC - Alternating Current

---

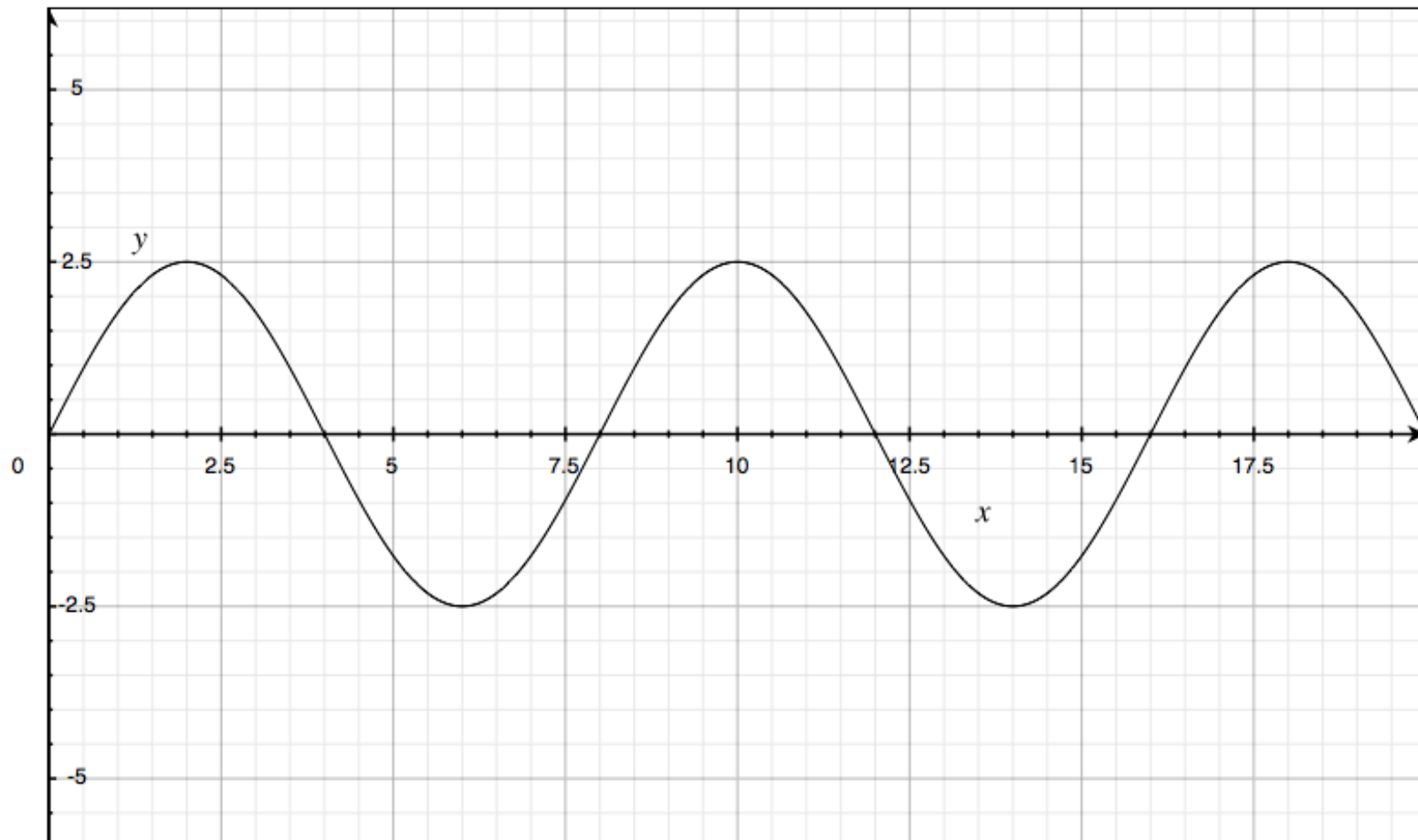


# AC - Alternating Current

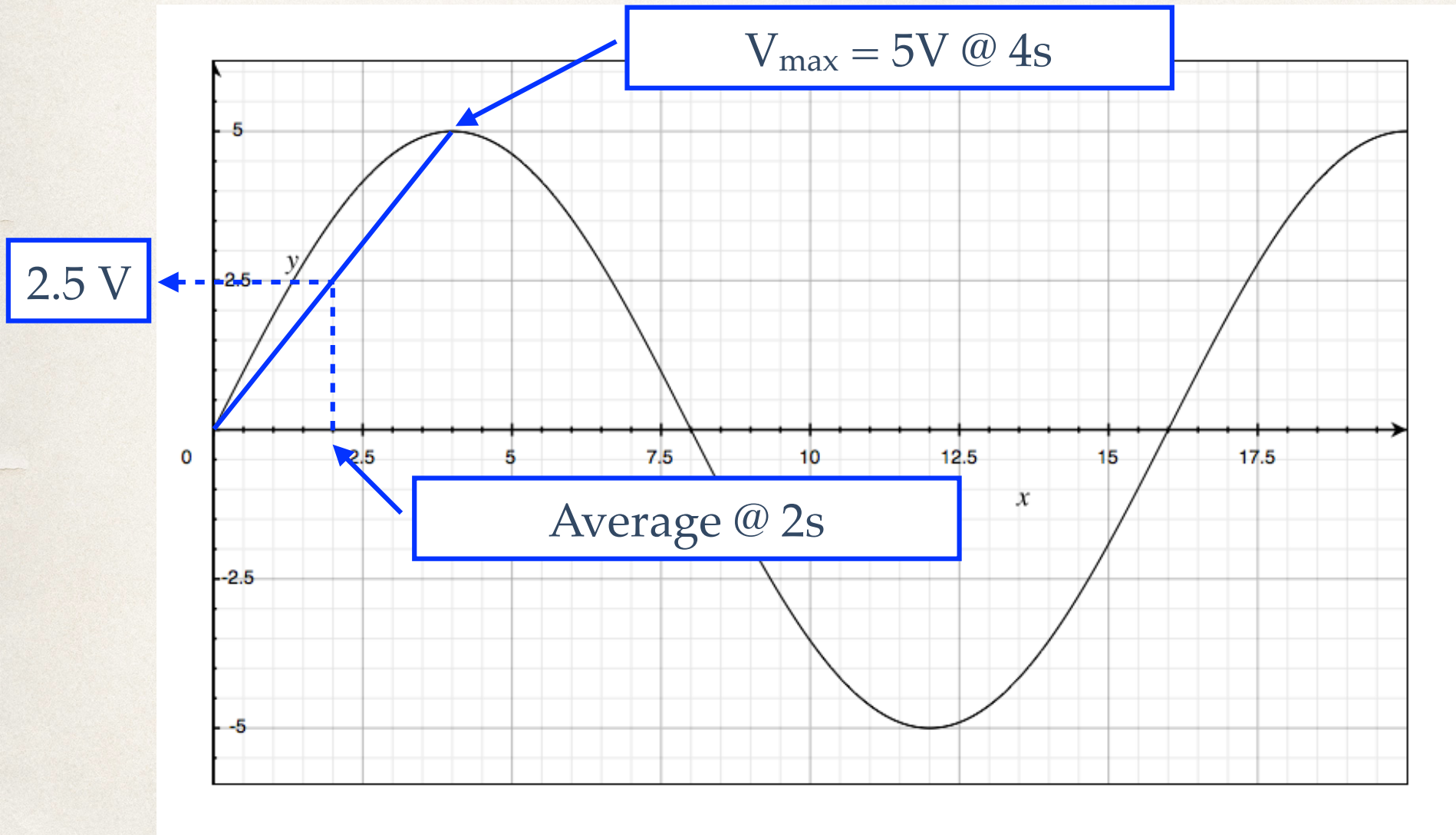



# AC - Alternating Current

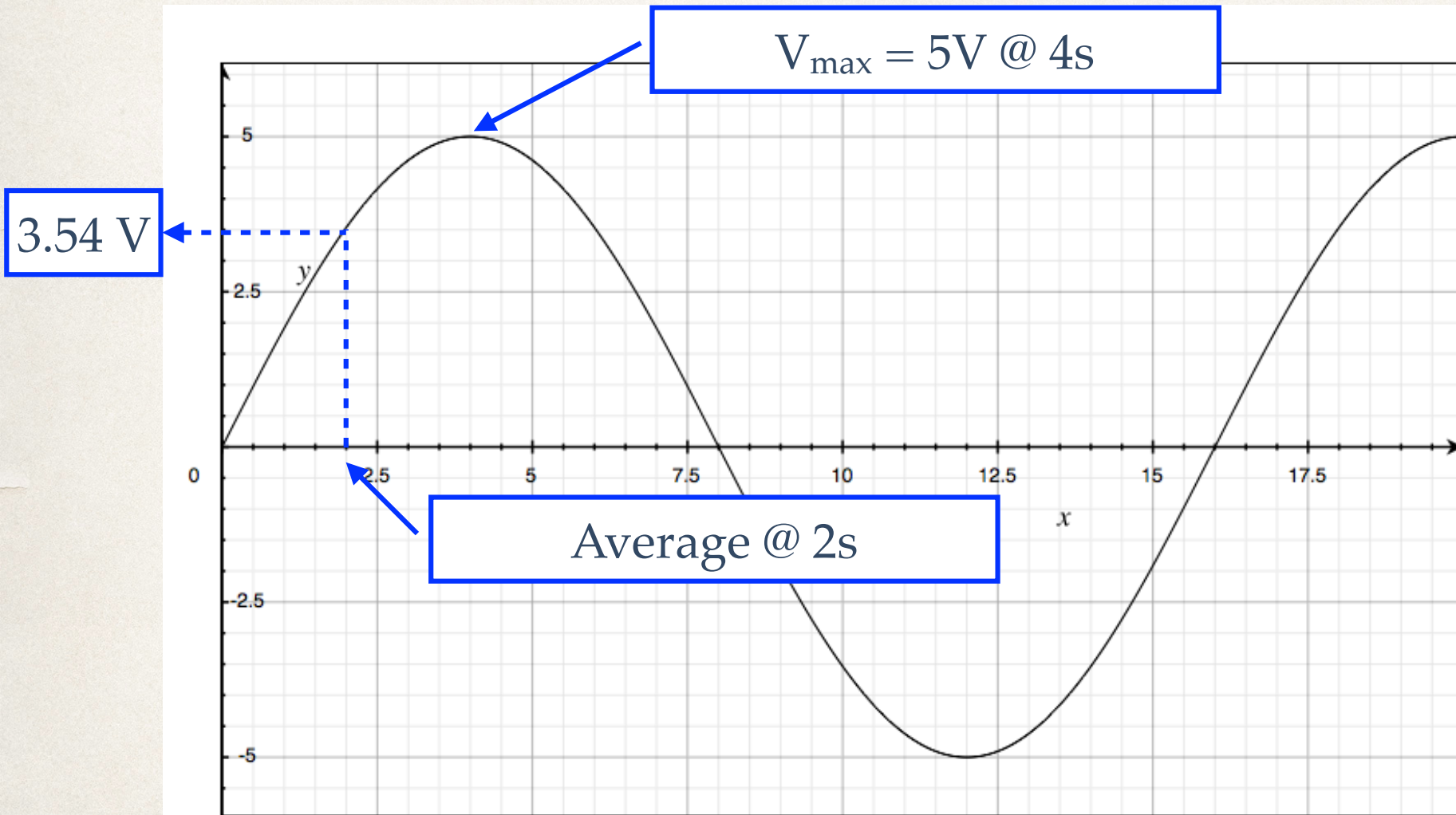



# AC - Direct Current

---

- ❖ What is the ratio of the average voltage to the maximum voltage in an AC circuit?

$$\frac{V_{average}}{V_{max}} = \frac{3.54 \text{ V}}{5 \text{ V}} = 0.707$$

$$V_{average} = 0.707(V_{max})$$

$$V_{max} = 1.414(V_{average})$$



# AC - Direct Current

---

- ❖ What is the ratio of the average voltage to the maximum voltage in an AC circuit?

$$V_{\max} = \sqrt{2} \left( V_{\text{average}} \right)$$

$$\boxed{V_o = \sqrt{2} \left( V_{\text{rms}} \right)}$$



# AC - Direct Current

---

❖ How does this effect Ohm's Law?

$$V = IR$$

$$V_o = I_o R$$

$$\sqrt{2}(V_{rms}) = I_o R$$

$$V_{rms} = \frac{I_o}{\sqrt{2}} R$$

$$I_{rms} = \frac{I_o}{\sqrt{2}} \quad ?$$

$$I_o = \sqrt{2}(I_{rms})$$

$$V_o = \sqrt{2}(V_{rms})$$



# Ohm's Law and the Power Eqn.

---

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

$$P = I(IR)$$

$$P = \left(\frac{V}{R}\right)V$$

$$P = IV$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$



# Max vs. RMS

---

$$V_o = I_o R$$

$$V_{rms} = I_{rms} R$$

$$P = I_o V_o$$

$$\bar{P} = I_{rms} V_{rms}$$

$$I_o = \frac{V_o}{R}$$

$$I_{rms} = \frac{V_{rms}}{R}$$

$$P = I_o^2 R$$

$$\bar{P} = I_{rms}^2 R$$

$$R = \frac{V_o}{I_o}$$

$$R = \frac{V_{rms}}{I_{rms}}$$

$$P = \frac{V_o^2}{R}$$

$$\bar{P} = \frac{V_{rms}^2}{R}$$



# Between MAX and rms

---

$$\bar{P} = I_{rms} V_{rms}$$

$$I_o = \sqrt{2} I_{rms}$$

$$V_o = \sqrt{2} V_{rms}$$

$$I_{rms} = \frac{I_o}{\sqrt{2}}$$

$$V_{rms} = \frac{V_o}{\sqrt{2}}$$

$$\bar{P} = I_{rms} V_{rms} = \frac{I_o}{\sqrt{2}} \frac{V_o}{\sqrt{2}} = \frac{1}{\sqrt{4}} I_o V_o$$

$$\bar{P} = \frac{1}{2} I_o V_o$$



# Complete Picture

---

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

$$P = IV$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

$$\bar{P} = \frac{1}{2} I_o V_o$$

$$\bar{P} = \frac{1}{2} I_o^2 R$$

$$\bar{P} = \frac{1}{2} \frac{V_o^2}{R}$$



# Household Electricity

---

- ❖ Standard = AC, 110-120V
- ❖ Air Conditioning, Electric Furnace, etc = 220V or 440V
- ❖ Circuit Breakers = Ensure current doesn't get too high.
  - ❖ Too High Current = Heat = BAD!

$$V_{\max} = 1.414 \left( V_{\text{average}} \right)$$



# Household Electricity

---

- ❖ 1 Kilowatt = power
- ❖ 1 Kilowatt-Hour = Energy

$$\text{Power} = \frac{\text{Energy}}{\text{Time}}$$

$$\text{Watts} = \frac{\text{Joules}}{\text{second}}$$



# Household Electricity

---

- ❖ How many Joules are in 1 Kilowatt-Hour?



# Example Questions

---

- ❖ A battery is made of two silver wires stuck into a lemon. Which of the following is the expected result?
  - A. The battery works, but not well because the lemon is a weak electrolyte.
  - B. The battery works well because citric acid reacts well with silver
  - C. The battery doesn't work because the metals are the same
  - D. The battery doesn't work because citric acid is not an electrolyte
  - E. The battery has a voltage of 0.78 V, it's what Volta used in his research.



# Example Questions

---

- ❖ A battery is made of two silver wires stuck into a lemon. Which of the following is the expected result?
  - A. The battery works, but not well because the lemon is a weak electrolyte.
  - B. The battery works well because citric acid reacts well with silver
  - C. The battery doesn't work because the metals are the same**
  - D. The battery doesn't work because citric acid is not an electrolyte
  - E. The battery has a voltage of 0.78 V, it's what Volta used in his research.



# Example Questions

---

- ❖ A circuit is connected to a 9.0V battery. If the current is 0.3 Amperes, what is the resistance?
  - A.  $0.03\ \Omega$
  - B.  $3.0\ \Omega$
  - C.  $9.3\ \Omega$
  - D.  $30\ \Omega$
  - E. Answer not provided



# Example Questions

---

- ❖ A circuit is connected to a 9.0V battery. If the current is 0.3 Amperes, what is the resistance?
  - A. 0.03  $\Omega$
  - B. 3.0  $\Omega$
  - C. 9.3  $\Omega$
  - D. 30  $\Omega$**
  - E. Answer not provided



# Example Questions

---

- ❖ If the length of a wire is doubled which of the following is true?
  - A. The resistivity doubles
  - B. The resistance doubles
  - C. The resistivity halves
  - D. The resistance halves
  - E. More information required



# Example Questions

---

- ❖ If the length of a wire is doubled which of the following is true?
  - A. The resistivity doubles
  - B. The resistance doubles**
  - C. The resistivity halves
  - D. The resistance halves
  - E. More information required



# Example Questions

---

- ❖ What is the power of the battery in problem 2?

$$(V = 9\text{V}, I = 3.0\text{ A}, R = 30\ \Omega)$$

A. 0.81 W

B. 0.81 J

C. 2.7 W

D. 2.7 J

E. 270 W



# Example Questions

---

- ❖ What is the power of the battery in problem 2?

$$(V = 9\text{V}, I = 3.0\text{ A}, R = 30\ \Omega)$$

A. 0.81 W

B. 0.81 J

**C. 2.7 W**

D. 2.7 J

E. 270 W



# Example Questions

---

- ❖ What effect does an increase in temperature have on a semi-conductor?
  - A. It increases the resistance
  - B. It increases the resistivity
  - C. It depends on the type of semi-conductor
  - D. it decreases the resistance
  - E. It decreases the resistivity



# Example Questions

---

- ❖ What effect does an increase in temperature have on a semi-conductor?
  - A. It increases the resistance
  - B. It increases the resistivity
  - C. It depends on the type of semi-conductor
  - D. it decreases the resistance
  - E. It decreases the resistivity**



# Example Questions

---

- ❖ What effect does an increase in temperature have on a semi-conductor?

$$\rho_T = \rho_o \left[ 1 + \alpha (T_f - T_o) \right]$$

- ❖ p.508-509 discusses this formula. Notice for a small section of materials that are semi-conductors  $\alpha$  is **negative** so as temperature increases then  $\rho_T$  will actually decrease. As a result the resistance will also decrease. (so the answer is both D and E)



# Batteries

---

- ❖ If I want to greatly increase the voltage in a circuit how could I accomplish that goal?
  - A. Change the materials used for the cathode and anode
  - B. Change the chemical used for the electrolyte
  - C. Connect multiple batteries in parallel
  - D. Connect multiple batteries in series



# Batteries

---

- ❖ If I want to greatly increase the voltage in a circuit how could I accomplish that goal?
  - A. Change the materials used for the cathode and anode
  - B. Change the chemical used for the electrolyte
  - C. Connect multiple batteries in parallel
  - D. Connect multiple batteries in series**



# Series

---

- ❖ Batteries connected from cathode of one battery to anode of the next
- ❖ Increases voltage of the combined batteries.

$$V_t = nV_{battery}$$



# Batteries

---

- ❖ What effect does connecting batteries in parallel have?
  - A. It makes the battery last longer
  - B. It increases the voltage of the battery
  - C. It increases the current from the battery
  - D. More than one of the above



# Batteries

---

- ❖ What effect does connecting batteries in parallel have?
  - A. It makes the battery last longer
  - B. It increases the voltage of the battery
  - C. It increases the current from the battery
  - D. More than one of the above (A & C with limits)**



# Parallel

---

- ❖ Batteries connected with all cathodes together and all anodes together
- ❖ Increases current from the combined batteries **OR** increases the longevity of the combined batteries.