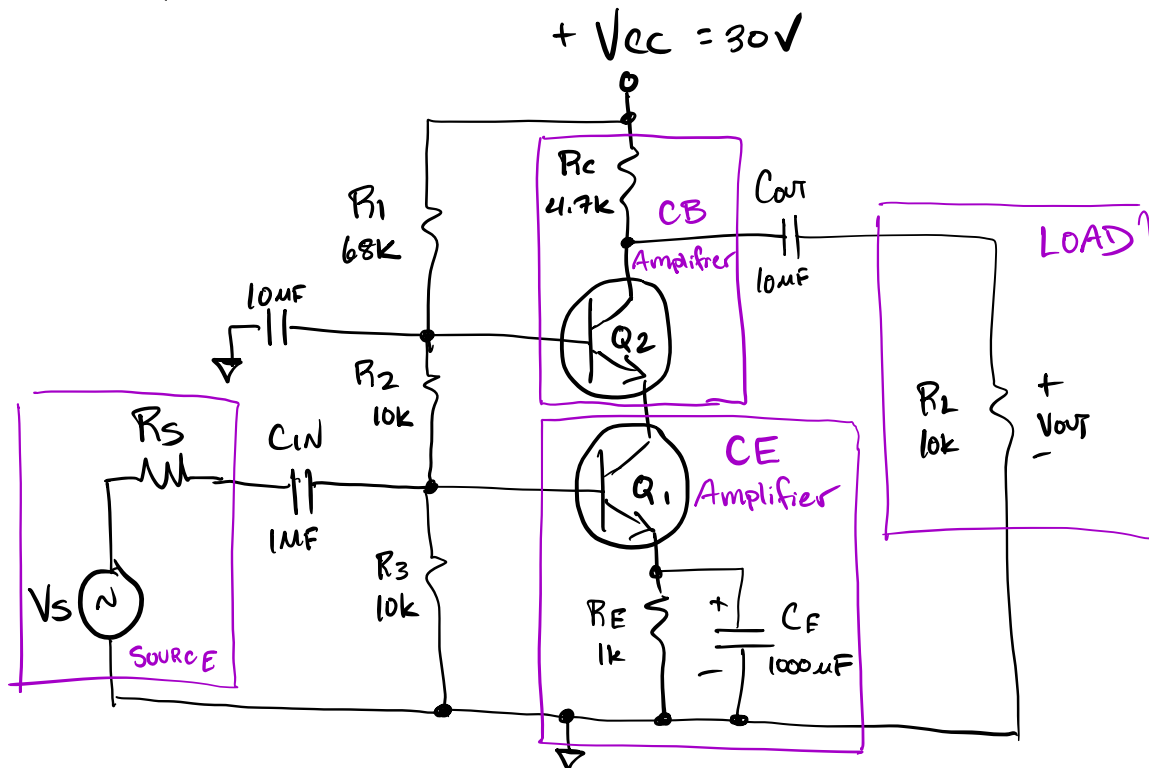


The Cascode Amplifier



... combining CE and CB amplifiers in one compound amplifier stage offers high gain and high R_{in} (not really) of CE with better HF response of CB!

... in the vacuum-tube era, when this circuit was developed, the anode of the common-cathode stage was cascaded into the cathode of the common-grid stage

... thus, cascode.

.. quick D.C. analysis, assuming high β :

$$V_{B1} = V_{CC} \left[\frac{R_3}{R_1 + R_2 + R_3} \right] = 30 \left[\frac{10k}{68k + 10k + 10k} \right]$$

$$V_{B1} = \underline{3.4V} \quad \therefore V_{E1} = 3.4 - 0.7 = \underline{2.7V}$$

$$I_{E1} \approx \underbrace{I_{C1}}_{\text{D.C. Coupled!}} = I_{E2} \approx I_{C2} = \frac{V_{E1}}{R_E} = \frac{2.7}{1k} = \underline{2.7mA}$$

$$V_{B2} = V_{CC} \left[\frac{R_2 + R_3}{R_1 + R_2 + R_3} \right] = 30 \left[\frac{10k + 10k}{68k + 10k + 10k} \right]$$

$$V_{B2} = 6.8V; \quad \therefore V_{E2} = V_{C1} = 6.8 - 0.7 = \underline{6.1V}$$

$$V_{CE1} = V_{C1} - V_{E1} = 6.1 - 2.7 = \underline{3.4V}$$

$$V_{C2} = V_{CC} - I_{C2} R_C = 30 - 2.7 \cdot 4.7 = 17.3V$$

$$\therefore V_{CE2} = V_{C2} - V_{E2} = 17.3 - 6.1 = \underline{11.2V}$$

.. note that V_{CE2} is more than three times V_{CE1}
.. more later!

Mid-Frequency Analysis of CE Stage

$$g_{m1} = 35 I_C = 35 \cdot 2.7 = \underline{94.5 \text{ mA/V}}$$

$$r_{b1} = \frac{\beta}{g_m} = \frac{200}{94.5} = \underline{2.116 \text{ k}\Omega}$$

$r_{o1} \rightarrow \text{ignore}$

$$R_{b1}' = R_2 \parallel R_3 \parallel r_{b1} = 10k \parallel 10k \parallel 2.116k = \underline{1.487 k\Omega}$$

$$A_{v1} = \frac{v_{be1}}{v_s} = \frac{R_{b1}'}{R_{b1}' + R_s} = \frac{1.487}{1.487 + 50}$$

$$\underline{A_{v1} = 0.97} \quad \leftarrow \text{same as CE example}$$

∵ since the collector of Q_1 is direct-coupled to the emitter of Q_2 , $R_{c1}' = R_c \parallel R_L$ is now replaced by the input resistance of the CB amplifier:

$$r_{e2}' \approx \frac{1}{g_{m2}}$$

$$A_{v2} = \frac{v_{c1}}{v_{be1}} = -g_{m1} \cdot \frac{1}{g_{m2}}$$

∵ since $I_{c2} \approx I_{c1}$, $g_{m2} \approx g_{m1}$

$$\therefore \underline{A_{v2} = -1} \quad \text{or } \underline{0\text{dB inverting}}$$

say what?

∴ thus, the CE amplifier provides no voltage gain (important later!)

- side note: remember when we noted in CE D.C. analysis that V_{CE} should ensure adequate "wiggle room" for small-signal amplification?
- the CE stage of the cascode doesn't need much wiggle room due to no amplification!
 - that's why we allow $V_{CE2} > 3 \times V_{CE1}$

\downarrow
 $11.2V$

\downarrow
 $3.4V$

Mid-Frequency Analysis of CB Stage

- we already know the gain between V_s and V_{be2}
- only need the output transfer, which we'll call A_{V3} .

$$A_{V3} = \frac{V_{OUT}}{V_{C1}} = \frac{V_{OUT}}{V_{e2}} \leftarrow \text{input of CB stage}$$

- our CB amplifier output gain was given as

$$\frac{V_{OUT}}{V_{be}} = -g_m (R_C \parallel R_L)$$

- BUT, since V_{b2} is grounded, $V_{be2} = 0 - v_{e2} = -v_{e2}$

$$\therefore A_{V3} = \frac{V_{OUT}}{v_{e2}} = \frac{V_{OUT}}{-V_{be2}} = +g_m (R_C \parallel R_L)$$

- remember, CB is non-inverting!

$$A_{v_3} = 94.5 \text{ (4.7k || 10k)}$$

$$\hookrightarrow 3.197\text{L}$$

$A_{r3} = 302$ or 49.6 dB

thus, $A_{v_1} \times A_{v_2} \times A_{v_3} = 0.97 \cdot 1.302$

$= -293$ or 49 dB
(inverting)

\therefore Same gain as CE!

∴ no 15 dB loss of CB from 50Ω source

Low-Frequency Analysis of Cascode Amplifier

- C_{IN} , C_E , and C_{OUT} essentially have same LF characteristics as CE amplifier

$$f_{LIN} = \frac{1}{2\pi \cdot C_{IN} (R_S + R_{b'})}$$

$$= \frac{1}{2\pi \cdot 1 \times 10^{-6} (50 + 1.487k)}$$

$$\underline{f_{LIN} = 103,5 \text{ Hz}}$$

$$f_{L\text{ out}} = \frac{1}{2\pi C_{\text{out}} (R_c + R_L)}$$

$$= \frac{1}{2\pi \cdot 10 \times 10^{-6} (4.7k + 10k)}$$

$$\underline{f_{L\text{ out}} = 1.083 \text{ Hz}}$$

$$f_{LE} \approx \frac{1}{2\pi \cdot C_E \cdot \frac{1}{g_m}}$$

$$= \frac{1}{2\pi \cdot 1000 \times 10^{-6} \cdot \frac{1}{94.5\text{m}}} = 10.62$$

$$\underline{f_{LE} = 15 \text{ Hz}}$$

∴ Dominant pole is $\underline{f_{LW} = 103.5 \text{ Hz} \approx f_L}$

HF Analysis of Cascode Amplifier

- ∴ this is where the reduction in gain of CE stage to unity becomes helpful!
- ∴ we know that for a CE amplifier,
 $C_{BC(IN)} = C_{BC} (1 - A_{v2})$ due to Miller Effect
 $C_{BC(IN)} = 4 (1 - -1) = \underline{8 \text{ pF}}$ ← compare to CE example of over INF!!!

$$f_{HIN} = \frac{1}{2\pi (C_{BE} + C_{BCIN}) (R_s \parallel R_{b'})}$$

$$f_{HIN} = \frac{1}{2\pi (18p + 8p) (50 \parallel 1.487k)}$$

$$\underline{f_{HIN} = 126.5 \text{ MHz}} \quad \dots \text{ over } \underline{40 \text{ times better}} \text{ than } 2.97 \text{ MHz of non-cascoded CE!}$$

-- high-frequency response at coupling between CE and CB stages may be assumed to be sufficiently high due to low emitter resistance ($\frac{1}{g_m}$) and no Miller Effect that we may ignore it

-- at the output of the amplifier, it is simply the HF response of CB:

$$f_{HOUT} = \frac{1}{2\pi \cdot C_{BC} (R_C \parallel R_L)}$$

$\hookrightarrow 4pF$ $\hookrightarrow 3.197k$

$$\underline{f_{HOUT} = 12.4 \text{ MHz} \approx f_H} \text{ (dominant pole)}$$

-- Summary: cascoding retains the gain and R_{in} of CE, but superior HF response of CB.