
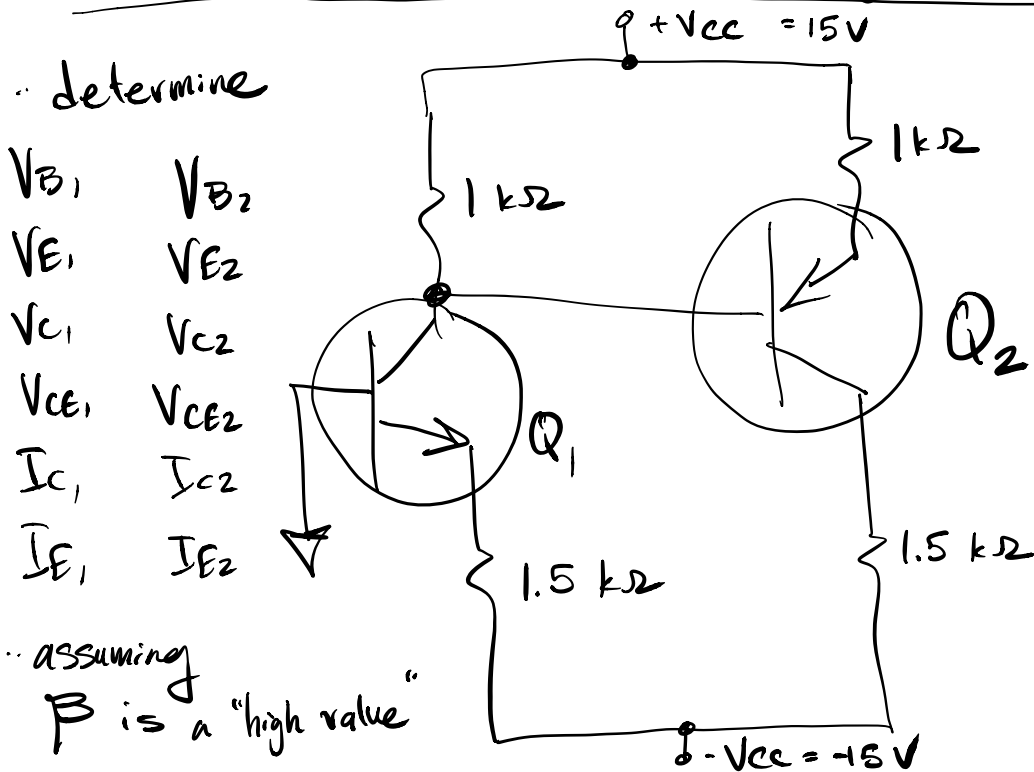


Direct-Coupled Active Region Circuits

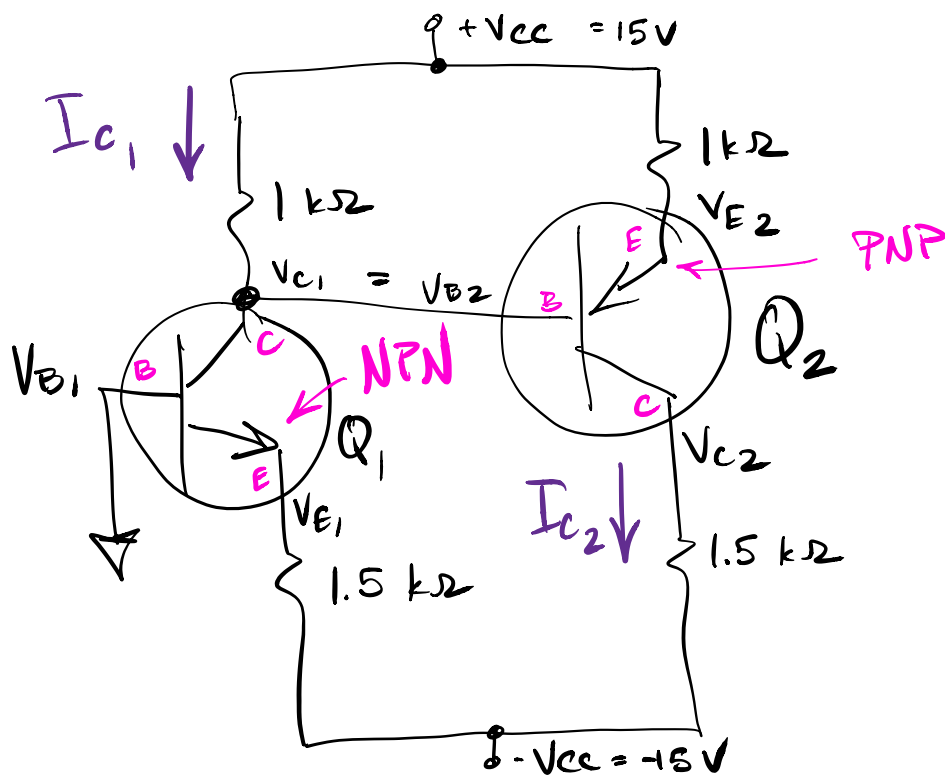

.. the key: Q_1 's collector voltage, V_{C1} ,
 is also Q_2 's base voltage, V_{B2}
 due to direct coupling.



no need to even label I_{B1} , I_{B2} , I_{E1} , I_{E2}
because "high- β " assumption means:

$$I_{B1} = 0, \quad I_{B2} = 0$$

$$I_{C1} = I_{E1}, \quad I_{C2} = I_{E2}$$

· let's start with Q_1 at the base terminal.

$$V_{B_1} = 0 \quad \leftarrow \text{because it's grounded}$$

· in the active region, $V_{BE_1} = 0.7V$ [Si]

$$\circ \circ \quad V_{BE_1} = V_{B_1} - V_{E_1}$$

$$\Rightarrow V_{E_1} = \underset{\downarrow 0}{V_{B_1}} - 0.7$$

$$\underline{V_{E_1} = -0.7V}$$

$$I_{E_1} = \frac{V_{E_1} - (-V_{CC})}{R_{E_1}} = \frac{-0.7 - (-15)}{1.5k}$$

$$\underline{I_{E_1} = 9.53 \text{ mA}}$$

because β is "high," $I_{C_1} = 9.53 \text{ mA}$

$$V_{C1} = V_{CC} - \underbrace{I_{C1} R_{C1}}_{\text{drop across collector resistor}}$$

$$= 15 - 9.53 \mu \cdot 1k$$

$$\underline{V_{C1} = 5.47 \text{ V}}$$

$$V_{CE1} = V_{C1} - V_{E1} = 5.47 - (-0.7)$$

$$\underline{V_{CE1} = 6.17 \text{ V}} \quad \Leftarrow \text{Verifies active region!} \\ (> 0.2 \text{ V})$$

Q_1 is done!

.. due to direct-coupling, $\underline{V_{B2} = V_{C1} = 5.47 \text{ V}}$

.. for PNP in active region: $\underline{V_{BE2} = -0.7 \text{ V}}$

$$V_{BE2} = V_{B2} - V_{E2}$$

$$\Rightarrow V_{E2} = V_{B2} - (-0.7) = 5.47 + 0.7$$

$$\underline{V_{E2} = 6.17 \text{ V}}$$

I_{E2}

$$I_{E2} = \frac{V_{CC} - V_{E2}}{R_{E2}}$$

$$= \frac{15 - 6.17}{1k}$$


$$\underline{I_{E2} = 8.83 \text{ mA}}$$

$$\text{high-}\beta \Rightarrow I_{C2} = I_{E2} = \underline{8.83 \text{ mA}}$$

$$V_{C2} - (-V_{CC}) = I_{C2} \cdot R_{C2}$$

$$V_{C2} = -V_{CC} + I_{C2} R_{C2} = -15 + 8.83 \cdot 1.5$$

$$\underline{V_{C2} = -1.76 \text{ V}}$$

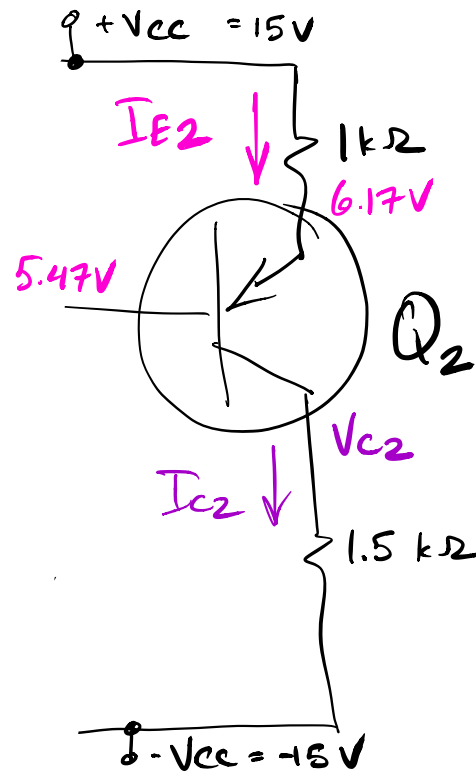


$$V_{CE2} = V_{C2} - V_{E2} = -1.76 - 6.17$$


$$\underline{V_{CE2} = -7.93 \text{ V}}$$

↑
yes, negative!

- yes, active region; $|V_{CE}| > 0.2 \text{ V}$
- why is the active region so important?
 - ~ permits linear amplification of small signals!
- back to simple NPN circuit:

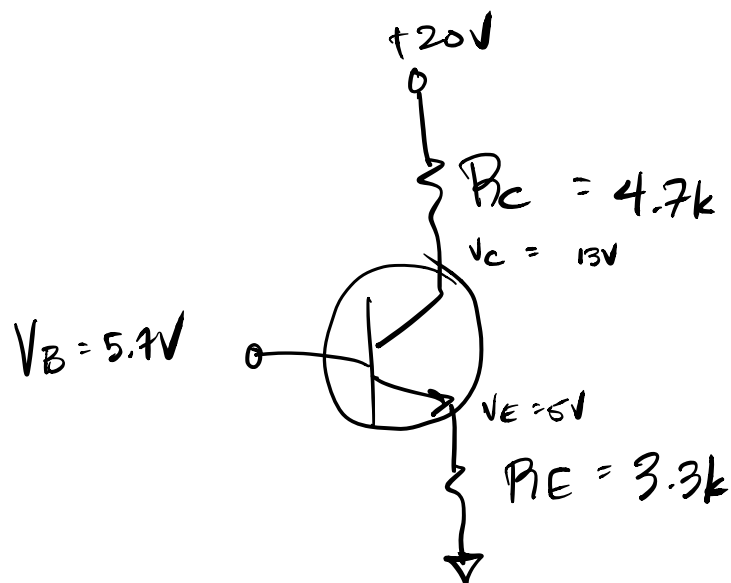

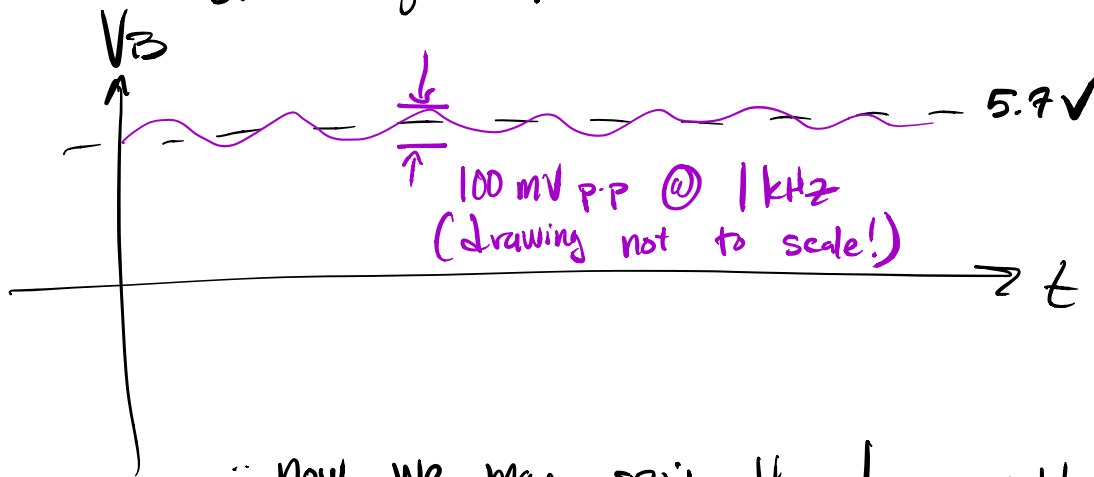.. What if, instead of holding V_B steady at 5.7V,
We wiggle it around 5.7V with some
small signal?



.. Now we may split the base voltage
into DC and AC components:

DC : $V_B = 5.7V$
 ↑
 capitalized!

AC : $v_b = 100 \text{ mV p-p @ } 1 \text{ kHz}$
 ↑
 lower case!
 ↑
 small-signal
 component

.. here's how linear amplification works.

-- "wiggling" V_B causes V_{BE} to wiggle

.. now we have a small-signal v_{be} !

.. Wiggling V_{BE} causes I_C to wiggle

.. creates a small-signal i_c !

.. this causes the drop across R_E to wiggle

→ this causes V_C to wiggle

.. creates a small-signal v_c , which, if we do everything right, is an amplified version of our original wiggle!!!!