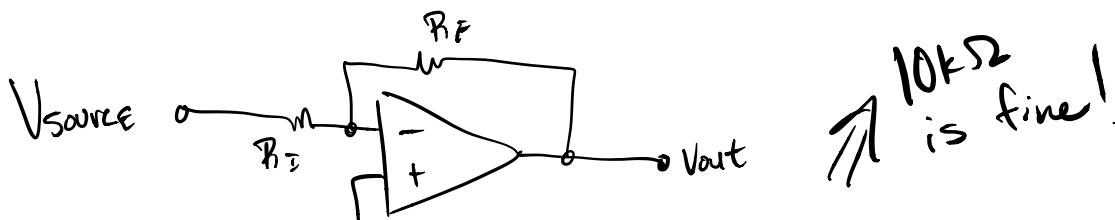


homework: design a circuit using ideal OP-amps that achieves

$$V_{\text{out}} = 3V_A + 2V_B - 5V_C$$

↑ negative!


- use as few op-amps as possible
- sketch  $V_{\text{out}}$  if  $V_A = 1V$  [D.C.]  
 $V_B = 10 \text{ mV}$  [D.C.]  
 $V_C = 50 \text{ mV}_{\text{P-P}}$  [sine, 1 kHz]
- need to get polarities right!  
 one way to "fix" polarity is with  
unity-gain inverting amplifier



$\nearrow 10k\Omega$  is fine!


$$\frac{V_{\text{out}}}{V_{\text{source}}} = A_V = -\frac{R_F}{R_I}$$

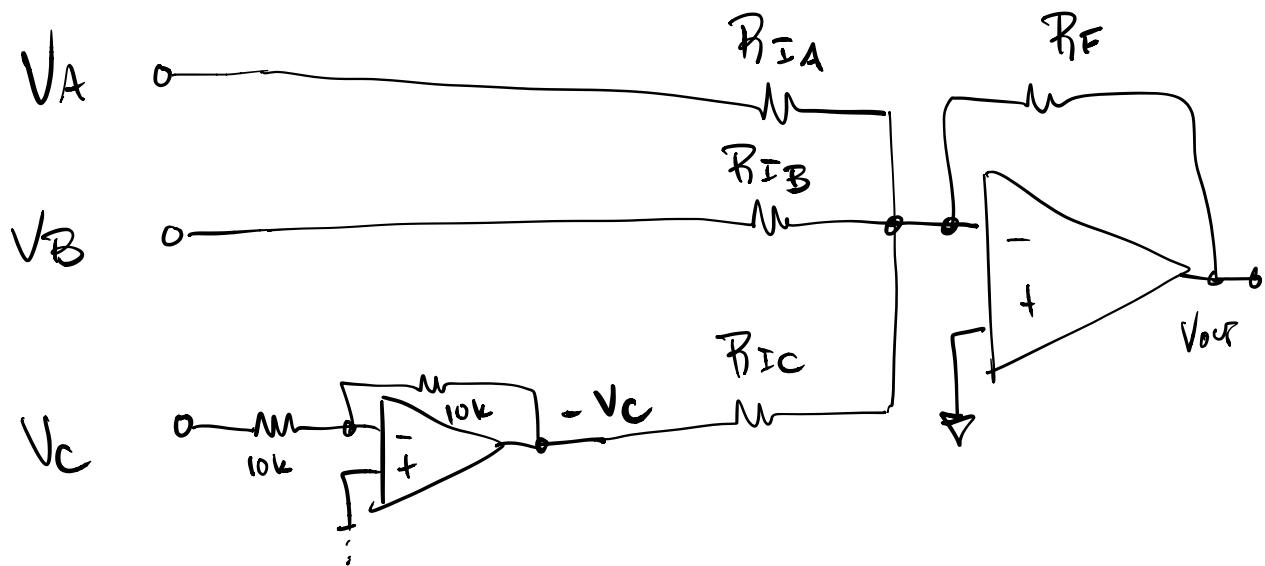make  $R_F = R_I$ ,  
 then  $V_{\text{out}} = -V_{\text{source}}$



- Since summing amp is inverting,  
V<sub>OUT</sub> must be function of -V<sub>A</sub>, -V<sub>B</sub>, and +V<sub>C</sub>.
- Will need another unity-gain inverting amplifier  
after V<sub>OUT</sub>!

Alternative :

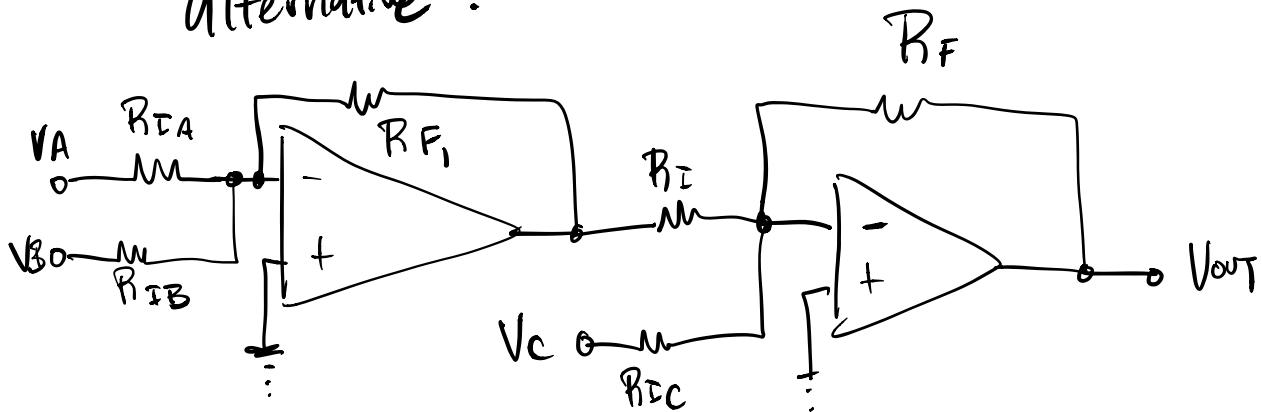

1st summing amp:

$$V_{\text{OUT},1} = V_A \left( \frac{-R_{F1}}{R_{I1A}} \right) + V_B \left( \frac{-R_{F1}}{R_{I1B}} \right)$$

Pick  $R_{F1} = 30\text{k}\Omega$ ; then  $R_{I1A} = 10\text{k}\Omega$

$$V_{\text{OUT}} = -V_A \left( \frac{30k}{10k} \right) - V_B \left( \frac{30k}{15k} \right) \quad R_{I1B} = 15\text{k}\Omega$$

$$V_{\text{OUT}} = -3V_A - 2V_B \quad (\text{closer!})$$

2nd summing amp:

$$V_{\text{OUT}} = \underbrace{(-3V_A - 2V_B)}_{\text{from previous}} \left( \frac{-R_F}{R_I} \right) + V_C \left( \frac{-R_F}{R_{Ic}} \right)$$

Pick  $R_F = 100\text{k}\Omega$ , then  $R_I = 100k$

$$\therefore R_{Ic} = 20k$$

$$\text{then } V_{\text{OUT}} = (-3V_A - 2V_B) \left( \frac{-100k}{100k} \right) + V_C \left( \frac{-100k}{20k} \right)$$

$$V_{\text{OUT}} = 3V_A + 2V_B - 5V_C$$

10k  
15k  
30k  
100k

Note: all resistors are already E24 / 5%!

- if  $V_A = 1V$ ,  $V_B = 10mV$ ,  $V_C = 50mV_{P-P}$


D.C. Voltages                          A.C.

$$V_{OUT(DC)} = 3 \cdot 1 + 2 \cdot 10m = 3.02V$$

$$V_{OUT(AC)} = -5 \cdot 50 = -250mV_{P-P}$$


or  $250mV_{P-P}$   
inverted sine wave!

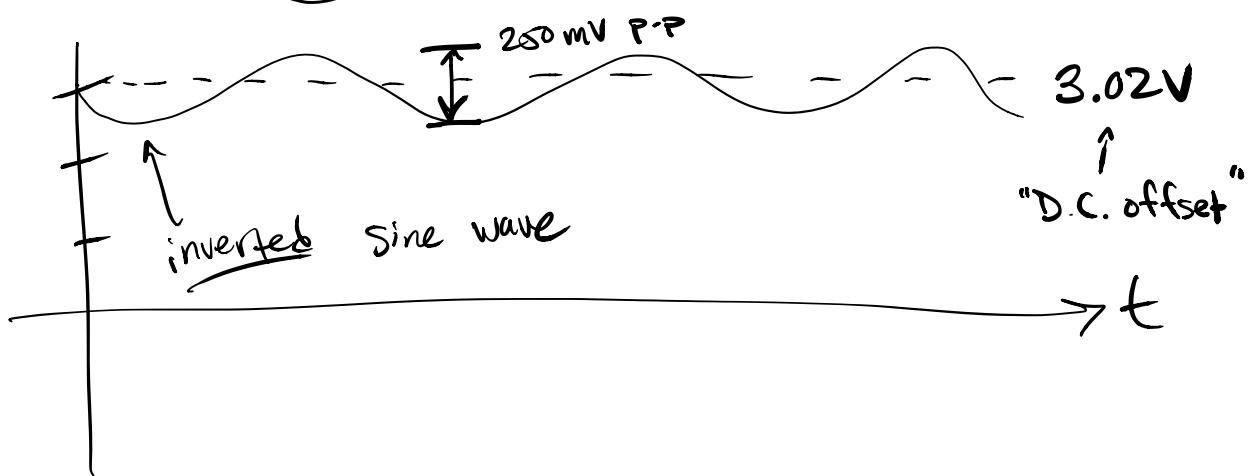- final waveform will be  $250mV_{P-P}$  sine wave, inverted,  
shifted upward  $3.02V$


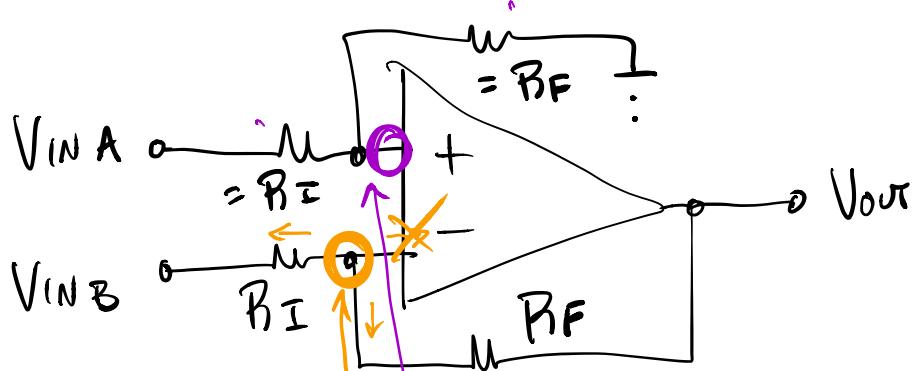
# Balanced Differential Amplifier

- crucial concept in electronic measurement!
- amplifies difference between two voltages, not referenced to ground  
(instrumentation)



- note equality of resistor values in  
balanced differential amplifier case!
- let's look at  $V_{int^+}$
- ideal op-amp has zero input current (rule # 2)

$$\therefore V_{int^+} = V_{INA} \left( \frac{R_F}{R_F + R_I} \right)$$

$$\therefore V_{in^-} = V_{INA} \left( \frac{R_F}{R_F + R_I} \right) \quad (\text{rule } \# 1)$$

$\uparrow$   
 $V_{in^+} = V_{in^-}$

KCL @  $V_{in^-}$ :

$$\frac{V_{in^-} - V_{INB}}{R_I} + \frac{V_{in^-} - V_{out}}{R_F} = 0$$

$$\frac{V_{in^-}}{R_I} - \frac{V_{INB}}{R_I} + \frac{V_{in^-}}{R_F} - \frac{V_{out}}{R_F}$$

$$V_{out} = V_{in^-} \left( \frac{R_F}{R_I} \right) - V_{INB} \left( \frac{R_F}{R_I} \right) + V_{in^-}$$

$$V_{out} = V_{in^-} \left( \frac{R_F + R_I}{R_I} \right) - V_{INB} \left( \frac{R_F}{R_I} \right)$$

$$V_{out} = V_{INA} \left( \frac{R_F}{R_F + R_I} \right) \left( \frac{R_F + R_I}{R_I} \right) - V_{INB} \left( \frac{R_F}{R_I} \right)$$

$$V_{out} = \underbrace{\left( V_{INA} - V_{INB} \right)}_{\text{difference !!!}} \left( \frac{R_F}{R_I} \right)$$

# Gain-Bandwidth Product

- .. ideal op-amps : perfect frequency response,  
no high- or low-pass filtering
- .. real op-amps : low-pass


.. LM741, for example :

$$A_{V(0.1)} = 100,000$$

$$20 \log_{10} (100,000) = \underline{100 \text{ dB}}$$


Very high!

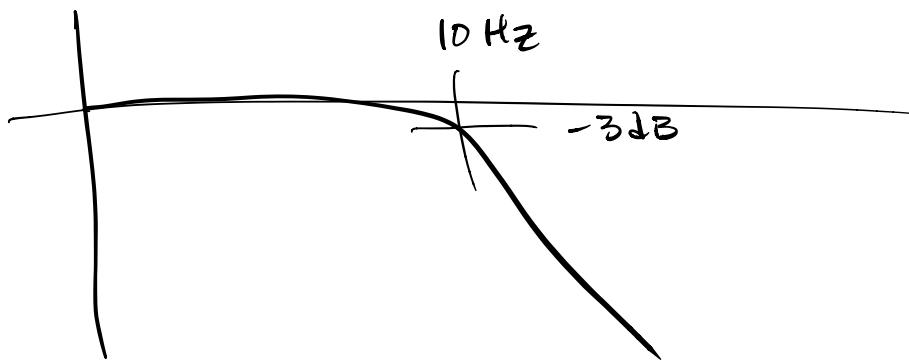- .. built-in low-pass filter w/ cutoff frequency  
of  $f_c = 10 \text{ Hz}$  (What?)



- Negative feedback proportionally raises the bandwidth!
- negative feedback also lowers gain.
- Product of gain and bandwidth is a constant, called the gain-bandwidth product
- mA741 has GBP of 1 MHz
- how do you use this concept?

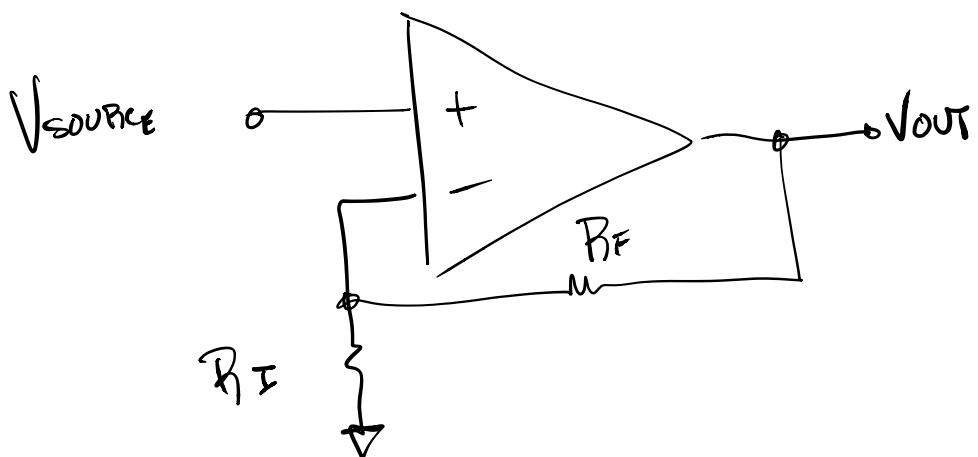example : Non-inverting amplifier w/ gain of 36



$$GBP = Av \cdot BW$$


↑                   ↑  
 gain              bandwidth

then  $BW = \frac{GBP}{Av} = \frac{1 \text{ MHz}}{36}$

$$= 27777.8$$

or  $27.8 \text{ kHz}$

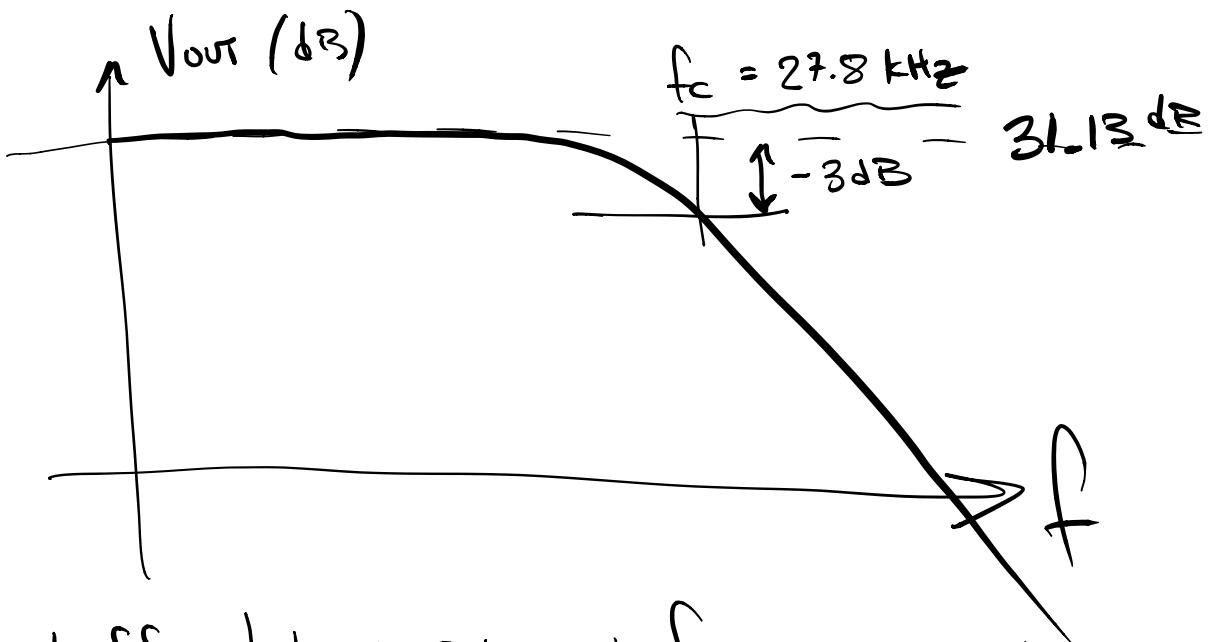side note: gain of 36 is  $20 \log_{10} 36 = \underline{31.13 \text{ dB}}$



- tradeoff between gain and frequency response!
  - higher gain  $\rightarrow$  lower bandwidth
- if you need wider bandwidth at higher gain,

