
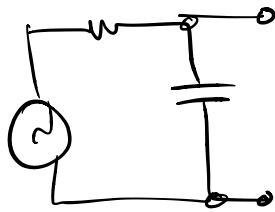



Series RLC Low-Pass Filter

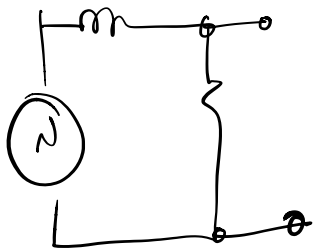

1st-order RC low-pass



1st-order RL low-pass

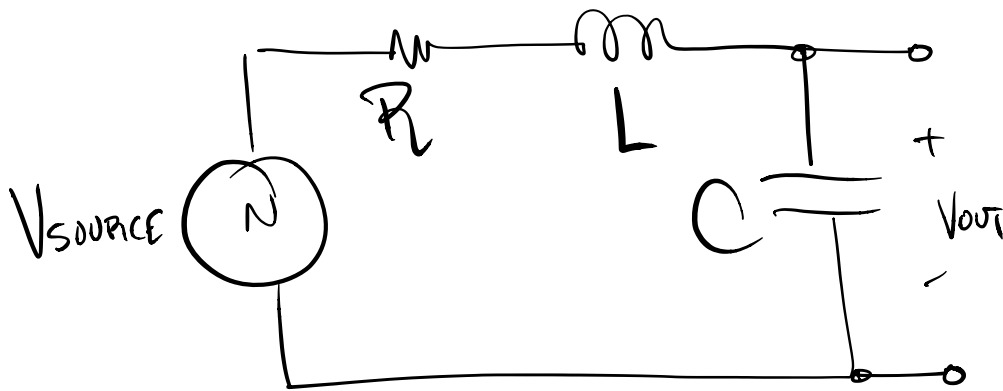

2nd-order LPF!

complex voltage divider:

$$\underline{V_{OUT} = V_{SOURCE} \left[\frac{Z_C}{Z_R + Z_L + Z_C} \right]}$$

$$\frac{V_{OUT}}{V_{SOURCE}} = \frac{Z_C}{Z_R + Z_L + Z_C} = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

× top and bottom by $j\omega C$:

$$\frac{V_{OUT}}{V_{SOURCE}} = \frac{1}{1 + \underbrace{(j\omega)^2 LC}_{\rightarrow -\omega^2} + j\omega RC} \Rightarrow \text{Signals class !!!}$$

÷ top and bottom by LC :

$$\frac{V_{OUT}}{V_{SOURCE}} = \frac{\frac{1}{LC}}{\frac{1}{LC} + (j\omega)^2 + j\omega \frac{R}{L}}$$

recall : $\underline{Q_{series} = \frac{1}{R} \sqrt{\frac{L}{C}}}$

all $\frac{RLC}{RLC} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore H(\omega) = \frac{\omega_0^2}{\omega_0^2 + j\omega \frac{\omega_0}{Q} + (j\omega)^2}$$

Correct final form for any 2nd-order low-pass filter!

~ at very low frequencies ($\omega \rightarrow 0$; approaching DC!)

$$H(\omega) \rightarrow \frac{\omega_0^2}{\omega_0^2 + j \text{SMALL} + (j \text{SMALL})^2} \approx \frac{\omega_0^2}{\omega_0^2}$$



\therefore low frequencies
are passed

~ at very high frequencies: ($\omega \rightarrow \infty$)

$$H(\omega) \rightarrow \frac{\omega_0^2}{\omega_0^2 + j \text{BIG} + (j \text{BIG})^2} = \frac{1}{\underbrace{j^2}_{-1} \text{BIG}^2}$$

\uparrow
this term
dominates denominator!



~ let's back up: first-order LPF approached -90° in
stopband
okie dokie!

what happens @ $\omega = \omega_0$?

↑
natural frequency

↙ corner frequency!

it's a little different from what happens @ ω_c in a first-order filter!

$$H(j\omega_0) = \frac{\omega_0^2}{\omega_0^2 + j\omega_0 \frac{\omega_0}{Q} + (j\omega_0)^2}$$

$$= \frac{\omega_0^2}{\cancel{\omega_0^2} + \omega_0^2 \frac{j}{Q} + \underbrace{j^2}_{=-1} \omega_0^2} = \frac{\cancel{\omega_0^2}}{\cancel{\omega_0^2} \frac{j}{Q}}$$

$$H(j\omega_0) = \frac{Q}{j} = -jQ$$

$$\Rightarrow Q \angle -90^\circ$$

at ω_0 , phase is -90° ; a first-order LPF had -45° phase @ ω_c , makes sense

.. much more importantly: the magnitude of the frequency response @ ω_0 isn't -3 dB like a 1st order, but $= Q \rightarrow$ related to damping!

$$|H(\omega_0)|_{dB} = 20 \log_{10} Q$$


recall: in time-domain, we characterized transient response as follows:

overdamped if $Q < 0.5$

critically-damped if $Q = 0.5$



underdamped if $Q > 0.5$

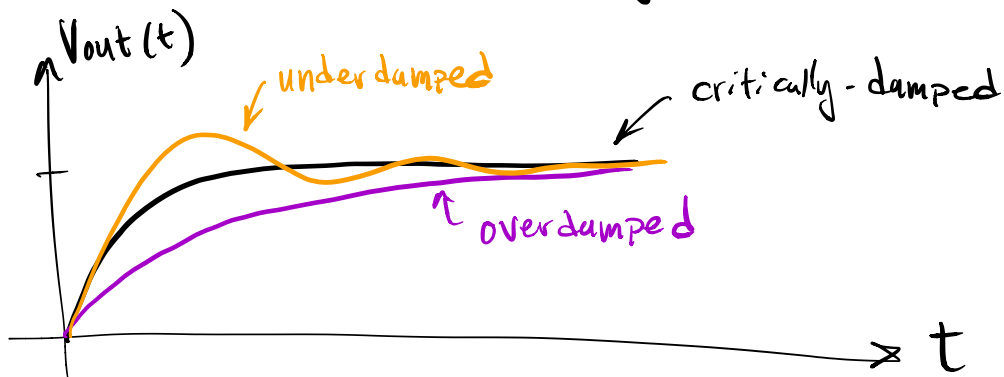\hookrightarrow overshoot, ringing, etc..



.. for frequency-domain analysis, we look at it entirely differently:

Q	filter type	freq. / time response
0.5	Linkwitz-Reilly	$20 \log_{10}(0.5)$ $= -6 \text{ dB} @ \omega_0$.. flattest time response (critically damped) .. no ringing or overshoot
$\frac{1}{\sqrt{3}}$ = 0.577	Bessel	$-4.77 \text{ dB} @ \omega_0$.. flattest <u>phase</u> response
$\frac{1}{\sqrt{2}}$ = 0.707	Butterworth *	$-3 \text{ dB} @ \omega_0$.. flattest <u>amplitude</u> response .. some overshoot, no ringing
> 0.707	Chebyshev	<u>Peak</u> @ ω_0 for $Q > 1$.. <u>sharpest</u> transition between pass and stop bands! .. ringing and overshoot

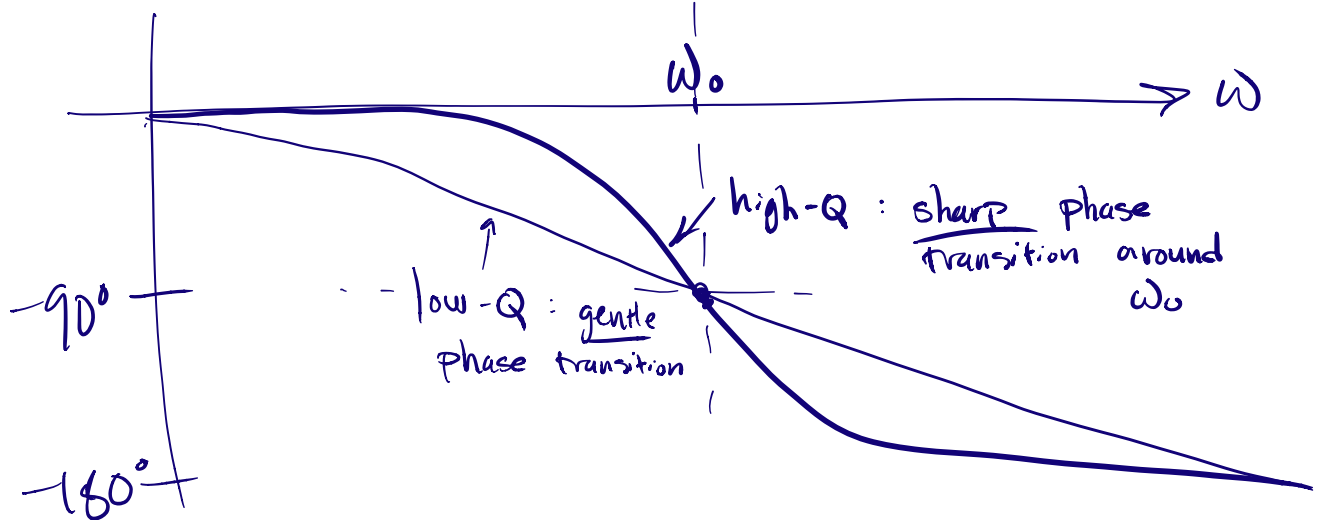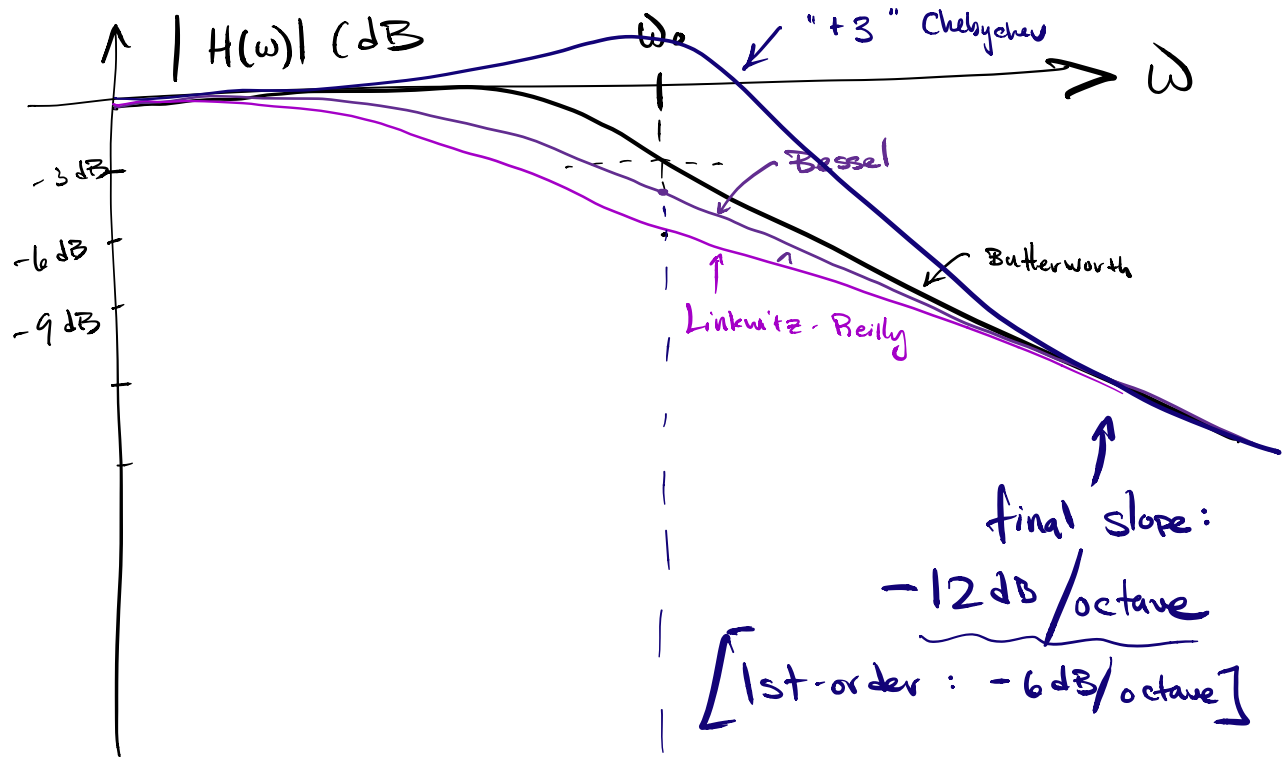

Homework: write transfer function for the following circuit:



... try to get it into final form in terms of Q