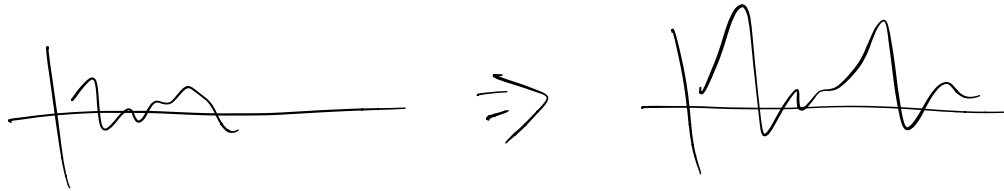


Bipolar Junction Transistors

prior to 1907 : no way to amplify small signals !



1883 : thermionic emission (Edison)

1904 : Fleming diode


1907 : Lee DeForest : vacuum tube triode

- .. first three-terminal electronic device
- .. grid electrode between cathode and anode could be used to modulate current through the device

.. now, we have solid-state devices

- .. field-effect transistor and bipolar junction transistor are main categories


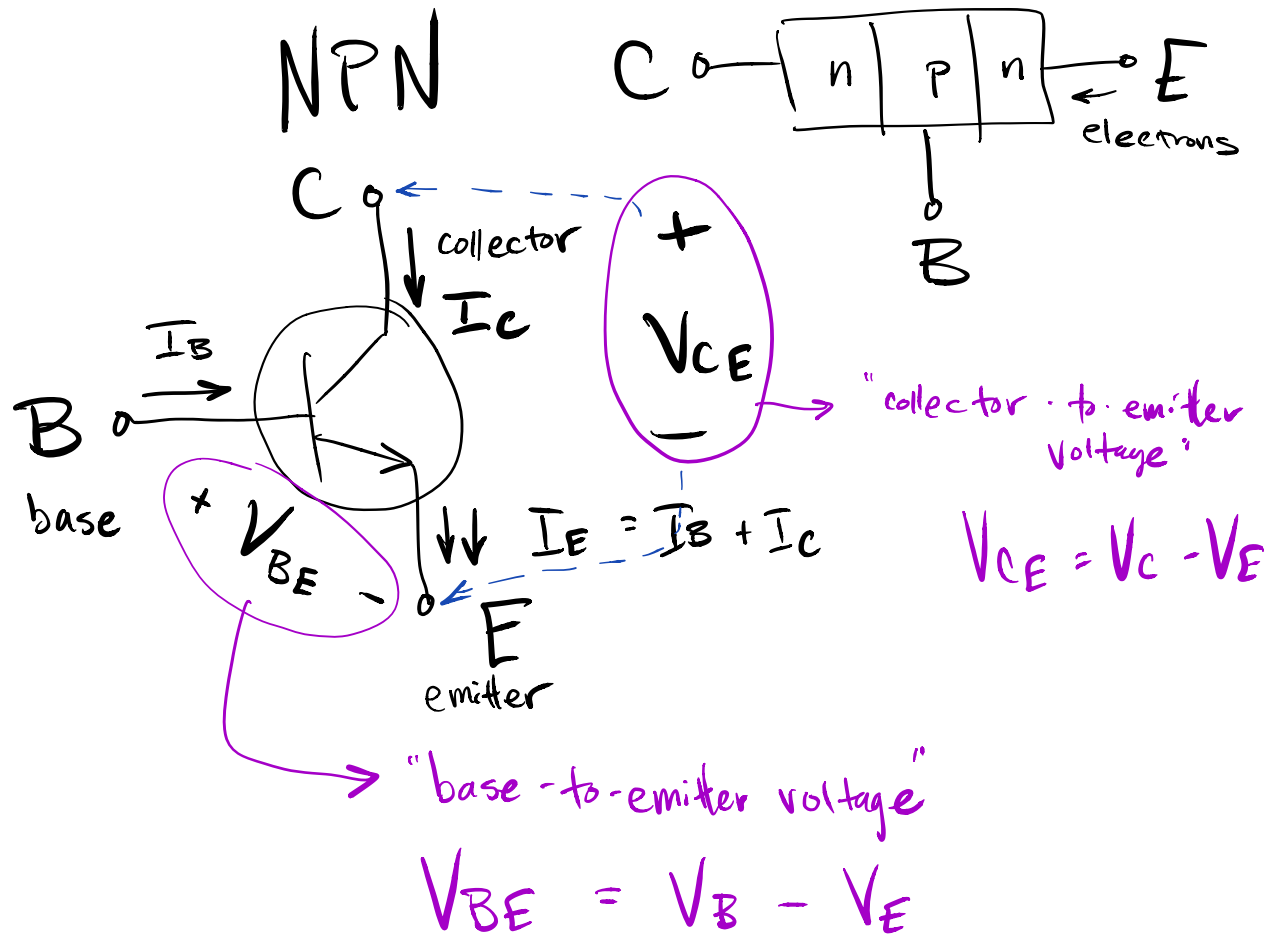
.. two types of bipolar junction transistor (BJT)




.. the base-to-emitter voltage can be used to modulate collector current; and if we're smart enough, we can use this collector current to drop a voltage, and get a large collector-to-emitter voltage

\Rightarrow = amplification!

PNP

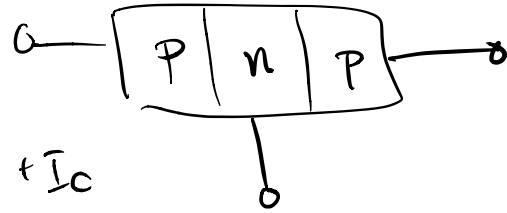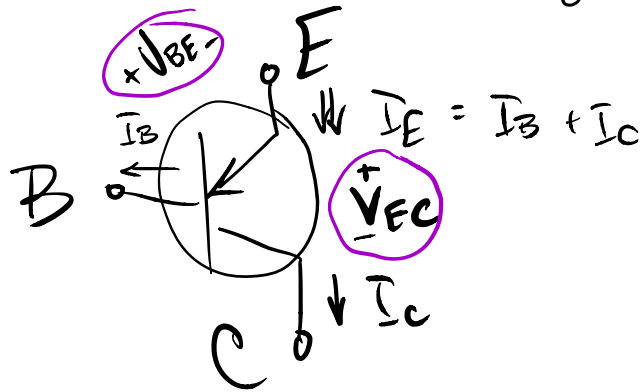

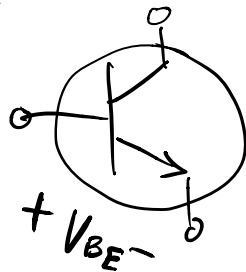
- .. PNP transistor is the mirror image of NPN;
all voltages and currents reversed.
- .. we'll usually refer to NPN transistors
- .. PNP amplify the same way
- .. the base-emitter junction is the key input port on a transistor amplifier.




.. for Si transistors, V_{BE} acts like a Si diode and drops $\sim 0.7V$ when ON.

.. also allows base current I_B to flow, as long as $V_{CE} \geq 0.2V$ (roughly)

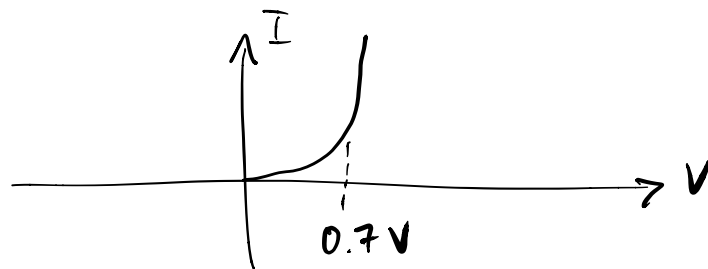.. unlike a diode, which has one current-voltage relationship:



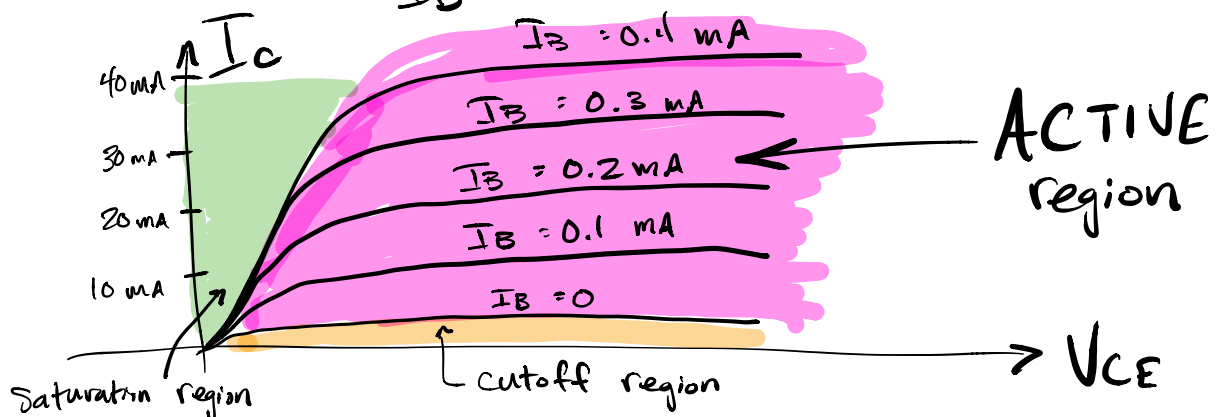... bipolar transistors have a family of curves that relate V_{CE} to I_C for different values of I_B :



- in fact, when used as switches, transistors are operated in saturation and cutoff regions
- when used to amplify small signals (linearly), we are interested only in the active region.
- in the active region, base and collector currents are roughly proportional by a parameter called β (current gain)

$$\alpha / \beta \text{ or } h_{FE}$$

$$I_C = \beta I_B$$

we know by KCL that $I_E = I_C + I_B$

$$\therefore \underline{I_E = I_B (1 + \beta)}$$

.. if β is "sufficiently high",

$$\underline{I_E \approx \beta I_B} \quad \text{and} \quad \underline{I_E \approx I_C}$$