

DC Bias of FETs

.. BJTs have the distinct convenience of $V_{BE} \sim 0.7V$ [or -0.7 if PNP] for Si transistors

.. FETs, on the other hand, have a relationship between V_{GS} and I_D of either:


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2 \quad \left[\text{JFET and depletion MOS} \right]$$

$$\text{or } I_D = K (V_{GS} - V_t)^2 \quad \left[\text{enhancement MOS} \right]$$

.. this makes DC analysis awkward!

ex:

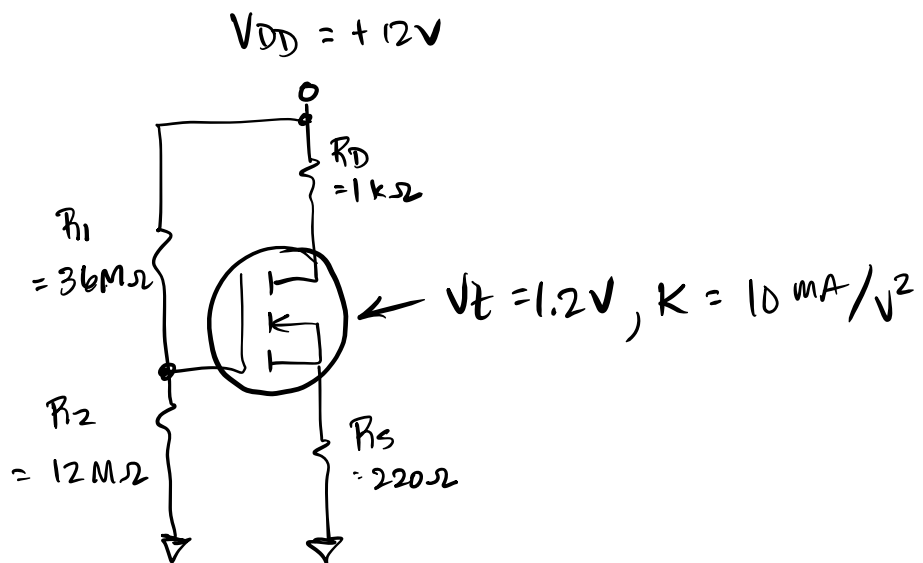note: we can have very large gate resistors due to no gate current!



.. we can easily determine V_G :

$$V_G = 12 \left[\frac{12M}{12M + 36M} \right] = \underline{\underline{3V}}$$

.. but since we don't know V_{GS} yet, we can't determine V_S to then determine I_S , which we could then use to determine V_{GS} !!!
Oh no! (rats...)

.. Fortunately, Very Smart People have recognized that the parabolic locus formulae for both types of FETs can be solved for V_{GS} as a quadratic, knowing

$$V_S = I_S R_S = I_D R_S$$

↑ no gate current!

$$V_{GS}|_{n\text{-channel}} = \frac{-b + \sqrt{b^2 - 4ac}}{2a}$$

$$V_{GS}|_{p\text{-channel}} = \frac{+b - \sqrt{b^2 - 4ac}}{2a}$$

} all
FETs

for JFET and depletion MOSFET:

$$a = \frac{I_{DSS} R_S}{V_{GS(off)}^2}$$

$$b = \frac{2I_{DSS} R_S}{|V_{GS(off)}|} + 1$$

$$c = I_{DSS} R_S - |V_G|$$

for enhancement MOSFET:

$$a = K R_S$$

$$b = 1 - 2K R_S |V_t|$$

$$c = K R_S V_t^2 - |V_G|$$

... So for this n-channel enhancement-type MOSFET example :

$$a = \underset{\substack{\uparrow \\ \text{mA/V}^2}}{10} \cdot \underset{\substack{\uparrow \\ \text{k}\Omega}}{0.220} = \underline{2.2}$$


$$b = 1 - 2 \cdot 10 \cdot 0.22 \cdot |1.2| = \underline{-4.28}$$

$$c = 10 \cdot 0.22 \cdot 1.2^2 - 3 = \underline{0.168}$$

$$V_{GS}|_n = \frac{-(-4.28) + \sqrt{4.28^2 - 4 \cdot 2.2 \cdot 0.168}}{2 \cdot 2.2}$$

$$\underline{V_{GS} = 1.905 \text{ V}}$$

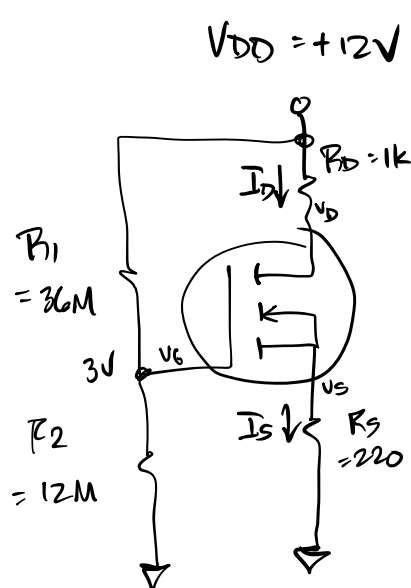... we may now proceed with D.C. analysis.



$$V_{DD} = +12\text{V}$$

$$V_{GS} = V_G - V_S$$

$$\begin{aligned} \rightarrow V_S &= V_G - V_{GS} \\ &= 3 - 1.905 = \underline{1.095 \text{ V}} \end{aligned}$$

$$I_S = \frac{V_S - 0}{R_S} = \frac{1.095}{0.220}$$

$$\underline{I_S = 4.977 \text{ mA} = I_D}$$

.. let's check this with the original equation:


$$I_D = K (V_{GS} - V_t)^2$$
$$= 10 (1.905 - 1.2)^2 = \underline{4.97 \text{ mA}} \quad (\text{yep!})$$

$$V_D = V_{DD} - R_D I_D = 12 - \underset{\substack{\uparrow \\ \text{k}\Omega}}{1} \cdot \underset{\substack{\uparrow \\ \text{mA}}}{4.977} = \underline{7.023 \text{ V}}$$

$$V_{DS} = V_D - V_S = 7.023 - 1.095 = \underline{5.928 \text{ V}} \quad \leftarrow \begin{array}{l} \text{yes,} \\ \text{active} \\ \text{region} \end{array}$$

$$P_{\text{diss}} = V_{DS} \cdot I_D = 5.928 \cdot 4.977 = \underline{29.50 \text{ mW}} \quad \left[> V_{D(\text{sat})} = V_{GS} - V_t \right]$$

ex :

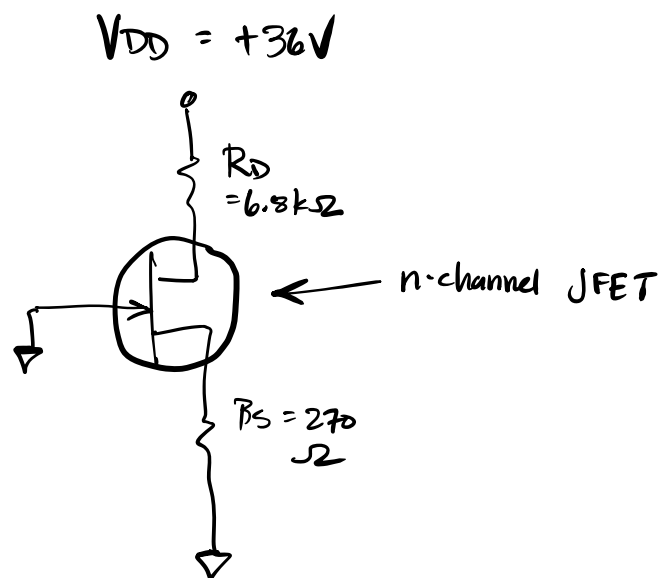

$$I_{DSS} = 9 \text{ mA}$$
$$V_{GS(\text{OFF})} = -1.0 \text{ V}$$

- .. Note that this n-channel JFET doesn't have a voltage divider at its input!
- .. that's because JFETs always have a negative V_{GS} ; so we can set $V_G = 0$ by grounding it, and the drain current will drop a positive voltage across R_S , creating a negative V_{GS} ; nice!!!

.. this is called self-bias, as opposed to voltage divider bias

.. using eqn's for JFET/depletion-mode MOSFET:

$$a = \frac{I_{DSS} R_S}{V_{GS(off)}^2} = \frac{9 \cdot .270}{1^2} = \underline{2.43}$$

$$b = \frac{2 I_{DSS} R_S}{|V_{GS(off)}|} + 1 = \frac{2 \cdot 9 \cdot .270}{1 \cdot 1.01} + 1 = \underline{5.86}$$

$$c = I_{DSS} R_S - |V_G| = 9 \cdot .270 - 0 = \underline{2.43}$$

$$V_{GS}|_n = \frac{-b + \sqrt{b^2 - 4ac}}{2a} = \frac{-5.86 + \sqrt{5.86^2 - 4 \cdot 2.43 \cdot 2.43}}{2 \cdot 2.43}$$

$$\underline{V_{GS} = -0.5321 \text{ V}}$$

$$V_S = 0 - (-0.5321) = +0.5321 \text{ V}$$

$$I_S = \frac{V_S - 0}{R} = \frac{0.5321}{0.270} = 1.971 \text{ mA} = I_D$$

--let's check this with Shockley's Equation:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

$$= 9 \left(1 - \frac{-0.5321}{-1} \right)^2$$

$$\underline{I_D = 1.97 \text{ mA} \text{ (yep!)}}$$

$$V_D = V_{DD} - I_D R_D$$

$$= 36 - 1.971 \cdot 6.8 = \underline{22.60 \text{ V}}$$

$$V_{DS} = V_D - V_S = 22.60 - 1.971 = \underline{20.63 \text{ V}}$$

$$P_{diss} = V_{DS} \cdot I_D = 20.63 \cdot 1.971 = \underline{40.65 \text{ mW}}$$